

**PROBLEM SET #7**

*Issued: Friday, October 18, 2019*

*Due: Friday, October 25, 2019, at 12:00 noon via Gradescope.*

1. What collector current is required for a bipolar transistor to achieve a transconductance of 25 mS?
2. What is the collector bias current,  $I_C$  which yields  $r_{\pi} = 5 \text{ k}\Omega$  for a bipolar transistor with  $\beta = 125$ ? What are the approximate values of  $g_m$  and  $r_o$  if  $V_A = 100 \text{ V}$ ?
3. A circuit requires the use of a transistor with a transconductance of 250 mS. A bipolar transistor with  $\beta_{DC} = 100$  and a MOSFET with  $K_n = 25 \text{ mA/V}^2$  are available. Which transistor would be preferred and why?
4. Sedra & Smith, Problem 7.92
5. Sedra & Smith, Problem 7.94
6. The circuit in Figure PS7.1 below illustrates a simple biasing method where a large feedback resistor,  $R_G$  connects the drain and gate of an NMOS transistor. If  $V_{DD} = 3 \text{ V}$ ,  $k'_n = 25 \text{ }\mu\text{A/V}^2$ ,  $V_{tn} = 0.7 \text{ V}$ , and  $R_G = 1 \text{ M}\Omega$ , design the circuit below to have a bias current  $I_D$  of 500  $\mu\text{A}$ . Pick a standard 5% resistor value for  $R_D$ , and find the actual current  $I_D$  and the drain voltage  $V_D$ .

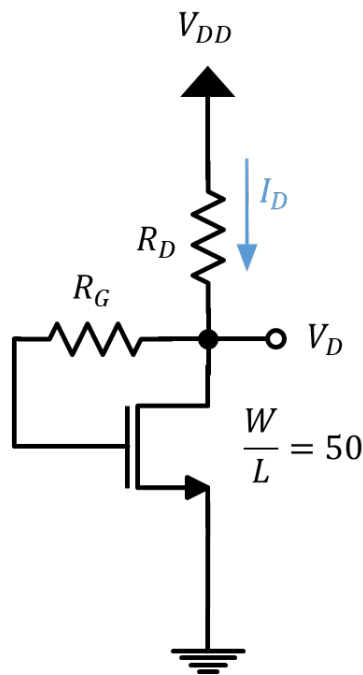


Figure PS7.1

7. Sedra & Smith, Problem 7.108
8. Sedra & Smith, Problem 7.24
9. Sedra & Smith, Problem 7.33