


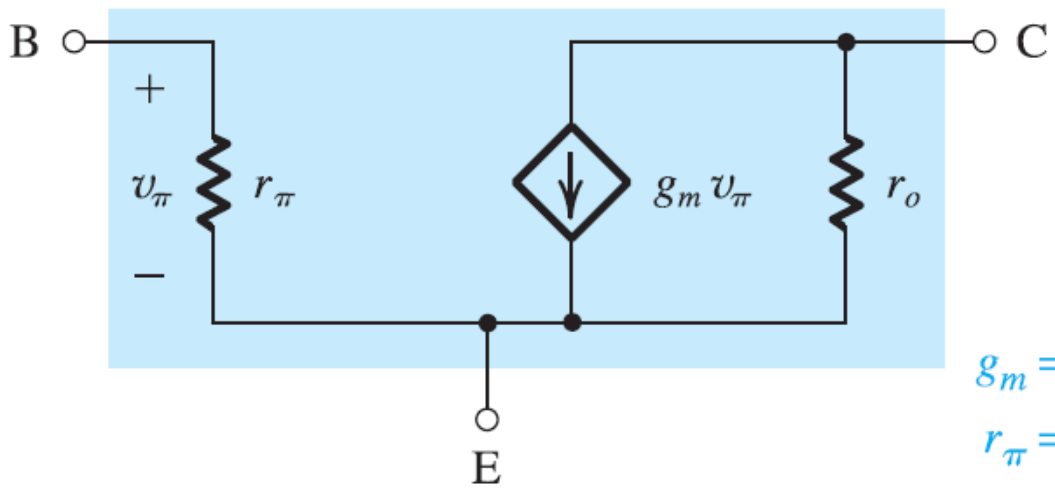


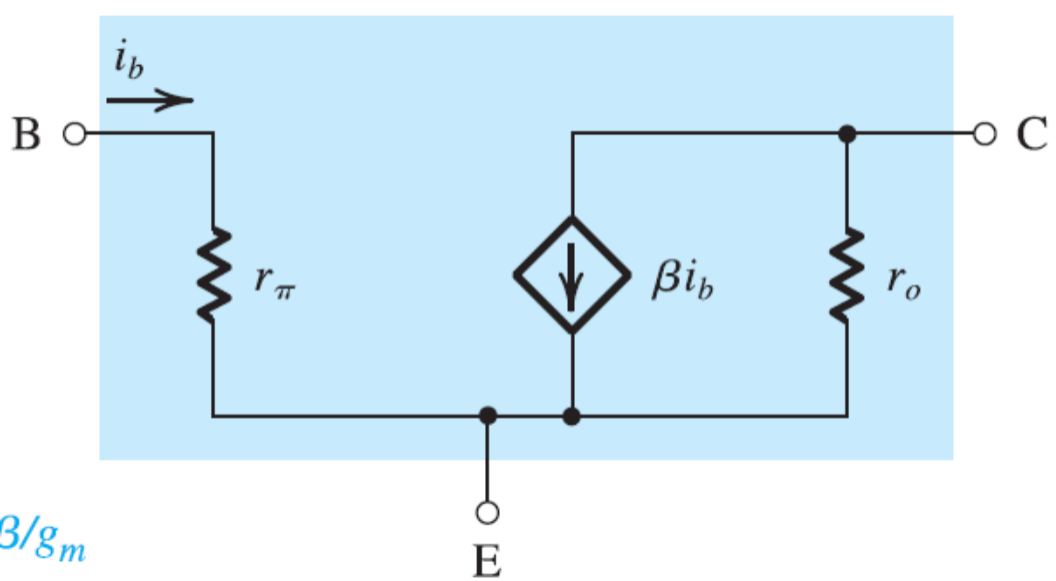**7.43** A BJT is biased to operate in the active mode at a dc collector current of 1 mA. It has a  $\beta$  of 100 and  $V_A$  of 100 V. Give the four small-signal models (Figs. 7.25 and 7.27) of the BJT complete with the values of their parameters.



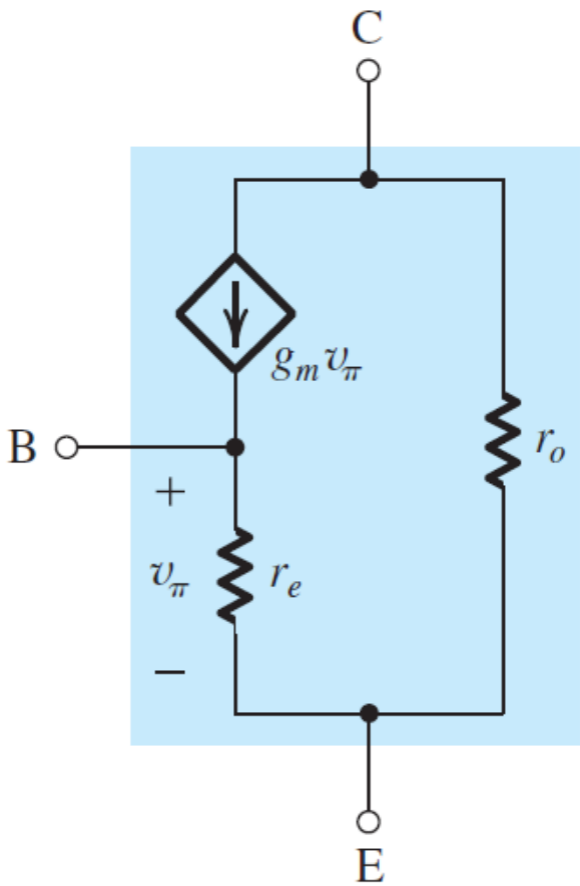

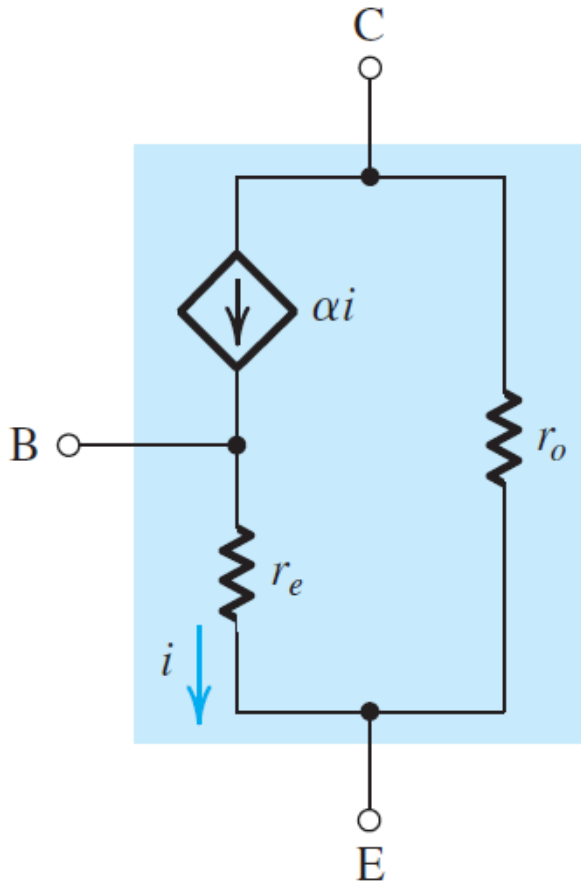




**\*7.58** The transistor in the circuit shown in Fig. P7.58 is biased to operate in the active mode. Assuming that  $\beta$  is very large, find the collector bias current  $I_C$ . Replace the transistor with the small-signal equivalent-circuit model of Fig. 7.26(b) (remember to replace the dc power supply with a short circuit). Analyze the resulting amplifier equivalent circuit to show that

$$\frac{v_{o1}}{v_i} = \frac{R_E}{R_E + r_e}$$

$$\frac{v_{o2}}{v_i} = \frac{-\alpha R_C}{R_E + r_e}$$

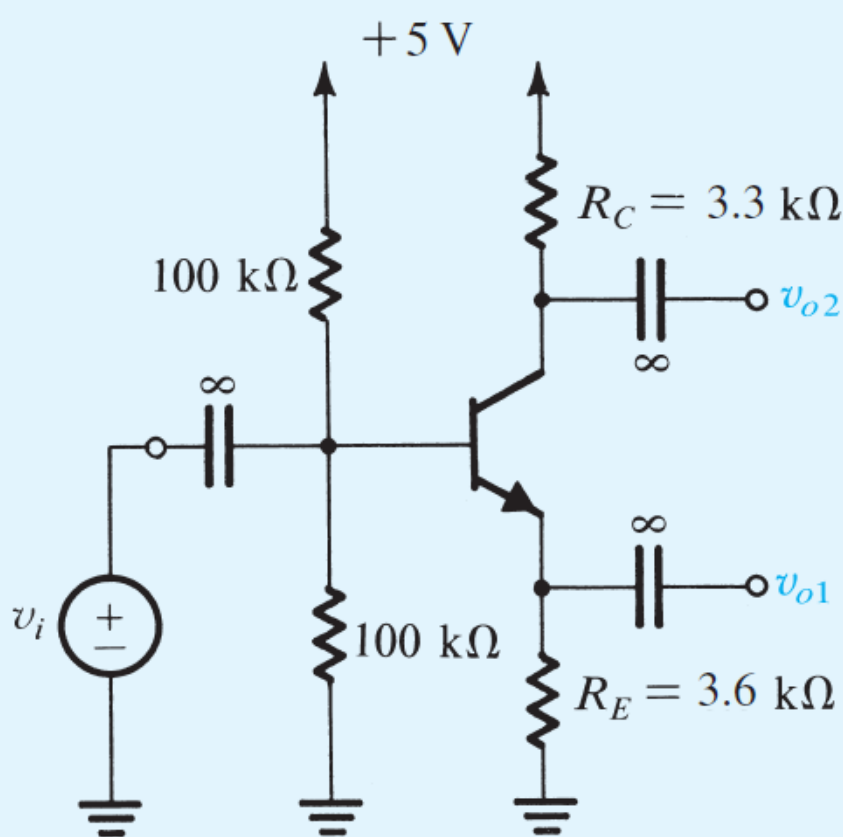

**Figure P7.58**

Find the values of these voltage gains (for  $\alpha \simeq 1$ ). Now, if the terminal labeled  $v_{o1}$  is connected to ground, what does the voltage gain  $v_{o2}/v_i$  become?

**10.21** Measurement of  $h_{fe}$  of an *npn* transistor at 50 MHz shows that  $|h_{fe}| = 10$  at  $I_C = 0.2$  mA and 12 at  $I_C = 1.0$  mA. Furthermore,  $C_\mu$  was measured and found to be 0.1 pF. Find  $f_T$  at each of the two collector currents used. What must  $\tau_F$  and  $C_{je}$  be?

**10.22** A particular small-geometry BJT has  $f_T$  of 10 GHz and  $C_\mu = 0.1$  pF when operated at  $I_C = 1.0$  mA. What is  $C_\pi$  in this situation? Also, find  $g_m$ . For  $\beta = 120$ , find  $r_\pi$  and  $f_\beta$ .



**\*10.25** Complete the table entries on the previous page for transistors (a) through (g), under the conditions indicated.

Neglect  $r_x$ .

Transistor	$I_E$ (mA)	$r_e$ ( $\Omega$ )	$g_m$ (mA/V)	$r_\pi$ (k $\Omega$ )	$\beta_0$	$f_T$ (MHz)	$C_\mu$ (pF)	$C_\pi$ (pF)	$f_\beta$ (MHz)	
(a)	2	25		2.5	100	500	2	10.7	4	
(b)										2
(c)										10.7
(d)	10				100	500	2			
(e)	0.1				100	150	2			
(f)	1				10	500	2			
(g)						800	1	9	80	