

# EE 105 | Lab 1

## Review of Passive Networks

*...aka, How Does an Oscilloscope Probe Work?*

# Prelab Review

## Basic low pass filter

- Frequency domain transfer function:

$$H(s) = \frac{V_o(s)}{V_i(s)} = \frac{1}{1 + sRC}$$

Where we can define the time constant,  $\tau = RC$  [sec]

and the pole frequency,  $\omega_p = \frac{1}{RC}$   $\left[\frac{rad}{sec}\right]$

- In the time domain:

$$V_o(t) = V_I (1 - e^{-t/RC})$$

Where  $V_I$  indicates the magnitude of an input step function,

and the rise time  $t_r = t_{0.9V_I} - t_{0.1V_I} \approx 2.197\tau$


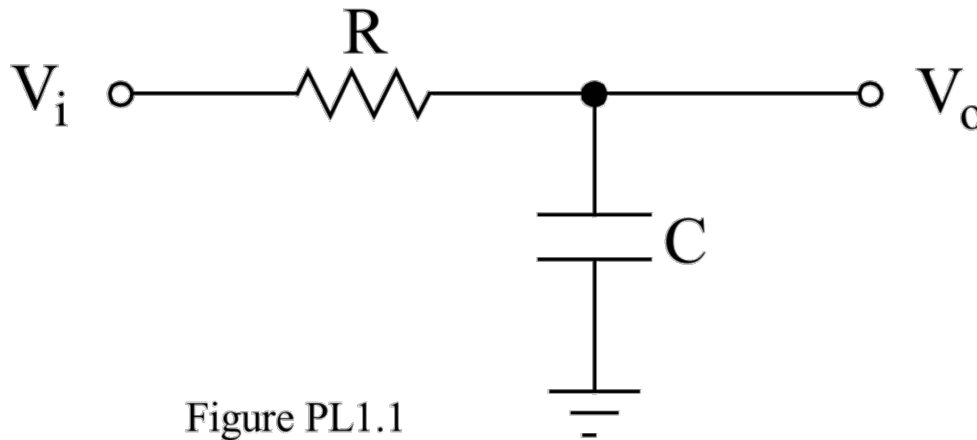


Figure PL1.1


- Any measurement tool is really a circuit
  - May seem obvious, but this means you are changing your circuit when you connect it to a tool!
  - This circuit consists of both intentionally chosen elements and *parasitics*
  - Most AC circuits will benefit from measurement with coaxial cables
    - Protection from electromagnetic interference (EMI)
    - Low loss in transmission line applications
    - Large parasitic capacitance!

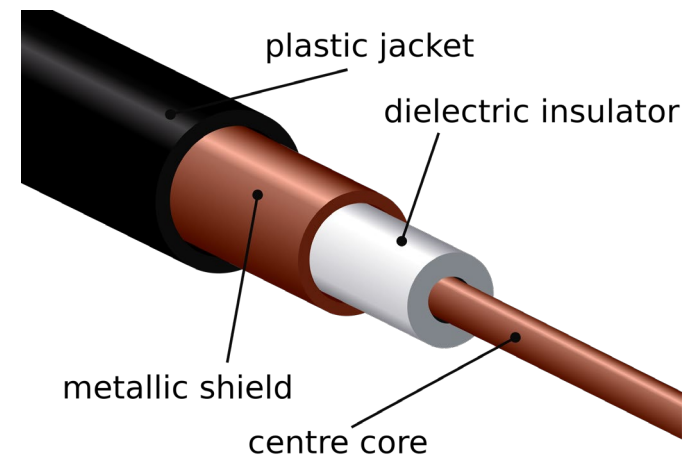

# Oscilloscope Loading
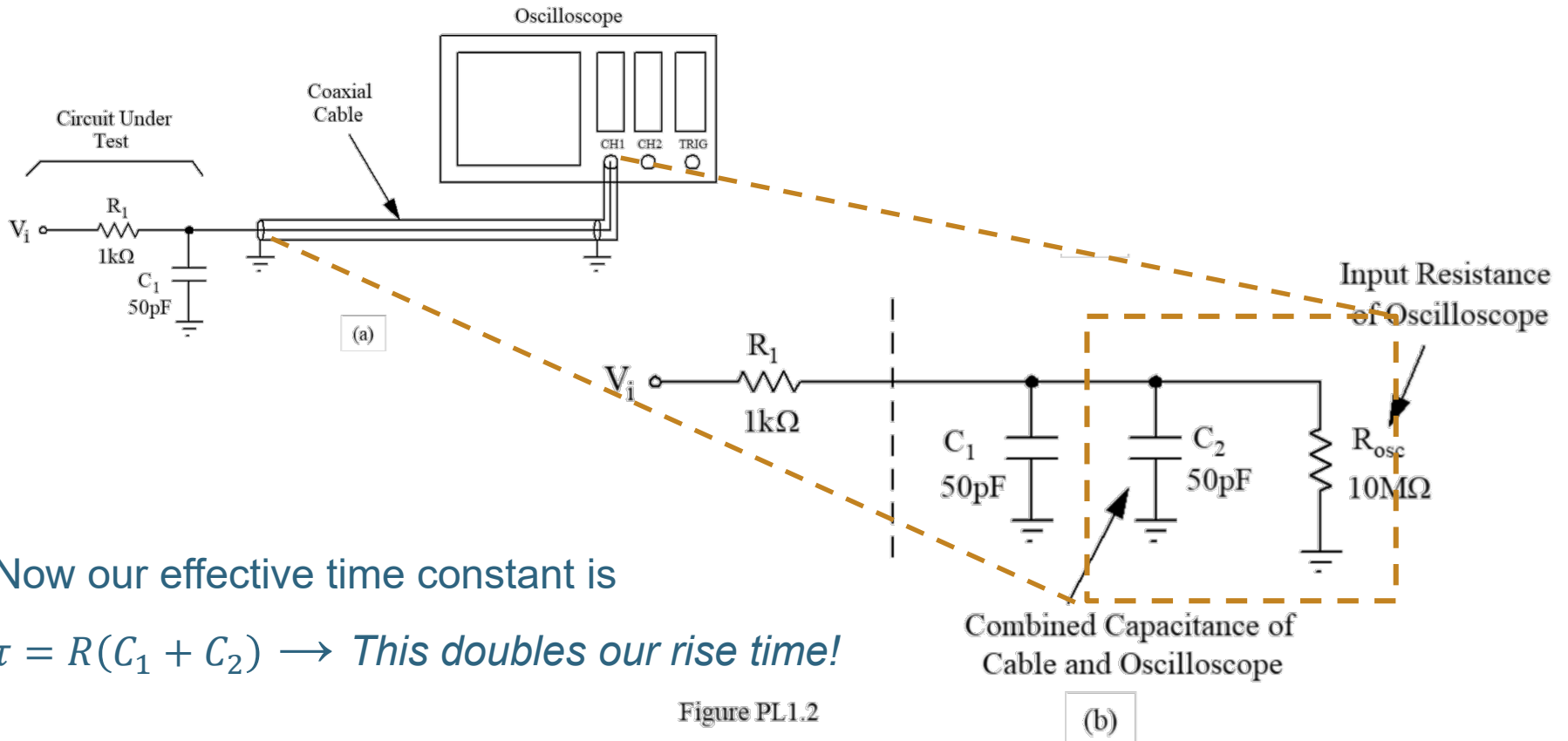
## Prelab Review

- Our oscilloscopes use coaxial probes with high input impedance
  - This capacitively loads any circuit we want to measure!



Now our effective time constant is

$$\tau = R(C_1 + C_2) \rightarrow \text{This doubles our rise time!}$$


Figure PL1.2

# Loading Effects on Rise Time

## Prelab Review

**Q:** If the probe capacitance introduces 100% error, how can it measure any arbitrary response accurately?

**A:** Clever circuit design!

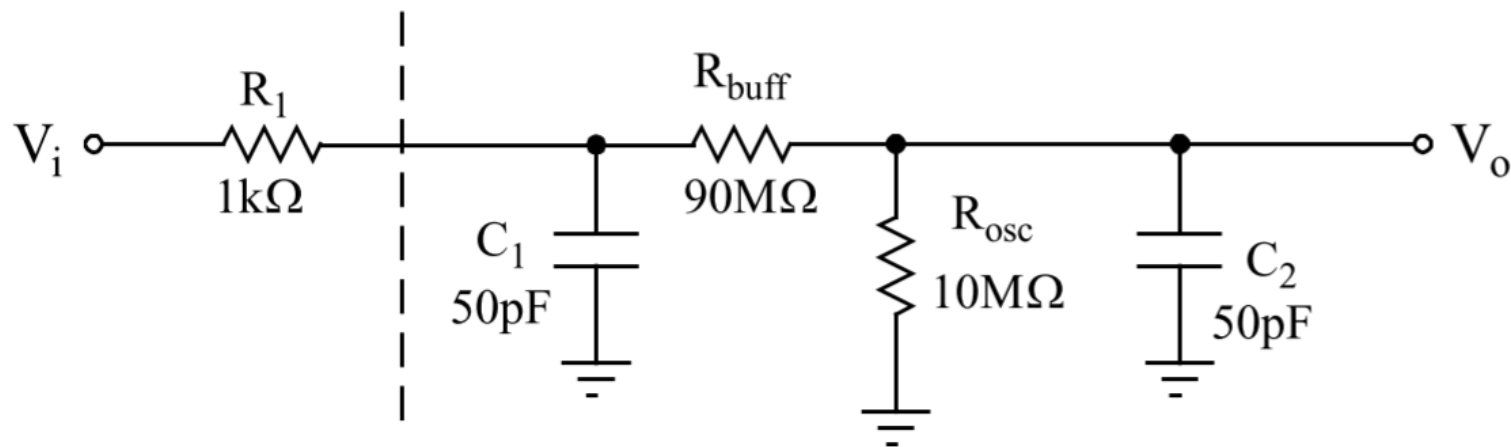

By using a buffer resistor in series with the input, the effective voltage across  $C_2$  is reduced by the voltage divider ratio


$$C_{2,\text{eff}} = \frac{R_{\text{osc}}}{R_{\text{osc}} + R_{\text{buff}}} C_2$$

This means for a given step/cycle, much less charge needs to be stored on  $C_2 \rightarrow$  **faster response!**

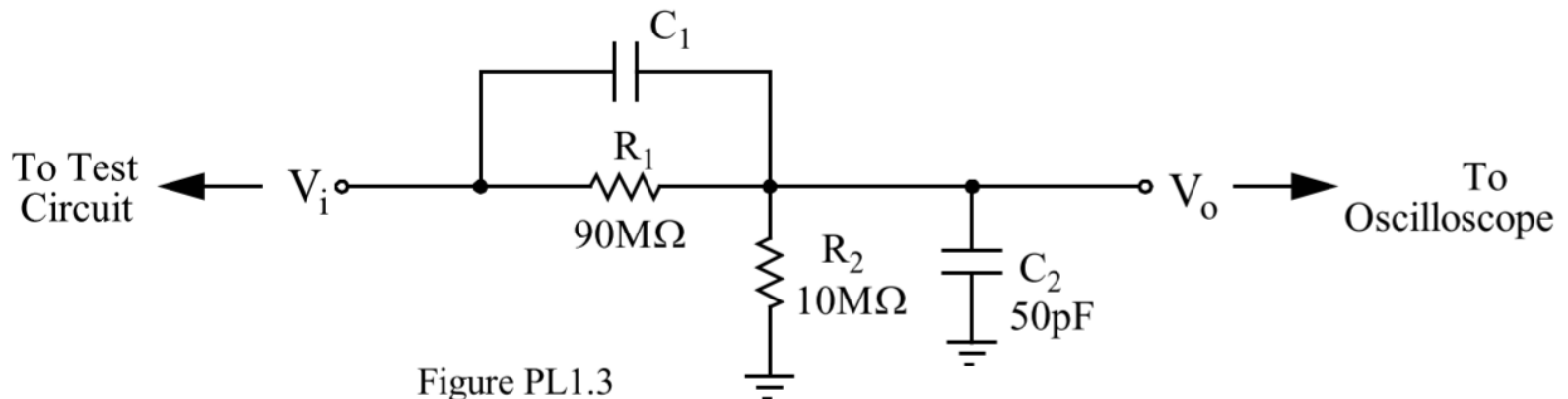**Problem:**  $R_{buffer}$  actually increases the rise time of the oscilloscope circuit through the resistive component of  $\tau$

$$\tau_{osc} = (R_{osc} \parallel R_{buffer})C_2$$

**Solution:** “Compensate” the probe by creating a parallel path at high frequencies



# Compensated Attenuators

## Prelab Review

- At low frequencies, we have a resistive divider (i.e., **attenuator**)

- $V_o = \frac{R_2}{R_1 + R_2} V_i$

- At high frequencies, we have a capacitive divider (the capacitor impedances will be much lower than  $R_1$  &  $R_2$  resistances)

- $V_o = \frac{C_1}{C_1 + C_2} V_i$


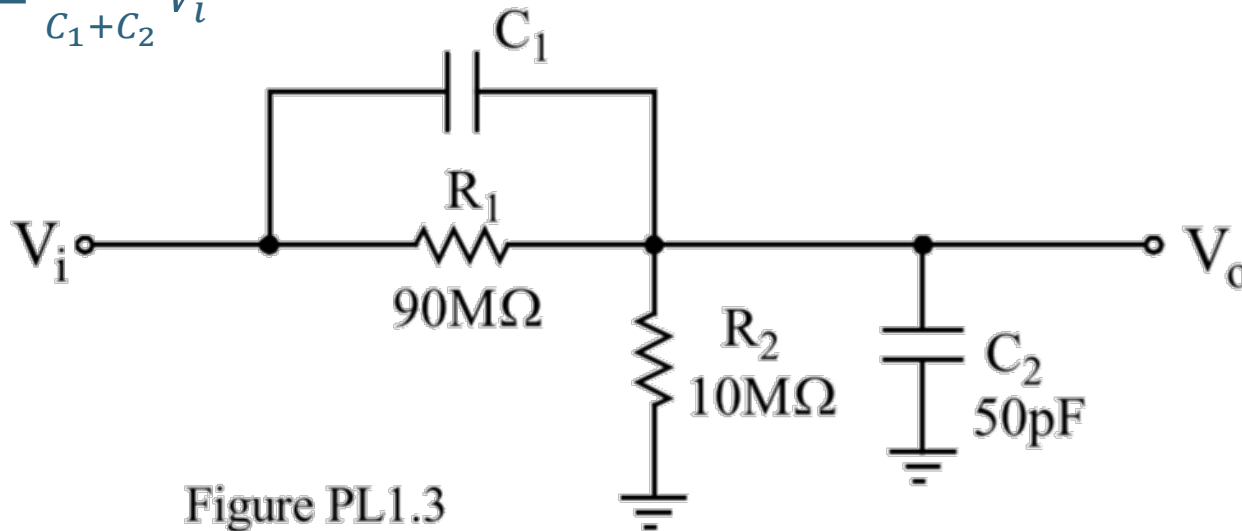


Figure PL1.3

If  $C_1 = \frac{R_2}{R_1} C_2$ , we will have the same transfer function across all frequencies, giving us a theoretical rise time of 0!

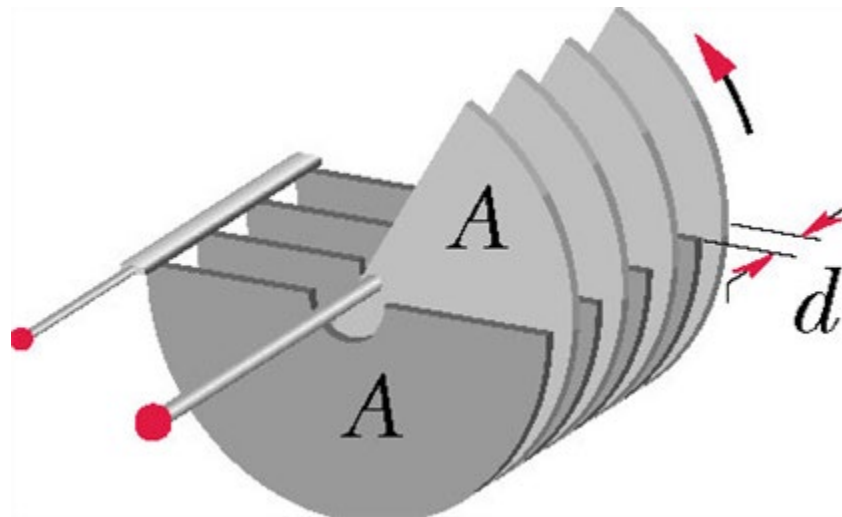- Previous analysis depends on precisely picking the value of  $C_1$  based on  $R_1, R_2$  &  $C_2 \rightarrow$  **these values cannot be reliably controlled or predicted**
- **Real oscilloscope probes allow for adjustment of  $C_1$**  (variable capacitor) to precisely tune the network
- We will use variable resistors instead...how could this work?



*One more thing...*



# Lab Overview

- Lab equipment
- Breadboard circuits

# Lab Equipment


- Arbitrary Function Generator
  - Agilent 33120A
- Digital Oscilloscope
  - Agilent DSO5014A



**Use proper cables!**
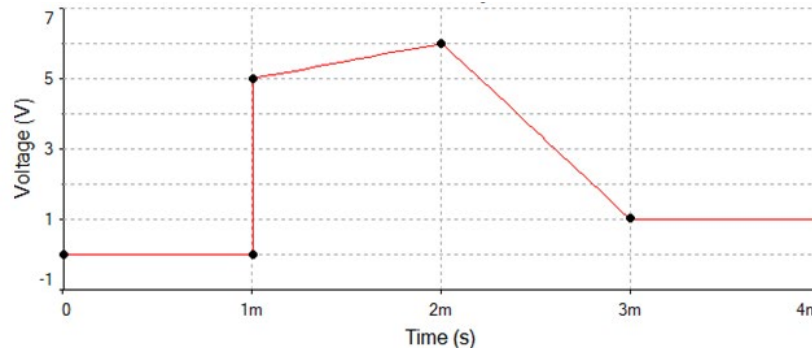
# Arbitrary Function Generator

- Generates arbitrary waveforms
  - Sinusoidal
  - Square
  - Triangle
  - Piecewise




# Arbitrary Function Generator



- Switch On/Off
- Sinusoidal Signal
- Frequency
- Amplitude
- Square Wave
- Tuning Resolution Adjustment
- Adjustment Knob
- Output
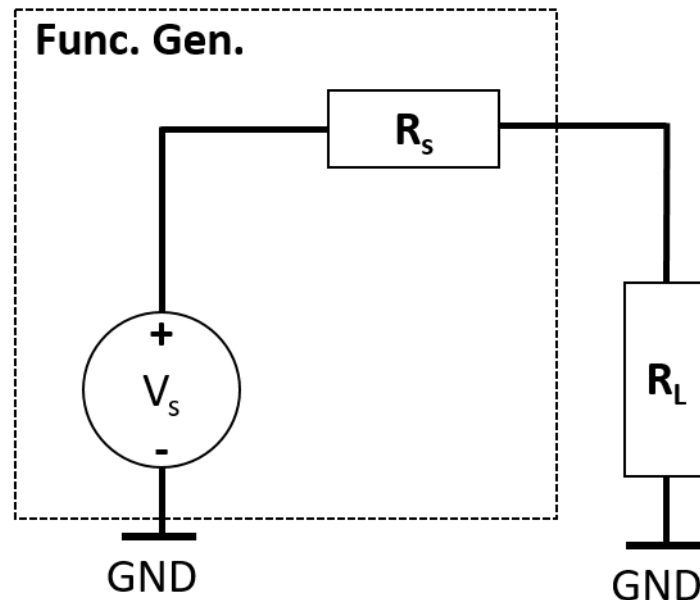
# Arbitrary Function Generator

- Frequency Range
  - ~15 MHz
- Output Impedance
  - **Figure it out!**



# Digital Oscilloscope



General Knob

Auto-Scale

Cursor & Measurement

Trigger Settings

Time Scale

Run/Stop/Single


Scale

Level

USB

Probe Compensation

Channels

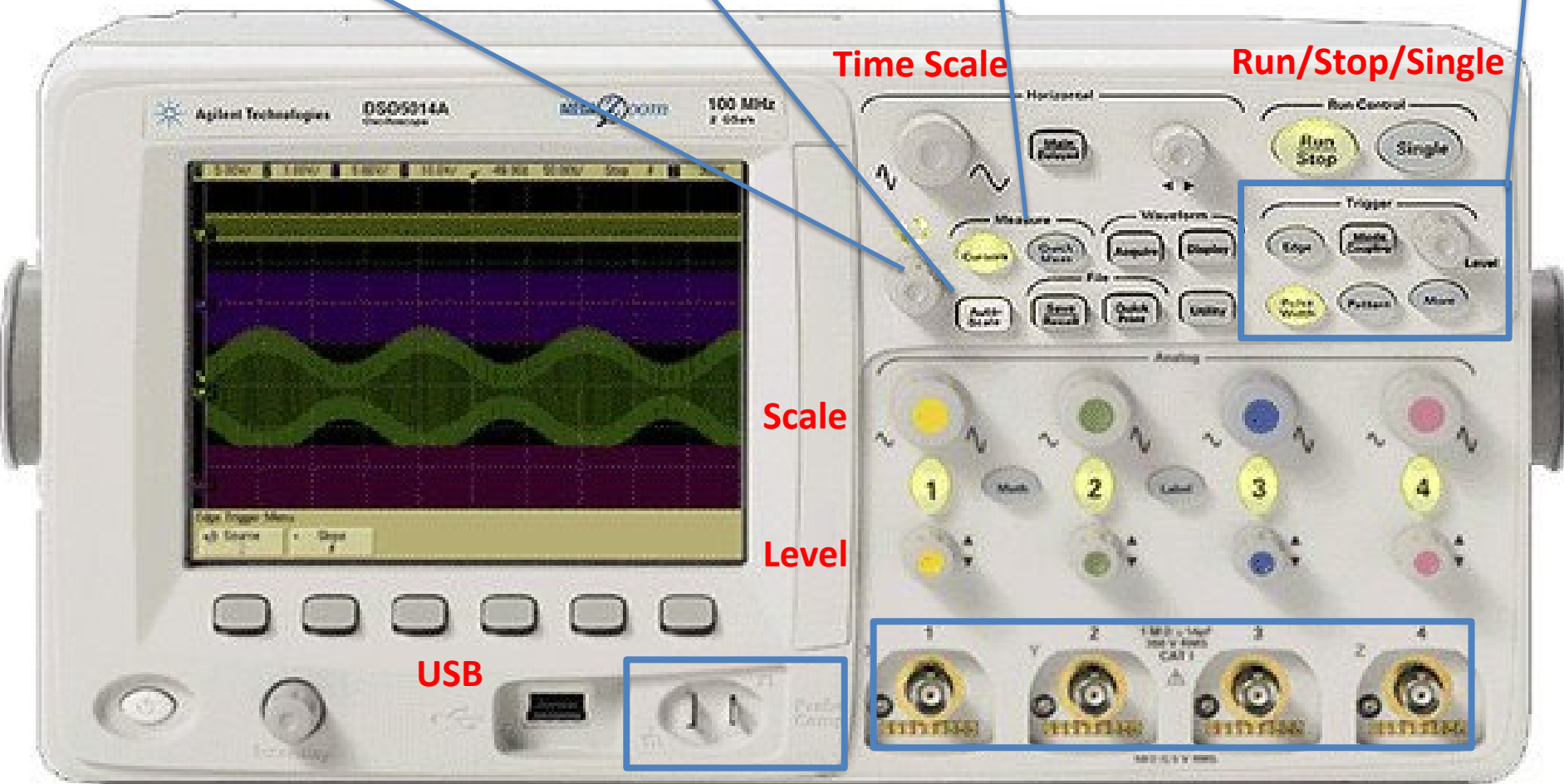

# Digital Oscilloscope

- Need to compensate probes
  - Otherwise your measurement will be incorrect

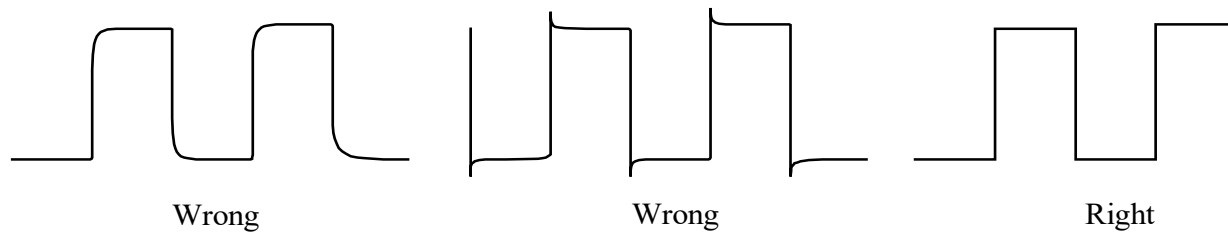


Figure L1.1


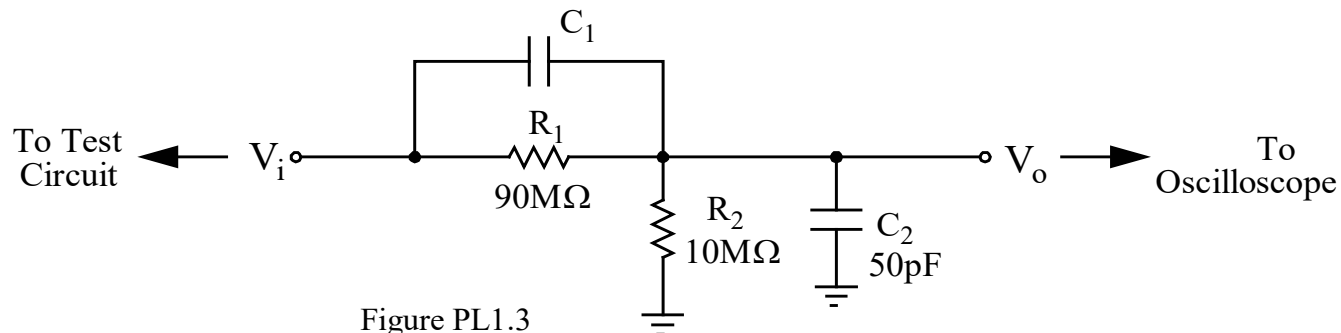


Figure PL1.3

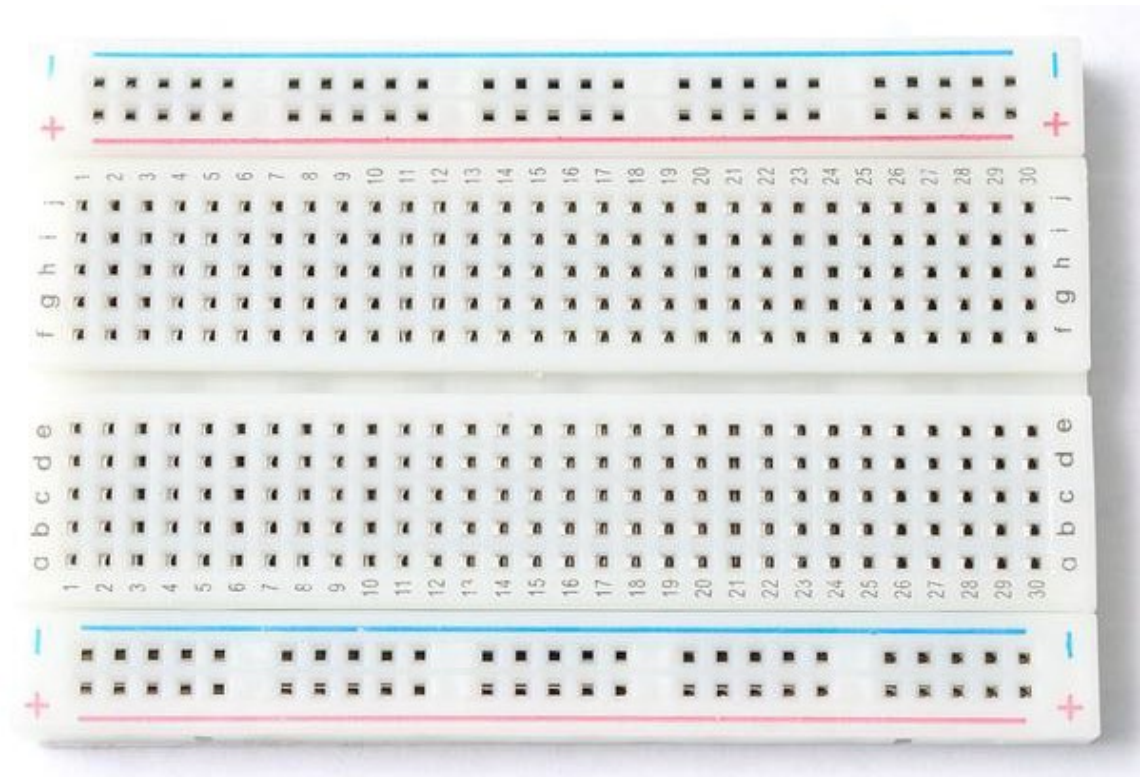


# Breadboard Circuits

- Proto-board
  - ‘Bread-board’



# Breadboard Circuits

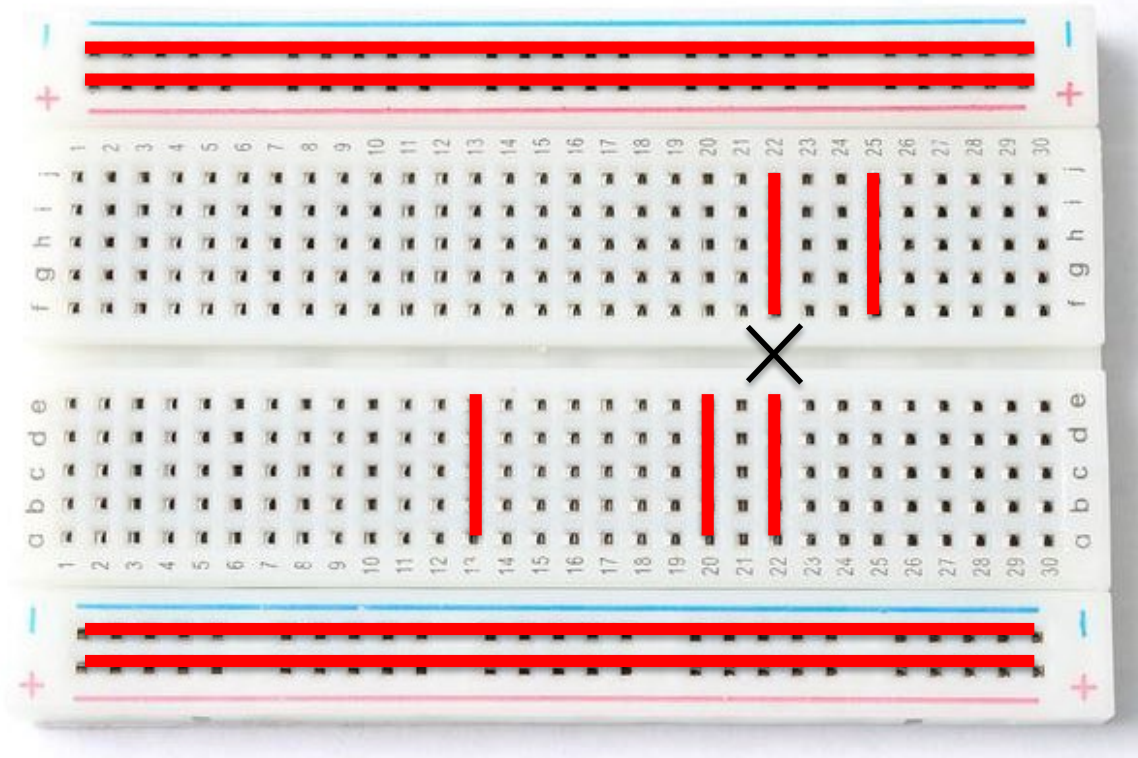

# Proto-board wiring

- Short wires
- Short legs
- Clear and Clean

