

Lecture 17: Bipolar Junction Transistors (BJTs) II

- **Announcements:**
- HW#6 online and due Friday, Oct. 18 (almost two weeks from now) via Gradescope
- Lab#3 continues this week
 - ↳ Prelab due before lab; Lab#3 due next week
- Lab#4 is online, with prelab due next week
- Midterm 1 on Friday, Oct. 11, 7-9 p.m., 160 Kroeber Hall
 - ↳ Midterm Info Sheet online
 - ↳ Review Session for Midterm, Tuesday, 6-8 p.m., in 293 Cory
 - ↳ For the review session, please post on Piazza specific problems you would like covered
- My Monday Office Hours will move to 5-6 p.m. on Oct. 14 and thereafter
- I am traveling today
 - ↳ This lecture is pre-recorded
 - ↳ I will be back on Wednesday, Oct. 9

Lecture Topics:

- ↳ BJT Forward-Active Region
 - Physics
 - Large Signal Circuit Model
 - Operating Pt. Example
- ↳ Reverse Active Region
- ↳ Saturation Region

Last Time:

- Went through BJT physics

$$p_{nE}(0) = \frac{n_i^2}{N_{dE}} \exp\left(\frac{V_{BE}}{V_T}\right)$$

$$p_{nE}(W_E) \approx 0$$

$$I_{pE} = q A D_{pE} \frac{n_i^2}{N_{dE} W_E} \exp\left(\frac{V_{BE}}{V_T}\right) = \textcircled{2}$$

$$\textcircled{3}: I_{rB} = \frac{Q_E}{\tau_b}$$

$$= \frac{1}{\tau_b} \left[\frac{1}{2} n_{pB}(0) W_B q A \right]$$

$$\therefore I_{rB} = \frac{1}{2} \frac{n_i^2 W_B q A}{N_{aB} \tau_b} \exp\left(\frac{V_{BE}}{V_T}\right) = \textcircled{3}$$

Define: Forward Current Gain = β_F


$$\beta_F = \frac{i_c}{i_B} = \frac{\textcircled{1}}{\textcircled{3} + \textcircled{2}} = \frac{q A D_{nB} n_i^2}{N_{aB} W_B \left[\frac{1}{2} \frac{n_i^2 W_B q A}{N_{aB} \tau_b} + \frac{q A D_{pE} n_i^2}{N_{dE} W_E} \right]}$$

$$\therefore \beta_F = \left[\frac{W_B^2}{2 \tau_b D_{nB}} + \frac{D_{pE} W_B N_{aB}}{D_{nB} W_E N_{dE}} \right]^{-1}$$

To maximize β_F , want:

- ① $W_B = \text{small}$
 - ② $N_{dE} \gg N_{dB} \xrightarrow{t_0} D_{pE} \ll D_{nE}$
 - ③ $\tau_b = \text{large} \rightarrow$ base si should be free of impurities/defects to prevent recombination of e^- 's & h^+ 's
- \rightarrow This is why emitter is nt.

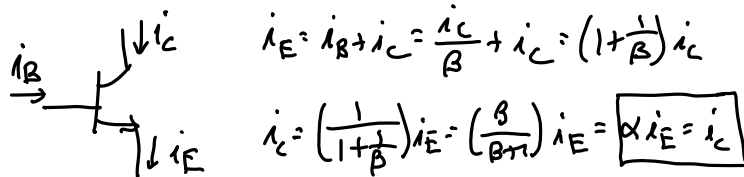So, β relates i_B & i_C . How about i_C & i_E ?




where $\alpha = \frac{\beta}{\beta + 1} \Rightarrow \beta = \frac{\alpha}{1 - \alpha}$


\hookrightarrow if $\beta = \text{large} \rightarrow \alpha \approx 1 \ \& \ i_C \approx i_E$

Equiv. Large Signal Ckt. Models for BJTs (in forward-active)

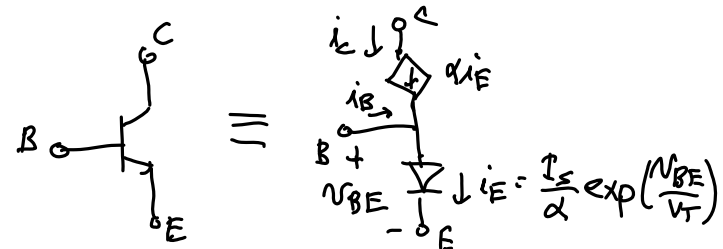\Rightarrow several of them \rightarrow two most popular accurate ones:





Common-Base (CCCS)

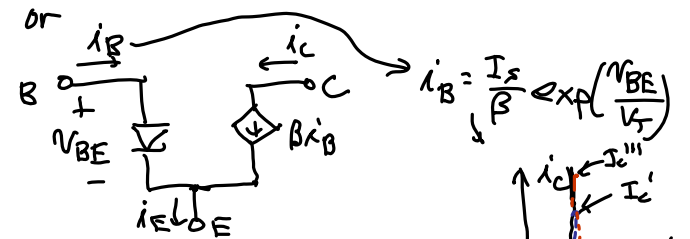

Common-Emitter (CCCS)

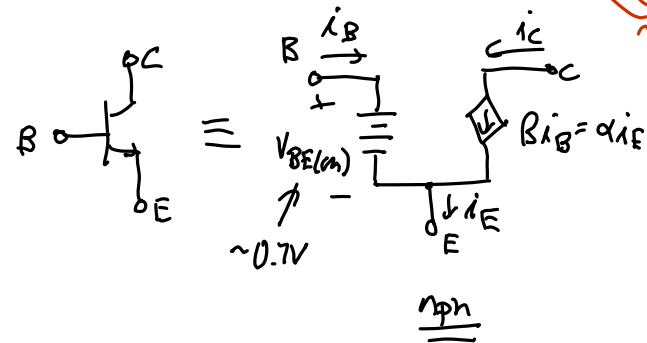\hookrightarrow usually, won't use the above, but rather will use: $\sim 0.7V$



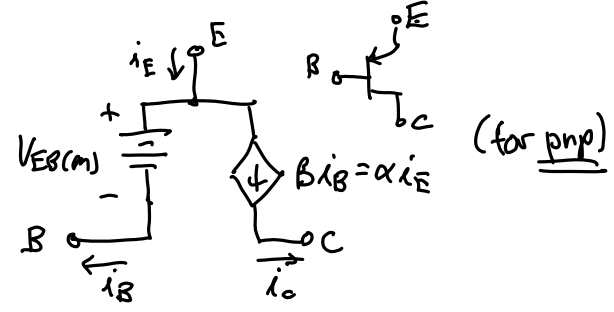


(for PNP)

$B i_B = \alpha i_E$

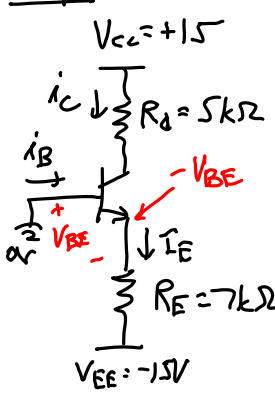Example. (exactitude)

Find the DC operating pt.
(i.e., find the DC voltages at each node and the currents through each branch)



$V_{CC} = +15$
 $R_d = 5k\Omega$
 $R_E = 7k\Omega$
 $V_{EE} = -15V$

$I_E = \frac{-V_{BE} - V_{EE}}{R_E}$

$I_C = \alpha I_E = \frac{\alpha(-V_{EE} - V_{BE})}{R_E}$

For npn transistor:
 $\beta = 100$
 $I_S = 2 \times 10^{-15} A$


$I_S \exp\left(\frac{V_{BE}}{V_T}\right) = \frac{\beta}{\beta + 1} \frac{(-V_{EE} - V_{BE})}{R_E}$
25mV (nonlinear equation)

iteration, numerical \rightarrow painful...

- \Rightarrow Get $V_{BE} = 0.717V$ $V_B = 0V$
- $\Rightarrow I_E = \frac{15 - 0.717}{7k} = 2.04mA$ $V_E = -0.717V$
- $\Rightarrow I_C = \alpha I_E = \left(\frac{100}{101}\right) I_E = 2.02mA$ $V_C = 15 - I_C(5k) = 4.9V$
- $\Rightarrow I_B = \frac{I_C}{\beta} = 0.02mA$

\Rightarrow What if we don't know β or I_S accurately? \rightarrow No need to be so accurate!

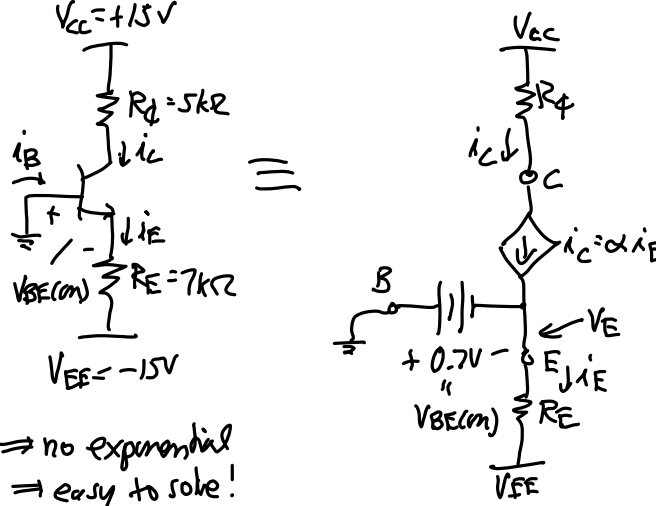\Rightarrow Do the problem again using approximations. \rightarrow esp. the model.



$V_{CC} = +15V$
 $R_d = 5k\Omega$
 $V_{BE(m)} = 0.7V$
 $V_{EE} = -15V$

$i_C = \alpha i_E$

\Rightarrow no exponential
 \Rightarrow easy to solve!

$V_B = 0V, V_E = -0.7V = -V_{BE(m)}$

$I_E = \frac{-0.7 - (-15)}{7k} \approx 2.04mA$

$I_C = \alpha I_E \approx I_E = 2.04mA$

$I_B = \frac{I_C}{\beta} = 0.02mA$

$V_C = 15 - (2.04m)(5k) = 4.8V$
 $10^{-3} \quad 10^3$

