

Lecture 18: Biasing

- Announcements:
- This lecture is a recording, since the actual class was cancelled do to the planned power outage that shut down the university
- HW#6 online and due Friday, Oct. 18 (next week) via Gradescope
- Those in the Wednesday lab section
  - ↳ can turn their Lab#3 prelabs in one day after the servers come back
  - ↳ and should finish their Lab#3 by going to the lab when the stations are free
- Lab#4 is online, with prelab due next week
- Midterm 1 moved to next week, most likely Wednesday, Oct. 16, 4-5 p.m., in our regular room
- My Monday Office Hours will move to 5-6 p.m. on Oct. 14 and thereafter
- 
- Lecture Topics:
  - ↳ BJT IV Curves
  - ↳ Parameter Independent Biasing for Discrete BJT's
  - ↳ Discrete MOS Biasing
- 
- Last Time:
- BJT biasing examples using approximations

IV Characteristics of BJT's

$i_C = I_S \exp\left(\frac{V_{BE}}{V_T}\right)$

(a diode-like characteristic)

⇒ often more interested in  $i_C = f(i_B, V_{CE})$ :  
 (get curves similar to MOS case)

Forward-Active

Saturation

increasing  $i_B$

$i_{B4}$   
 $i_{B3}$   
 $i_{B2}$   
 $i_{B1}$

$-V_A$   
 ↑  
 Early Voltage  $\cong V_A$

Finite Slope:  $\frac{1}{V_A}$

$i_C = \left[ I_S \exp\left(\frac{V_{BE}}{V_T}\right) \right] \left[ 1 + \frac{V_{CE}}{V_A} \right]$

↳ Why  $V_{CE}$ ?  $V_{CE} = V_{CB} + V_{BE}$   
 ↙ diode turn-on = constant  
 reverse-bias across BCJ →  $\Delta V_{CE} \uparrow \cong \Delta V_{CB} \uparrow$

What happens physically?

$x_1$  = depl. region width at B-CJ for  $N_{CE1} = N_{CE1}$   
 $x_2$  = " " " " " for  $N_{CE} = N_{CE2}$   $x_1$

① Case:  $N_{CE1} \rightarrow x_1 \rightarrow i_{C1} \propto$  slope of this line

② Case: increase  $N_{CE}$ :  $N_{CE} \rightarrow N_{CE2}$  ( $N_{CE1} < N_{CE2}$ )  
 $\rightarrow N_{CE} \uparrow \rightarrow x \uparrow \rightarrow x_1 \rightarrow x_2 \rightarrow i_{C2} \propto$  slope of this line  
 ( $x_2 > x_1$ )  $\therefore i_{C2} > i_{C1}$

$\rightarrow$  Thus:  $N_{CE} \uparrow \rightarrow i_C \uparrow$  due to  $x_{Bcd} \uparrow$

Result:  $i_C = f(i_B, N_{CE})$  in forward-active!

$$i_C = I_S \exp\left(\frac{V_{BE}}{V_T}\right) \left[1 + \frac{N_{CE}}{V_A}\right]$$

Parameter-Independent Biasing for Discrete BJTs

$\Rightarrow$  behavior of an analog ckt. depends heavily on its DC operating pt. (or DC Bias Point)

$\Rightarrow$  for BJTs,  $I_C$  is most important


$\Rightarrow$  must insure that  $I_C$  is stable against variations in  $\beta, V_{BE}, \& I_S$

- ①  $\beta$  is hard to control  $\rightarrow$  varies from process to process
- ②  $I_S$  " " " "  $\rightarrow$
- ③  $V_{BE} = \frac{KT}{q} \ln\left(\frac{I_C}{I_S}\right) \rightarrow$  depends on  $T$  &  $I_S$
- ④  $V_T = \frac{KT}{q} \rightarrow$  depends on  $T$

$\Rightarrow$  need biasing strategies that suppress dependence on these

Compare Some Biasing Strategies

① Voltage Sources and  $R_B$ :

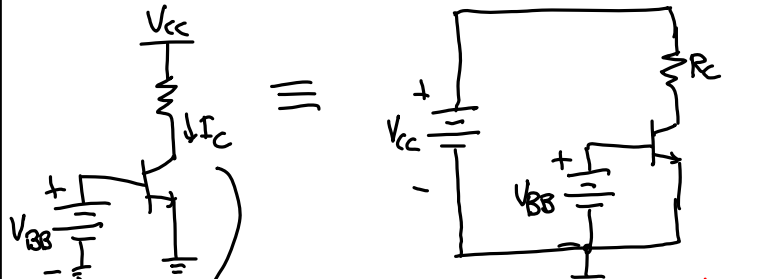


$$I_C = I_S \exp\left(\frac{V_{BE}}{V_T}\right) = I_S \exp\left(\frac{V_{BB}}{V_T}\right)$$

*must be very precisely set! X*  
*exponential w/  $V_T$  X*  
*Varies directly w/  $I_S$  X*

$\therefore$  strong dependence on  $I_S, V_T \rightarrow$  NOT GOOD!  
 (plus, we don't normally have a  $V_{BB}$  in integrated ckt's ... just  $V_{CC}$ )

② Base Resistor to  $V_{CC}$ :

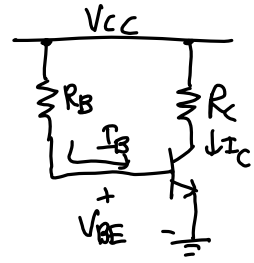


$$I_B = \frac{V_{CC} - V_{BE(on)}}{R_B}$$

$$\Rightarrow I_C = \beta I_B = \frac{V_{CC} - V_{BE(on)}}{R_B / \beta}$$

*less dependence on  $V_T$  &  $I_S$  when  $V_{CC} \gg V_{BE}$  BETTER!*  
*heavily dependent on  $\beta$ ! X*  
*NOT GOOD!*

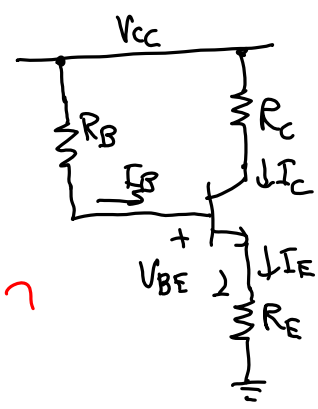③ Base Resistor to  $V_{CC}$  Plus Emitter Resistor:




Apply KVL:  $V_{CC} = I_B R_B + V_{BE} + I_E R_E$

$$= \frac{I_C}{\beta} R_B + V_{BE} + \frac{I_C}{\alpha} R_E$$

$$I_C = \frac{V_{CC} - V_{BE}}{\frac{R_E}{\alpha} + \frac{R_B}{\beta}}$$

For stability against  $\Delta V_{BE}$ : Choose  $V_{CC} \gg V_{BE}$   
For stability against  $\Delta \beta$ : Need  $\frac{R_E}{\alpha} \gg \frac{R_B}{\beta}$   
 e.g.,  $\frac{R_E}{\alpha} \gg 10 \frac{R_B}{\beta}$  is a good choice!  
 $\Rightarrow$  Problem: To get needed  $I_B$ , need large  $R_B$   
 $\Rightarrow$  reduce  $R_B$  by reducing voltage applied across it... needed

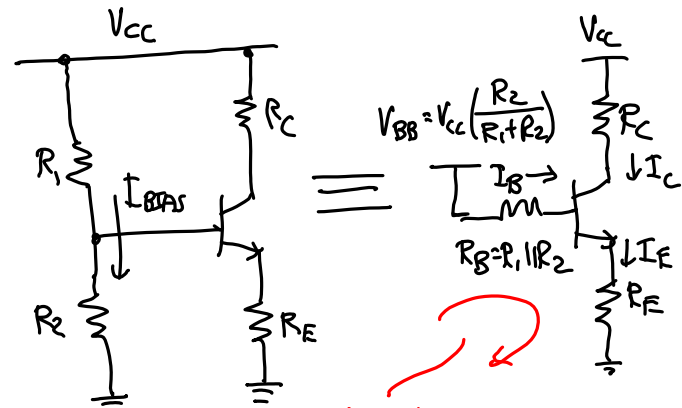④ Standard Parameter Independent Biasing:  
(for discrete BJT ccts, as opposed to IC's)



voltage divider

Apply KVL:

$$I_C = \frac{V_{BB} - V_{BE}}{\frac{R_E}{\alpha} + \frac{R_B}{\beta}}$$

Thus, for bias stability, want:

- ①  $V_{BB} \gg V_{BE}$  → for insensitivity to  $V_{BE}$
- ②  $\frac{R_E}{\alpha} \gg \frac{R_B}{\beta}$  → for insensitivity to  $\beta$   
rule of thumb:  $\frac{R_E}{\alpha} \geq 10 \frac{R_B}{\beta}$   
want  $R_B = \text{small} \rightarrow R_1, R_2 \text{ small}$
- ③  $I_{BBIAS} \geq 10 I_B$   
want  $\beta = \text{large} \rightarrow I_B = \text{small}$   
 $I_{BBIAS} = \text{large}$


For practical amplification requirements: compromise:

- ①  $V_{BB} \approx \frac{1}{3} V_{CC}$
- ②  $V_{CE} \approx \frac{1}{3} V_{CC}$
- ③  $V_{RE} = I_E R_E \approx \frac{1}{3} V_{CC}$
- ④  $0.1 I_E < I_{BBIAS} < I_E$

Good starting pt.  
... but not rules!  
↓  
must adjust for a given design

MOS Biasing

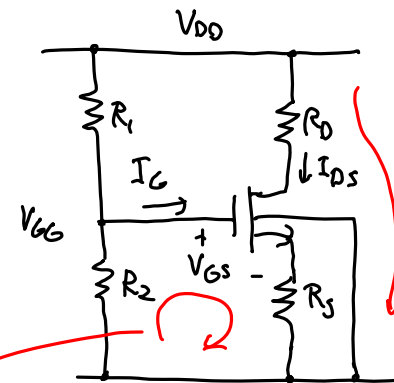⇒ can use a similar biasing strategy for discrete MOS ccts



KVL:  $V_{GG} = V_{DD} \left( \frac{R_2}{R_1 + R_2} \right)$ ,  $I_G = 0 \rightarrow V_G = V_{GG}$

KVL:  $V_{GG} = V_{GS} + I_{DS} R_S$  (2)

KVC:  $V_{DD} = I_{DS} R_D + V_{DS} + I_{DS} R_S + V_{SS}$  (1)

To find the DC operating point: (by hand)

① Assume saturation: *can often neglect*

$$I_{DS} = \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (V_{GS} - V_t)^2 (1 + \lambda V_{DS})$$

$$\text{w/ } V_t = f(V_{SB}) = V_{t0} + \gamma (\sqrt{2\phi_f - V_{SB}} - \sqrt{2\phi_f})$$

$$\Rightarrow \text{using (2): } V_{GS} = V_{DS} + \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (V_{GS} - V_t)^2 R_S \quad (3)$$

② Solve for  $V_{DS}$  assuming  $V_t = V_{t0}$ .

③  $V_S = V_{GS} - V_{GS} \rightarrow V_{SB} = V_S - V_{SS} \rightarrow$  find  $V_t(V_{SB}) = V_t'$

④ Plug  $V_t' = V_t(V_{SB})$  into (3)  $\rightarrow$  Get  $V_{GS}'$

⑤ Back to ③  $\rightarrow$  iterate to convergence

⋮

⑥ Check operating pt.  $\rightarrow$  saturated?

if yes  $\rightarrow$  done

if no  $\rightarrow$  assume linear & start over

$\Rightarrow$  tedious, but effective for discrete (i.e., off-chip) MOS ccts.

$\Rightarrow$  on-chip, we generally use current mirrors...