

Lecture 20: Transistors As Amplifiers

- Announcements:
- HW#6 online and due Friday via Gradescope
- Those in the Wednesday lab section should finish their Lab#3 by going to the lab when the stations are free
- Per Piazza, Lab#3 is due on Friday at 8 p.m. for everyone
- Lab#4 this week
- Midterm 1 today, during class. (This is a recorded lecture.)


 • Lecture Topics:

- ↳ Small Signal Analysis
 - Linearizing Non-Linear Elements
 - DC and Small-Signal AC Components
 - Taylor Series Approximation
- ↳ Transistors As Amplifiers
- ↳ Small-Signal Model for the BJT

 • Last Time:

- Discussing how Taylor series leads to the small-signal method for solving nonlinear problems
- Now, continue with this ...

Using this notation:

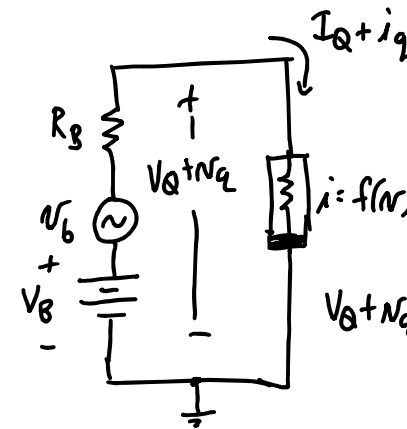

$$V_Q + N_Q = V_B + N_b - f[V_Q + N_Q] R_B$$

↳ For this: Use Taylor series approx. for $f(v)$ around the bias pt. $V = V_Q$.

Review Taylor Series:

⇒ function $f(x)$ can be approximated for points near $x=a$ by:

$$f(x) = f(a) + f'(a)(x-a) + \frac{f''(a)}{2!}(x-a)^2 + \dots + \frac{f^{(n)}(a)}{n!}(x-a)^n + \dots$$

1st derivative: $\left. \frac{df}{dv} \right|_{v=a}$ *small signal*
 $\approx f(a) + f'(a)(x-a)$ $f(a)$ $(x-a)$ = small
 linear! easy to solve! *total signal* *bias pt.*

$$\rightarrow V_Q + N_Q = V_B + N_b - f[V_Q] R_B - f'[V_Q] N_Q R_B$$


$$V_Q + N_Q = V_B + N_b - I_Q R_B - \frac{R_B}{R_{s.s.}} N_Q$$

Evaluate nonlinear fcn $I_Q = f(V_Q)$

$$R_{s.s.} = \frac{1}{\frac{df}{dV}|_{V_Q}} \triangleq \text{small-signal resistance}$$


\Rightarrow Can split this into two equations \rightarrow two ckt.

DC Components: $V_Q = V_B - I_Q R_B$

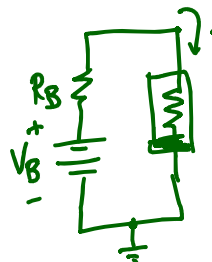

$I_Q = f(V_Q)$
 must deal w a nonlinear calculation ... but only one!
 want: (V_Q, I_Q) operating pt.

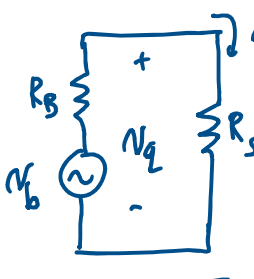
Small-Signal AC Components: $N_Q = N_b - \frac{R_B}{R_{s.s.}} N_Q \leftarrow \text{linear!}$



$R_{s.s.} = \frac{1}{\frac{df}{dV}|_{V_Q}}$
 \Rightarrow all linear analysis! \rightarrow Good!


small-signal ckt.

Graphically, here's what we're doing:

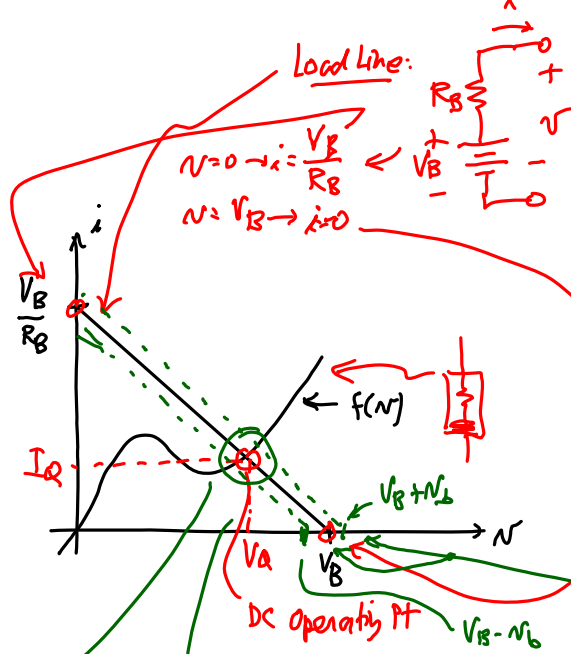


Load Line: $N=0 \rightarrow i = \frac{V_B}{R_B}$
 $N = V_B \rightarrow i=0$

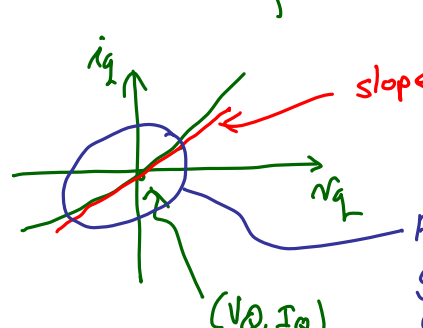As N_b varies, the load line vacillates between these dotted lines.




slope: $\frac{1}{R_{s.s.}}$

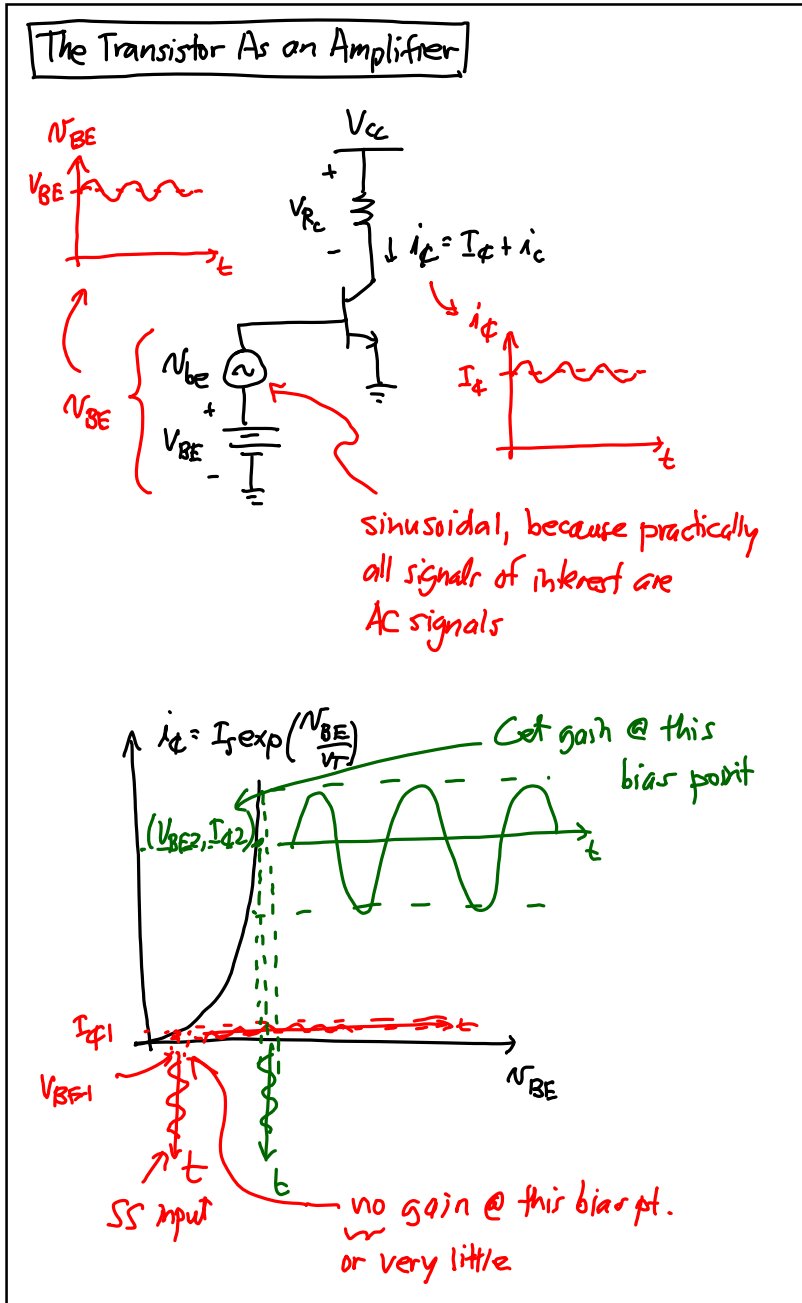Red line approximates the green curve adequately within small excursions (inside the blue circle)



- So far, we have shown how to obtain the small-signal circuit model for a two-terminal nonlinear resistor
- How about for three-terminal transistors?
- Look back to our general amplifier networks
- Any of the networks apply ... but the most popular one is the y-parameter model:

Y-Parameter Model


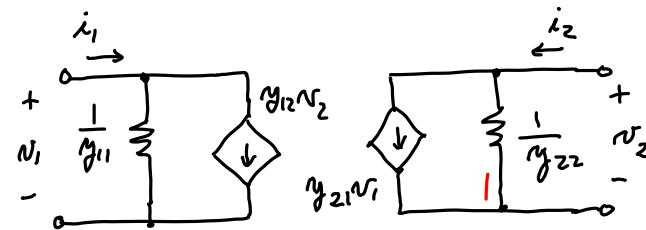


$$y_{11} = \left. \frac{i_1}{v_1} \right|_{v_2=0}$$

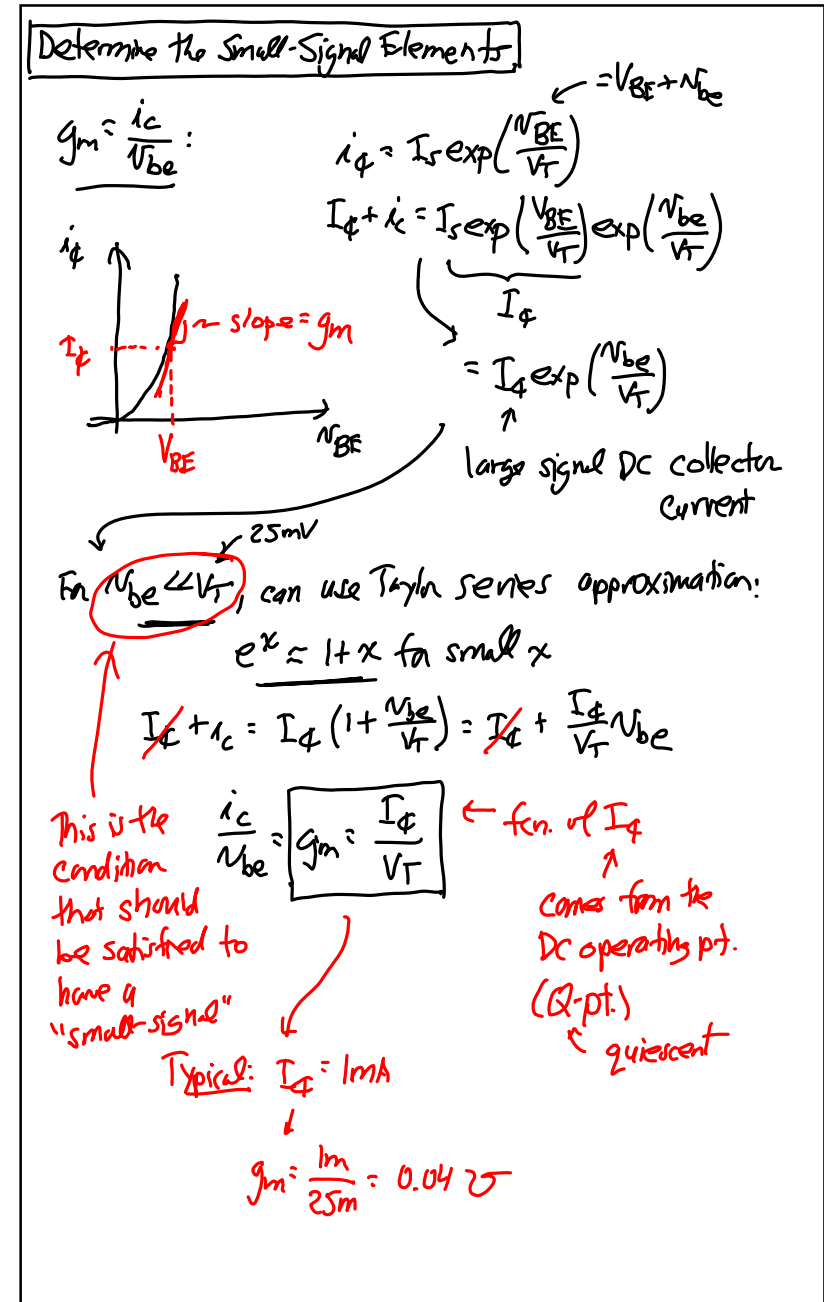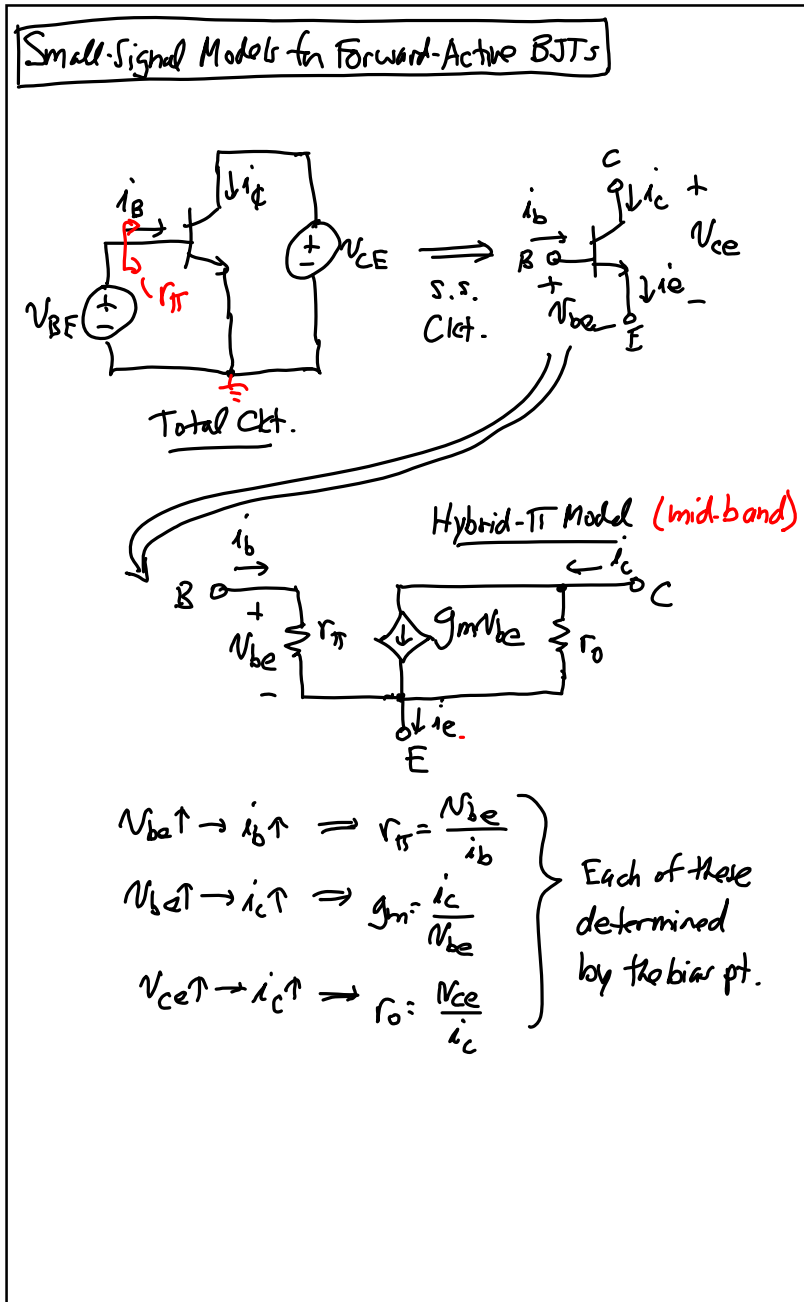
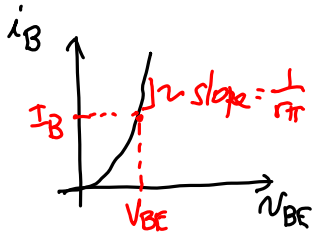
$$y_{21} = \left. \frac{i_2}{v_1} \right|_{v_2=0}$$

$$y_{12} = \left. \frac{i_1}{v_2} \right|_{v_1=0}$$

$$y_{22} = \left. \frac{i_2}{v_2} \right|_{v_1=0}$$



$r_{\pi} = \frac{v_{be}}{i_b}$






$r_{\pi} = \frac{v_{be}}{i_b} = \frac{v_{be}}{\frac{i_c}{\beta}} = \frac{\beta}{g_m} = \frac{\beta}{\frac{I_C}{V_T}} = \frac{\beta V_T}{I_C} = r_{\pi}$

again, for op DC operating pt.

Typical: $\beta = 100$
 $r_{\pi} = \frac{100}{0.04} = 2.5 \text{ k}\Omega$

$r_o = \frac{v_{ce}}{i_c}$

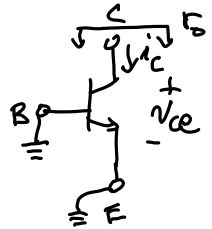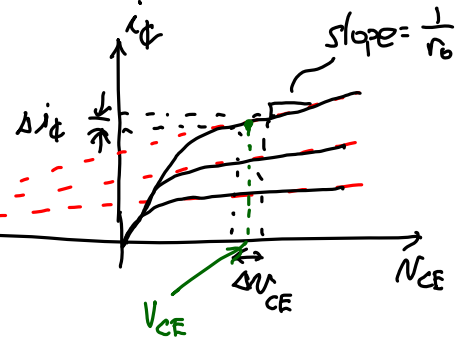$i_c = I_{se} \exp\left(\frac{v_{BE}}{V_T}\right) \left(1 + \frac{v_{CE}}{V_A}\right)$


$r_o = \left[\frac{\partial i_c}{\partial v_{CE}} \bigg|_{Q \text{ pt.}} \right]^{-1} = \left[I_{se} \exp\left(\frac{v_{BE}}{V_T}\right) \frac{1}{V_A} \bigg|_{v_{BE}=V_{BE}} \right]^{-1}$

$r_o = \frac{V_A}{I_C}$

Typical: $V_A = 100 \text{V}$
 $r_o = \frac{100}{1 \text{m}} = 100 \text{ k}\Omega$

Large, so often we neglect!


Hybrid- π Model Summary (for npn BJT)

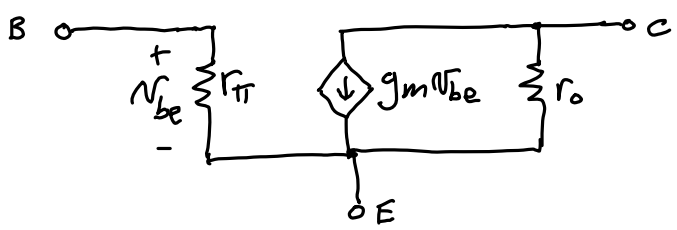

$r_{\pi} = \frac{\beta}{g_m} = \frac{V_T}{I_B}$
 $g_m = \frac{I_C}{V_T}$
 $r_o = \frac{V_A}{I_C}$


- **Remarks:**
- g_m is independent of device specifics, i.e., β , I_c
- Depends only on temperature (via V_T) and biasing (I_c)
- Small-signal model valid for $v_{be} \ll V_T$

What about emitter resistance?

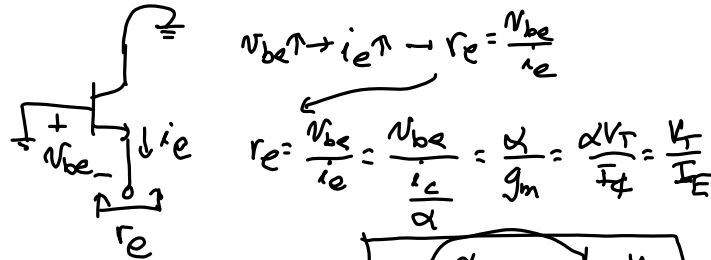

$$r_e = \frac{\alpha}{g_m} \approx \frac{1}{g_m} = \frac{V_T}{I_E}$$

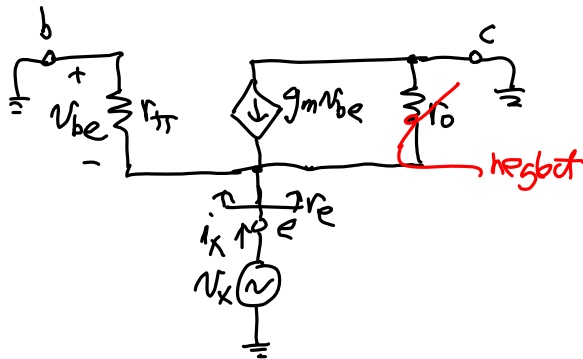Why is this not included in the hybrid- π model?
↳ well... it is!



$$i_x = -\frac{v_{be}}{r_{\pi}} - g_m v_{be}$$


$$(v_x = -v_{be}) \Rightarrow i_x = v_x \left(\frac{1}{r_{\pi}} + g_m \right)$$

$$r_e = \frac{v_x}{i_x} = \frac{1}{\frac{1}{r_{\pi}} + g_m} = \frac{r_{\pi}}{1 + g_m r_{\pi}} = \frac{r_{\pi}}{1 + \beta} = \frac{\beta}{g_m(1 + \beta)}$$

$$r_e = \frac{\alpha}{g_m} \checkmark$$

- To explicitly show the emitter resistance in the small-signal model, use the T-model:

T-Model (Common Base Model)

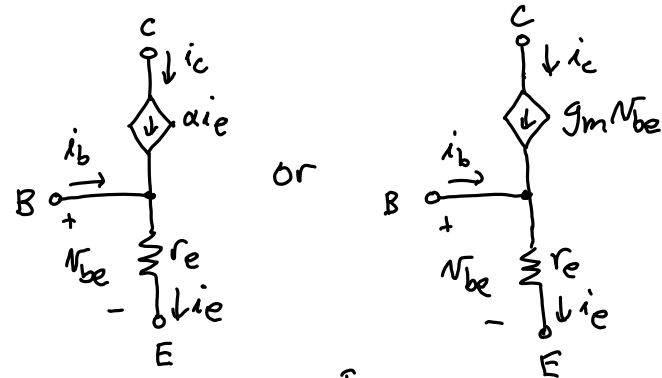

where (as before): $g_m = \frac{I_C}{V_T}$

$$r_e = \frac{V_T}{I_E} = \frac{\alpha}{g_m}$$