

Lecture 21: MOS Model and Common Emitter Amp

- Announcements:
- HW#7 online and due Friday via Gradescope
- Lab#5 online (this is your first project)
 - ↳ Due Tuesday, Nov. 12, 5 p.m.
- Graded Midterm coming back today


• Lecture Topics:

- ↳ T Model
- ↳ Pnp Transistor Hybrid- π Model
- ↳ Saturated NMOS Hybrid- π Model
- ↳ Example: Common Emitter Amplifier

• Last Time:

- Derived the BJT Hybrid- π Model
- Now, continue with models ...

Hybrid- π Model Summary (for npn BJT)

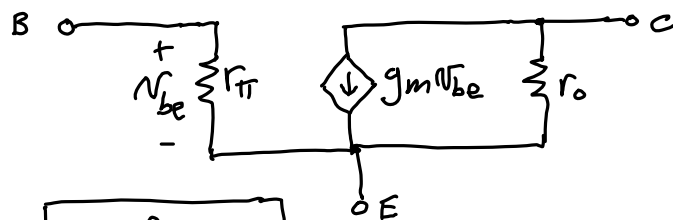

$$r_{\pi} = \frac{\beta}{g_m} = \frac{V_T}{I_B}$$


$$g_m = \frac{I_C}{V_T}$$

$$r_o = \frac{V_A}{I_C}$$

• Remarks:


- g_m is independent of device specifics, i.e., β , I_s
- Depends only on temperature (via V_T) and biasing (I_C)
- Small-signal model valid for $v_{be} \ll V_T$

What about emitter resistance?

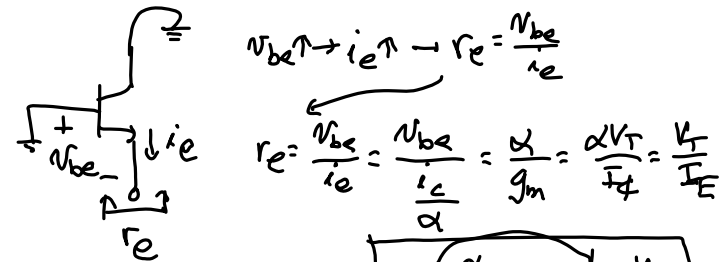

Why is this not included in the hybrid- π model?
 ↳ well... it is!
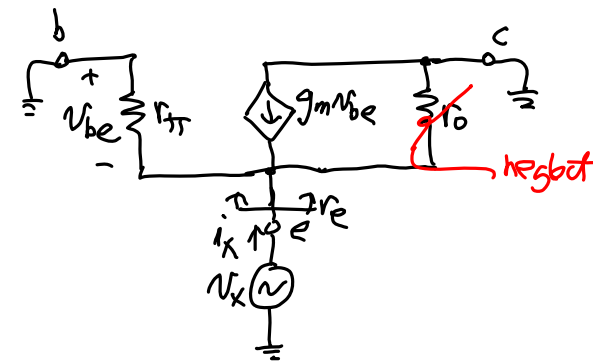
$$r_e = \frac{\alpha}{g_m} \approx \frac{1}{g_m} = \frac{V_T}{I_E}$$



$$i_x = -\frac{v_{be}}{r_{\pi}} - g_m v_{be}$$


$$(v_x = -v_{be}) \Rightarrow i_x = v_x \left(\frac{1}{r_{\pi}} + g_m \right)$$

$$r_e = \frac{v_x}{i_x} = \frac{1}{\frac{1}{r_{\pi}} + g_m} = \frac{r_{\pi}}{1 + g_m r_{\pi}} = \frac{r_{\pi}}{1 + \beta} = \frac{\beta}{g_m(1 + \beta)}$$

$$r_e = \frac{\alpha}{g_m} \quad \checkmark$$

- To explicitly show the emitter resistance in the small-signal model, use the T-model:


T-Model (Common Base Model)

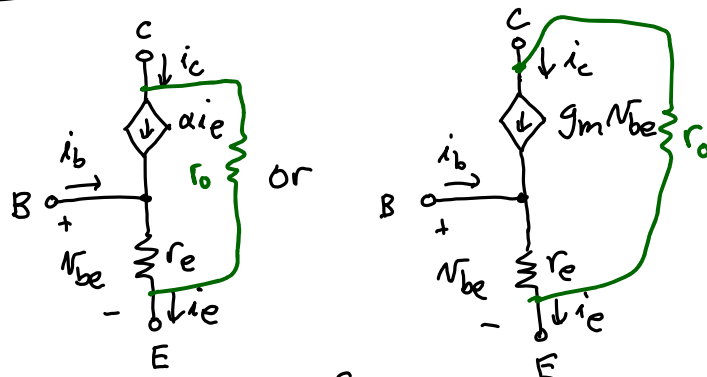

Where (as before): $g_m = \frac{I_C}{V_T}$
 $r_e = \frac{V_T}{I_E} = \frac{\alpha}{g_m}$


Small-Signal Models for Forward-Active pnp Xsistors

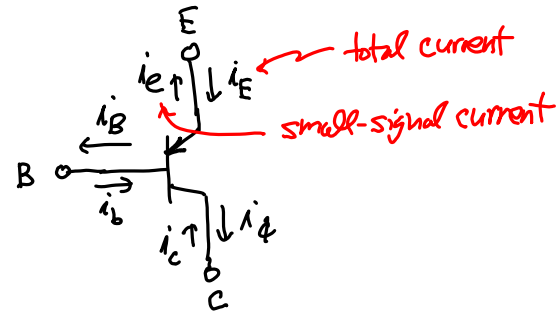- For pnp transistors, use the same small-signal models as npn with NO change in polarities




Hybrid-PI Model:

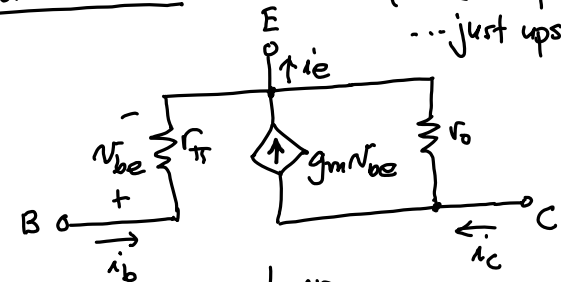(same as npn model
 ... just upside down)




or

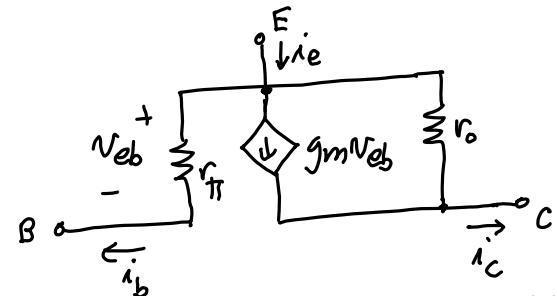

(again, same as npn model,
 but upside down)

T-Model:

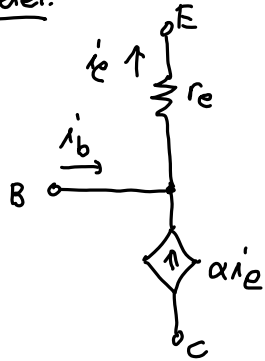

- Note that in the above small-signal models, the current directions are the same as used for npn, i.e., no change in polarities
- Large signal directions, however, are as before

Need Proof?

$$i_b = I_s \exp\left(\frac{V_{EB}}{V_T}\right)$$

$$I_c - i_c = I_s \exp\left(\frac{V_{EB} - V_{be}}{V_T}\right)$$

$$= I_s \exp\left(\frac{V_{EB}}{V_T}\right) \exp\left(-\frac{V_{be}}{V_T}\right) = I_b \exp\left(-\frac{V_{be}}{V_T}\right)$$


(2 terms of Taylor expansion) $\Rightarrow I_c - i_c = I_b \left(1 - \frac{V_{be}}{V_T}\right) = I_b - \frac{I_b}{V_T} V_{be}$

$$i_c = \frac{I_b}{V_T} V_{be} \quad \therefore g_m = \frac{i_c}{V_{be}} = \frac{I_b}{V_T}$$


(as with npn, and with the same directions as npn)

Small-Signal Model for Saturated NMOS Transistor

for analog applications

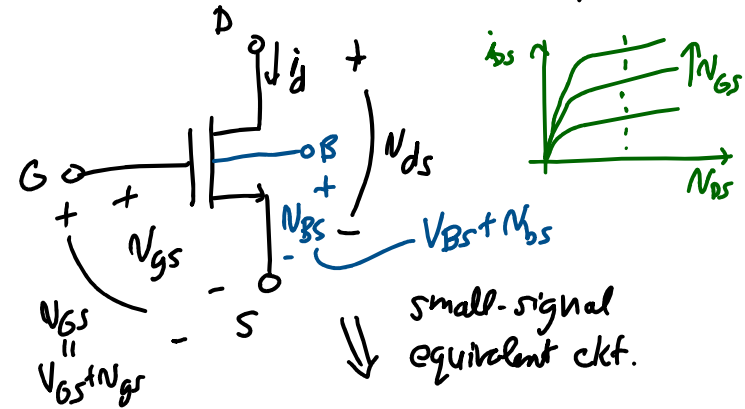

small-signal equivalent ckt.

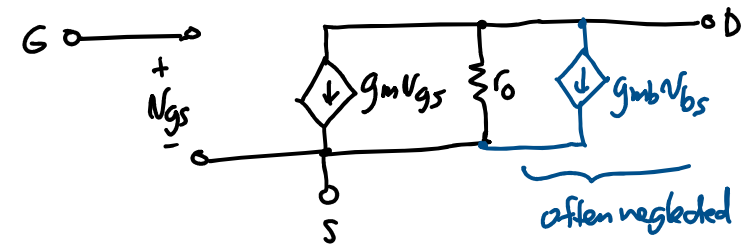

often neglected

Where:

$$g_m = \frac{i_d}{V_{gs}} = \left. \frac{\partial i_D}{\partial V_{GS}} \right|_{Q\text{-pt}} = \left. \frac{\partial}{\partial V_{GS}} \left(\frac{1}{2} \mu_n C_{ox} \frac{W}{L} (V_{GS} - V_{TH})^2 \right) \right|_{Q\text{-pt}}$$

still C_{ox} $\rightarrow \mu_n C_{ox} \frac{W}{L} (V_{GS} - V_{TH}) \Big|_{V_{GS} = V_{GS}}$

$$\therefore g_m = \mu_n C_{ox} \frac{W}{L} (V_{GS} - V_{TH}) = \sqrt{2 \mu_n C_{ox} \frac{W}{L} I_D}$$

$$I_D = \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (V_{GS} - V_{TH})^2$$

$$(V_{GS} - V_{TN}) = \sqrt{\frac{2I_D}{\mu_n C_{ox} \frac{W}{L}}} = V_{OV} \triangleq \text{Overdrive Voltage}$$

$$r_o = \frac{V_{ds}}{i_d} = \left[\frac{\partial i_D}{\partial v_{ds}} \Big|_{Q-pt} \right]^{-1}$$

$$= \left[\frac{\partial}{\partial v_{ds}} \left(\frac{1}{2} \mu_n C_{ox} \frac{W}{L} (V_{GS} - V_{TN})^2 (1 + \lambda v_{ds}) \right) \Big|_{Q-pt} \right]^{-1}$$

$$= \left[i_D \lambda \Big|_{i_D = I_D} \right]^{-1} = \left[\lambda I_D \right]^{-1}$$

$$\Rightarrow r_o = \frac{1}{\lambda I_D}$$


Threshold Voltage $V_t = f(V_{BS})$:

\Rightarrow gives rise to a Body Effect Transconductance:

$$g_{mb} = \frac{\partial i_D}{\partial v_{BS}} \Big|_{Q-pt} = \frac{g_m \gamma}{2\sqrt{2\phi_f + V_{SB}}} = g_{mb}$$

Procedure for Small-Signal Analysis

• (Common Emitter Example)

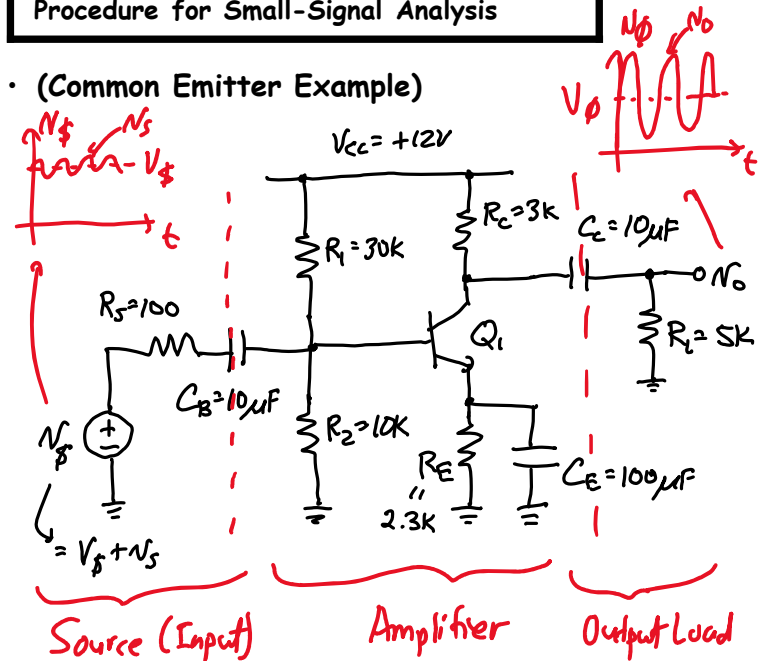

[Thevenin Equivalent]

For Q: $\beta = 100$, $V_A = 100V$

Find the voltage gain, $\frac{v_o}{v_s}$.

Draw the collector voltage waveform for

$$v_s = \underbrace{(0.014) \cos \omega t}_{\text{AC small-signal component}} + \underbrace{1V}_{\text{DC component}}$$

