

Lecture 24: High Frequency Small-Signal Models

• Announcements:

- HW#8 online and due Friday via Gradescope
- Lab#5 due Tuesday, Nov. 12, 5 p.m.


• Lecture Topics:

- ↳ Frequency Response
- ↳ High Frequency Model for BJT
- ↳ High Frequency Model for MOSFET

• Last Time:

- Finished Common Emitter Amplifier small-signal analysis example
- Now, start on Frequency Response ...

Frequency Response of Amplifiers

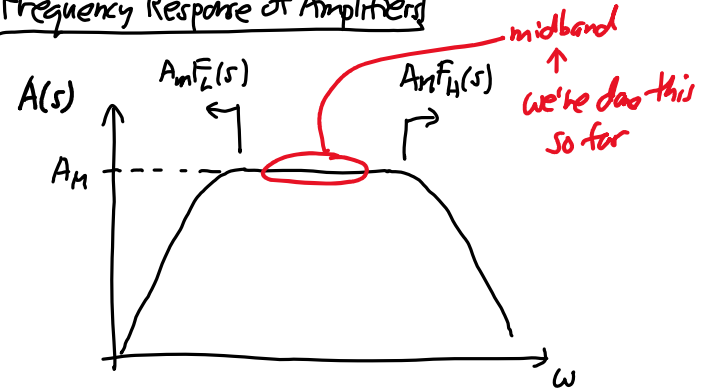

General Form: $A(s) = A_M F_L(s) F_H(s)$



Where $A_M =$ midband gain (constant ω freq.)

$F_L(s)$ models the low frequency behavior generally governed by coupling capacitors:

$$\left. \begin{array}{l} \text{For } \omega \rightarrow 0: F_L(s) \rightarrow 0 \\ \omega \rightarrow \infty: F_L(s) \rightarrow 1 \end{array} \right\} \text{It's a HPF}$$

$F_H(s)$ models the high frequency behavior governed by parasitic capacitors (often inside the transistor)
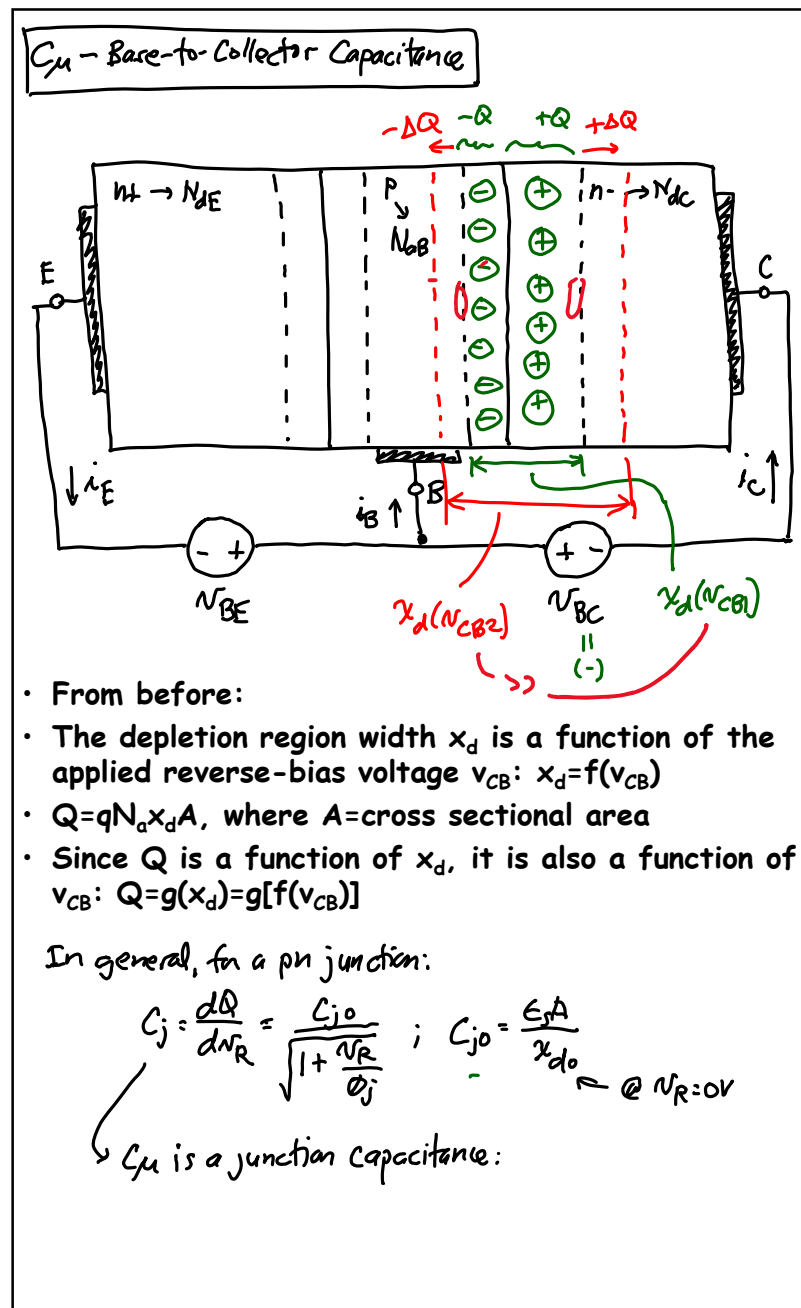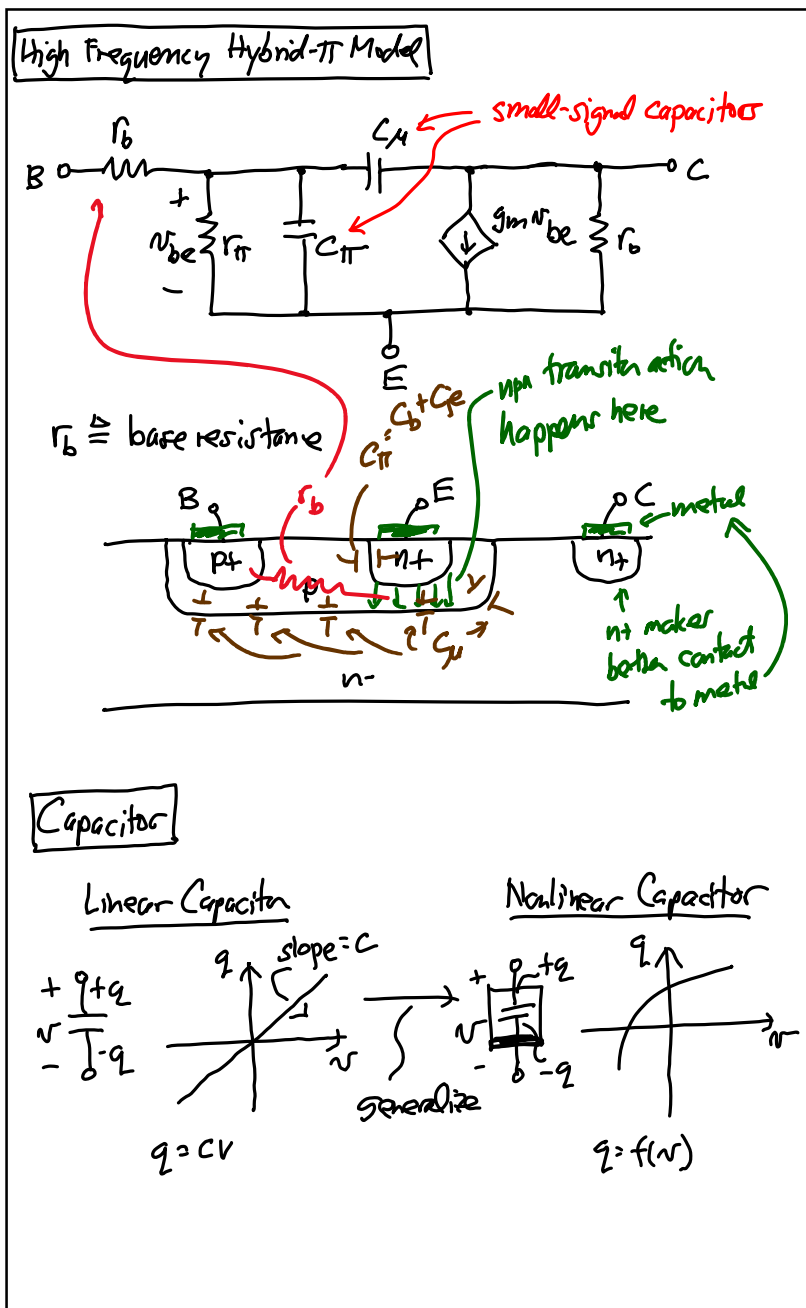
$$\left. \begin{array}{l} \text{For } \omega \rightarrow 0: F_H(s) \rightarrow 1 \\ \omega \rightarrow \infty: F_H(s) \rightarrow 0 \end{array} \right\} \text{It's a LPF}$$



$$C_{\mu} = \frac{C_{j0}}{\sqrt{1 + \frac{V_{CB}}{\phi_j}}} \quad (\text{for an abrupt junction})$$

Where C_{j0} = capacitance for $V_{CB} = 0V$

ϕ_j = built-in potential between p & n type semiconductors

$$= \frac{kT}{q} \ln \left(\frac{N_A N_D}{n_i^2} \right); \quad n_i = 1.45 \times 10^{10} \text{ cm}^{-3}$$

More generally: $C_{\mu} = \frac{C_{j0}}{\left(1 + \frac{V_{CB}}{\phi_j}\right)^m}$; $m = \text{fcn of junction interface}$
 (CJC in SPICE, MJC in SPICE)
 (VJC in SPICE)
 We assume this $\rightarrow (= \frac{1}{2} \text{ for abrupt})$

C_{π} — Base-to-Emitter Capacitance

\Rightarrow two components comprise C_{π} :

- ① Junction capacitance, C_{je}
- ② Diffusion capacitance, C_b

The diagram shows a BJT cross-section with emitter (N⁺), base (P), and collector (n⁻) regions. It illustrates the injection of electrons (e⁻) from the emitter into the base, and the resulting charge storage (Q) in the base. The diagram also shows a circuit model with current sources i_E , i_B , and i_C , and capacitors C_{BE} and C_{BC} .

Junction Capacitance:
 $C_{je} = \frac{C_{je0}}{\sqrt{1 + \frac{V_{EB}}{\phi_{je}}}}$
 (CJE in SPICE, VJE in SPICE)
 Forward Bias: C_{je} is significant

Diffusion Capacitance:
 \Rightarrow define base transit time: average time a carrier takes to cross the base
 $\tau_F = \frac{Q}{I_C}$ — think of I_C as the rate of transfer of charge through the base
 $Q = \tau_F I_C$
 $\Delta Q = \tau_F \Delta I_C$

⇒ switch to small-signal parameters:

$q = I_F i_c$ small-signal variable → "dq" = q

$$C_b = \frac{q}{V_{be}} = I_F \frac{I_c}{V_{be}} = I_F g_m = I_F \frac{I_F}{V_T} = C_b$$

$\frac{dq_c}{dV_{be}}$


∴ $C_b \propto I_F$

Putting it all together:


$$C_{\pi} = C_b + C_{je} = I_F g_m + \frac{C_{je0}}{\sqrt{1 + \frac{V_{EB}}{\phi_{je}}}}$$

Determining C_{π} and C_{μ}

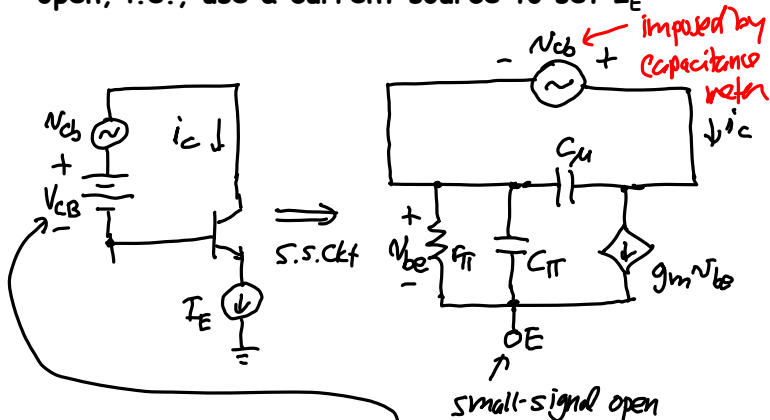- Can experimentally determine C_{μ} by measuring the small-signal capacitance between the base and collector terminals with the emitter incrementally open, i.e., use a current source to set I_E




⇒ can measure C_{μ} vs. V_{CB}

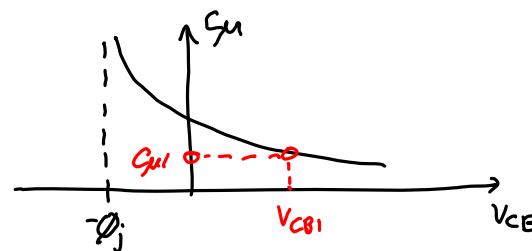

- To find C_{π} , find an expression for C_{π} in terms of C_{μ} and known measurable parameters
- One parameter we can conveniently measure is the short-circuit current gain:

$$h_{fe} = \frac{i_c}{i_b} \Big|_{N_c=0}$$

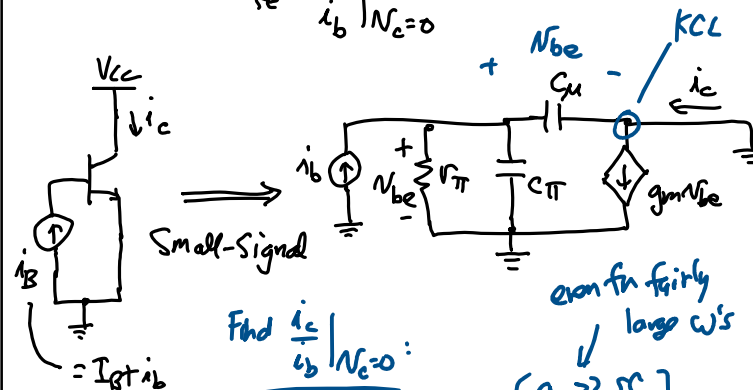

even for fairly large ω 's
[$g_m \gg s C_{\mu}$]

$$N_{be} = i_b \left(r_{\pi} \parallel \frac{1}{s C_{\pi}} \parallel \frac{1}{s C_{\mu}} \right)$$

$$i_c = g_m N_{be} - s C_{\mu} N_{be} = (g_m - s C_{\mu}) N_{be} \approx g_m N_{be}$$


$$i_c = g_m \left(r_{\pi} \parallel \frac{1}{s C_{\pi}} \parallel \frac{1}{s C_{\mu}} \right) i_b$$

$$\frac{i_c}{i_b} = \frac{g_m}{\frac{1}{r_\pi} + s(C_\pi + C_\mu)} = \frac{g_m r_\pi}{1 + s r_\pi (C_\pi + C_\mu)} = \frac{\beta_0}{1 + s r_\pi (C_\pi + C_\mu)}$$

[$\beta_0 = g_m r_\pi \rightarrow$ low freq β]

$$\beta(j\omega) = \frac{\beta_0}{1 + \frac{j\omega}{\omega_\beta}}, \text{ where } \omega_\beta = \frac{1}{r_\pi (C_\pi + C_\mu)}$$

Plot $|\beta(j\omega)|$: (Bode plot)

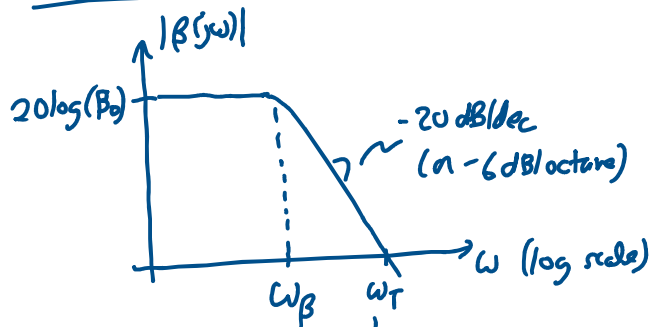

Δ defined as the radian frequency where $|\beta(j\omega)| = 1$

$$|\beta(j\omega_T)| \approx \frac{\beta_0}{\omega_T r_\pi (C_\pi + C_\mu)} = 1$$

$$\omega_T = \frac{g_m}{C_\pi + C_\mu}$$

$$\Rightarrow f_T = \frac{\omega_T}{2\pi}$$

Figure of Merit for the

freq. performance of a Xsistor

*

$$C_\pi = \frac{g_m}{\omega_T} - C_\mu$$

(to determine C_π from measurable parameter)