

Lecture 26: Low Frequency Circuit Analysis

• Announcements:

- HW#8 online and due Friday via Gradescope
- Lab#5 due Tuesday, Nov. 12, 5 p.m.
- Hopefully, you watched Monday's video lecture



• Lecture Topics:

- ↳ Short Circuit Time Constant (SCTC) Analysis
- ↳ Intro. to Inspection Analysis
- ↳ C.E. Design Project Hints


• Last Time:

- Finished OCTC analysis for high frequency

C.E. High Freq. Analysis Using OCTC

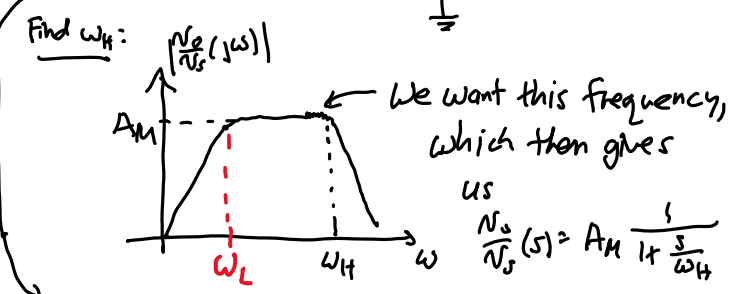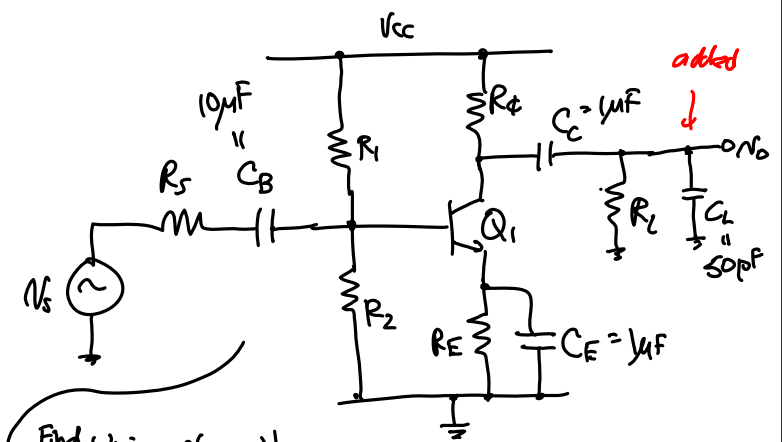


Small Signal Ckt.

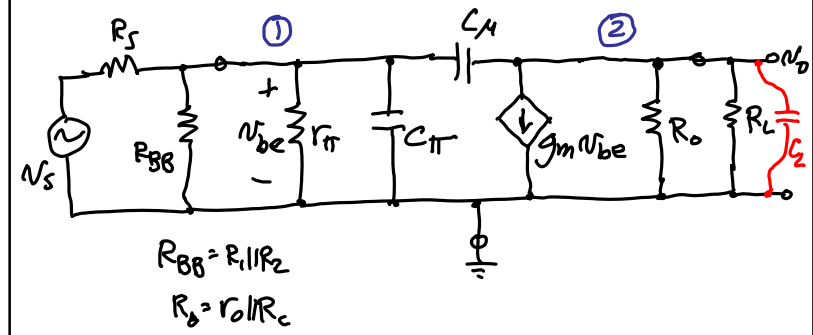

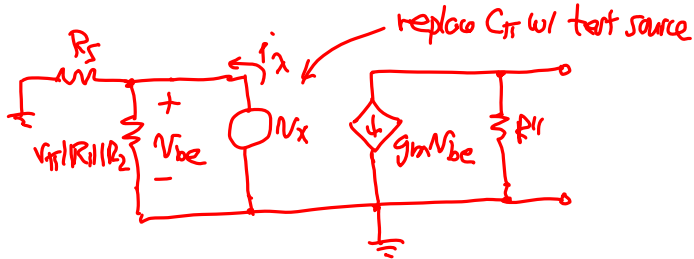(a) Determine  $\tau_{\pi} = C_{\pi} R_{\pi}$

$\Rightarrow$  open ckt. all C's, zero out all sources, and determine the driving point impedance,  $R_{\pi}$ :




$$R_{\pi} = \frac{V_x}{i_x} = R_1 || R_2 || R_5 = R' \quad (\text{by inspection})$$

$$\therefore \tau_{\pi} = C_{\pi} R'$$

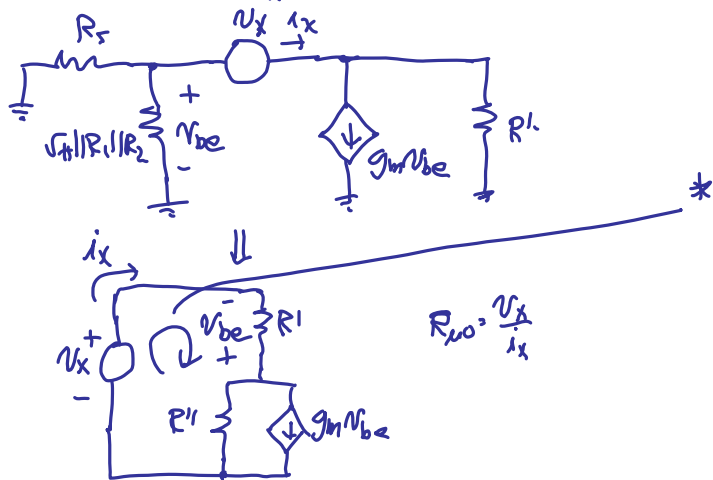(b) Determine  $\tau_{\mu} = C_{\mu} R_{\mu}$ :

$\Rightarrow$  need  $R_{\mu}$ : replace  $C_{\mu}$  w/ test source



$$R_{\mu} = \frac{V_x}{i_x}$$


\* KVL:  $V_x = i_x R' + R''(i_x - g_m V_{be})$

$[V_{be} = -i_x R'] \rightarrow V_x = i_x R' + R''(i_x + i_x R' g_m)$

$$\therefore R_{\mu} = \frac{V_x}{i_x} = R' + R'' + g_m R' R''$$

$$\therefore \tau_{\mu} = C_{\mu} (R' + R'' + g_m R' R'')$$

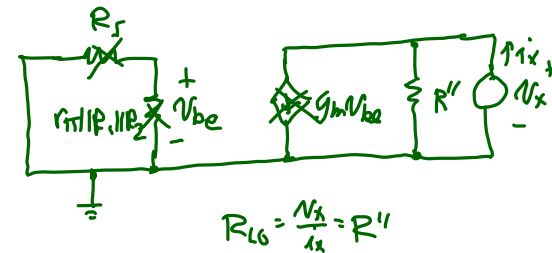(c) Determine  $\tau_{L0} = C_L R_{L0}$ :



$$R_{L0} = \frac{V_x}{i_x} = R''$$

$$\therefore \tau_{L0} = C_L R''$$


Thus:

$$\omega_H = \frac{1}{\sum_j \tau_{j0}} = \frac{1}{C_{\pi} R' + C_{\mu} (R' + R'' + g_m R' R'') + C_L R''}$$

=

Low Freq. Amplifier Response Using Short-Circuit Time Constant Analysis (SCTC)

Recall:

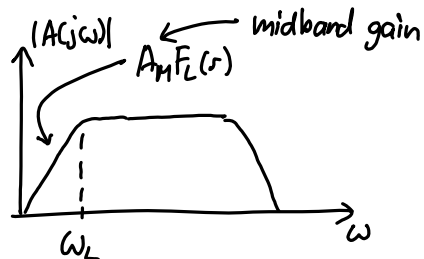

In general, for the low freq. response:

$$F_L(s) = \frac{s^{n_z} + d_1 s^{(n_z-1)} + \dots}{s^{n_p} + e_1 s^{(n_p-1)} + \dots}, \quad n_z = \# \text{ poles} = \# \text{ zeros}$$

We can express the coefficient  $e_1$  by:

$$e_1 = \omega_{p1} + \omega_{p2} + \dots + \omega_{pn}$$

For the case of a dominant pole:

↳ i.e., the highest freq. pole

$$F_L(s) \approx \frac{s}{s + \omega_L} = \frac{s}{s + e_1} \rightarrow e_1 \approx \omega_{p1} = \omega_L$$

$$\omega_L \approx e_1 = \sum_j \omega_{pj} = \sum_j \frac{1}{C_j R_{j,s}} = \sum_j \frac{1}{\tau_{j,s}}$$

where  $C_j \triangleq$  various large ( $> 10 \text{ nF}$ ) capacitors in the ckt. (e.g., the bypass caps.)

$R_{j,s} \triangleq$  driving point resistance seen between the terminals of  $C_j$  determined with:

For readability, can go to Sedra & Smith


- all large capacitors short-circuited, except  $C_j$ , which is replaced by the test voltage source for  $R$  determination

- all independent sources eliminated (i.e., short voltage sources, open current sources)
- open all H.F. capacitors (i.e., small caps in the pF range, or  $< 1 \text{ nF}$ )


Again, for the case where there are no dominant poles, a reasonable approximation is:

$$\omega_L \approx \sqrt{\omega_{p1}^2 + \omega_{p2}^2 - 2\omega_{z1}^2 - 2\omega_{z2}^2}$$

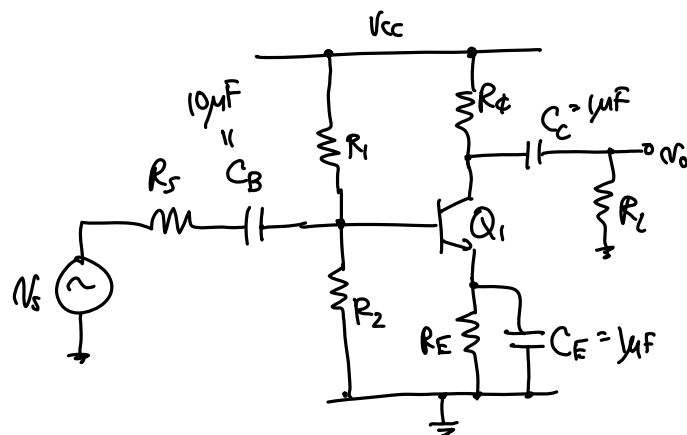Ex: Determine the L.F. response of the C.E. Amplifier



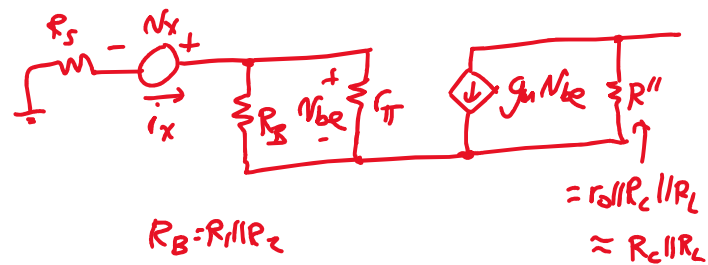(a)  $C_B$ : short ckt.  $C_E$  &  $C_C$ , then determine  $R_{B,s}$



$$R_B = R_1 || R_2$$

$$= r_s || R_C || R_L \approx R_C || R_L$$

(b)  $C_B$ : Short ckt.  $C_B$  &  $C_E$ , then determine  $R_{CS}$  & zero out  $N_S$

$R_{CS} = R_L + r_o || R_C \approx R_L + R_C$  [  $r_o \gg R_C$  ]  $\omega_{p2}$

$\tau_{CS} = C_C (R_L + R_C) \rightarrow \omega_{CS} = \frac{1}{\tau_{CS}} = \frac{1}{C_C (R_L + R_C)}$

(c)  $C_E$ : short  $C_B$  &  $C_C$ ; zero out  $N_S$ ; determine  $R_{ES}$

$R_{ES} = R_E || R_e$  (neglect  $r_o$  assuming  $r_o \gg R_C$ )

$R_e = \frac{-r_{\pi} N_x}{\beta + 1}$

$i_x = \frac{N_x}{r_{\pi} + (R_S || R_B)} - g_m N_{be} = N_x \left( \frac{1}{r_{\pi} + (R_S || R_B)} + \frac{g_m r_{\pi}}{r_{\pi} + (R_S || R_B)} \right)$

$R_e = \frac{N_x}{i_x} = \frac{r_{\pi} + (R_S || R_B)}{\beta + 1}$   $\omega_{p3}$

$R_{ES} = R_E || R_e = R_E || \frac{r_{\pi} + (R_S || R_B)}{\beta + 1}$   $\omega_{p3}$

$\tau_{ES} = C_E \left( R_E || \frac{r_{\pi} + (R_S || R_B)}{\beta + 1} \right) \rightarrow \omega_{ES} = \frac{1}{C_E \left( R_E || \frac{r_{\pi} + (R_S || R_B)}{\beta + 1} \right)}$


$\omega_c \approx \sum_j \frac{1}{\tau_j} = \sum_j \omega_{pj}$

**Summarize:**

- Which capacitors to use for OCTC? Which for SCTC?
- Separate caps into two categories:
  - ↳ Large caps  $\rightarrow C_{Lj}$ 's
  - ↳ Small caps  $\rightarrow C_{Sj}$ 's



Determined by large caps  $C_{Lj}$ 's

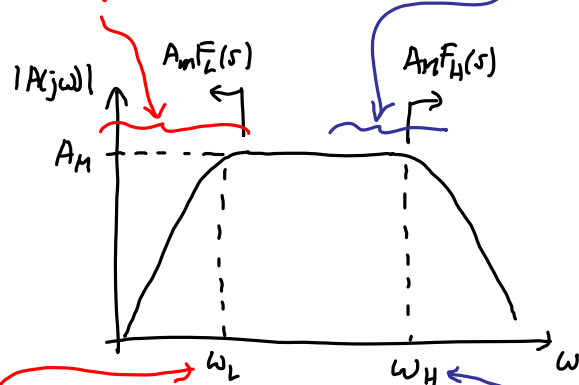Shape determined by small caps  $C_{Sj}$ 's



- Find using SCTC
  - ↳ Get time constants using capacitors that contribute to low frequency poles and zeros, which generally means bypass or coupling caps
  - ↳ Open smaller capacitors (e.g., hybrid- $\pi$  ones)
  - ↳ Use  $C_{Lj}$ 's; open  $C_{Sj}$ 's
- Find using OCTC
  - ↳ Get time constants using capacitors that contribute high freq. poles & zeros, which generally means hybrid- $\pi$  or any small caps
  - ↳ Short larger caps (e.g., bypass or coupling capacitors)
  - ↳ Use  $C_{Sj}$ 's; short  $C_{Lj}$ 's

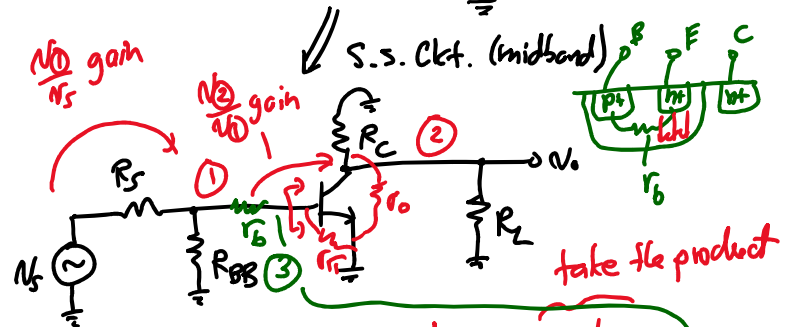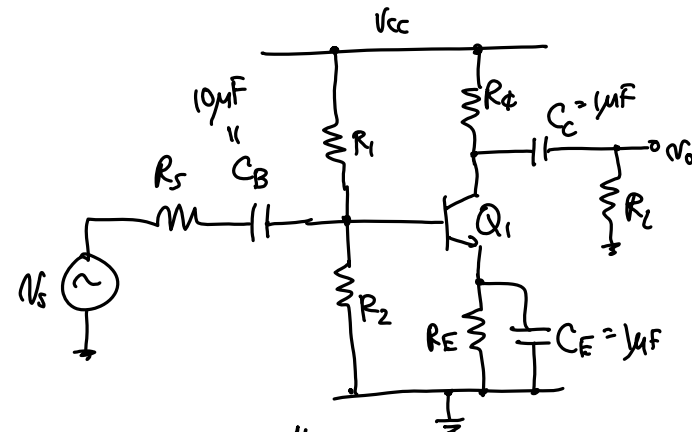Intro. to Inspection Analysis (w) Lab #5 hints



*No gain*  $\frac{N_O}{N_S}$

*No gain*  $\frac{N_O}{N_S}$


*take the product*

$\Rightarrow$  get gains from node to node, then combine

$\Rightarrow$  account for load variation for each gain calculation for each stage

*might need to account for  $r_o$  in your lab*

1st Stage:

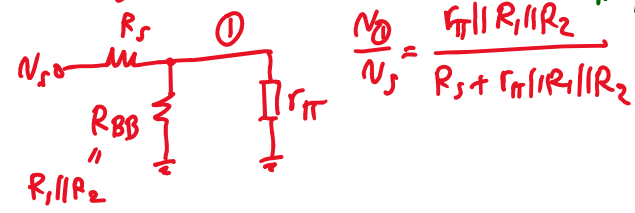

$$\frac{N_O}{N_S} = \frac{r_{\pi} \parallel R_C \parallel R_L}{R_S + r_{\pi} \parallel R_C \parallel R_L}$$

2<sup>nd</sup> Stage:

$$R'' = r_o \parallel R_C \parallel R_L$$

$$\frac{N_2}{N_D} = \frac{N_0}{N_D} = -g_m R'' = -g_m (r_o \parallel R_C \parallel R_L)$$

from memory

$r_o = \text{large}$

$$-g_m (R_C \parallel R_L)$$

$$\frac{N_0}{N_5} = \frac{N_D}{N_5} \cdot \frac{N_0}{N_D} = -\frac{r_{\pi} \parallel R_1 \parallel R_2}{R_5 + r_{\pi} \parallel R_1 \parallel R_2} g_m (R_C \parallel R_L)$$