

Lecture 27: Inspection Analysis & Miller Effect

• Announcements:

- HW#9 online and due Friday via Gradescope
- Lab#5 due Tuesday, Nov. 12, 5 p.m.



• Lecture Topics:

- ↳ Intro. to Inspection Analysis
- ↳ C.E. Design Project Hints
- ↳ Other Amplifier Configurations
- ↳ Generally-Loaded Transistor

• Last Time:


- Started introduction to inspection analysis
- Now continue with this ...

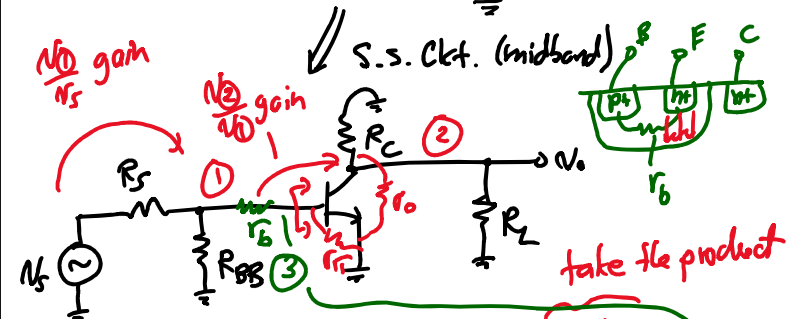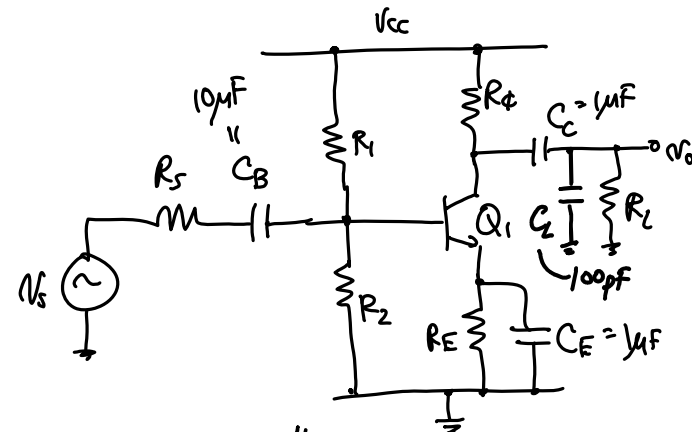Intro. to Inspection Analysis (w/ Lab#5 hints)





⇒ get gains from node to node, then combine
 ⇒ account for load resistance for each gain calculation for each stage
 take the product
 might need to account for r_0 in your lab

1st Stage:

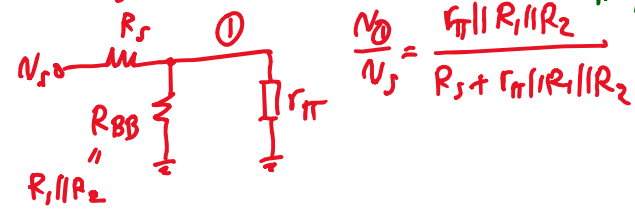
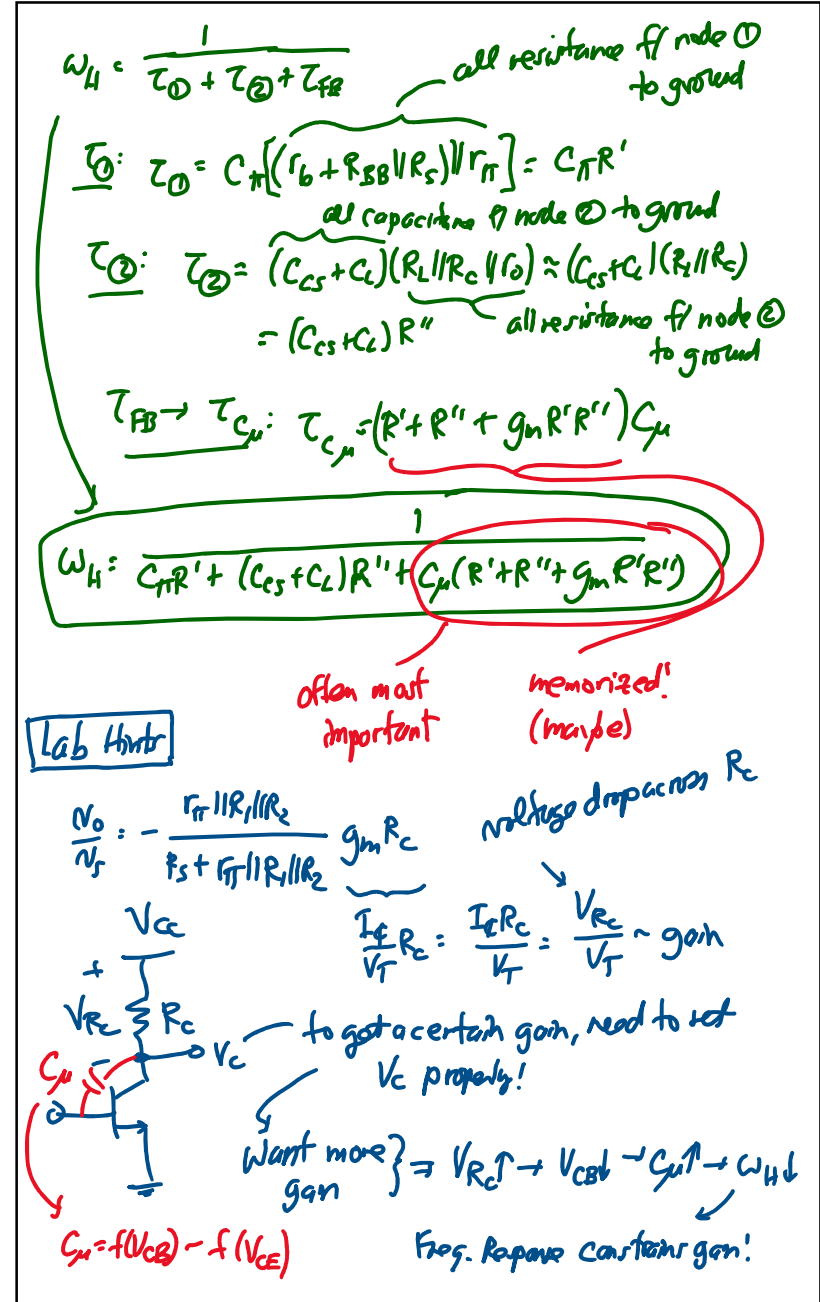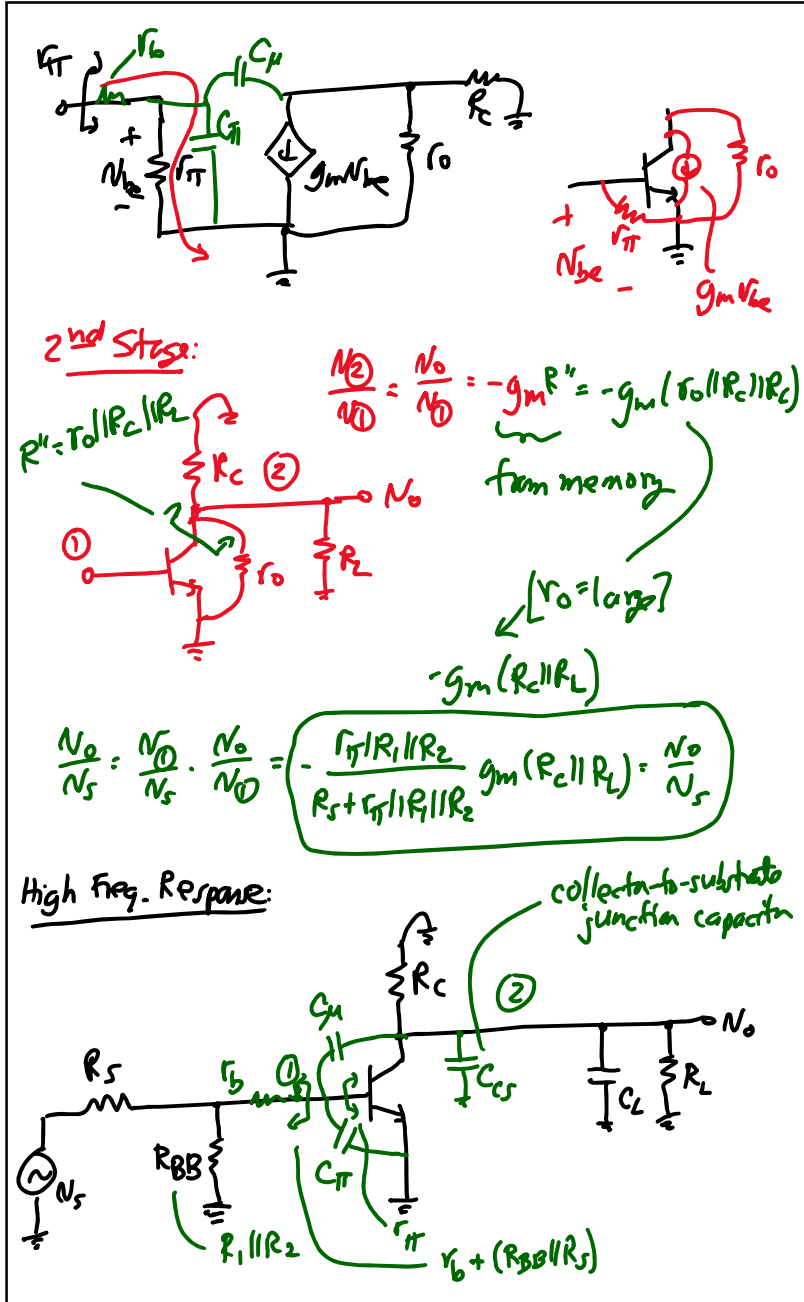
$$\frac{V_0}{V_s} = \frac{r_{\pi} \parallel R_1 \parallel R_2}{R_s + r_{\pi} \parallel R_1 \parallel R_2}$$



Output Swings:

to avoid clipping

nonlinear clipping

must stay higher than $V_{CE(sat)} = 0.2V$ for the transistor to stay in forward active, i.e., to avoid saturation!

stays @ V_E

$N_E = V_E + V_C = V_E$

0 \rightarrow because of $C_E \rightarrow$ S.S. AC ckt.

no AC amplitude

The Miller Effect

\Rightarrow useful to transform a ckt. w/ feedback into a simpler ckt. w/o feedback

Formal Derivation: $K = \text{gain}$

Miller transformation \Rightarrow

Find Y_1 :

(original)

$$i_1 = Y(N_1 - N_2)$$

$$= Y(N_1 - KN_1)$$

$$= Y(1-K)N_1$$

(Miller)

$$i_1 = Y_1 N_1$$

$Y_1 = Y(1-K)$

Find Y_2 :

(original)

$$i_2 = (N_2 - N_1)Y$$

$$= (N_2 - \frac{1}{K}N_2)Y = (1 - \frac{1}{K})Y N_2$$

(Miller)


$$i_2 = Y_2 N_2$$

$Y_2 = Y(1 - \frac{1}{K})$

$[N_1 = \frac{1}{K}N_2]$

\Rightarrow no longer have FB \rightarrow easy...

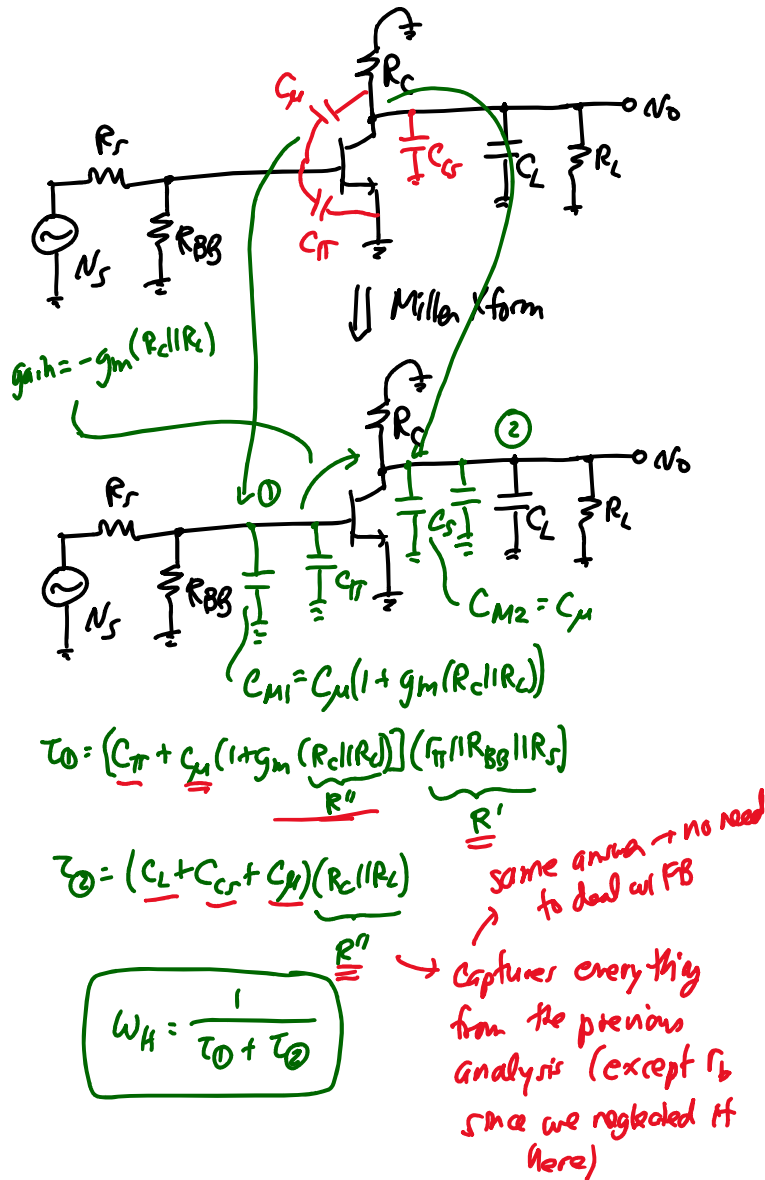C.F. Inspection Analysis for HF Using the Miller Effect



Other Popular Amplifier Configurations

- By merely altering the placements of input/output signals and bypass/coupling capacitors, one can realize other amplifier configurations
- Some examples:

