

Lecture 28: Generally Loaded Transistor

- Announcements:
- HW#9 online and due Friday via Gradescope
- Lab#5 due Tuesday, Nov. 12, 5 p.m.
- Midterm 2 coming up in about 2 weeks
 - ↳ Friday next week, Nov. 15, @ 7 p.m., in 160 Kroeber Hall
 - ↳ More info this coming Friday
 - ↳ Review Session will likely be Tuesday, 6-8 p.m., next week

 • Lecture Topics:


- ↳ Other Amplifier Configurations
- ↳ Generally-Loaded Transistor

 • Last Time:


- Introduced inspection analysis and Miller effect
- Now provide the knowledge needed to properly inspect analyze general circuits



Other Popular Amplifier Configurations

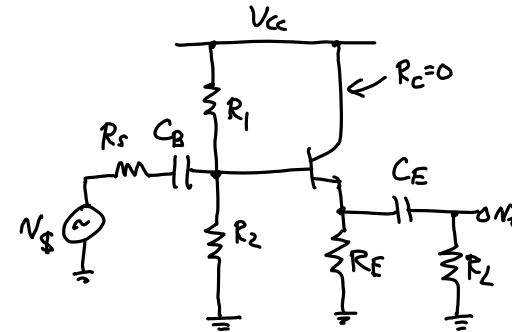- By merely altering the placements of input/output signals and bypass/coupling capacitors, one can realize other amplifier configurations
- Some examples:



↓ s.s. det.

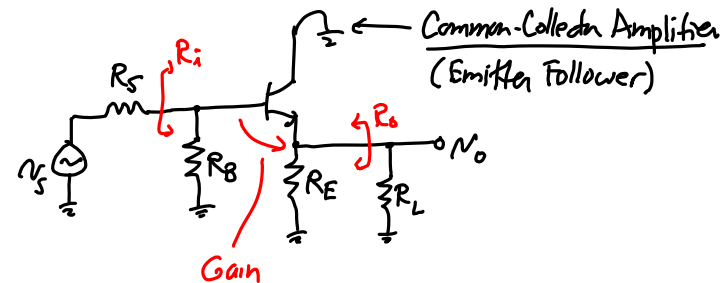

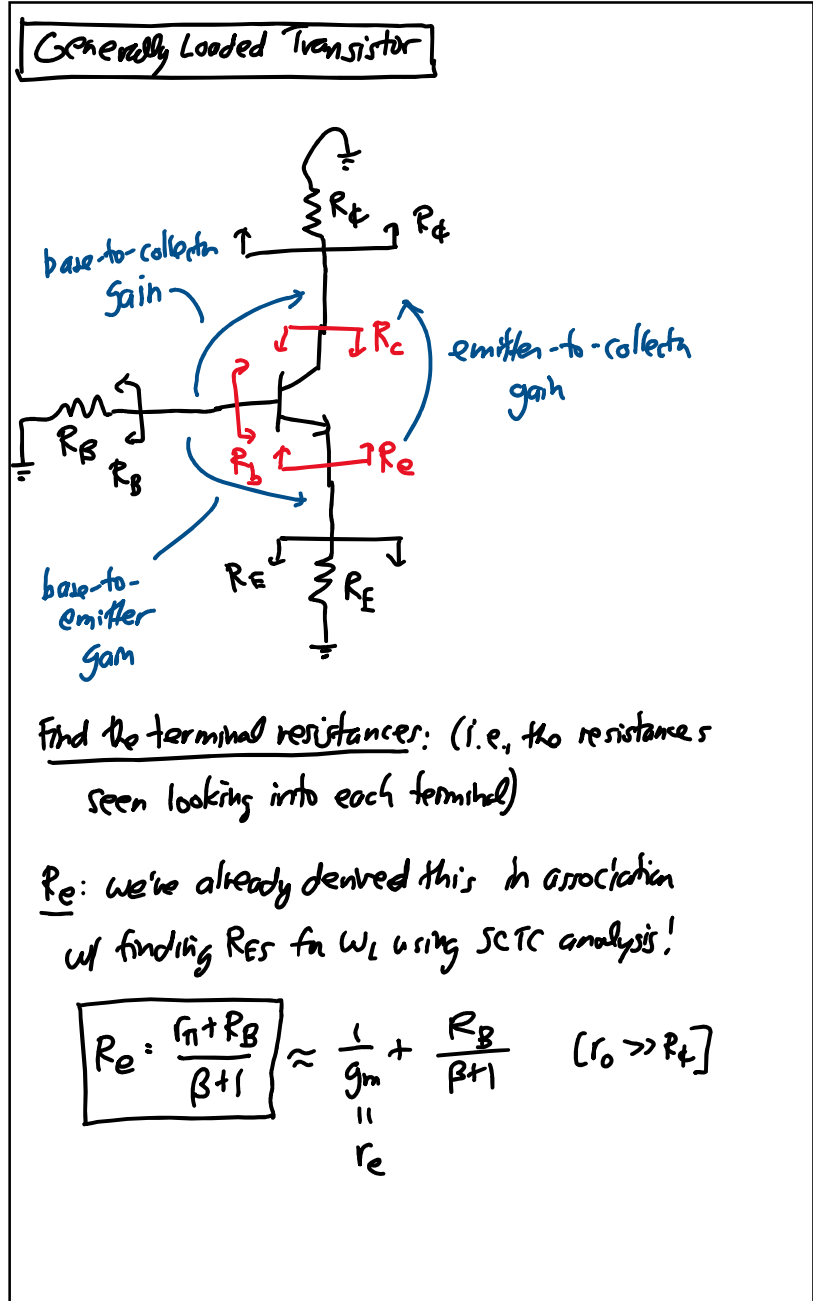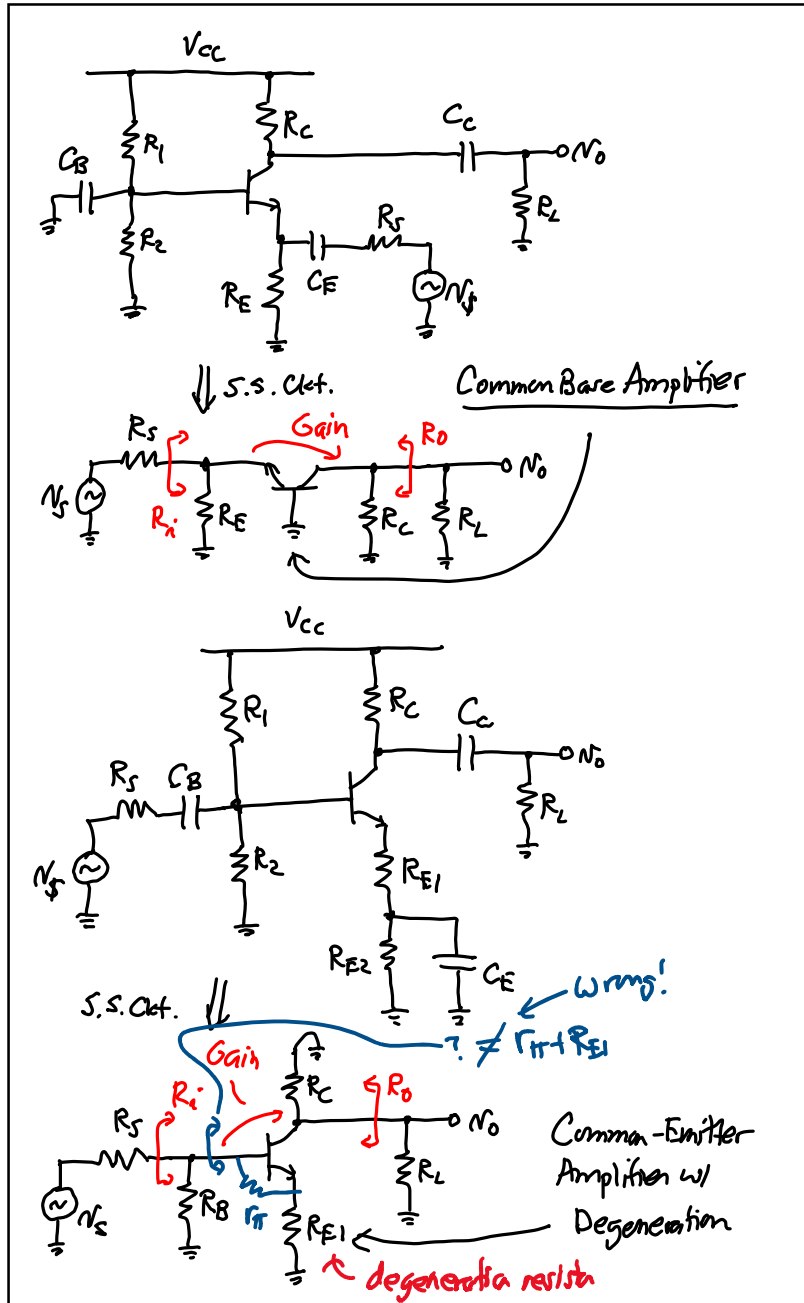

R_b :

neglect, since r_o is large

KVL: $v_x = v_{be} + v_e$

$v_{be} = i_x r_{\pi}$

$v_e = (i_x + g_m v_{be}) R_E = i_x (1 + g_m r_{\pi}) R_E$

$v_x = i_x r_{\pi} + i_x (1 + g_m r_{\pi}) R_E$

$= i_x (r_{\pi} + (\beta + 1) R_E)$ *typ. $\sim 2.5k\Omega$ $\sim 4k\Omega$*

$R_b = \frac{v_x}{i_x} = r_{\pi} + (\beta + 1) R_E \approx r_{\pi} (1 + g_m R_E)$

$\approx \checkmark [\beta = g_m r_{\pi} \gg 1]$

$v_x = i_x r_{\pi} + (\beta + 1) i_x R_E$

$R_b = \frac{v_x}{i_x} = r_{\pi} + (\beta + 1) R_E$

This comes from amplification of $i_b \rightarrow i_c$ following the currents

T-Model:

$\alpha i_e = \beta i_b = \beta i_x$

$v_x = (\beta + 1) i_x (r_e + R_E)$

$R_b = \frac{v_x}{i_x} = (\beta + 1) (r_e + R_E)$

$= (\beta + 1) (\frac{1}{g_m} + R_E)$

Yet another form of the same R_b equation

Find R_c : (note that R_B can influence, so include in analysis)

KVL: $v_x = r_o (i_x - g_m v_{be}) + v_e$

[Usually, for cases that matter, $R_E \ll R_B + r_{\pi}$]
 for this class
 \therefore most of i_x flow thru R_E
 $\therefore v_e \approx i_x R_E$

$$i_{\pi} = -\frac{v_e}{r_{\pi} + R_B} = -\frac{i_x R_E}{r_{\pi} + R_B}$$


$$\therefore v_{be} = -\frac{i_x r_{\pi} R_E}{r_{\pi} + R_B}$$

*
$$v_{ix} = i_x \left(1 + \frac{g_m r_{\pi} R_E}{r_{\pi} + R_B}\right) r_o + i_x R_E$$

$$\therefore R_c = \frac{v_{ix}}{i_x} = r_o \left(1 + \frac{g_m R_E}{1 + (R_B/r_{\pi})}\right) + R_E$$

$$\therefore R_c \approx r_o \left(1 + \frac{g_m R_E}{1 + (R_B/r_{\pi})}\right) \approx r_o (1 + g_m R_E)$$

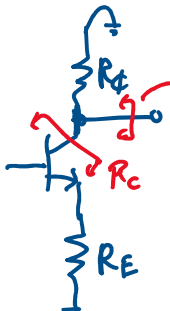
$(r_{\pi} \gg R_B)$ even bigger than r_o !



$R_o = R_E \parallel R_c \approx R_E$
 huge


Remarks:

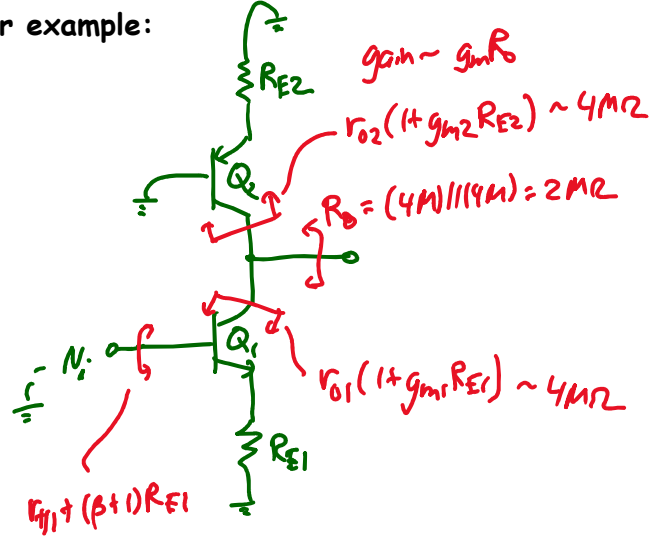- $R_c \sim (1 + (0.04)(1k))(100k\Omega) \sim 4.1M\Omega$ (this is huge)
- Rarely use R_c in discrete circuits, since it is generally much larger than R_c
- In integrated circuits, however, the loading can be very large, especially if it comes from another transistor
- For example:




$g_m \sim g_m R_o$
 $r_{o2}(1 + g_{m2} R_{E2}) \sim 4M\Omega$
 $R_B = (4M\Omega \parallel 19M\Omega) = 2M\Omega$
 $r_{o1}(1 + g_{m1} R_{E1}) \sim 4M\Omega$
 $r_{\pi 1} + (\beta + 1)R_{E1}$

Base-to-Collector Gain

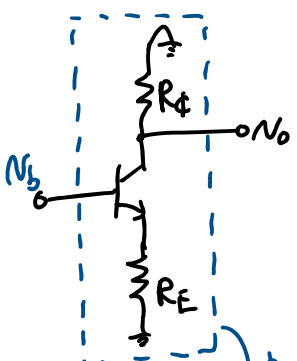

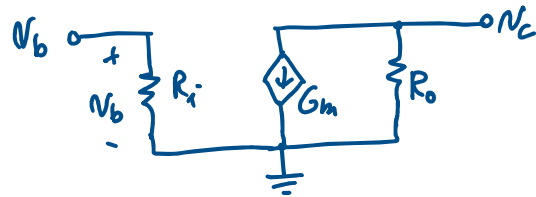* Convert to an "equivalent system" y-parameter model:



$$\frac{V_c}{V_b} = -G_m R_o$$

$\leftarrow \kappa ?$

All we need is $G_m \triangleq$ short ckt. transconductance

$$G_m = \left. \frac{i_c}{V_b} \right|_{V_c=0}$$