

**Lecture 29: Transistor Terminal Gains**


- **Announcements:**
- HW#9 online and due Friday via Gradescope
- Lab#5 due Tuesday, Nov. 12, 5 p.m.
  - ↳ If you are using excel or matlab to compute equations for Lab#5 → you will regret doing this when taking midterm 2
  - ↳ You need to design by hand at least 3 times before going to a computer
  - ↳ This is the only way to get familiar with the process
  - ↳ You cannot see the trade-offs without analyzing by hand
  - ↳ You need to put the work in to be able to recognize things
- Midterm 2 coming up in about 2 weeks
  - ↳ Friday next week, Nov. 15, @ 7 p.m., in 160 Kroeber Hall
  - ↳ Review Session will be next Tuesday, 6-8 p.m., in 400 Cory

-----  
 • **Lecture Topics:**

- ↳ **Generally-Loaded Transistor**
  - Terminal Resistances
  - Terminal-to-Terminal Gains
  - Inspection Analysis Sheet
  - Examples

-----  
 • **Last Time:**

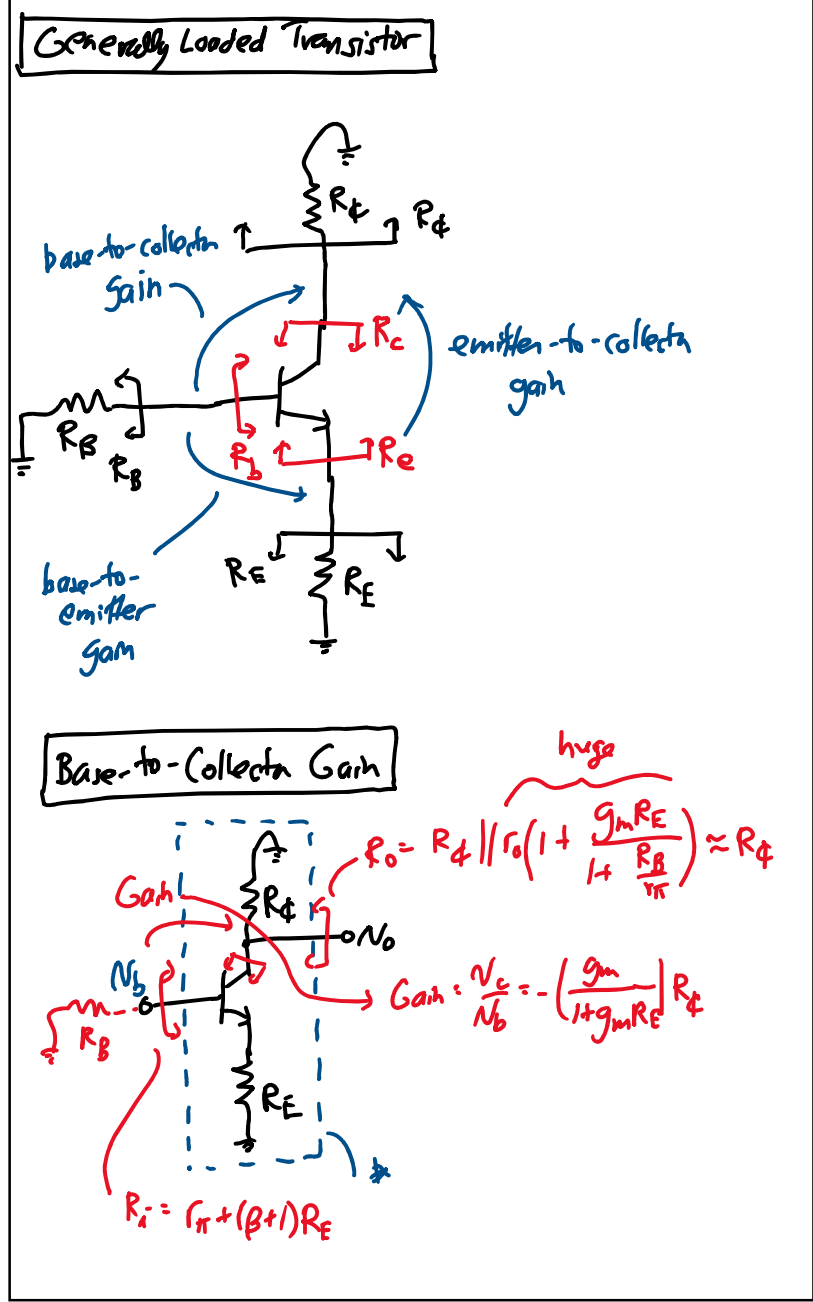- In the midst of getting terminal-to-terminal gains
- Now, continue with this ...



\* Convert to an "equivalent system" y-parameter model:

$$\frac{N_c}{N_b} = -G_m R_o$$

All we need is  $G_m \triangleq$  short ckt. transconductance

$$G_m = \frac{i_c}{N_b} \Big|_{N_c=0}$$

$$N_c = \left( \frac{N_{be}}{r_{\pi}} + g_m N_{be} \right) R_E = N_{be} \left( \frac{1}{r_{\pi}} + g_m \right) R_E$$

KVL:  $N_b = N_{be} + N_e = N_{be} \left( 1 + \left( \frac{1}{r_{\pi}} + g_m \right) R_E \right)$

$$G_m = \frac{i_c}{N_b} \Big|_{N_c=0} = \frac{g_m N_{be}}{N_b \left( 1 + \left( \frac{1}{r_{\pi}} + g_m \right) R_E \right)}$$

$\frac{1}{r_{\pi}} \ll g_m$

$$G_m = \frac{g_m}{1 + g_m R_E}$$

$$Gain = \frac{N_c}{N_b} = -G_m R_o$$

$$G_m = \frac{g_m}{1 + g_m R_E} = \frac{g_m}{1 + \frac{R_E}{r_e}}$$

**Base-to-Emitter Gain**

$R_i = r_{\pi} + (\beta + 1) R_E$


Voltage divider!

**Voltage Divider:** ( $r_o \gg R_E$ )  $\leftarrow KR$

$$\frac{N_e}{N_b} \approx \frac{R_E \parallel r_o}{r_e + R_E \parallel r_o} \approx \frac{R_E}{r_e + R_E} = \frac{g_m R_E}{1 + g_m R_E} \approx 1$$

$\frac{\alpha}{g_m} \approx \frac{1}{g_m} \approx 25 \Omega$   
[ $I_c = 1 \text{ mA}$ ]  $\therefore$  call this a "Voltage follower"

**Emitter-to-Collectn  $G_m$**

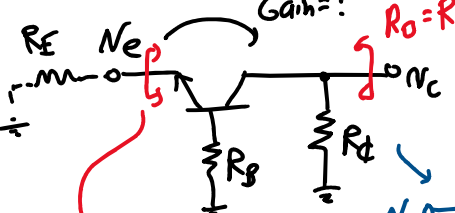


$R_o = R_L \parallel r_o \left(1 + \frac{g_m R_E}{1 + \frac{R_E}{r_e}}\right) \approx R_L$

$R_i = \frac{r_{\pi} + R_B}{\beta + 1} = \frac{1}{g_m} + \frac{R_B}{\beta + 1}$

Again,  $G_m = \frac{N_c}{N_e} = -G_m R_o$

Again, all we need  $G_m = \frac{i_c}{N_e} \Big|_{N_c=0} \triangleq$  short-ckt transconductance

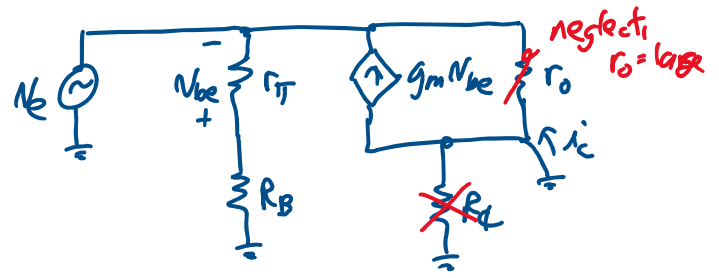

neglect  $r_o$  = large

$$N_{be} = -\frac{v_e r_{\pi}}{r_{\pi} + R_B}$$

$$\therefore i_c = g_m N_{be} = -\frac{g_m r_{\pi}}{r_{\pi} + R_B} N_e$$

$G_m = -g_m$

$G_m = \frac{i_c}{N_e} \Big|_{N_c=0} = -g_m \left( \frac{r_{\pi}}{r_{\pi} + R_B} \right)$   $R_B = 0$

Thus, if  $R_B = 0$

$$\frac{N_c}{N_e} = -G_m R_o = +g_m \left( \frac{r_{\pi}}{r_{\pi} + R_B} \right) R_L \approx g_m R_L$$

- Now go through the Inspection Analysis Handout