

Lecture 30: Multi-Transistor Circuit

- **Announcements:**
- Lab#5 due Tuesday, Nov. 12, 5 p.m.
- Midterm 2 next Friday, Nov. 15, @ 7 p.m., in 160 Kroeber Hall
 - ↳ Review Session will be next Tuesday, 6-8 p.m., in 400 Cory
 - ↳ Midterm Info Sheet online today
 - ↳ Handing out sample Midterm 2 today

• **Lecture Topics:**


- ↳ Generally-Loaded Transistor
 - Terminal Resistances
 - Terminal-to-Terminal Gains
 - Inspection Analysis Sheet
 - Examples

• **Last Time:**

- Went through inspection analysis sheet
- Now, use this to analyze a multi-transistor circuit
- ...

Example. Multi-Transistor Amplifier Inspection Analysis

(C.E. w/ Degeneration, C.C. Cascade)

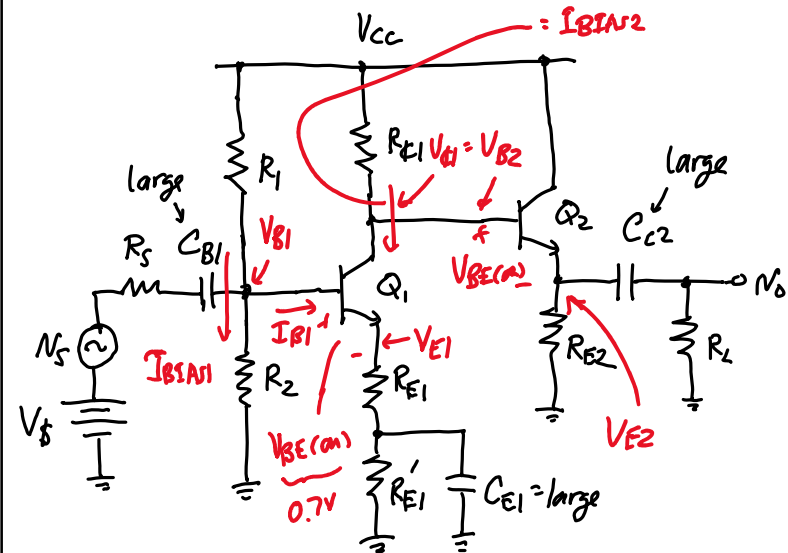

Find R_i , R_o , $A_v = \frac{V_o}{V_s}$, and f_H .

First, find the DC operating pt.:

Good Design: (stable bias pt.) $\Rightarrow I_{B1} > 10 I_{B1}$

$$V_{B1} = \frac{R_2}{R_1 + R_2} V_{CC} \rightarrow V_{E1} = V_{B1} - \underbrace{V_{BE(on)}}_{0.7V}$$

$$I_{E1} \approx I_{E1} = \frac{V_{E1}}{R_{E1} + R_{E1}'} = \frac{V_{B1} - V_{BE(on)}}{R_{E1} + R_{E1}'}$$

$$V_{C1} = V_{CC} - I_{C1} R_{C1} = V_{B2} \rightarrow V_{E2} = V_{B2} - V_{BE(on)}$$

$$I_{E2} \approx I_{E1} = \frac{V_{E2}}{R_{E2}}$$

Remarks.


① Look for the $V_{BE}(m)$'s \rightarrow well-defined voltages

② Current usually determined by $\frac{V_E}{R_E}$'s.

for bias stability:

$$I_{BIAS1} > 10I_{B1}, \text{ also } I_{Q1} = I_{BIAS2} > 10I_{E2}$$

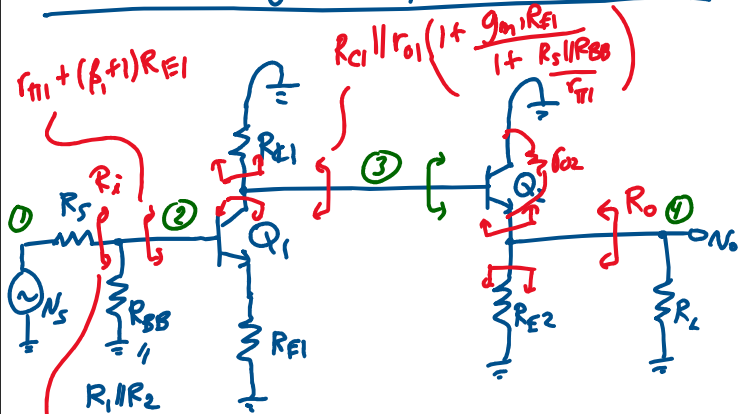Midband Small-Signal Analysis for Gain, R_i , and R_o :



$$R_i = R_{BB} \parallel (r_{\pi 1} + (\beta_1 + 1)R_{E1})$$

$$R_o = R_{E2} \parallel r_{o2} \parallel \left\{ r_{\pi 2} + R_{C1} \parallel r_{o1} \left(1 + \frac{g_{m1} R_{E1}}{1 + R_s \parallel R_{B1}} \right) \right\}$$

↑ $\beta_2 + 1$

$$R_o = R_{E2} \parallel \left(\frac{r_{\pi 2} + R_{C1}}{\beta_2 + 1} \right)$$

Get gain $\frac{N_o}{N_s}$: (gain from ① to ④)

$$\frac{N_o}{N_s} = \frac{N_2}{N_s} \cdot \frac{N_3}{N_2} \cdot \frac{N_o}{N_3}$$

$$\frac{N_2}{N_s} = \frac{R_i}{R_s + R_i} = \frac{R_{BB} \parallel (r_{\pi 1} + (\beta_1 + 1)R_{E1})}{R_s + R_{BB} \parallel (r_{\pi 1} + (\beta_1 + 1)R_{E1})}$$

(voltage divider)

$$\frac{N_3}{N_2} = -G_{m1} R_{C1}$$

$$= -\frac{g_{m1}}{1 + g_{m1} R_{E1}} \left\{ R_{C1} \parallel r_{o1} \left(1 + \frac{g_{m1} R_{E1}}{1 + \frac{R_s \parallel R_{B1}}{r_{\pi 1}}} \right) \parallel \left(r_{\pi 2} + (\beta_2 + 1)(R_{E2} \parallel R_L \parallel r_{o2}) \right) \right\}$$

$$\frac{N_3}{N_2} \approx -\frac{g_{m1} R_{C1}}{1 + g_{m1} R_{E1}}$$

$$\frac{N_o}{N_3} = \frac{R_{E2} \parallel R_L \parallel r_{o2}}{r_{o2} + R_{E2} \parallel R_L \parallel r_{o2}} \approx 1$$

↑ $\frac{1}{g_{m2}}$

$$\therefore \frac{N_0}{N_5} = \frac{N_0}{N_5} \cdot \frac{N_1}{N_2} \cdot \frac{N_3}{N_4}$$

$$= \frac{R_{B1} \parallel (C_{in1} + (\beta + 1)R_{E1})}{R_S + R_{B1} \parallel (C_{in1} + (\beta + 1)R_{E1})} \frac{g_{m1}R_{E1}}{1 + g_{m1}R_{E1}} = \frac{N_0}{N_5}$$

Procedure for Midband Gain Inspection Analysis:

- Identify and label all signal path nodes
- Get stage gain from node to node
 - ↳ For each stage, be sure to account for loading by the next stage, specifically load resistance to ground
 - ↳ For transistor terminal-to-terminal gains, will likely need to determine output node resistance to ground
 - including loading by the next stage, and
 - even the influence of loading by the previous stage, e.g., when determining R_c
- Take the product of all node-to-node gains to get the total gain
- Can do all of this by inspection if
 - ↳ There is no feedback
 - ↳ You know all the terminal-to-terminal gain equations or can “see” or “derive” them quickly
 - ↳ You know all the equations for resistances looking into the transistor terminals (to ground) or can “see” or “derive” them quickly
 - ↳ “see” or “derive” quickly can often be done by following the currents