

Lecture 31: Multi-Transistor High Frequency

- **Announcements:**
- HW#10 online, but not due till Friday next week
- Lab#6 coming soon
- Midterm 2 this Friday, Nov. 15, @ 7 p.m., in 160 Kroeber Hall

 • **Lecture Topics:**


- ↳ **Multi-Transistor Example (Inspection Analysis)**
 - Input/Output Resistances
 - Gain
 - High Frequency
- ↳ **MOS Inspection Analysis**

 • **Last Time:**

- Got the gain of the amplifier
- Now, get the high frequency cut-off

Example. Multi-Transistor Amplifier Inspection Analysis

(C.E. w/ Degeneration, C.C. Cascade)

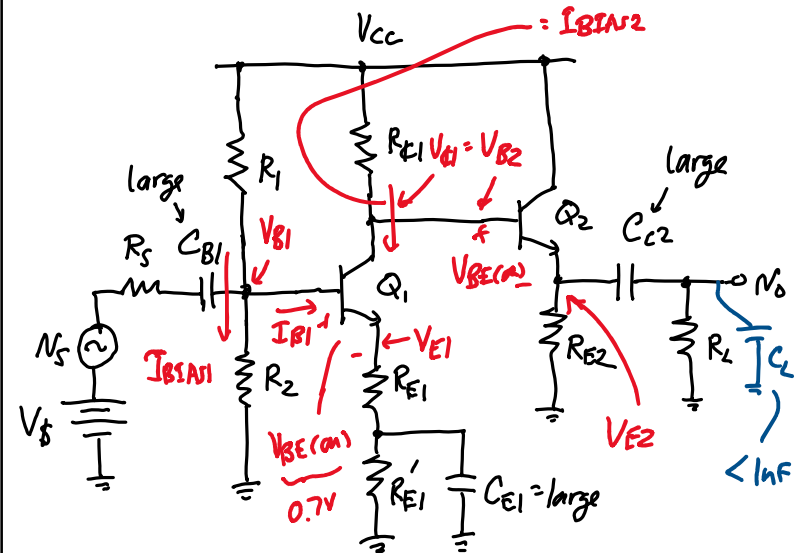

Find R_i , R_o , $A_v = \frac{V_o}{V_s}$, and f_H .

First, find the DC operating pt:

Good Design: (stable bias pt.) $\Rightarrow I_{BAS1} > 10 I_{B1}$

$$V_{B1} = \frac{R_2}{R_1 + R_2} V_{CC} \rightarrow V_{E1} = V_{B1} - \underbrace{V_{BE(on)}}_{0.7V}$$

$$I_{E1} \approx I_{E1} = \frac{V_{E1}}{R_{E1} + R_{E1}'} = \frac{V_{B1} - V_{BE(on)}}{R_{E1} + R_{E1}'}$$

$$V_{C1} = V_{CC} - I_{C1} R_{C1} = V_{B2} \rightarrow V_{E2} = V_{B2} - V_{BE(on)}$$

$$I_{E2} \approx I_{E2} = \frac{V_{E2}}{R_{E2}}$$


Remarks.

- ① Look for the $V_{BE}(m)$'s → well-defined voltages
- ② Current usually determined by $\frac{V_E}{R_E}$'s.

for bias stability:

$$I_{BIAS1} > 10I_{B1}, \text{ also } I_{Q1} = I_{BIAS2} > 10I_{E2}$$

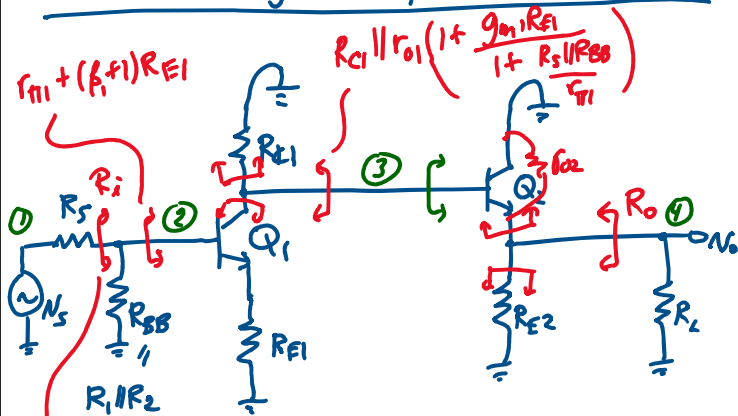Midband Small-Signal Analysis for Gain, R_i , and R_o :



$$R_i = R_{B3} \parallel (r_{\pi1} + (\beta_1 + 1)R_{E1})$$

$$R_o = R_{E2} \parallel r_{o2} \parallel \left\{ r_{\pi2} + R_{C1} \parallel r_{o1} \left(1 + \frac{g_{m1}R_{E1}}{1 + \frac{R_{S1} \parallel R_{B3}}{r_{\pi1}}} \right) \right\}$$

↑ $\beta_2 + 1$

$$R_o = R_{E2} \parallel \left(\frac{r_{\pi2} + R_{C1}}{\beta_2 + 1} \right)$$

Get gain $\frac{N_o}{N_s}$: (gain from ① to ④)

$$\frac{N_o}{N_s} = \frac{N_{(2)}}{N_s} \cdot \frac{N_{(3)}}{N_{(2)}} \cdot \frac{N_o}{N_{(3)}}$$

$$\frac{N_{(2)}}{N_s} = \frac{R_i}{R_s + R_i} = \frac{R_{B3} \parallel (r_{\pi1} + (\beta_1 + 1)R_{E1})}{R_s + R_{B3} \parallel (r_{\pi1} + (\beta_1 + 1)R_{E1})}$$

(voltage divider)

$$\frac{N_{(3)}}{N_{(2)}} = -G_{m1}R_{C1}$$

$$= -\frac{g_{m1}}{1 + g_{m1}R_{E1}} \left\{ R_{C1} \parallel r_{o1} \left(1 + \frac{g_{m1}R_{E1}}{1 + \frac{R_{S1} \parallel R_{B3}}{r_{\pi1}}} \right) \parallel \left(r_{\pi2} + (\beta_2 + 1)(R_{E2} \parallel R_L \parallel r_{o2}) \right) \right\}$$

$$\frac{N_{(3)}}{N_{(2)}} \approx -\frac{g_{m1}R_{C1}}{1 + g_{m1}R_{E1}} \rightarrow -\frac{g_{m1}R_{C1}}{g_{m1}R_{E1}} \approx -\frac{R_{C1}}{R_{E1}}$$

[$g_{m1}R_{E1} \gg 1$]

$$\frac{N_o}{N_{(3)}} = \frac{R_{E2} \parallel R_L \parallel r_{o2}}{r_{o2} + R_{E2} \parallel R_L \parallel r_{o2}} \approx 1$$

↑ $\frac{1}{g_{m2}}$

$$\therefore \frac{N_0}{N_5} = \frac{N_1}{N_5} \cdot \frac{N_2}{N_2} \cdot \frac{N_3}{N_3} \cdot \frac{N_0}{N_3}$$



$$= \frac{R_{\beta\beta} \parallel (C_{\pi 1} + (\beta + 1)R_{E1})}{R_S + R_{\beta\beta} \parallel (C_{\pi 1} + (\beta + 1)R_{E1})} \frac{g_{m1}R_{E1}}{1 + g_{m1}R_{E1}} = \frac{N_0}{N_5}$$

Procedure for Midband Gain Inspection Analysis:

- Identify and label all signal path nodes
- Get stage gain from node to node
 - ↳ For each stage, be sure to account for loading by the next stage, specifically load resistance to ground
 - ↳ For transistor terminal-to-terminal gains, will likely need to determine output node resistance to ground
 - including loading by the next stage, and
 - even the influence of loading by the previous stage, e.g., when determining R_c
- Take the product of all node-to-node gains to get the total gain
- Can do all of this by inspection if
 - ↳ There is no feedback
 - ↳ You know all the terminal-to-terminal gain equations or can “see” or “derive” them quickly
 - ↳ You know all the equations for resistances looking into the transistor terminals (to ground) or can “see” or “derive” them quickly
 - ↳ “see” or “derive” quickly can often be done by following the currents

Procedure for High Frequency Inspection Analysis:

- Identify and label all signal path nodes
- Draw in the small transistor capacitors
- Use the Miller transform to turn the base-to-collector or gate-to-drain capacitor into shunt capacitors to ground
- For the base-to-emitter or gate-to-source capacitor you will need to know the equation for driving point resistance, i.e., resistance in parallel
- Get the time constant for each node by
 - ↳ Determining the total capacitance C_{node} from that node to ground
 - ↳ Determining the total resistance R_{node} from that node to ground
 - ↳ Time constant = $R_{node} * C_{node}$
- Handle each feedback capacitor separately using knowledge of its driving point R equation (or derive the equation from scratch using the hybrid- π model)
- Add up all the time constants and take the reciprocal to get the ω_H

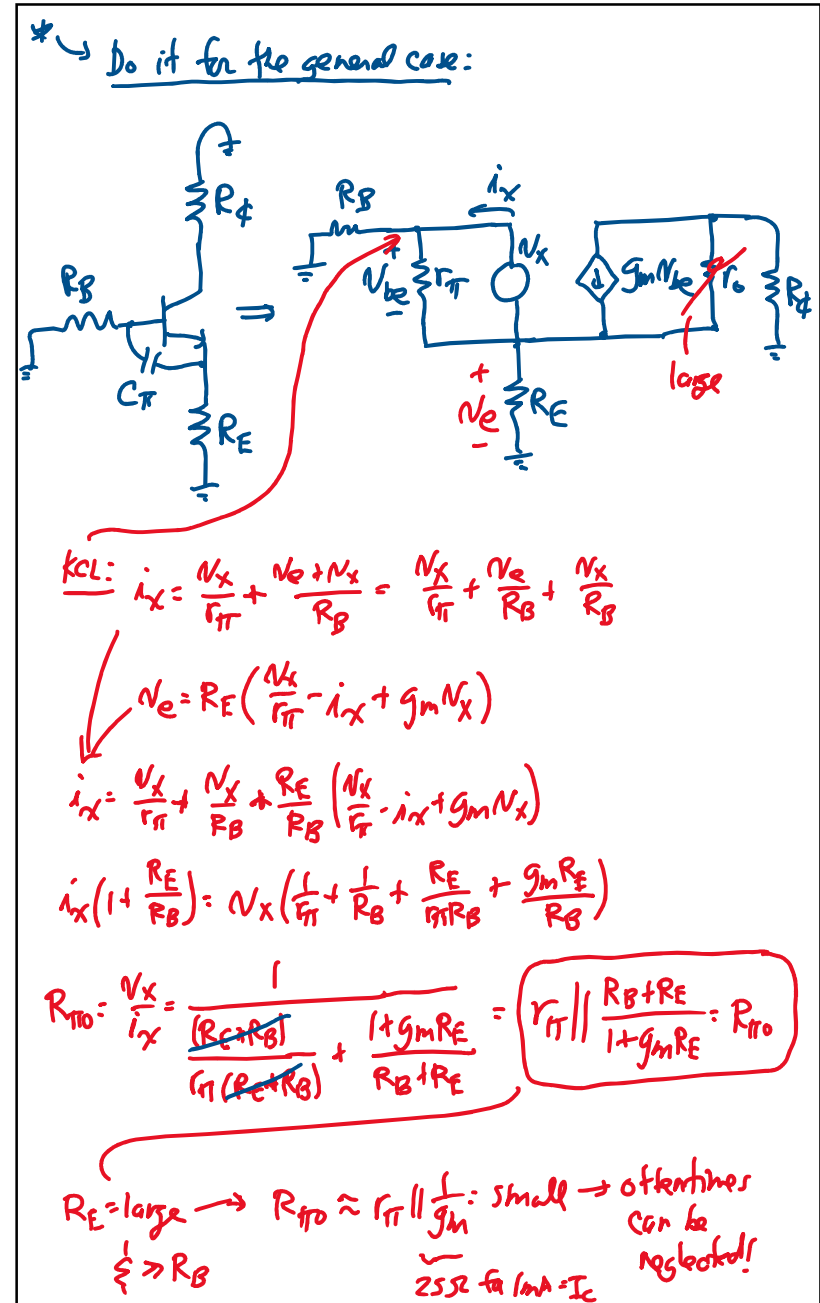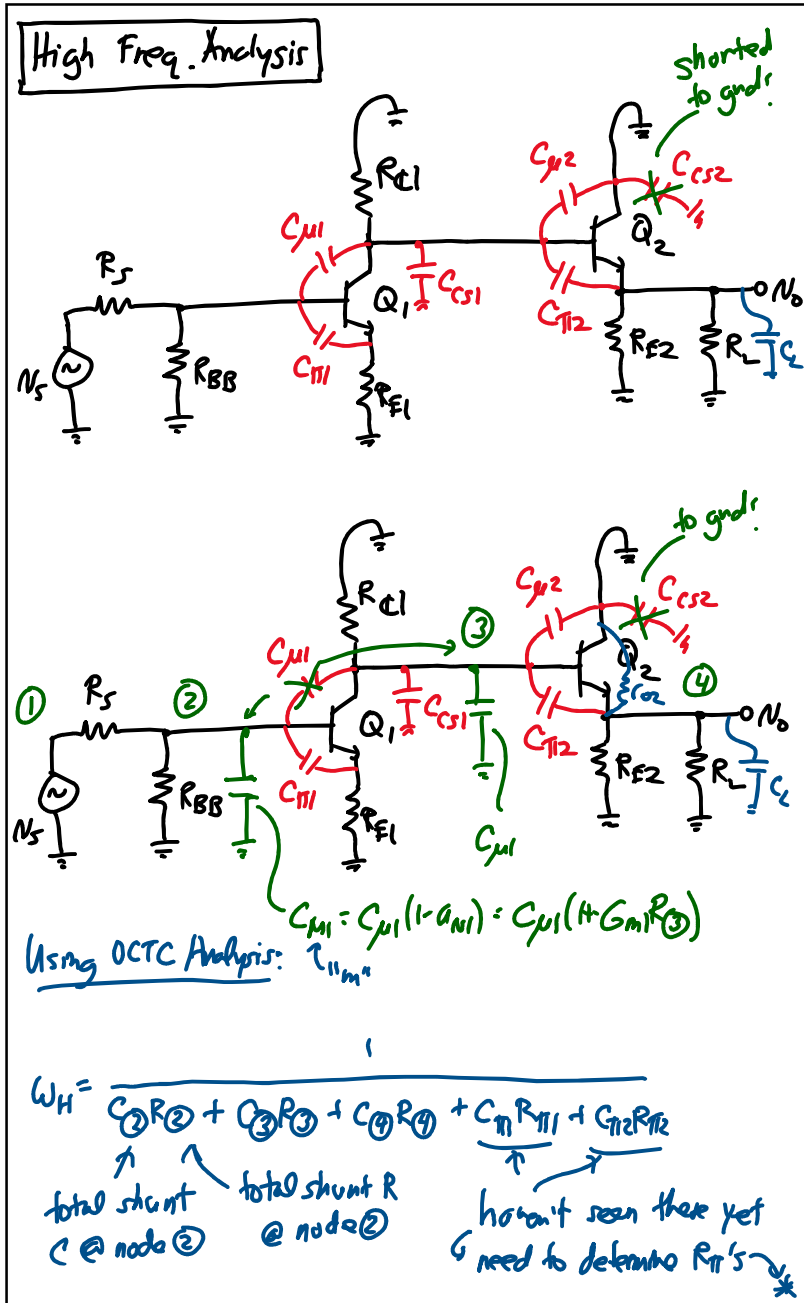

$$\frac{N_o}{N_i} = \frac{R_E}{\frac{1}{g_m} + R_E} \approx 1$$

25Ω

$1k\Omega$

$N_i - N_i = 0 \rightarrow C_{\pi}$ is effectively not there!

Now, get the τ 's to get ω_H :

$$C_{\textcircled{2}} = C_{\mu 1} (1 + G_m R_{\textcircled{3}})$$

$$= C_{\mu 1} \left(1 + \frac{g_m}{1 + g_m R_E} \left\{ R_{E1} \parallel r_{o1} \left(1 + \frac{g_m R_E}{1 + R_S \parallel R_{BB}} \right) \parallel \right\} \right)$$

$$r_{\pi 2} + (\beta_2 + 1) (R_{E2} \parallel R_L \parallel r_{o2})$$

$$C_{\textcircled{2}} = C_{\mu 1} \left(1 + \frac{g_m R_{E1}}{1 + g_m R_E} \right)$$

$$R_{\textcircled{2}} = R_S \parallel R_{BB} \parallel (r_{\pi 1} + (\beta_1 + 1) R_{E1}) \approx R_S \parallel R_{BB} \approx R_S$$

$$\tau_{\textcircled{2}} = C_{\mu 1} \left(1 + \frac{g_m R_{E1}}{1 + g_m R_E} \right) R_S$$

$$C_{\textcircled{3}} = C_{cs1} + C_{\mu 1} + C_{\mu 2}$$

$$R_{\textcircled{3}} = R_{E1} \parallel r_{o1} \left(1 + \frac{g_m R_E}{1 + R_S \parallel R_{BB}} \right) \parallel (r_{\pi 2} + (\beta_2 + 1) (R_{E2} \parallel R_L \parallel r_{o2}))$$

$$\approx R_{E1}$$

$$\tau_{\textcircled{3}} = (C_{cs1} + C_{\mu 1} + C_{\mu 2}) R_{E1}$$

$$C_{\textcircled{4}} = C_L$$

$$R_{\textcircled{4}} = R_{E2} \parallel R_L \parallel \frac{r_{\pi 2} + R_{E1} \parallel r_{o1} \left(1 + \frac{g_m R_E}{1 + R_S \parallel R_{BB}} \right)}{\beta_2 + 1}$$

$$\approx R_{E2} \parallel R_L \parallel \left(\frac{r_{\pi 2} + R_{E1}}{\beta_2 + 1} \right)$$

$$\tau_{\textcircled{4}} = C_L (R_{E2} \parallel R_L \parallel \left(\frac{r_{\pi 2} + R_{E1}}{\beta_2 + 1} \right))$$