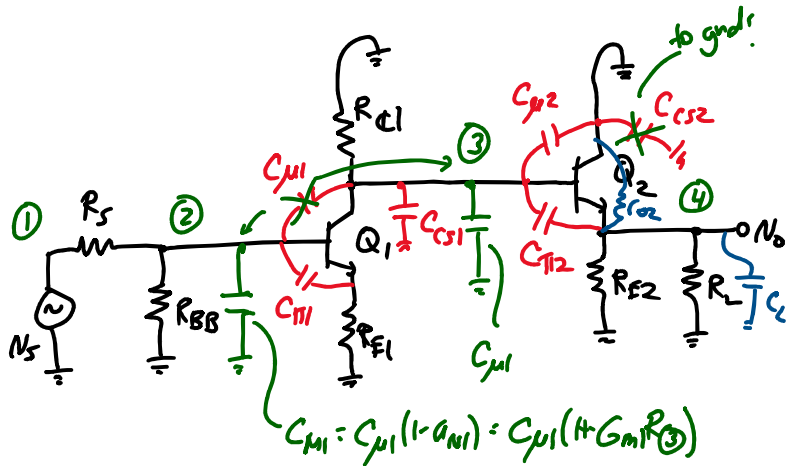


Lecture 32: MOS Inspection Analysis

- **Announcements:**
- HW#10 online and due Friday Nov. 22
- Lab 6 online and due 5 p.m., Friday, Dec. 13
- Midterm 2 today @ 7 p.m., in 160 Kroeber Hall
-
- **Lecture Topics:**
 - ↳ Multi-Transistor Example (Inspection Analysis)
 - Input/Output Resistances
 - Gain
 - High Frequency
 - ↳ MOS Inspection Analysis
-
- **Last Time:**
- Practically finished high frequency cut-off
- Finish it off, then move to MOS inspection analysis



Using OCTC Analysis:

$$\omega_H = \frac{1}{C_2 R_2 + C_3 R_3 + C_4 R_4 + C_{\pi 1} R_{\pi 1} + C_{\pi 2} R_{\pi 2}}$$

total shunt @ node 2
 total shunt @ node 3

C_{π} 's in FB \therefore determined their driving pts R_{π} 's via hybrid- π model

Incorporating Results f/ Last Time

$$\omega_H = \frac{1}{\left\{ C_{\mu 1} \left(1 + \frac{g_{m1} R_E}{1 + g_{m1} R_{E1}} \right) (R_S || R_B) + (C_{cs1} + C_{\mu 1} + C_{\mu 2}) R_{C1} \right.}$$


$$\left. + C_L (R_{E2} || R_L || \frac{r_{\pi 2} + R_{E1}}{\beta_2 + 1}) + C_{\pi 1} \left(r_{\pi 1} || \left(\frac{R_B || R_S + R_{E1}}{1 + g_{m1} R_{E1}} \right) \right) \right\}}$$

$$+ C_{\pi 2} \left(r_{\pi 2} || \left(\frac{R_{C1} + R_{E2}}{1 + g_{m2} R_{E2}} \right) \right) \quad R_{E1} \text{ is not large}$$

$R_{E2} = \text{large!}$

✓ = include
 ✗ = maybe neglect

X = neglect

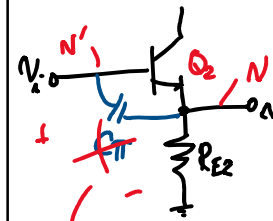

$$\frac{V_o}{N_i} = \frac{R_{E2}}{\frac{1}{\beta_2} + R_{E2}} \approx 1 \text{ when } R_{E2} \gg \frac{1}{g_{m2}}$$

$\Delta N = V' - N' = 0 \rightarrow$ No voltage across $C_{\pi} \therefore$ no C_{π}

MOS Xristm Cktr. (short bulk to source)

⇒ for now, ignore body effect (i.e., ignore g_{mb})
 ↳ use the same inspection formulas as bipolar, but $\beta \rightarrow \infty$, $r_{\pi} = \frac{\beta}{g_m} \rightarrow \infty$

⇒ refer to the bipolar "Inspection Formula Sheet":

Bipolar		MOS
$R_b = (\frac{1}{g_m} + R_E)(\beta + 1)$	$\xrightarrow{\beta \rightarrow \infty}$	$R_g = \infty$
$R_e = \frac{1}{g_m} + \frac{R_B}{\beta + 1}$	$\xrightarrow{\beta \rightarrow \infty}$	$R_s = \frac{1}{g_m}$
$R_c = r_o \left[1 + \frac{g_m R_E}{1 + R_B/r_{\pi}} \right]$	$\xrightarrow{\beta \rightarrow \infty}$	$R_d = r_o (1 + g_m R_E)$

$\frac{N_d}{N_g} = -G_m R_D$, $G_m = \frac{g_m}{1 + g_m R_S}$

$\frac{N_d}{N_s} = -G_m R_D$, $G_m = -g_m$

$\frac{N_s}{N_g} = \frac{g_m R_S}{1 + g_m R_S} = \frac{R_S}{\frac{1}{g_m} + R_S}$

MOS Inspection Analysis

Ex. Common-Source Common-Drain Cascade

↓ S.S. Ckt.

$R_i = \infty$

$R_o = R_{S2} \parallel r_{o2} \parallel \frac{1}{g_{m2}} \approx R_{S2} \parallel \frac{1}{g_{m2}}$

$$\frac{N_o}{N_s} = \frac{N_{D1}}{N_s} \cdot \frac{N_{D2}}{N_{D1}} \cdot \frac{N_o}{N_{D2}}$$

$$= (1)(-g_m R_{D1}) \left(\frac{R_{D2}}{\frac{1}{g_{m2}} + R_{D2}} \right) \approx \frac{N_o}{N_s}$$

Problem: Simulate via SPICE → the gain will be 80-90% of what a calculator using

the problem is w/ g_{mb} in the source follower

↑ this is the difference between bipolar & MOS hybrid- π models!

Source Follower:

$N_{g_s} = N_i - N_o$
 $N_{b_s} = -N_o$

$R_s = \frac{1}{G_s}$

$$g_m(N_i - N_o) = N_o(g_{ds} + G_s + g_{mb})$$

$$\Rightarrow A_{vf} = \frac{N_o}{N_i} = \frac{g_m}{g_m + g_{mb} + g_{ds} + G_s}$$

$R_s \rightarrow \infty \rightarrow G_s \rightarrow 0$
 $g_{ds} \ll g_m + g_{mb}$ Body factor

$$A_{vf} \approx \frac{g_m}{g_m + g_{mb}} = \frac{1}{1 + \eta}, \quad \eta = \frac{\gamma}{2\sqrt{V_{SB} + 2\phi_f}}$$

$\neq 1$

To make it '1' do this:

\Rightarrow not always practical!

Effect of g_{mb} on Impedance

$$\begin{bmatrix} N_{gs} = -N_x = N_{bs} \\ N_{ds} = -N_x \end{bmatrix}$$

$$g_m + g_{mb} + g_{ds}$$

$$R_s = \frac{1}{g_m + g_{mb} + g_{ds}} = \frac{1}{g_m} \parallel \frac{1}{g_{mb}} \parallel r_o$$

$$R_s \approx \frac{1}{g_m + g_{mb}}$$

⇒ more extensive analysis shows that other inspection formulas change to accommodate a grounded body by replacing " g_m " in the denominator w/ " $g_m + g_{mb}$ "

⇒ end up w/ the following: ↷ over

MOS Inspection Formula w/ Substrate Grounded

only difference from substrate tied to source case is that g_m is replaced by $g_m + g_{mb}$ in some of the formulas particularly over where the source is involved!

$R_g = \infty$
 $R_s = \frac{1}{g_m + g_{mb}}$
 $R_d = r_o [1 + (g_m + g_{mb})R_b]$
 $\frac{N_d}{N_g} = -G_m R_d$, $G_m = \frac{g_m}{1 + (g_m + g_{mb})R_b}$
 $\frac{N_d}{N_s} = -G_m R_d$, $G_m = -(g_m + g_{mb})$
 $\frac{N_s}{N_o} = \frac{g_m R_b}{1 + (g_m + g_{mb})R_b}$

Remark When the substrate is tied to the source, $g_{mb} = 0$.