

Lecture 34: Cascade Amplifier

• Announcements:

- HW#10 online and due Friday Nov. 22
- Lab 6 online and due 5 p.m., Friday, Dec. 13
- Graded Midterm 2 passed back last time

• Lecture Topics:

- ↳ Purposeful Design
- ↳ Cascade Amplifier
- ↳ Differential Pair

• Last Time:

- Explored amplifier stages and cascading
- Now, continue with an example ...


Multi-Stage Amplifier Design Guidelines

(for voltage amplifiers) ($i \rightarrow i$ amps, etc., would have different charts)

	Ideal Voltage Amp	C.E.	C.E. w/ R_E	C.C.	C.B.
R_i	∞	med. X	large ✓	large ✓	small X
R_o	0	large X	large X	small ✓	large X
a_v	∞	large ✓	med. X	small X	large ✓
f_H	∞	small X	med. X	large ✓	large ✓

To Get Better Performance \rightarrow Cascade Amplifiers

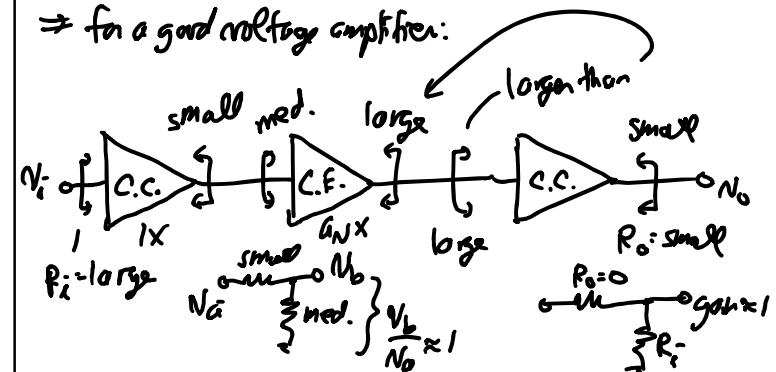\Rightarrow for a good voltage amplifier:



⇒ in the S.S. sense, we want:

⇒ add biasing:

Biasing: for stability, $I_{B3} \approx 10 I_{B1}$

$$V_{B1} = V_{CC} \left(\frac{R_2}{R_1 + R_2} \right) \rightarrow V_{E1} = V_{B1} - V_{BE(m)}$$

$$I_{C1} \approx I_{E1} = \frac{V_{E1}}{R_{E1}} \quad \downarrow \quad V_{E2} = V_{E1} - V_{BE(m)}$$

$$= V_{B1} - 2V_{BE(m)}$$

$$I_{C2} \approx I_{E2} = \frac{V_{E2}}{R_{E2}} \rightarrow V_{C2} = V_{CC} - I_{C2} R_{C2} = V_{B3}$$

$V_{E3} = V_{C2} - V_{BE(m)} \rightarrow I_{C3} \approx I_{E3} = \frac{V_{E3}}{R_{E3}}$

* Large Output Swing:

Does this violate our small-signal design criterion? $\rightarrow V_{be} \ll V_T = 25\text{mV}$

$N_{be} \approx N - 0.99V = 10\text{mV} < 25\text{mV}$ ✓ Satisfies small-signal

Emitter Follower Output Stage

⇒ What is the max voltage swing @ the output?
⇒ Need to think in both large & small signal domains!

$V_{E2max} = V_{CC}$
 $V_{E3max} = V_{E2max} - V_{BE(on)} = V_{CC} - V_{BE(on)}$

$V_{E2min} = V_{E2} + V_{CE2(sat)}$
 $V_{E3min} = (V_{E2} + V_{CE2(sat)}) - V_{BE(on)}$ or 0V

Case: max voltage
⇒ Q_3 sources enough current to push N_o up across $R_{E3} || R_L$
⇒ max voltage limit determined by Q_2 stage

$\therefore V_{omax} = \frac{V_{E3max} - V_{E3min}}{2} \Rightarrow V_{swing} = 2 \times V_{omax}$

Differential Pair → A Simple Op Amp

Assumption:
 Q_1 & Q_2 identical
 R_{C1} & R_{C2} identical


Purpose: Amplify the difference between two signals regardless of their common-mode values.

Definitions:
 $V_{ID} = V_{I1} - V_{I2}$ (differential input)
 $V_{ICM} = \frac{V_{I1} + V_{I2}}{2}$ (common-mode input)
 $V_{O1} = V_{ICM} + \frac{V_{ID}}{2}$
 $V_{O2} = V_{ICM} - \frac{V_{ID}}{2}$

Differential Gain: $A_d = \frac{V_{o1} \cdot V_{o2}}{V_{id}} = \frac{V_{od}}{V_{id}}$ (want BIG)


Common-Mode Gain: $A_{cm} = \frac{V_{o1}}{V_{icm}} = \frac{V_{o2}}{V_{icm}}$ (want SMALL)

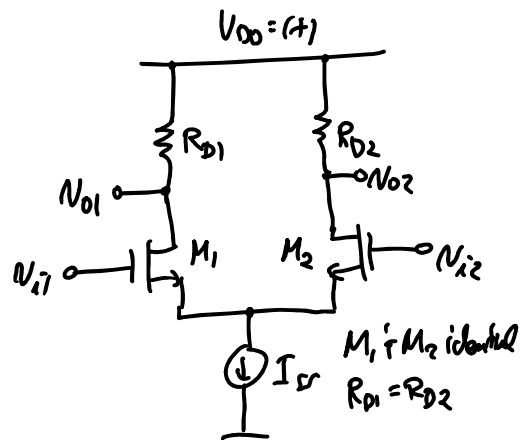Common-Mode Rejection Ratio = CMRR = $\frac{A_{dm}}{A_{cm}}$
 (want BIG)



Want $A_d = \frac{V_{o1} \cdot V_{o2}}{V_{i1} - V_{i2}}$

S.S. Ckt.

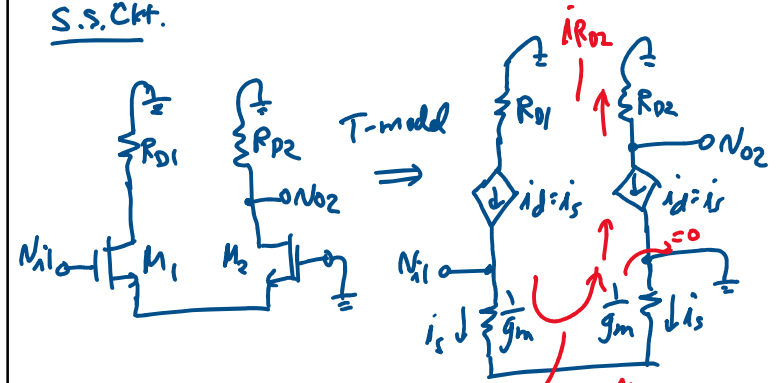

$V_{o2} = i_{R_{D2}} R_{D2}$
 $i_{R_{D2}} = \frac{V_{i1}}{2} = \frac{1}{2} g_m V_{i1}$

$= + \frac{1}{2} g_m V_{i1} R_{D2} \rightarrow \therefore \frac{V_{o2}}{V_{i1}} = \frac{1}{2} g_m R_D$

$[R_D = R_{D1} = R_{D2}]$

$[g_m = g_{m1} = g_{m2}]$