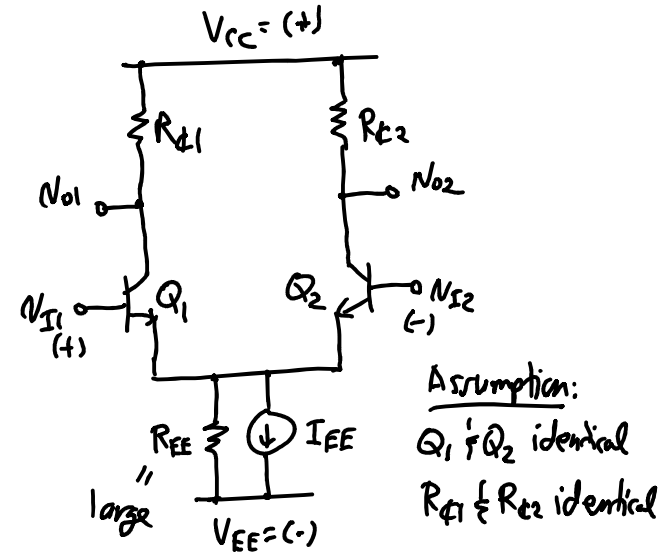


Lecture 35: Differential Pairs

- Announcements:
- HW#11 will be online soon and due Tuesday, Dec. 10 (more than two weeks from now)
- Lab 6 online and due 5 p.m., Friday, Dec. 13
- -----
- Lecture Topics:
- ↪ Differential Pair
- ↪ MOS Op Amp Design
- ↪ Review of Digital Electronics
- -----
- Last Time:
- Started on differential pairs
- Now, continue with this ...

Differential Pair → A Simple Op Amp



Purpose: Amplify the difference between two signals regardless of their common-mode values.

Definitions:

$$V_{ID} = V_{I1} - V_{I2} \quad (\text{differential input})$$

$$V_{ICM} = \frac{V_{I1} + V_{I2}}{2} \quad (\text{common-mode input})$$


$$V_{I1} = V_{ICM} + \frac{V_{ID}}{2}$$

$$V_{I2} = V_{ICM} - \frac{V_{ID}}{2}$$

Differential Gain: $A_d = \frac{V_{o1} \cdot V_{o2}}{V_{id}} = \frac{V_{od}}{V_{id}}$ (want BIG)

Common-Mode Gain: $A_{cm} = \frac{V_{oc}}{V_{icm}} = \frac{V_{o2}}{V_{icm}}$ (want SMALL)

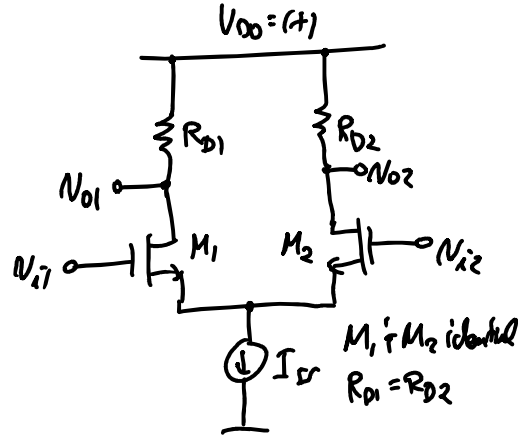Common-Mode Rejection Ratio = CMRR = $\frac{A_{dm}}{A_{cm}}$ (want BIG)




Want $A_d = \frac{V_{o1} \cdot V_{o2}}{V_{id} - V_{i2}}$

⇒ use superposition:

- get $V_{o2}' = f(V_{i1})$ & $V_{o2}'' = f(V_{i2})$
- then $V_{o2} = V_{o2}' + V_{o2}''$
- then repeat for V_{o1}

S.S. Ckt.

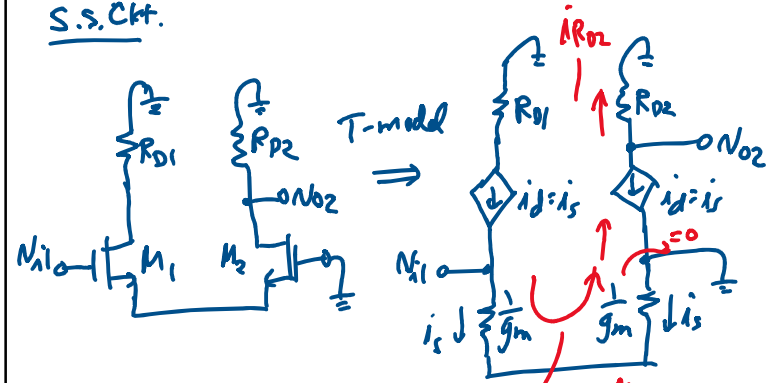


$V_{o2}' = i_{R_{D2}} R_{D2}$
 $i_{R_{D2}} = \frac{V_{i1}}{2} = \frac{1}{2} g_m V_{id}$

$= + \frac{1}{2} g_m v_{i1} R_{D2} \rightarrow \therefore \frac{V_{o2}'}{V_{i1}} = \frac{1}{2} g_m R_D$

$[R_D = R_{D1} = R_{D2}]$
 $[g_m = g_{m1} = g_{m2}]$

Get $\frac{V_{o2}''}{V_{i2}}$:


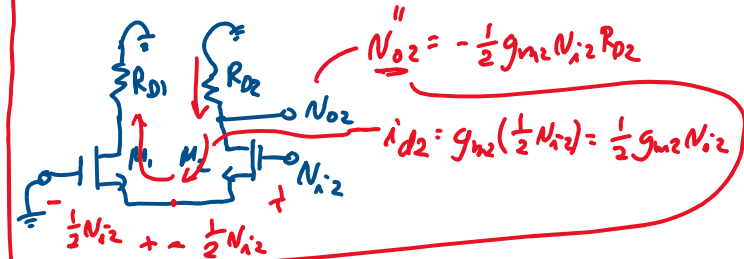


$V_{o2}'' = -\frac{1}{2} g_m v_{i2} R_{D2}$

$i_{d2} = g_m (\frac{1}{2} V_{i2}) = \frac{1}{2} g_m V_{i2}$

$V_{o2} = V_{o2}' + V_{o2}'' = \frac{1}{2} g_m R_D V_{i1} - \frac{1}{2} g_m R_D V_{i2}$

→ want v_{o1}

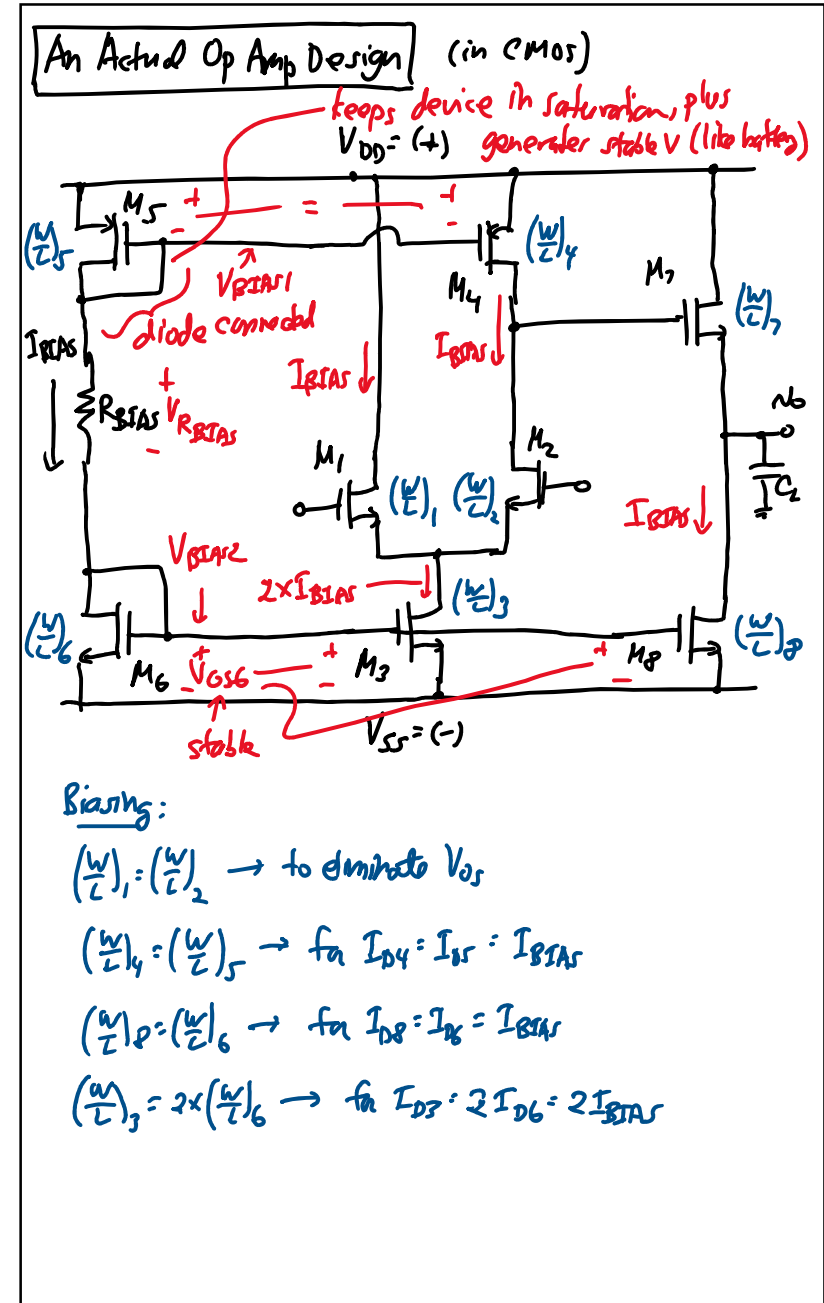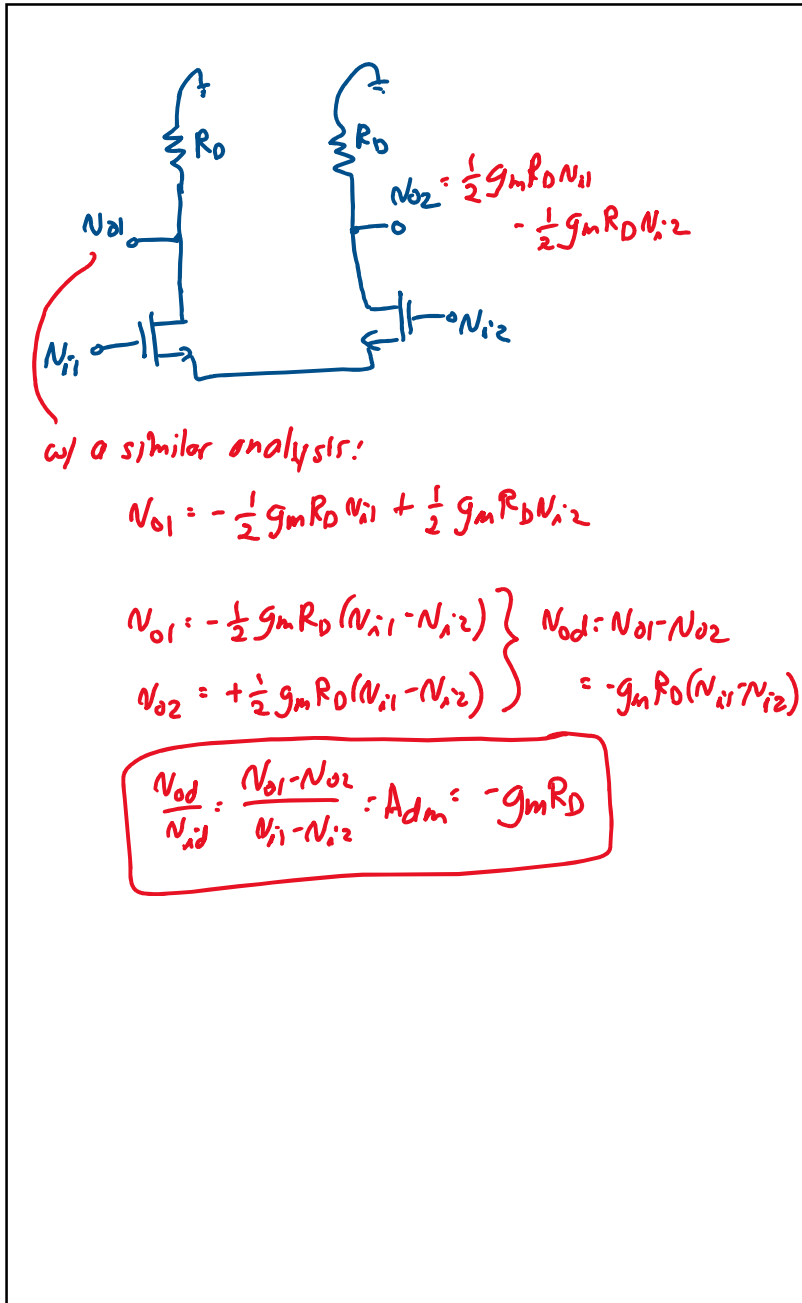

To Specify $I_{B2AS} \rightarrow$ Specify R_{B2AS} :

$$R_{B2AS} = \frac{V_{R_{B2AS}}}{I_{B2AS}} = \frac{V_{DD} - |V_{GS1}| - V_{GS6} - V_{SS}}{I_{B2AS}}$$

$$I_{DS} = \frac{1}{2} \mu_p C_{ox} \left(\frac{W}{L}\right)_S (V_{GS1} - V_{tpl})^2$$


$$\rightarrow |V_{GS1}| = |V_{tpl}| + \sqrt{\frac{2I_{B2AS}}{\mu_p C_{ox} (W/L)_S}}$$

Similarly: $V_{GS6} = V_{tn} + \sqrt{\frac{2I_{B2AS}}{\mu_n C_{ox} (W/L)_6}}$

Pick on $I_{B2AS} \rightarrow$ Get the needed R_{B2AS}

Gain \Rightarrow focus on the signal path only!

S.S. Ckt:

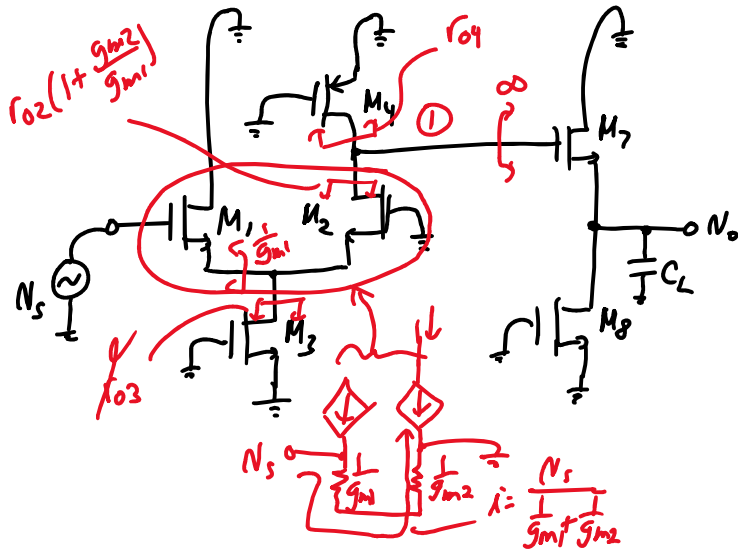


$$\frac{N_o}{N_s} = \frac{N_{O1}}{N_s} \cdot \frac{N_o}{N_{O1}}$$

$$\frac{N_o}{N_s} = \underbrace{G_{m\text{diff}} R_{O1}}_{G_{m\text{diff}}} = \frac{1}{\frac{1}{g_{m1}} + \frac{1}{g_{m2}}} \left[r_{o4} \parallel r_{o2} \left(1 + \frac{g_{m1}}{g_{m2}} \right) \right]$$

$$= \frac{1}{2} g_{m1} (r_{o4} \parallel 2r_{o2})$$

$$\frac{N_o}{N_{O1}} = \frac{g_{m7}}{g_{m7} + g_{mb7}} \approx 1$$
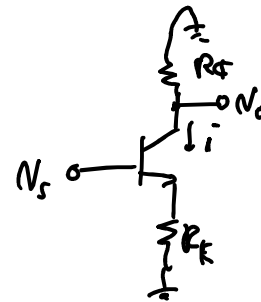
$$\therefore \frac{N_o}{N_s} = + \frac{1}{2} g_{m1} (r_{o4} \parallel 2r_{o2})$$



$$\frac{N_o}{N_s} = -G_m R_F$$

$$G_m \cdot \frac{i}{N_s} = \frac{g_m}{1 + g_m R_F}$$