

Lecture 3: Frequency Response

- Announcements:
- HW#1 online and due this Friday
- Discussions this week
- Lab#1 online
- Labs start next week
 - ↳ You will need to do your prelabs for Lab 1 before your lab period

 • Lecture Topics:


- ↳ Finish Digital Communications Example
- ↳ Review Impedance
- ↳ Frequency Response
- ↳ Bode Plots

 • Last Time:

- Going through an example digital communication transmitter as motivation
- Now, continue with this ...

- Review of Analog Circuit Concepts:
- We assume you understand the following concepts from previous courses:
 - ↳ Transfer functions
 - ↳ Gain (voltage, current, power)
 - ↳ Input resistance
 - ↳ Output resistance
 - ↳ Two-port models for amplifiers
 - ↳ Bode plots
 - ↳ Ideal op amp ckt design and analysis
- We'll review some of these now to jog your memory

Review Impedance

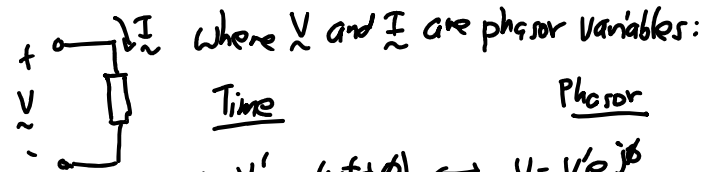

Time $v(t) = V' \cos(\omega t + \phi) \iff \underline{V} = V' e^{j\phi}$ Phasor

$i(t) = I' \cos(\omega t + \phi) \iff \underline{I} = I' e^{j\phi}$

and impedance: $\underline{Z} = \frac{\underline{V}}{\underline{I}}$

Resistor - $R = \frac{v(t)}{i(t)} \iff \underline{R} = \frac{\underline{V}}{\underline{I}}$


Capacitor - $i(t) = C \frac{dv}{dt} \iff \tilde{I} = C j\omega \tilde{V}$

$\frac{\tilde{V}}{\tilde{I}} = Z = \frac{1}{j\omega C} \leftarrow Z = \frac{1}{sC}$
 switch $s = j\omega$

Inductor - $v = L \frac{di}{dt} \iff \tilde{V} = L j\omega \tilde{I}$

$\frac{\tilde{V}}{\tilde{I}} = Z = j\omega L = sL$

Example. Determine a transfer function

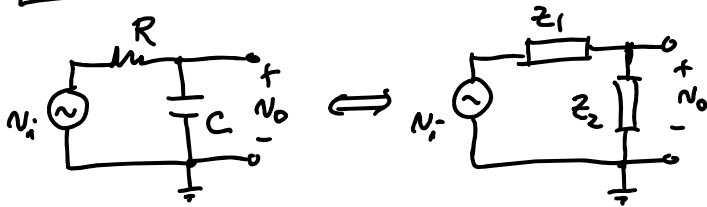


Recognize a voltage divider:
 $Z_1 = R$
 $Z_2 = \frac{1}{sC}$
 $\therefore N_o = \frac{Z_2 N_i}{Z_1 + Z_2} \Rightarrow \frac{N_o}{N_i}(s) = \frac{1}{R + \frac{1}{sC}}$

$\frac{N_o}{N_i}(s) = \frac{s}{1 + sRC} = \frac{1}{1 + s\tau_p} = \frac{1}{1 + \frac{s}{\omega_p}}$
 $[\tau_p = RC] \quad [\omega_p = \frac{1}{RC}]$

Frequency Response:


To measure the frequency response of a given network:

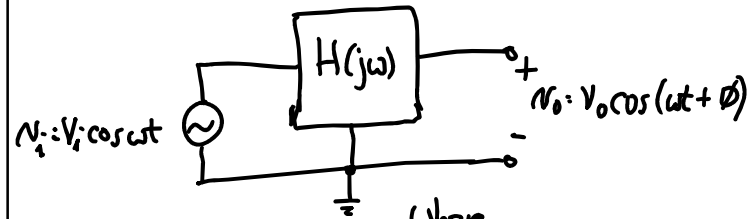- Excite the network with a variable-frequency, sinusoidal, constant amplitude source
- Measure the magnitude and phase of the output signal for different values of input frequency




where
 $|N_o(j\omega)| = V_o = \text{magnitude}$
 $\angle N_o(j\omega) = \phi = \text{phase}$

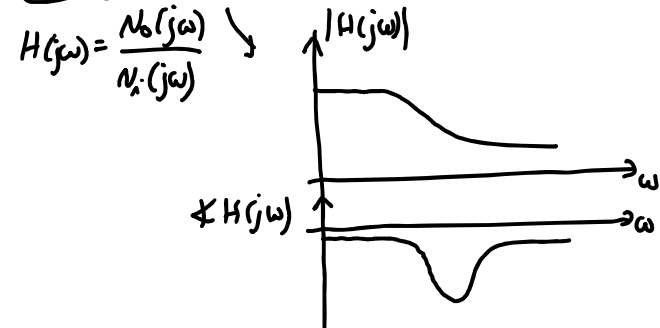The frequency response of a given network is commonly described by a plot of magnitude and phase versus frequency. Usually, such a plot is of the transfer function of a given network:



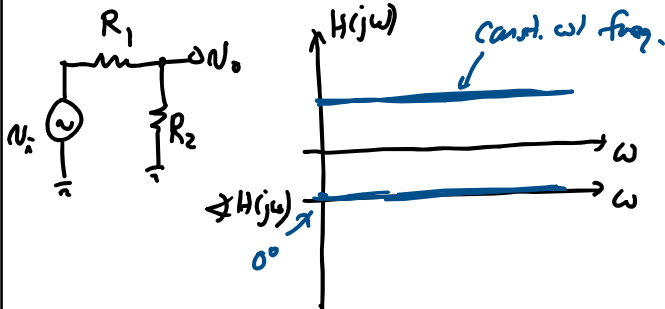- For a purely resistive network, the frequency response is constant (i.e., a straight line), both magnitude and phase



- The addition of reactive (energy storage) components, e.g., capacitors, inductors
 - Shapes the frequency response
 - Adds singularities, i.e., poles and zeros
 - Yields the general transfer function:

$$H(s) = \frac{N_o(s)}{N_i(s)} = H_0 \frac{(s-z_1)(s-z_2)\dots(s-z_m)}{(s-p_1)(s-p_2)\dots(s-p_n)} = H_0 \frac{\prod_{j=1}^m (s-z_j)}{\prod_{i=1}^n (s-p_i)}$$

↑
resistive term

where

$$z_j = \sigma_{zj} + j\omega_{zj}; \quad \sigma_{zj} = \text{Re}(z_j), \quad \omega_{zj} = \text{Im}(z_j)$$

$$p_i = \sigma_{pi} + j\omega_{pi}; \quad \sigma_{pi} = \text{Re}(p_i), \quad \omega_{pi} = \text{Im}(p_i)$$

$N_i(s) \triangleq$ input variable (not necessarily a voltage)

$N_o(s) \triangleq$ output variable (" " " " ")

\Rightarrow Given this, you should be able to generate a Bode plot!