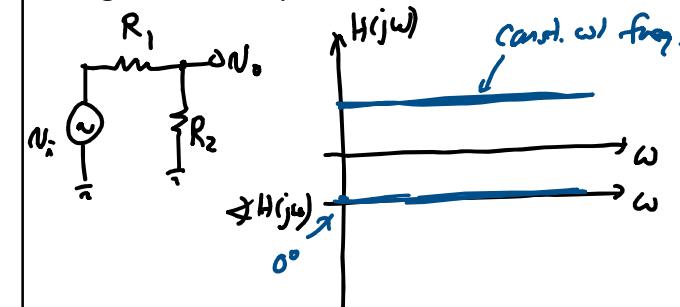


Lecture 4w: AmplifiersLecture 4: Amplifiers

- Announcements:
- HW#2 online and due next Friday
  - Need to run software, so make sure you can access the software
  - Go to discussion for help with Spice
- Lab#1 online
- Labs start next week
  - You will need to do your prelabs for Lab 1 before your lab period
- 
- Lecture Topics:
  - Finish Bode Plots
  - Amplifiers
  - Amplifier Models (2-port networks)
  - Input  $R_i$
  - Output  $R_o$
  - Ideal Voltage Amplifier
- 
- Last Time:
- Going through procedure for doing a Bode plot
- Now, continue with this ...

- For a purely resistive network, the frequency response is constant (i.e., a straight line), both magnitude and phase



- The addition of reactive (energy storage) components, e.g., capacitors, inductors
  - Shapes the frequency response
  - Adds singularities, i.e., poles and zeros
  - Yields the general transfer function:

$$H(s) = \frac{N_o(s)}{N_i(s)} = H_0 \frac{(s - z_1)(s - z_2) \cdots (s - z_m)}{(s - p_1)(s - p_2) \cdots (s - p_n)} = H_0 \frac{\prod_{j=1}^m (s - z_j)}{\prod_{i=1}^n (s - p_i)}$$

resistive term (scalar gain term)

$$z_j = \sigma_{zj} + j\omega_{zj}; \quad \sigma_{zj} = \operatorname{Re}(z_j), \quad \omega_{zj} = \operatorname{Im}(z_j)$$

$$p_i = \sigma_{pi} + j\omega_{pi}; \quad \sigma_{pi} = \operatorname{Re}(p_i), \quad \omega_{pi} = \operatorname{Im}(p_i)$$

$N_i(s) \triangleq$  input variable (not necessarily a voltage)

$N_o(s) \triangleq$  output variable (" " " " ")

Given this, you should be able to generate a Bode plot!

Lecture 4w: AmplifiersBode Plot

① Plot magnitude in decibels (dB) vs. log(freq.)

$$(H(s) \cdot H(j\omega)) \Rightarrow |H(j\omega)| = H_0 \frac{\prod_{j=1}^m |j\omega - z_j|}{\prod_{i=1}^n |j\omega - p_i|}$$

$$= H_0 \frac{\prod_{j=1}^m |j(\omega - \omega_{zj}) - \sigma_{zj}|}{\prod_{i=1}^n |j(\omega - \omega_{pi}) - \sigma_{pi}|} = H_0 \frac{\prod_{j=1}^m \sqrt{(\omega - \omega_{zj})^2 + \sigma_{zj}^2}}{\prod_{i=1}^n \sqrt{(\omega - \omega_{pi})^2 + \sigma_{pi}^2}}$$

convert to dB → allow combination by addition instead by multiplication  
→ easier to graph

$$20\log|H(j\omega)| = 20\log H_0 + \sum_{j=1}^m (20\log|j\omega - z_j|) - \sum_{i=1}^n (20\log|j\omega - p_i|)$$

② Plot phase vs. log(freq.)

$$\angle H(j\omega) = \sum_{j=1}^m [\angle(j\omega - z_j)] - \sum_{i=1}^n [\angle(j\omega - p_i)]$$

$$\text{where } \angle(j\omega - s) = \tan^{-1}\left(\frac{\omega - \omega_s}{-\sigma_s}\right)$$

$$[s = \sigma_s + j\omega_s]$$

- Because everything reduces to addition, one can determine the plot for each term then add/subtract them together
- Basically, can use superposition for both the magnitude and phase plots

Bode Plot Step-By-Step Procedure

① Get all factors into the form  $s$  or  $(1 + \frac{s}{a})$

$$\text{e.g., } s+b = b(1 + \frac{s}{b})$$

② Plot the Bode plot for each factor, one factor at a time. (Note that there are only a few cases.)

③ Sum all decibel magnitude plots to obtain the total magnitude plot.

④ Sum all phase plots to obtain the total phase plot.

Example



$$H(s) = \frac{100s(s+10^5)}{(s+10)(s+10^3)} = \frac{100(10^5)}{(10)(10^3)} \frac{s(1 + \frac{s}{10^5})}{(1 + \frac{s}{10})(1 + \frac{s}{10^3})}$$

$$\underbrace{10^3}_{\text{constant value}} = H_0 \rightarrow \text{factoring brings out the scalar gain term}$$

Case: constant value


$$\Rightarrow \text{constant amplitude} = 20\log H_0$$

$$\Rightarrow \text{constant phase} = 0^\circ$$

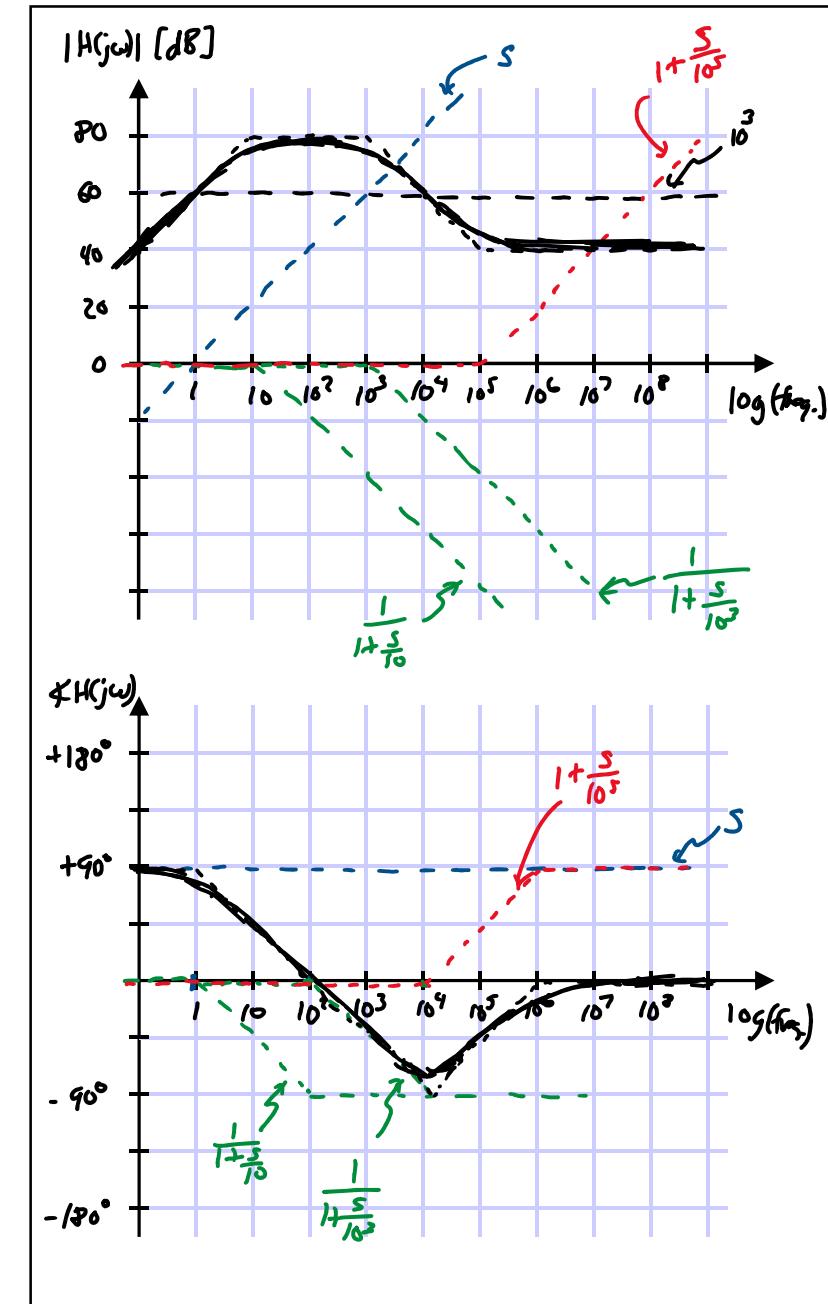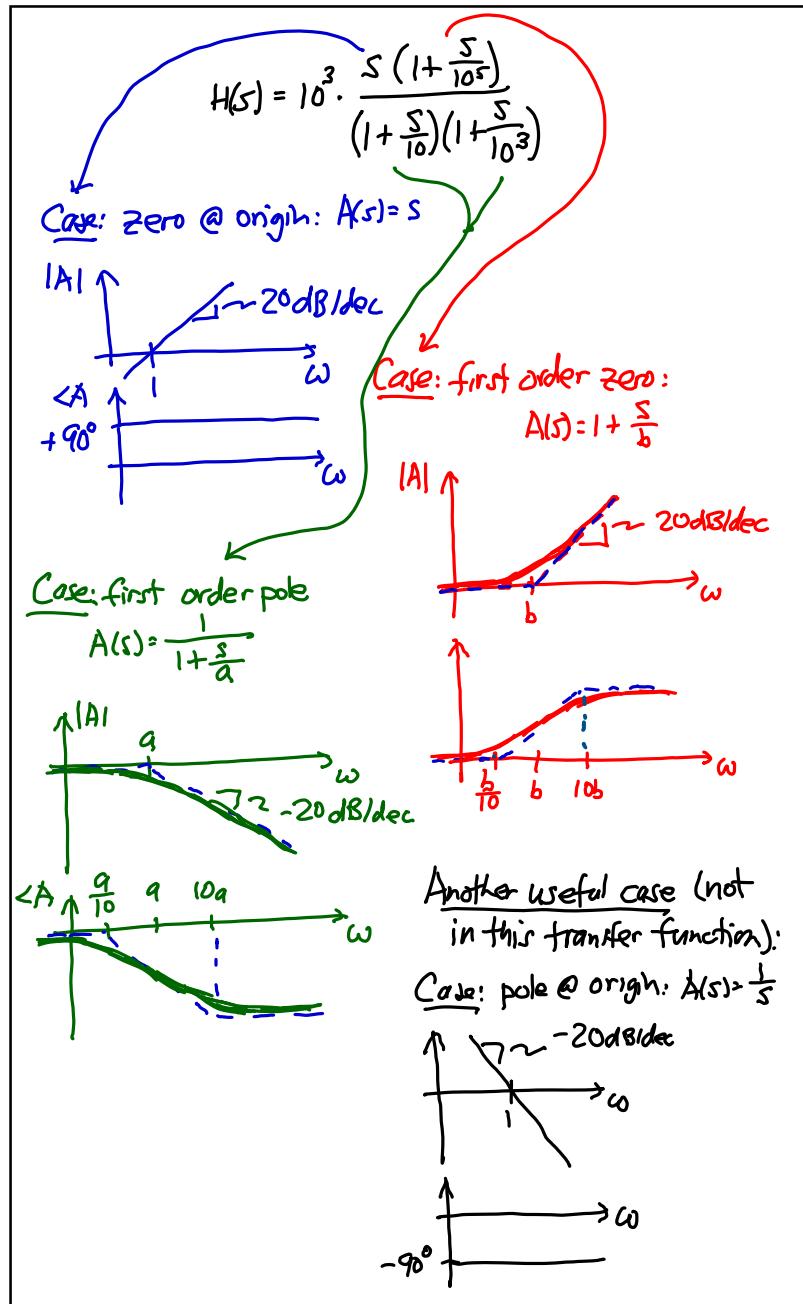Lecture 4w: Amplifiers

Lecture 4w: Amplifiers

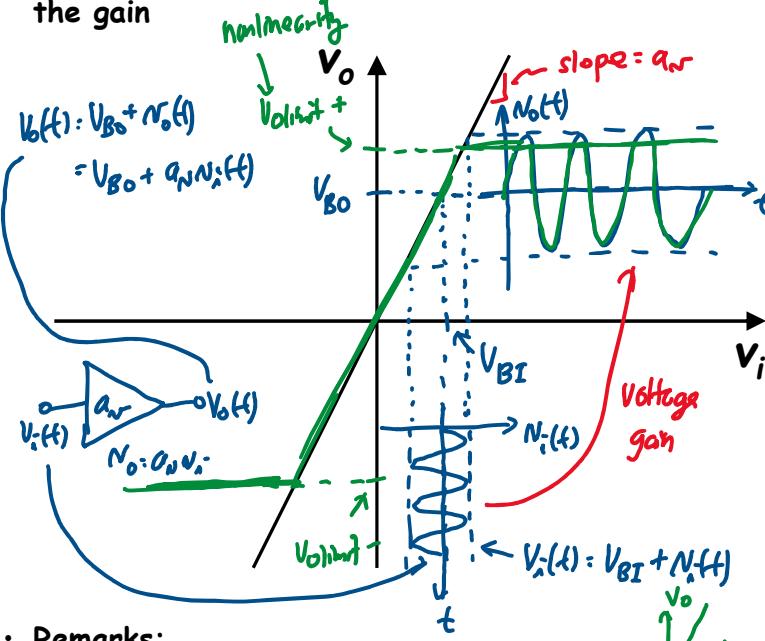
- Amplification:
- Really just boils down to creating a transfer function with a large slope, where the slope equals the gain




- Remarks:
- The large slope does not come for free
  - generally requires power if you want power gain
- Ideal amplifier generally has an infinite linear line transfer function
- Power and device non-ideality prevent a truly ideal amplifier
  - Power rails limit the acceptable input/output range
  - Device nonlinearity limits the linear range
  - Noise limits the minimum detectable signal
  - Parasitic elements, e.g., capacitors, limit the frequency range (i.e., the bandwidth)

Amplifier Models

⇒ generally given the symbol:

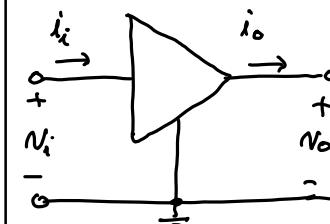

or more  
Simply

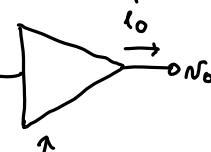

Here, it is understood  
that everything  
refers to the same  
ground

We can interpret a given amplifier as any of four types:

- ① Voltage Amplifier:  $V_i \rightarrow V_o$   
(g-parameter model fits best)
- ② Current Amplifier:  $i_i \rightarrow i_o$   
(h-parameter model fits best)
- ③ Transconductance Amplifier:  $V_i \rightarrow i_o$   
(y-parameter model fits best)
- ④ Transresistance Amplifier:  $i_i \rightarrow N_o$   
(z-parameter model fits best)

This class will mainly  
see these

Lecture 4w: Amplifiers


- All of these are equivalent representations, each comprising a gain factor along with an input and output resistance that model the resistance seen looking into the amplifier terminals
- Take for example a voltage amplifier:

Voltage Amplifier

$\Rightarrow$  most appropriate general model is the

g-parameter model  $\rightarrow$  Defining Equations:

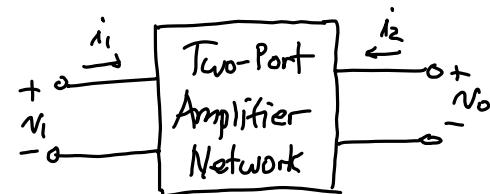Note the matrix form  $\begin{cases} i_1 = g_{11}V_1 + g_{12}i_2 \\ V_2 = g_{21}V_1 + g_{22}i_2 \end{cases}$



|||

