

Lecture 5: Ideal Op Amps

- Announcements:
- HW#2 online and due next Friday via Gradescope
- Labs have started
- -----
- Lecture Topics:
 - ↳ Amplifier Models (2-port networks)
 - ↳ Input R_i
 - ↳ Output R_o
 - ↳ Ideal Voltage Amplifier
 - ↳ Ideal Op Amps
 - ↳ Negative Feedback
 - ↳ Op Amp Circuits
- -----
- Last Time:
- Going through amplifier models
- Now, continue with this ...


- All of these are equivalent representations, each comprising a gain factor along with an input and output resistance that model the resistance seen looking into the amplifier terminals
- Take for example a voltage amplifier:

Voltage Amplifier


⇒ most appropriate general model is the


g-parameter model → Defining Equations:

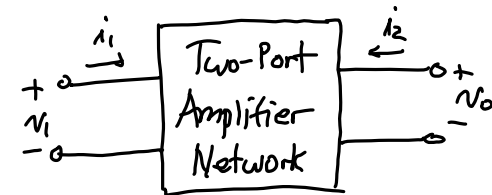Note the matrix form →
$$\begin{cases} i_1 = g_{11}v_1 + g_{12}i_2 \\ v_2 = g_{21}v_1 + g_{22}i_2 \end{cases}$$



|||

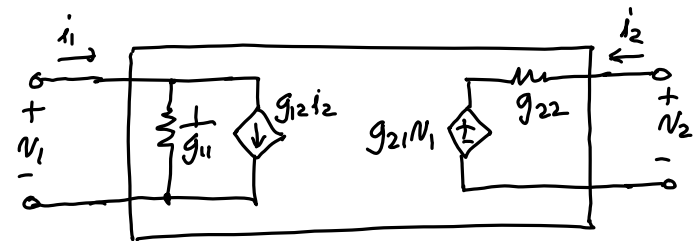

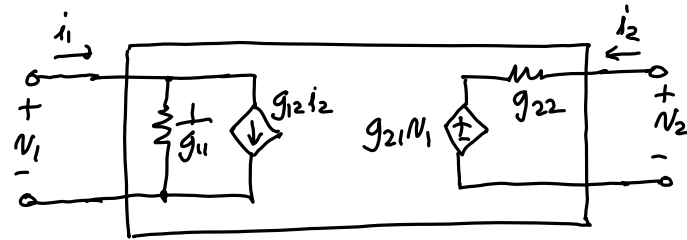

where:


$g_{11} = \frac{i_1}{v_1} \Big|_{i_2=0}$ = open-circuit input conductance
 input \rightarrow i_1 \leftarrow v_1 \leftarrow $i_2=0$ \leftarrow open-ckt the output

$g_{12} = \frac{i_1}{i_2} \Big|_{v_1=0}$ = reverse short-circuit current gain
 input \rightarrow i_1 \leftarrow i_2 \leftarrow $v_1=0$ \leftarrow short-ckt the input


$g_{21} = \frac{v_2}{v_1} \Big|_{i_2=0}$ = forward open-circuit voltage gain

$g_{22} = \frac{v_2}{i_2} \Big|_{v_1=0}$ = short-circuit output resistance

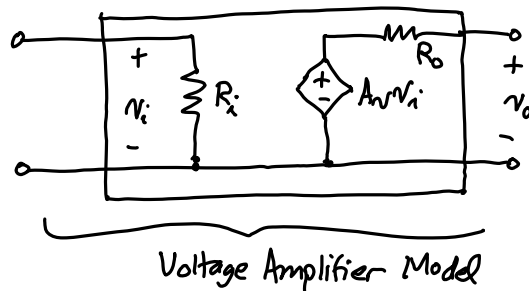Assuming a design to amplify in the forward direction \rightarrow neglect the current source $g_{12}i_2$ in the g -parameter model \rightarrow the result:



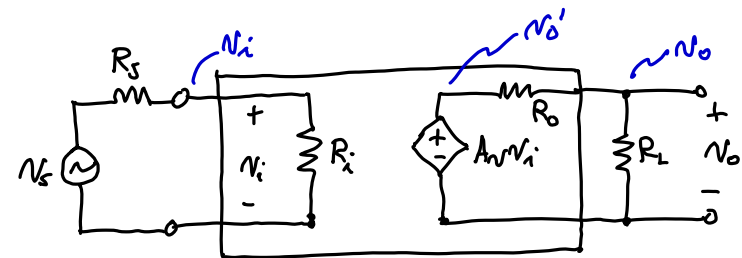$\Rightarrow R_i \neq R_o$ directly influence the total voltage gain via the input & output voltage dividers:




$$\frac{v_i}{v_s} = \frac{R_i}{R_i + R_s} \quad \frac{v_o'}{v_i} = A_v \quad \frac{v_o}{v_o'} = \frac{R_L}{R_L + R_o}$$

$$\therefore \frac{v_o}{v_s} = \frac{R_i}{R_i + R_s} A_v \frac{R_L}{R_L + R_o} = \text{total voltage gain} \neq A_v$$

$\frac{v_o}{v_s} = \frac{v_i}{v_s} \cdot \frac{v_o'}{v_i} \cdot \frac{v_o}{v_o'}$ \leftarrow these terms attenuate the intended gain! \uparrow ideal

\rightarrow get when $R_i = \infty \neq R_o = 0 \leftarrow$ These values define an ideal voltage amplifier!

To Determine R_i

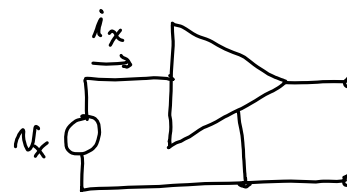


① Apply test voltage source, v_x .

② Measure resulting current, i_x .

③ $R_i = \frac{v_x}{i_x} \leftarrow$ same as $\frac{1}{g_{11}} = \frac{v_1}{i_1} \Big|_{i_2=0}$ from the g -parameter model

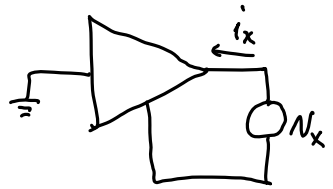
To Determine R_o (for a voltage amplifier)



- ① Ground input. (Zero out all independent sources.)
- ② Apply test voltage source, N_x .
- ③ Measure resulting current, i_x .
- ④ $R_o = \frac{N_x}{i_x}$ ← same as $g_{22} = \frac{v_2}{i_2} |_{v_1=0}$ from the g-parameter model

Ideal Operational Amplifier (op amps)

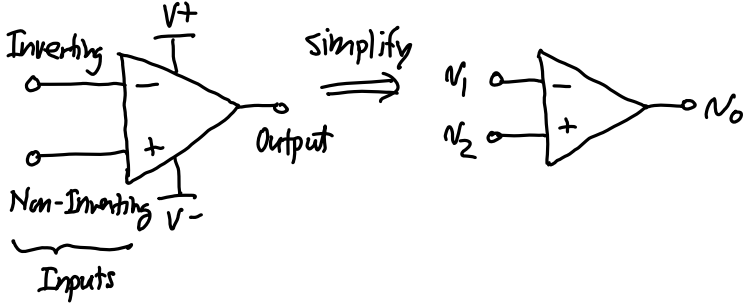
⇒ the work horse of analog electronics
 ⇒ combinations of op amps w/ feedback components allow realization of analog computers, sampled-data systems, A/D converters, DAC's, instrumentation amplifiers, ...
 ⇒ in general, have a minimum of 5 terminals:




Why Have 2 Inputs?

- ① To get a virtual ground for op amp ckt.
- ② To suppress common-mode noise.

Suppose we had only a single input:

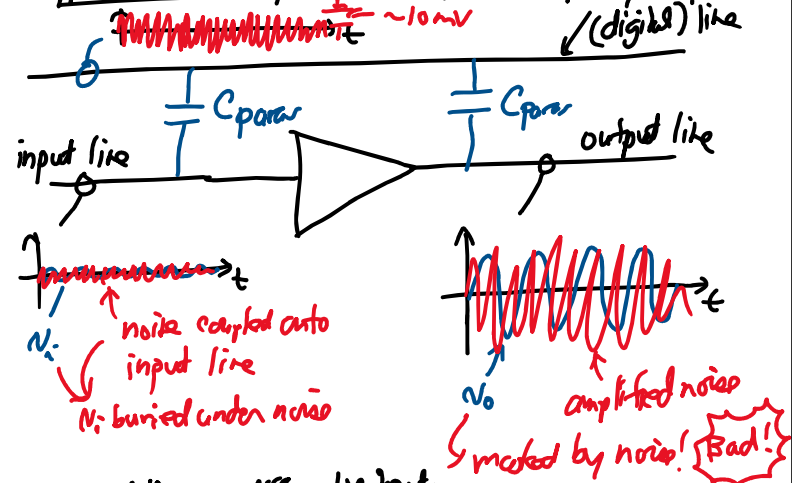


Can avoid this w/ differential input:

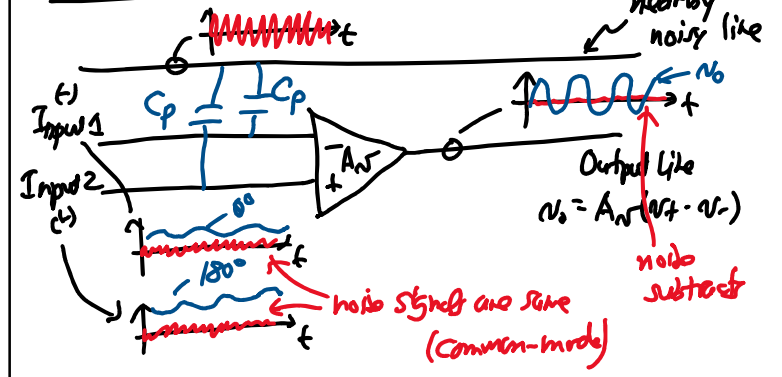

- Remarks: (on neg. FB)
- Neg. FB can insure $v_o = \text{finite}$ even with $a = \text{infinity}$
- Overall closed-loop gain (or transfer function) is dependent only on external components (e.g., β)
- Overall closed-loop gain S_o/S_i is independent of amplifier gain a
- This is very important, since it's easy to get large amplifier gain, but it's hard to get an exact value
 - ↳ If you're shooting for $a = 50,000$, you might get 47,000 or 60,000 instead
 - ↳ But it won't matter much in the feedback ckt.

Op Amp Ckts.

Example. Inverting Amplifier

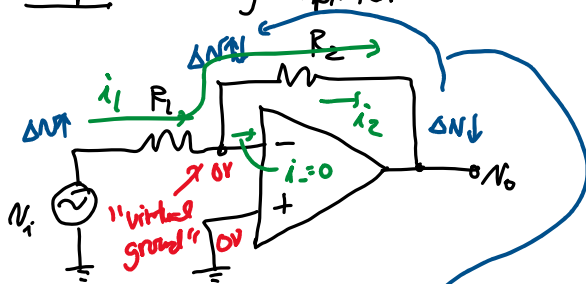

- ① Verify that we have neg. FB $\checkmark \therefore$ ideal op amp rules apply!
- ② $v_o = \text{finite} \rightarrow v_+ = v_- = \text{virtual ground}$

③ $i = 0$

$$i_1 = \frac{v_i - 0}{R_1} = \frac{v_i}{R_1} = i_2$$

$$v_o = -i_2 R_2$$

$$v_o = -\left(\frac{v_i}{R_1}\right) R_2 = -\frac{R_2}{R_1} v_i$$

$$\therefore \boxed{\frac{v_o}{v_i} = -\frac{R_2}{R_1}}$$