

Lecture 6: Finite Gain & Bandwidth

- Announcements:
- HW#2 online and due Friday via Gradescope
- Lab#2 online
- Lots of SPICE this week


- Lecture Topics:
  - ↳ Ideal Op Amp Circuits
  - ↳ Non-Ideal Op Amp Bode Plot
  - ↳ Finite Gain & Bandwidth
  - ↳ Closed Loop Amplifier Freq. Response
    - Non-Inverting Amplifier
    - Inverting Amplifier

- Last Time:
- Op amp circuit example
- Now, continue with this ...

- Remarks: (on neg. FB)
- Neg. FB can insure  $v_o = \text{finite}$  even with  $a = \text{infinity}$
- Overall closed-loop gain (or transfer function) is dependent only on external components (e.g.,  $\beta$ )
- Overall closed-loop gain  $S_o/S_i$  is independent of amplifier gain  $a$
- This is very important, since it's easy to get large amplifier gain, but it's hard to get an exact value
  - ↳ If you're shooting for  $a = 50,000$ , you might get 47,000 or 60,000 instead
  - ↳ But it won't matter much in the feedback ckt.

Op Amp Ckts.

Example. Inverting Amplifier

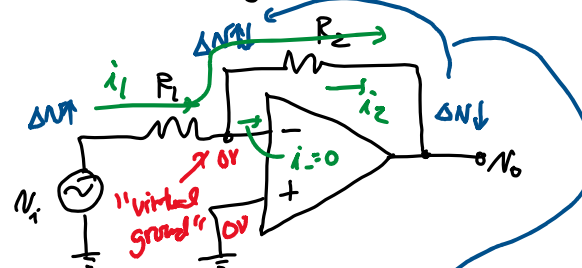

- ① Verify that we have neg. FB  $\checkmark$   $\therefore$  ideal op amp rules apply.
- ②  $v_o = \text{finite} \rightarrow v_+ = v_- = \text{virtual ground}$

③  $i_3 = 0$

$$i_1 = \frac{v_i - 0}{R_1} = \frac{v_i}{R_1} = i_2$$

$$v_o = -i_2 R_2$$

$$\therefore \frac{v_o}{v_i} = -\frac{R_2}{R_1}$$

Another Example:

Blow up!  
 ↓  
 Head for the supply rails:  
 either L+ or L-

① Verify neg. FBX  
 ↓  
 Can no longer say  $V_+ = V_-$   
 Can still say:  $i_- = i_+ = 0$ , since  $R_i = \infty$

Non-Ideal Op Amps

Finite Op Amp Gain & Bandwidth

For an ideal op amp,  $A = \infty$ . (gain) finite DC gain  
 In reality, the gain goes as:  $A(s) = \frac{A_0}{1 + \frac{s}{\omega_b}}$

$|A(j\omega)|$  [dB]

open-loop op amp response  
 $\sim 20 \text{ dB/dec}$   
 0 dB  
 $\uparrow$   
 gain=1  
 $\omega_b$   
 $\omega_T$   
 $\omega$  (log)

$\omega_T \triangleq$  unity gain frequency = freq. @ which  $|A(j\omega)| = 1$  (= 0dB)

At  $\omega_T$ :  $|A(j\omega_T)| = \frac{A_0}{\sqrt{1 + (\frac{\omega_T}{\omega_b})^2}} \xrightarrow{[\omega_T \gg \omega_b]} \frac{A_0}{\frac{\omega_T}{\omega_b}} = 1 \rightarrow \boxed{\omega_T = A_0 \omega_b}$   
gain bandwidth

$[ \text{For } \omega \gg \omega_b ] \Rightarrow A(s) = \frac{A_0}{s} = \frac{A_0 \omega_b}{s} = \frac{\omega_T}{s} \Rightarrow \frac{f_T}{f}$

$A(s) = \frac{A_0}{1 + \frac{s}{\omega_b}} \Rightarrow A(j\omega) = \frac{A_0}{1 + j\frac{\omega}{\omega_b}} \Rightarrow |A(j\omega)| = \frac{A_0}{\sqrt{1 + (\frac{\omega}{\omega_b})^2}}$

$[ \omega \gg \omega_b ] \rightarrow \frac{A_0}{\sqrt{(\frac{\omega}{\omega_b})^2}}$

An op amp ultimately is an integrator with time constant  $\tau = \frac{1}{\omega_T}$ .

$\omega_T$  in datasheet

Frequency Response of a Closed Loop Amplifier

Example. Non-Inverting Amplifier

$v_+ = v_i$   
 $i_- = 0$   
 $v_- = v_+ - \frac{v_o}{A(s)}$   
 $v_- = v_i - \frac{v_o}{A(s)}$

Find an expression for gain as a function of freq.

① Brute force Determination:

KCL ①:  $\frac{v_o - v_-}{R_2} = \frac{v_-}{R_1} + \frac{v_o}{R_2} = v_- \left( \frac{1}{R_1} + \frac{1}{R_2} \right)$

$\frac{v_o}{R_2} = (v_i - \frac{v_o}{A(s)}) \left( \frac{1}{R_1} + \frac{1}{R_2} \right) \Rightarrow \frac{v_o}{v_i}(s) = \frac{1 + \frac{R_2}{R_1}}{1 + \frac{1}{A(s)} \left( 1 + \frac{R_2}{R_1} \right)}$

$A(s) = \frac{A_0}{1 + \frac{s}{\omega_b}}$

Accounting for finite gain & BW

$\frac{v_o}{v_i}(s) = \frac{1 + \frac{R_2}{R_1}}{1 + \frac{1}{A_0} \left( 1 + \frac{R_2}{R_1} \right) + \frac{s}{\omega_b} \frac{1}{A_0} \left( 1 + \frac{R_2}{R_1} \right)}$


$[A_0 = \text{large}] \Rightarrow \left( \frac{1}{A_0} \left( 1 + \frac{R_2}{R_1} \right) \ll 1 \right)$

Here, we're essentially saying that the op amp gain is close to ideal & the non-ideality is mostly finite BW


$\frac{v_o}{v_i}(s) = \left( 1 + \frac{R_2}{R_1} \right) \frac{1}{1 + \frac{s}{A_0 \omega_b \left( \frac{R_1}{R_1 + R_2} \right)}}$

Near Ideal Gain, but Finite BW

② More insightful way to do this:

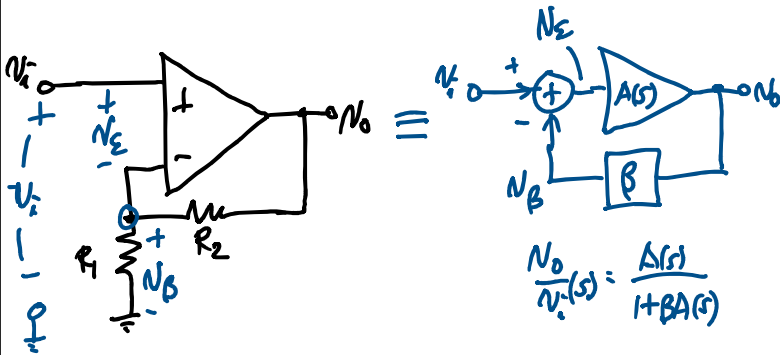

What is \$\beta\$?

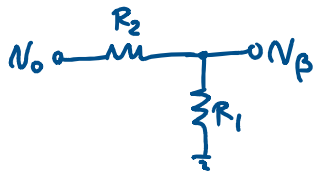

$$\beta = \frac{N_B}{N_o} = \frac{R_1}{R_1 + R_2}$$

Recall fr previous analysis:


$$\frac{N_o}{N_i}(s) = \frac{A(s)}{1 + \beta A(s)}$$

$$\left[ A(s) \cdot \frac{A_0}{1 + \frac{s}{\omega_b}} \right] \frac{N_o}{N_i}(s) = \frac{\frac{A_0}{1 + \frac{s}{\omega_b}}}{1 + \beta \left( \frac{A_0}{1 + \frac{s}{\omega_b}} \right)}$$

\*

$$\frac{N_o}{N_i}(s) = \underbrace{\frac{A_0}{1 + \beta A_0}}_{\text{DC Gain Term (midband gain)}} \underbrace{\frac{1}{1 + \frac{s}{\omega_b(1 + \beta A_0)}}}_{\text{Frequency Shaping Term}}$$

For lab 12:

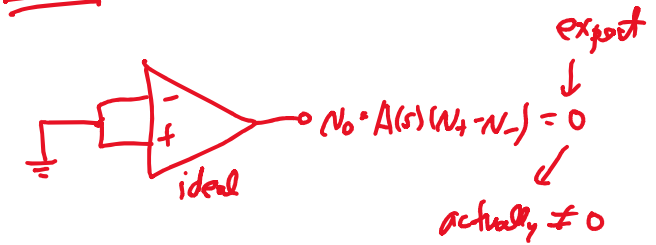

actually \$\neq 0\$

