

Lecture 7: Non-Ideal Op Amp Circuits

- **Announcements:**
- HW#3 online and due Friday via Gradescope
- Due in lab session next week:
 - ↳ Lab#2 prelab
 - ↳ Lab#1 writeup
-
- **Lecture Topics:**
 - ↳ Closed Loop Amplifier Freq. Response
 - Non-Inverting Amplifier
 - Inverting Amplifier
-
- **Last Time:**
- Non-inverting amplifier using finite gain-BW op amp
- Now, continue with this ...


Non-Ideal Op Amps

Finite Op Amp Gain & Bandwidth

For an ideal op amp, $A = \infty$. (gain)

In reality, the gain goes as: $A(s) = \frac{A_0}{1 + \frac{s}{\omega_b}}$

finite DC gain

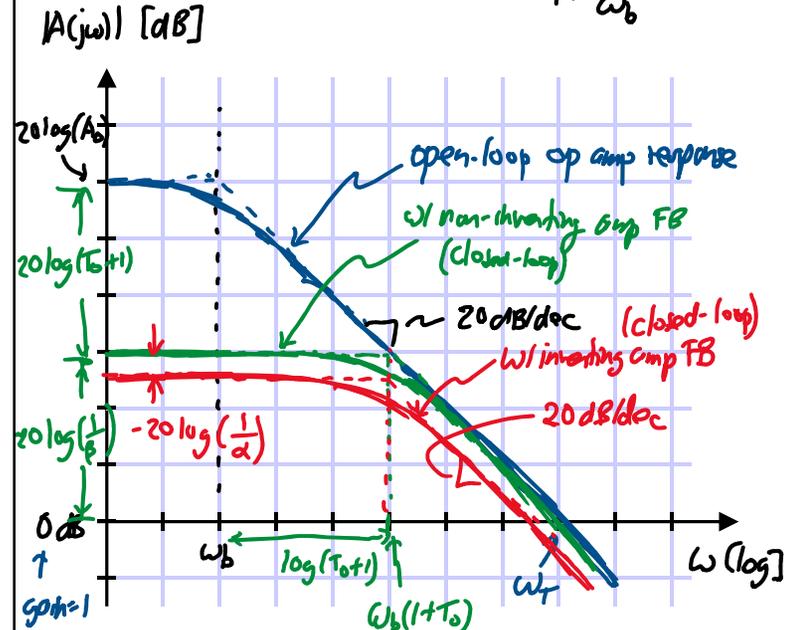

$\omega_T \triangleq$ unity gain frequency = freq. @ which $|A(j\omega)| = 1$ (= 0dB)

$$At \omega_T: |A(j\omega_T)| = \frac{A_0}{\sqrt{1 + \left(\frac{\omega_T}{\omega_b}\right)^2}} \approx \frac{A_0}{\frac{\omega_T}{\omega_b}} = 1 \rightarrow \boxed{\omega_T = A_0 \omega_b}$$

$[\omega_T \gg \omega_b]$ gain bandwidth

[For $\omega \gg \omega_b$] $\Rightarrow A(s) = \frac{A_0}{s} = \frac{A_0 \omega_b}{s} = \frac{\omega_T}{s} \Rightarrow \frac{f_T}{f}$

$A(s) = \frac{A_0}{1 + \frac{s}{\omega_b}} \Rightarrow A(j\omega) = \frac{A_0}{1 + j\frac{\omega}{\omega_b}} = |A(j\omega)| = \frac{A_0}{\sqrt{1 + (\frac{\omega}{\omega_b})^2}}$

$[\omega \gg \omega_b] \rightarrow \frac{A_0}{\sqrt{(\frac{\omega}{\omega_b})^2}}$

An op amp ultimately is an integrator with time constant $\tau = \frac{1}{\omega_T}$.

ω_T in datasheet

Frequency Response of a Closed Loop Amplifier

Example. Non-Inverting Amplifier

v_i (input), $v_o = A(s)(v_+ - v_-)$ (output)

$v_+ = v_i$, $v_- = v_o \cdot \frac{R_1}{R_1 + R_2}$

$v_+ - v_- = v_i - v_o \cdot \frac{R_1}{R_1 + R_2}$

$v_o = A(s) \left(v_i - v_o \cdot \frac{R_1}{R_1 + R_2} \right)$

Find an expression for gain as a function of freq.

① Brute force Determination:

KCL @ v_- : $\frac{v_o - v_-}{R_2} = \frac{v_- - v_i}{R_1} + \frac{v_o - v_-}{R_2} = v_- \left(\frac{1}{R_1} + \frac{1}{R_2} \right)$

$\frac{v_o}{R_2} = (v_i - \frac{v_o}{A(s)}) \left(\frac{1}{R_1} + \frac{1}{R_2} \right) \Rightarrow \frac{v_o}{v_i}(s) = \frac{1 + \frac{R_2}{R_1}}{1 + \frac{1}{A(s)} \left(1 + \frac{R_2}{R_1} \right)}$

$A(s) = \frac{A_0}{1 + \frac{s}{\omega_b}}$ (Accounting for finite gain & BW)

$\frac{v_o}{v_i}(s) = \frac{1 + \frac{R_2}{R_1}}{1 + \frac{1}{A_0} \left(1 + \frac{R_2}{R_1} \right) + \frac{s}{\omega_b} \frac{1}{A_0} \left(1 + \frac{R_2}{R_1} \right)}$


$[A_0 = \text{large}] \Rightarrow \left(\frac{1}{A_0} \left(1 + \frac{R_2}{R_1} \right) \ll 1 \right)$ Here, we're essentially saying that the op amp gain is close to ideal & the non-ideality is mostly finite BW

$\frac{v_o}{v_i}(s) \approx \left(1 + \frac{R_2}{R_1} \right) \frac{1}{1 + \frac{s}{A_0 \omega_b \left(\frac{R_1}{R_1 + R_2} \right)}}$

Near Ideal Gain, but Finite BW

Closed-loop T.F.


② More insightful way to do this:

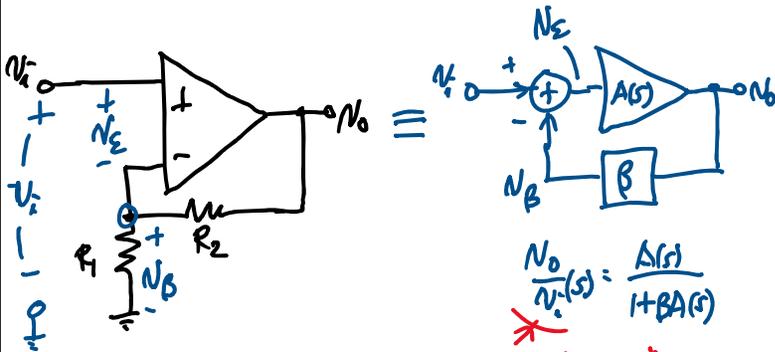

$$\frac{N_o}{N_i}(s) = \frac{A(s)}{1 + \beta A(s)}$$

✗
Closed-loop gain

What is β ?

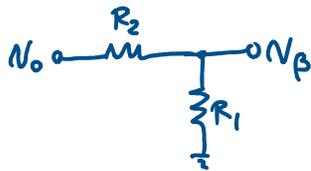

$$\beta = \frac{N_B}{N_o} = \frac{R_1}{R_1 + R_2}$$

Recall fr previous analysis:

$$\frac{N_o}{N_i}(s) = \frac{A(s)}{1 + \beta A(s)}$$

$$\left[A(s) \cdot \frac{A_o}{1 + \frac{s}{\omega_b}} \right] \rightarrow \frac{N_o}{N_i}(s) = \frac{A_o}{1 + \frac{s}{\omega_b}}$$

↑
open-loop gain

↓
*

$$\frac{N_o}{N_i}(s) = \frac{A_o}{1 + \beta A_o} \frac{1}{1 + \frac{s}{\omega_b (1 + \beta A_o)}}$$

*
↓

DC Gain Term (midband gain) → $T_o: \beta A_o \hat{=} \text{"loop gain" @ } \omega=0 \text{ (i.e., @ DC)}$
 Frequency Shaping Term
 If $A_o \rightarrow \infty$ or $\beta A_o \gg 1$ } $\Rightarrow \text{DC gain} = \frac{1}{\beta}$

plug in β :

$$[\beta A_o \gg 1] \Rightarrow \frac{N_o}{N_i}(s) \cong \frac{1}{\beta} \frac{1}{1 + \frac{s}{\omega_b \beta A_o}}$$


$$\left[\beta = \frac{R_1}{R_1 + R_2} \right] \Rightarrow \left(1 + \frac{R_2}{R_1} \right) \frac{1}{1 + \frac{s}{\omega_b A_o \left(\frac{R_1}{R_1 + R_2} \right)}} = \frac{N_o}{N_i}(s)$$

closed-loop T.F.

Observations:


- ① Closed loop DC gain = $\frac{A_o}{1+\beta A_o} = \frac{A_o}{1+T_o} \approx \frac{A_o}{T_o}$
 i.e., the closed loop gain is reduced from the open loop gain by $1+T_o \rightarrow$ show this on graph [$T_o \gg 1$]
- ② Alternatively, closed loop DC gain $\approx \frac{A_o}{\beta A_o} = \frac{1}{\beta}$ [$T_o \gg 1$]
- ③ ω_{-3dB} has increased from $\omega_b \rightarrow \omega_b(1+A_o\beta) = \omega_b(1+T_o)$
 ↳ To draw the Bode plot, just find the dc gain, draw a horizontal line across, then follow the open loop response after running into it!
- ④ Gain-BW Product = $\frac{A_o}{1+\beta A_o} \omega_b(1+\beta A_o) = A_o \omega_b = \omega_T$
 \therefore the Gain-BW product remains the same for the open & closed loop FB cases!

Example. Inverting Amplifier

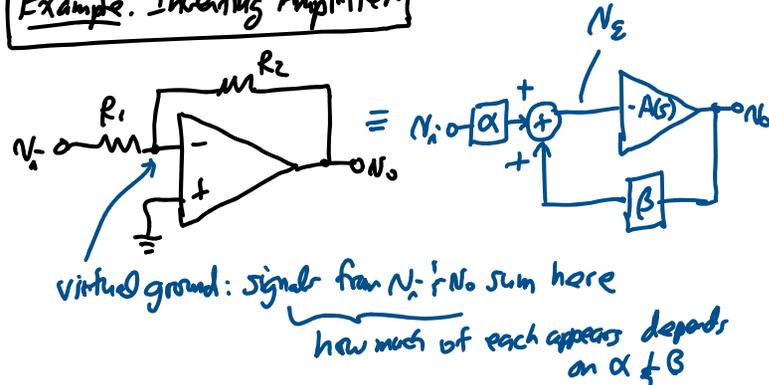


Determine α :

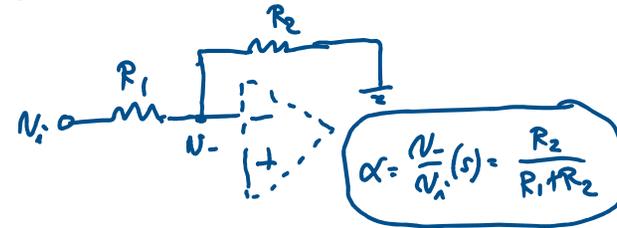- ① Ground output & open loop
- ② Feed N_i forward to get T.F. to the summing pt.



Determine β :

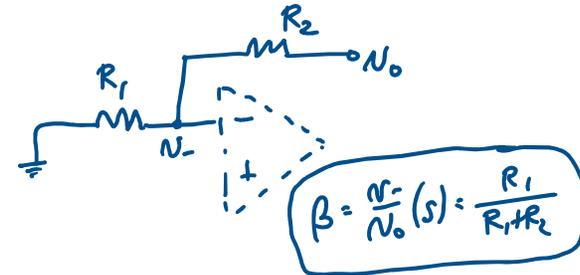- ① Ground input, open loop
- ② Feedback N_o to get T.F. to the summing pt.



Now, get the T.F. for the system block diagram:

$$\begin{cases} N_o = -A(s)N_\Sigma \\ N_\Sigma = \alpha N_i + \beta N_o \end{cases} \Rightarrow \begin{cases} N_o = -\alpha A(s)N_i - \beta A(s)N_o \\ N_o(1 + \beta A(s)) = -\alpha A(s)N_i \end{cases}$$

$$\therefore \frac{N_o}{N_i}(s) = -\frac{\alpha A(s)}{1 + \beta A(s)}$$

$$[A(s) = \frac{A_0}{1 + \frac{s}{\omega_b}}] \Rightarrow \frac{N_o(s)}{N_i(s)} = \frac{-\alpha \frac{A_0}{1 + \frac{s}{\omega_b}}}{1 + \frac{\beta A_0}{1 + \frac{s}{\omega_b}}}$$

$$\therefore \frac{N_o}{N_i}(s) = \frac{-\alpha A_0}{1 + \beta A_0} \frac{1}{1 + \frac{s}{\omega_b(1 + \beta A_0)}}$$

↑ for an inverting amplification

Remarks.

- ① Closed loop DC gain now modified by α .
- ② BW still $\omega_b(1 + \beta A_0) \rightarrow$ same as for non-inverting case
- ③ ω_T or Gain-BW product now smaller than that of open-loop amplifiers:

$$\text{gain-BW} = \alpha \omega_T$$

↑

[remember, $\alpha < 1$]

Output Saturation

