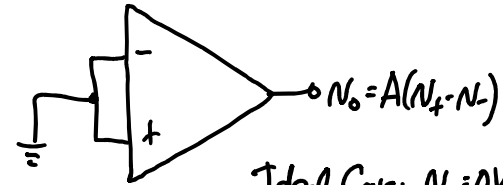


Lecture 9: Vos and Input Bias Current

- Announcements:
  - HW#3 online and due Friday via Gradescope
  - Lab#2 is a two week lab
    - ↳ Prelab is due in the second week
    - ↳ But you should have proof of having started it when you go to lab this week
    - ↳ You will still do the lab this week and continue next week
- -----
- Lecture Topics:
  - ↳ Input Offset Voltage
  - ↳ Input Bias Current
  - ↳ Generalized Circuit Elements
- -----
- Last Time:
  - Covering input offset voltage
  - Now, continue with this ...

Input Offset Voltage, Vos




Ideal Case:  $N_o = 0V$

Reality:  $N_o \neq 0V$

(usually,  $N_o = I^+ \alpha I^-$ )  
↑  
it rails out

Model this w/ equivalent ckt:


↳ contains input offset  $V_{os}$ :

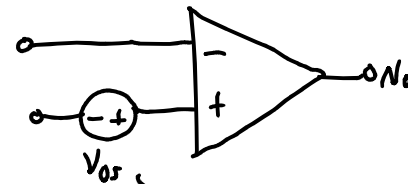



typically,  $V_{os} \sim 1mV - 5mV$

**Effect of Vos on Op Amp Ckts**

Example. Non-Inverting Amplifier

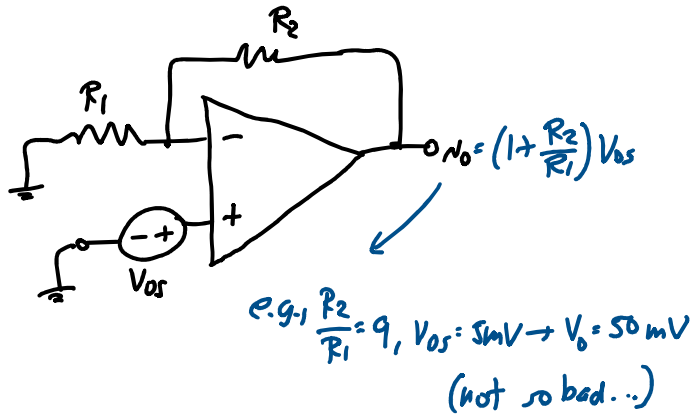

Example. Integrator

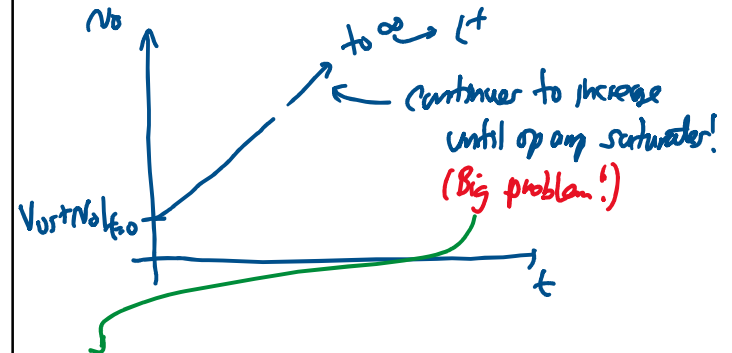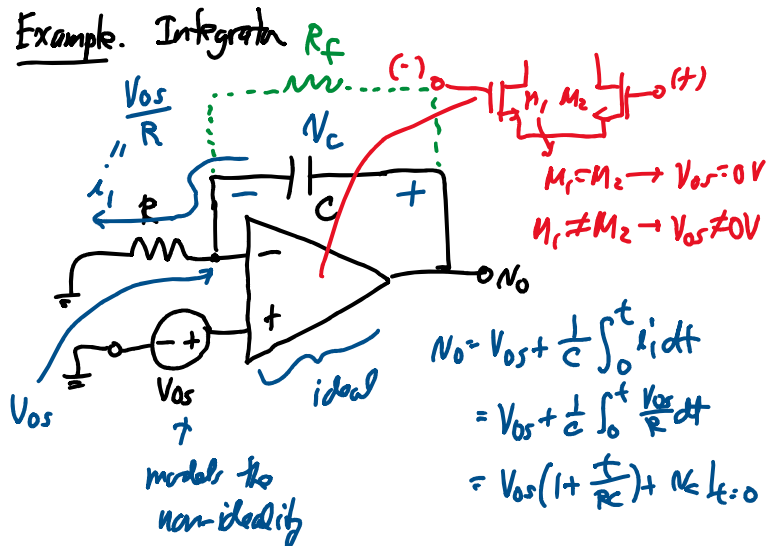

Solution: Place resistor  $R_f$  in parallel w/  $C$  (shunt)

large  $\rightarrow$  so  $R_f \parallel \frac{1}{sC} \approx \frac{1}{sC}$  @ AC

But @ DC,  $R_f$  determines the bias pt.


$V_o = V_{os} (1 + \frac{R_f}{R}) \rightarrow$  prevents the output from railing out!

**Input Bias Current**

- Many op amps require small currents into their input transistors that allow the transistors to function
- Currents are independent of Rin



Schematically:

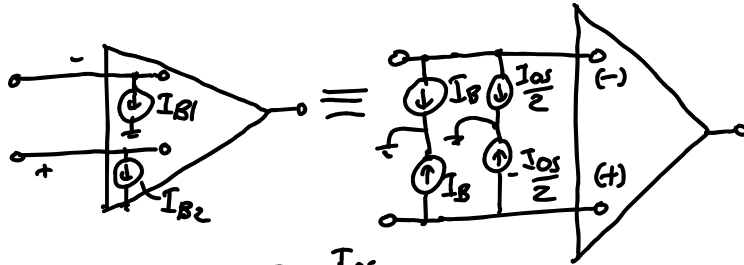


$$I_{B1} = I_B + \frac{I_{os}}{2}$$

$$I_{B2} = I_B - \frac{I_{os}}{2}$$


Average or Common-Mode Value }  $I_B = \frac{I_{B1} + I_{B2}}{2} \triangleq$  input bias current  
 (typ.: 100 nA for bipolar op amp)

Difference or Differential-Mode Value }  $I_{os} = |I_{B1} - I_{B2}| \triangleq$  input offset current  
 (typ.: 10 nA for bipolar op amp)

Example.

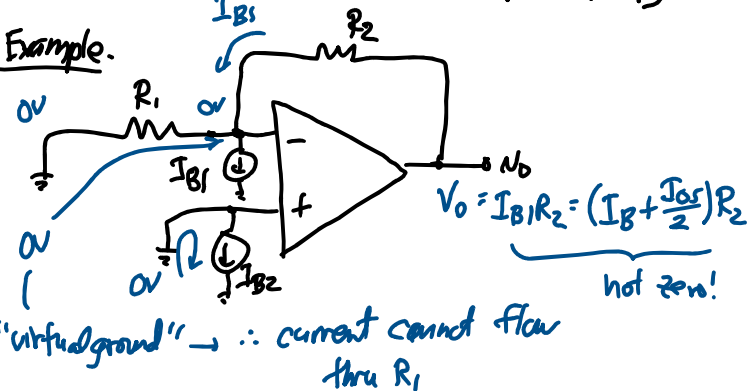

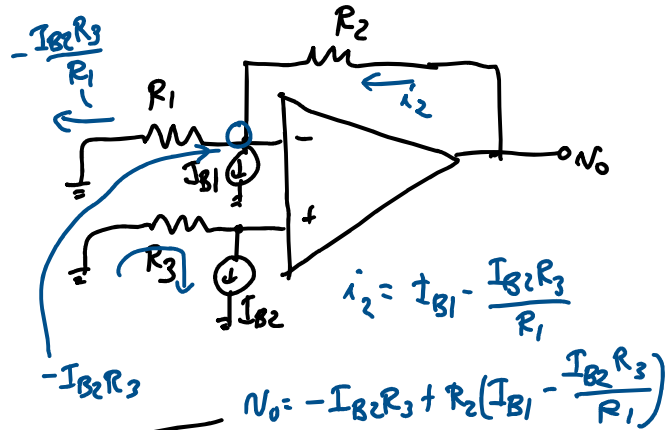To reduce this effect: add resistor to the (+) input



What value of  $R_3$  makes  $V_o \rightarrow 0V$ ?

Case  $I_{os} = 0$ : (i.e.,  $I_{B1} = I_{B2} = I_B$ )

$$V_o = I_B (R_2 - R_3 \left( 1 + \frac{R_2}{R_1} \right))$$

$$[ \text{For } V_o = 0 ] \Rightarrow R_2 = R_3 \left( 1 + \frac{R_2}{R_1} \right) \rightarrow R_3 = \frac{R_2}{1 + \frac{R_2}{R_1}} = \frac{1}{\frac{1}{R_1} + \frac{1}{R_2}}$$

$$\therefore R_3 = R_1 \parallel R_2 \rightarrow V_o = 0$$

with  $I_{os} = 0$

Case:  $I_{os} \neq 0$  (i.e.,  $I_{B1} = I_B + \frac{I_{os}}{2}$ ,  $I_{B2} = I_B - \frac{I_{os}}{2}$ )

$$V_o = -I_{B2}R_3 + R_2 \left( I_{B1} - \frac{I_{B2}R_3}{R_1} \right)$$

$$V_o = -I_B R_3 + \frac{I_{os} R_3}{2} + R_2 \left( I_B + \frac{I_{os}}{2} - \frac{I_B R_3}{R_1} + \frac{I_{os} R_3}{2 R_1} \right)$$

$[R_3 = R_1 || R_2] \Rightarrow$

$$= I_B \left( \frac{R_2}{R_1 + R_2} - \frac{R_2 R_2}{R_1 R_2} - \frac{R_1 R_2}{R_1 R_2} \right) + \frac{I_{os}}{2} \left( \frac{R_1 R_2}{R_1 R_2} + R_2 + \frac{R_2 R_2}{R_1 R_2} \right)$$

$\uparrow$   $\frac{R_2 + R_2}{R_1 R_2}$                        $\frac{I_{os} R_2 (R_1 + R_2)}{2 R_1 R_2}$

$$\therefore V_o = I_{os} R_2 \ll \left( I_B + \frac{I_{os}}{2} \right) R_2$$

$\uparrow$  10nA                       $\uparrow$  100nA     $\uparrow$  5nA

$\therefore$  setting  $R_3 = R_1 || R_2$  still helps even if  $I_{os} \neq 0!$

Generalized Circuit Elements

Resistor

Linear Resistor

$i = \frac{v}{R}$

Nonlinear Resistor

$i = f(v)$

Generalize  $\rightarrow$