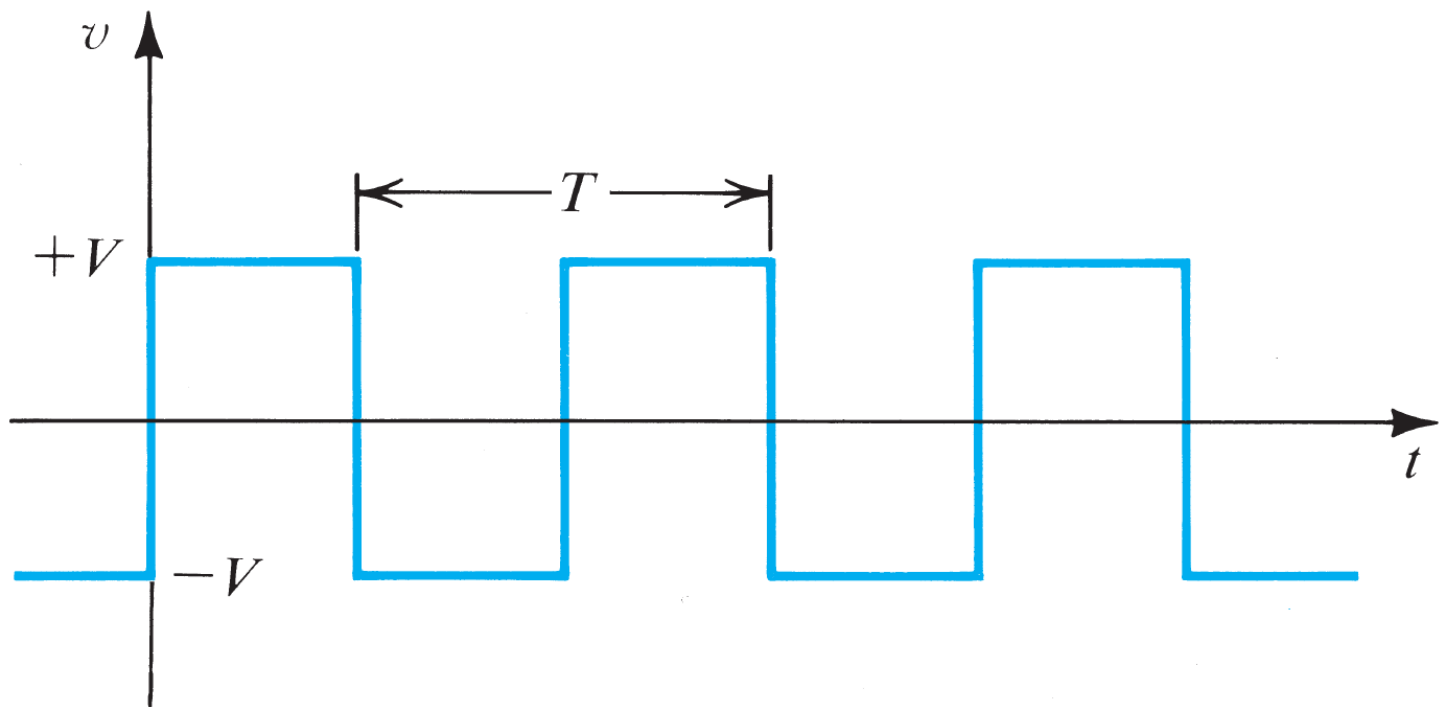


**1.32** Measurements taken of a square-wave signal using a frequency-selective voltmeter (called a spectrum analyzer) show its spectrum to contain adjacent components (spectral lines) at 98 kHz and 126 kHz of amplitudes 63 mV and 49 mV, respectively. For this signal, what would direct measurement of the fundamental show its frequency and amplitude to be? What is the rms value of the fundamental? What are the peak-to-peak amplitude and period of the originating square wave?


$$v(t) = \frac{4V}{\pi} \left( \sin \omega_0 t + \frac{1}{3} \sin 3\omega_0 t + \frac{1}{5} \sin 5\omega_0 t + \dots \right) \quad (1.2)$$



**Figure 1.5** A symmetrical square-wave signal of amplitude  $V$ .

**1.46** A buffer amplifier with a gain of 1 V/V has an input resistance of 1 M $\Omega$  and an output resistance of 20  $\Omega$ . It is connected between a 1-V, 200-k $\Omega$  source and a 100- $\Omega$  load. What load voltage results? What are the corresponding voltage, current, and power gains (in dB)?

**1.69** For the circuit shown in Fig. P1.69, find the transfer function  $T(s) = V_o(s)/V_i(s)$ , and arrange it in the appropriate standard form from Table 1.2. Is this a high-pass or a low-pass network? What is its transmission at very high frequencies? [Estimate this directly, as well as by letting  $s \rightarrow \infty$  in your expression for  $T(s)$ .] What is the corner frequency  $\omega_0$ ? For  $R_1 = 10$  k $\Omega$ ,  $R_2 = 40$  k $\Omega$ , and  $C = 1$   $\mu$ F, find  $f_0$ . What is the value of  $|T(j\omega_0)|$ ?

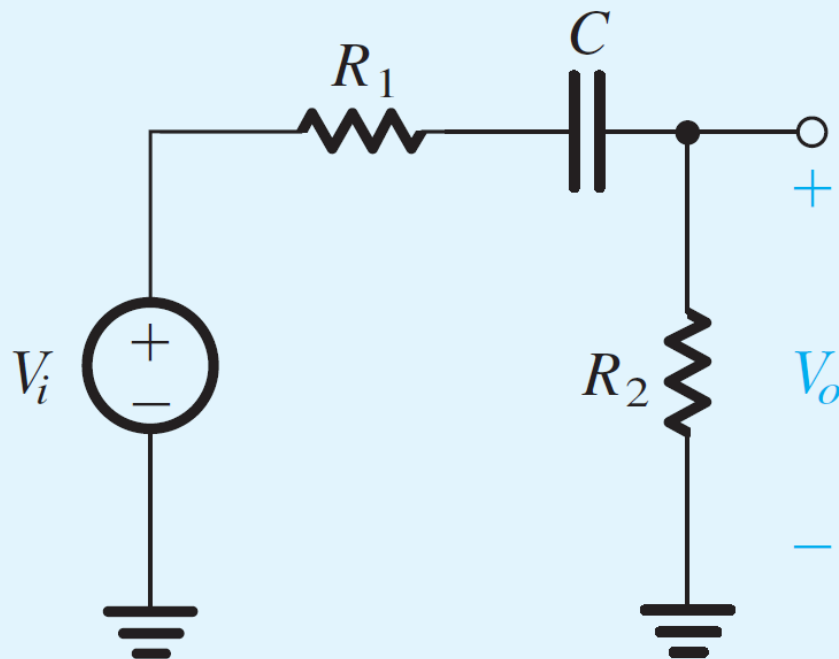

**Figure P1.69**

**Table 1.2** Frequency Response of STC Networks

	Low-Pass (LP)	High-Pass (HP)
Transfer Function $T(s)$	$\frac{K}{1 + (s/\omega_0)}$	$\frac{Ks}{s + \omega_0}$
Transfer Function (for physical frequencies) $T(j\omega)$	$\frac{K}{1 + j(\omega/\omega_0)}$	$\frac{K}{1 - j(\omega_0/\omega)}$
Magnitude Response $ T(j\omega) $	$\frac{ K }{\sqrt{1 + (\omega/\omega_0)^2}}$	$\frac{ K }{\sqrt{1 + (\omega_0/\omega)^2}}$
Phase Response $\angle T(j\omega)$	$-\tan^{-1}(\omega/\omega_0)$	$\tan^{-1}(\omega_0/\omega)$
Transmission at $\omega = 0$ (dc)	$K$	$0$
Transmission at $\omega = \infty$	$0$	$K$
3-dB Frequency	$\omega_0 = 1/\tau; \tau \equiv$ time constant $\tau = CR$ or $L/R$	
Bode Plots	in Fig. 1.23	in Fig. 1.24



**1.71** Measurement of the frequency response of an amplifier yields the data in the following table:

$f$ (Hz)	$ T $ (dB)	$\angle T$ ( $^\circ$ )
0	40	0
100	40	0
1000		
$10^4$	37	$-45$
$10^5$	20	
	0	


**\*1.77** A voltage amplifier has the transfer function

$$A_v = \frac{1000}{\left(1 + j\frac{f}{10^5}\right)\left(1 + \frac{10^2}{jf}\right)}$$


Using the Bode plots for low-pass and high-pass STC networks (Figs. 1.23 and 1.24), sketch a Bode plot for  $|A_v|$ . Give approximate values for the gain magnitude at  $f = 10$  Hz,  $10^2$  Hz,  $10^3$  Hz,  $10^4$  Hz,  $10^5$  Hz,  $10^6$  Hz,  $10^7$  Hz, and  $10^8$  Hz. Find the bandwidth of the amplifier (defined as the frequency range over which the gain remains within 3 dB of the maximum value).

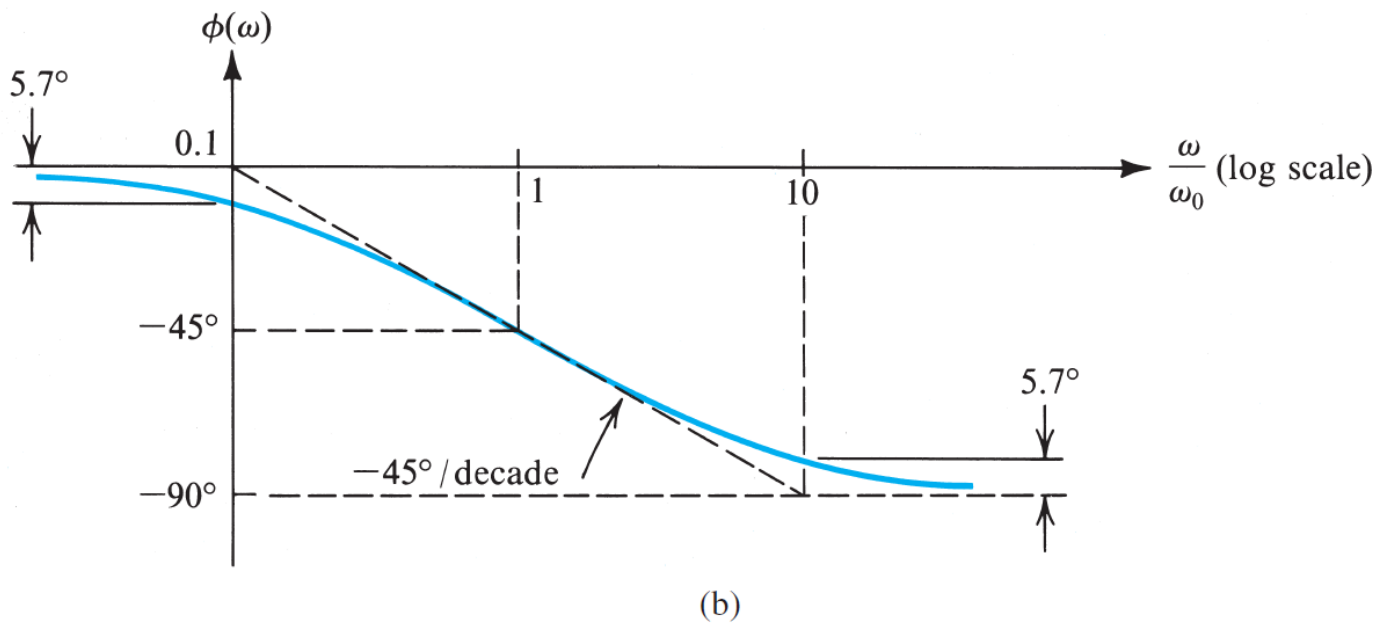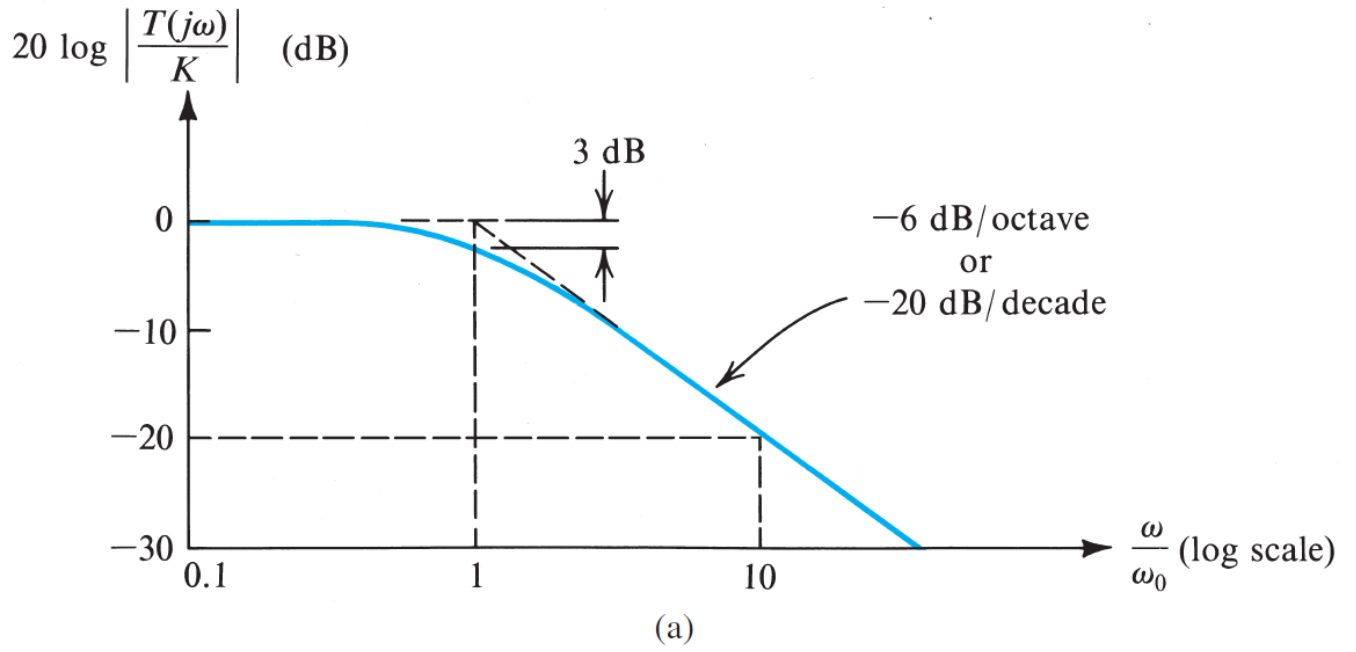

**Figure 1.23** (a) Magnitude and (b) phase response of STC networks of the low-pass type.

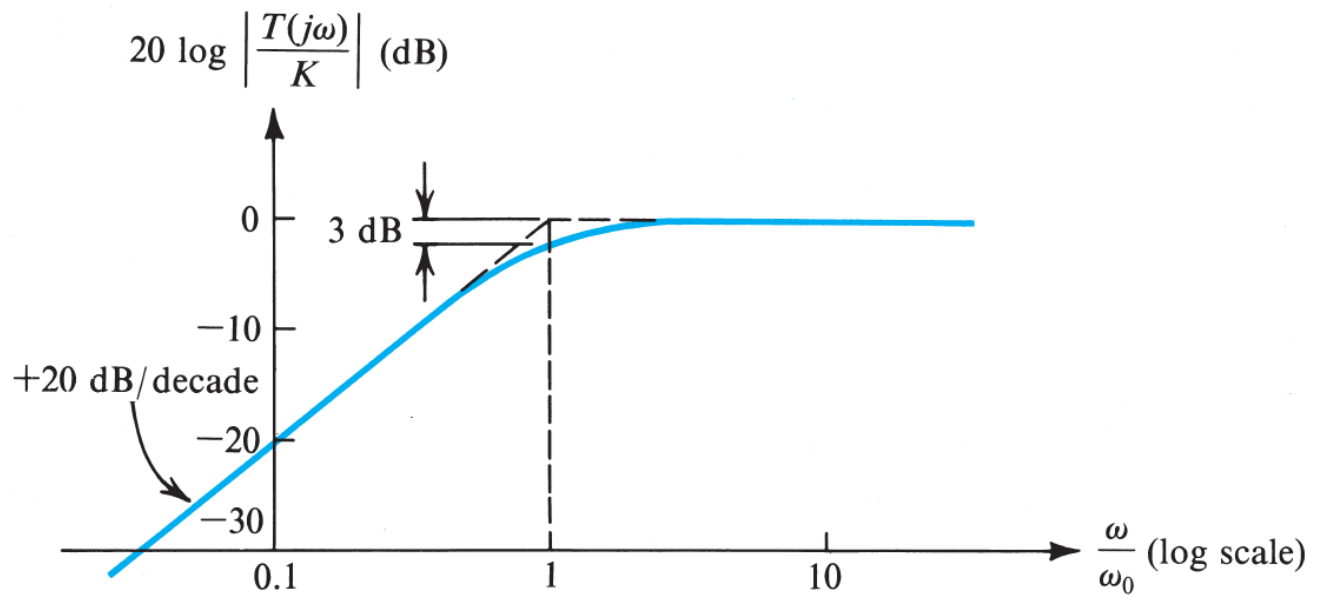

(a)

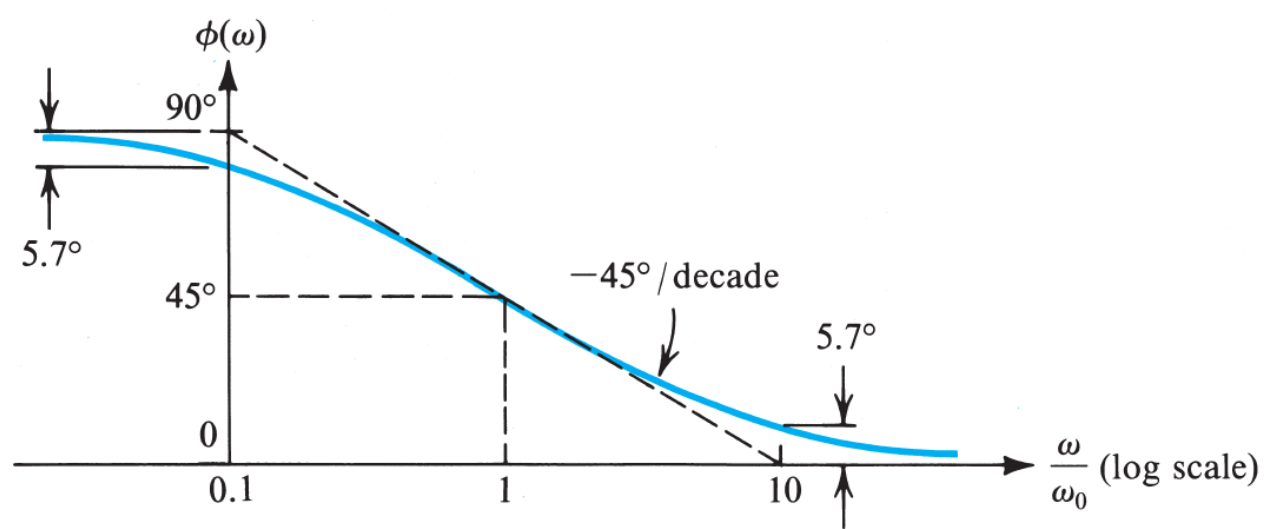

(b)

**Figure 1.24** (a) Magnitude and (b) phase response of STC networks of the high-pass type.