

**PROBLEM SET #2**

Issued: Friday, September 4, 2020

Due: Friday, September 11, 2020, at 12:00 noon via Gradescope.

Reading Assignment: Sedra & Smith, §2.1–2.5, §2.7

Unless otherwise stated, you may assume all op amps are ideal.

1. Sedra & Smith, Problem 2.23
2. For this problem, refer to the op amp circuit in Fig. PS2.1.

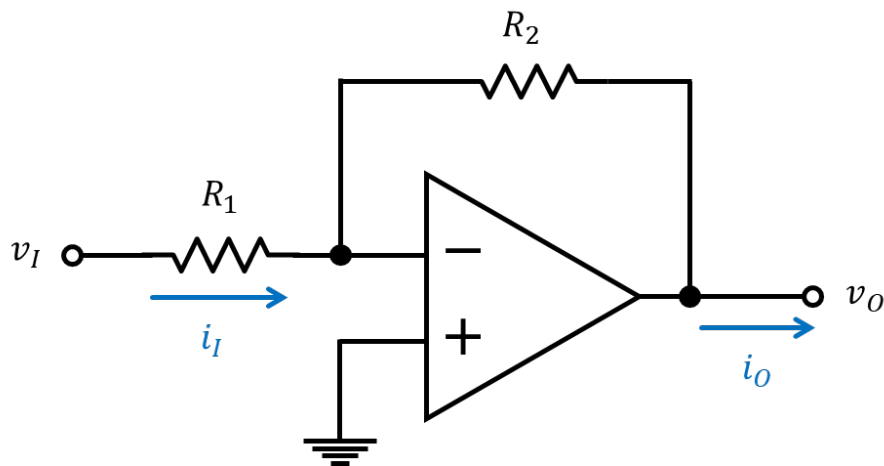


Figure PS2.1

- (a) What are the voltage gain ( $v_O/v_I$ ), input resistance, and output resistance if  $R_1 = 22 \text{ k}\Omega$  and  $R_2 = 110 \text{ k}\Omega$ ?
- (b) What is the output voltage if  $v_I = 0 \text{ V}$ ?
- (c) What is the output voltage if a dc signal  $V_I = 0.22 \text{ V}$  is applied to the circuit?
- (d) What is the output voltage if an ac signal  $v_I = (0.15) \sin(2500\pi t) \text{ V}$  is applied to the circuit?
- (e) What is the output voltage if the input signal is  $v_I = 0.22 - (0.15) \sin(2500\pi t) \text{ V}$ ?
- (f) What are the input current  $i_I$ , op amp output current  $i_O$ , and voltage at the inverting input of the op amp,  $v^-$  for the input signal in part (d)?

- (g) If the op amp operates with  $\pm 12$  V power supplies and the signal  $v_I = 0.22 - V_i \sin(2500\pi t)$  is applied, what is the maximum amplitude of the input signal  $V_i$  for an undistorted output?

3. For this problem, refer to the op amp circuit in Figure PS2.2.

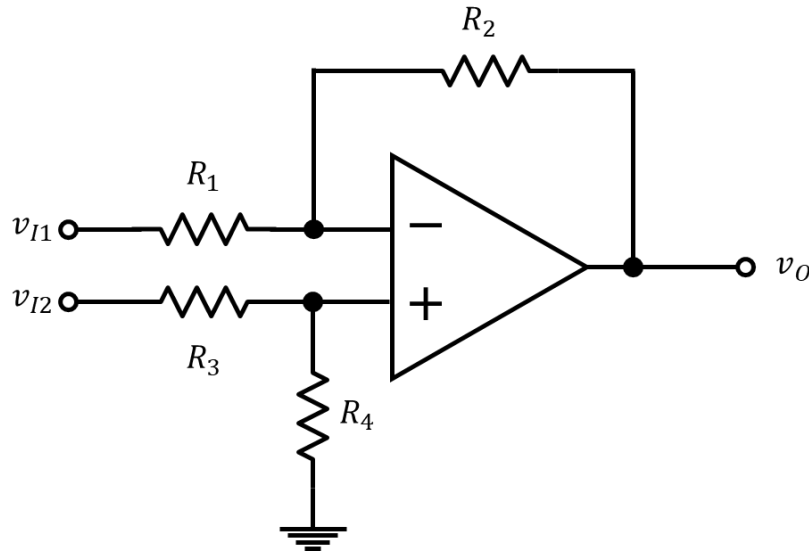


Figure PS2.2

- (a) Find the output voltage,  $v_o$  in terms of the two input voltages,  $v_{I1}$  &  $v_{I2}$ , and  $R_1$ ,  $R_2$ ,  $R_3$  and  $R_4$ .
- (b) In the special case where  $R_1 = R_2 = R_3 = R_4 = R$ , what does the expression for  $v_o$  reduce to? What “operation” is this op amp performing?
- (c) Find the input resistance seen for the following cases
- A source connected only to the  $v_{I1}$  port
  - A source connected only to the  $v_{I2}$  port
  - A source connected between the  $v_{I1}$  and  $v_{I2}$  ports.
  - A source connected to both of the  $v_{I1}$  and  $v_{I2}$  ports simultaneously.
4. Sedra & Smith, Problem 2.92. Additionally, draw the magnitude and phase Bode plots for the transfer function of your final design.