

Homework 3 Book Exercises:

2.113 Find the f_t required for internally compensated op amps to be used in the implementation of closed-loop amplifiers with the following nominal dc gains and 3-dB bandwidths:

- (a) -50 V/V; 100 kHz
- (b) $+50$ V/V; 100 kHz
- (c) $+2$ V/V; 5 MHz
- (d) -2 V/V; 5 MHz
- (e) -1000 V/V; 10 kHz
- (f) $+1$ V/V; 1 MHz
- (g) -1 V/V; 1 MHz

2.123 An op amp having a slew rate of 10 V/ μ s is to be used in the unity-gain follower configuration, with input pulses that rise from 0 to 2 V. What is the shortest pulse that can be used while ensuring full-amplitude output? For such a pulse, describe the output resulting.

2.126 For an amplifier having a slew rate of 40 V/ μ s, what is the highest frequency at which a 20-V peak-to-peak sine wave can be produced at the output?