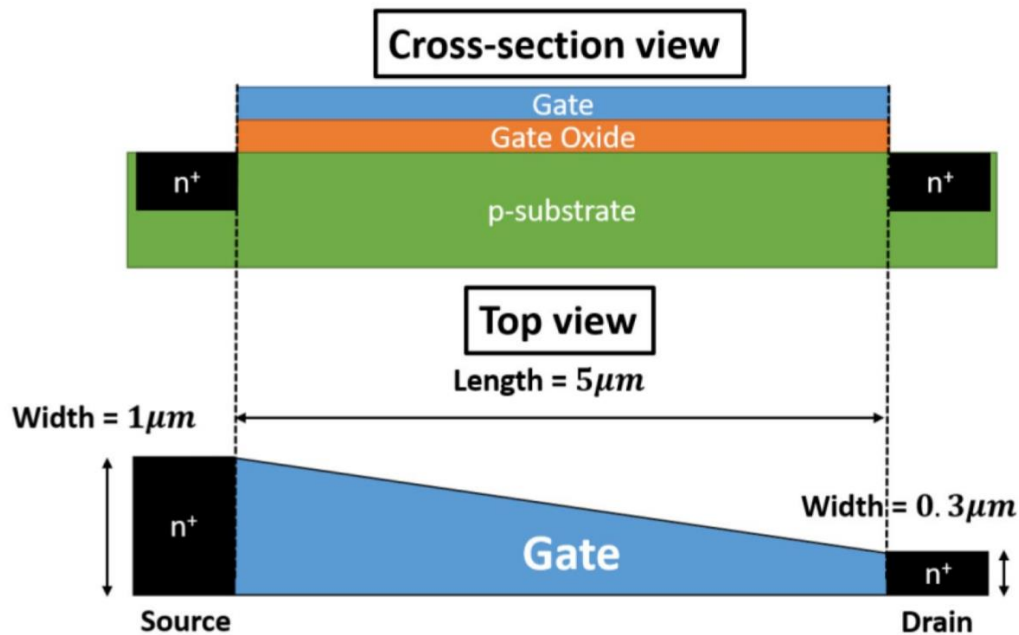


PROBLEM SET #7

Issued: Friday, October 9, 2020

Due: Friday, October 16, 2020 at 12:00 noon via **Gradescope**.

- The cross-section and top-view of an NMOS transistor are shown below. The length of the channel is $5\mu\text{m}$. The width of the channel changes linearly from $1\mu\text{m}$ at the source to $0.3\mu\text{m}$ at the drain. Derive the expression for the device current when operating in the **linear region** as a function of μ_n , C_{ox} , V_{GS} , V_{DS} and V_{TH} . Assume $\lambda=0$.



- Sedra & Smith, Problem 6.15
- Indicate the region of operation for a npn transistor biased as follows:
 - $V_{BE} = 0.7V$, $V_{BC} = 0.7V$
 - $V_{BE} = 0.7V$, $V_{BC} = -2V$
 - $V_{BE} = -0.7V$, $V_{BC} = -2V$
 - $V_{BE} = -1V$, $V_{BC} = -2V$
 - $V_{BE} = -1V$, $V_{BC} = 0.7V$
- Sedra & Smith, Problem 6.51
- Sedra & Smith, Problem 6.59
- Find the transistor operating points, V_C and V_E in the following circuits. $\beta = 60$, $V_{BE} = 0.7V$

