

Laboratory 3: Configurable Amplifiers Using Small-Signal MOS Resistors

Preliminary Exercises

This lab focuses on the use of MOS transistors as voltage-controlled variable resistors. In the lab, we will specifically demonstrate a gain-controllable (i.e., configurable) inverting amplifier and a bandwidth-controllable lowpass filter using op amps, resistors, capacitors, and a discrete MOS transistor.

The preliminary exercises in this section aim to prepare you for this lab. In completing these exercises, you should assume an NMOS transistor with the following parameters:

Transconductance Parameter, $K_n = \mu_n C_{ox}(W/L)$:	451.9 $\mu\text{A}/\text{V}^2$
Nominal Threshold Voltage, V_{t0} :	1.4 V
Surface Potential, $2\phi_f$:	0.66V
Body Effect Parameter, γ :	$0.49\text{V}^{1/2}$

Other device parameters can be found in the 'cd4007ub.mod' file online, which is a SPICE model.

1. Gain-Controllable Amplifier

- (a) For the MOS transistor circuit shown in Fig. PL3.1(a) below, calculate and tabulate (using the *Results Sheet for Preliminary Exercises*) the values of the small-signal resistance R_{MOS} from drain to source for values of control voltage V_C ranging from 0V to 10V, in steps of 1V. Then, plot your values of R_{MOS} versus V_C on a graph. Again, assume the MOS device parameters given at the beginning of this pre-lab.

 


Figure PL3.1(a)

- (b) For the inverting amplifier circuit shown in Fig. PL3.1(b) (which uses an op amp defined by 'lmc6482.mod' and an MOS transistor with parameters as in the beginning of this pre-lab defined by 'cd4007ub.mod'), calculate and tabulate (using the *Results Sheet for Preliminary Exercises*) the gain V_o/V_i of this amplifier for values of control voltage V_C ranging from 0V to 10V, in steps of 1V. Then, plot the gain versus V_C on a graph. (Hint: Be careful when determining gain at $V_C=0\text{V}$)

Assume for this pre-lab that the MOS transistors have zero leakage currents.


 


Figure PL3.1(b)

- (c) Calculate and tabulate (using the *Results Sheet for Preliminary Exercises*) the 3-dB bandwidth of the amplifier for values of V_C ranging from 2V to 10V, in steps of 1V. Use SPICE to generate Bode plots for this amplifier, for values of V_C ranging from 1V to 10V. (Plot all curves on the same graph.)

2. Bandwidth-Controlled (Unity-Gain) Filter

 - (a) For the filter circuit shown in Fig. PL3.2(a), the op amp uses the model given in 'lmc6482.mod', and the MOS transistors M_1 and M_2 use the model given at the beginning of this pre-lab and in 'cd4007ub.mod'. Assuming for now that M_1 and M_2 are identical, calculate and tabulate (using the *Results Sheet for Preliminary Exercises*) the 3dB bandwidth of the filter for values of control voltage V_C from 2V to 10V, in steps of 1V.
- (b) Using SPICE, generate Bode plots (all on the same graph) for the circuit of Fig. PL3.2(a) for values of V_C from 2V to 10V, in steps of 1V. Use the SPICE model 'cd4007ub.mod' for each NMOS transistor and use the model in 'lmc6482.mod' for the op amp.
- (c) Suppose that due to fabrication mismatches, the channel length of M_1 was 10% larger than that of M_2 (everything else remains identical). What then is the passband gain of this filter?
- (d) Suppose that due to fabrication mismatches, the nominal threshold voltage V_{t0} of M_1 was 20% larger than that of M_2 (everything else remains identical). Calculate and tabulate (using the *Results Sheet for Preliminary Exercises*) the gain V_o/V_i of the filter for control voltage V_C values from 2V to 10V, in steps of 1V. Plot the gain V_o/V_i versus V_C on a graph.



Helpful Hints for SPICE Simulation

Some notes on creating a MOSFET instance for this lab:

- (1) For the NMOS transistor, you should use the model file on the course website, 'cd4007.mod'.
- (2) To use an NMOS transistor in your netlist, you must first include the model file using a .include statement:

```
.include <path_to_model_file>
```

- (3) Then, to create an instance of the MOSFET use the following code:

```
M<name> <drain> <gate> <source> <body> <model_name> (W=<value>  
L=<value>)
```

Replace <name> with the desired name of your NMOS instance and <model_name> with the name of the NMOS model, which is defined within 'cd4007.mod'. For the CD4007UB the W is 42 μm and L is 10 μm .

- (4) To run a nested DC sweep (i.e., to sweep two sources in the same simulation), the syntax is very similar to the standard DC sweep:

```
.dc <source1> <start1> <stop1> <step1> <source2> <start2> <stop2>  
<step2>
```

Note that in this analysis, <source1> is swept while <source2> is stepped.

- (5) To run a nested AC sweep (i.e., to step a DC source while running ac sweeps for each step), the syntax is very similar to the standard AC sweep:

```
.ac <LIN|DEC|OCT> <number of samples> <fstart> <fstop> SWEEP <source>  
<start> <stop> <step>
```

Replace <source> with the name of an independent voltage source and use <start>, <stop> and <step> to set the starting voltage, final voltage and voltage step, respectively.

Laboratory 3: Configurable Amplifiers Using Small-Signal MOS Resistors
Results Sheet for Preliminary Exercises

1. Gain-Controllable Amplifier

Table PLR3.1. Gain-Controllable Amplifier Characteristics

V_C [V]	(a) R_{MOS}	(b) Gain, V_o/V_i	(c) 3dB Bandwidth
0			
1			
2			
3			
4			
5			
6			
7			
8			
9			
10			

Attach the necessary annotated plots for parts (a), (b), and (c).

2. Bandwidth-Controlled (Unity-Gain) Filter

Table PLR3.2. Bandwidth-Controllable Amplifier Characteristics

V_C [V]	(a) 3dB Bandwidth	(d) Gain, V_o/V_i
2		
3		
4		
5		
6		
7		
8		
9		
10		

(a) Fill in the table above.

(b) Attach annotated SPICE plot.

(c) Gain, $V_o/V_i =$ _____

(d) Fill in the table above and attach the necessary annotated plot.