



## Homework Assignment # 1, Due January 26, 2001

**Announcements for Week of January 16-19 see web for full details:**


**Discussion:** Sections will meet and review material from EE40

**Laboratories:** Will not meet this week. Purchase an inexpensive laboratory notebook (such as a Mead Composition book ~\$2.00) and number about 30 pages. Also procure a floppy disk to carry just in case the printer is not working.

**Textbooks:** Copies of the Howe and Sodini texts are available at ASUC (36) and Ned's Berkeley Bookstore (30).


**Reading:** H&S Chapter 1, (emphasis on circuits rather than physics), 8.4 (idealized current source), 8.2.2, 9.1 (just use of dependent sources in block stages and gain)

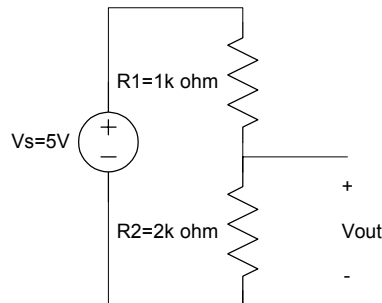1.1) **Fundamental equivalents.** Consider the following circuit:



- Find the Thevinin equivalent circuit.
- Find the Norton equivalent circuit.

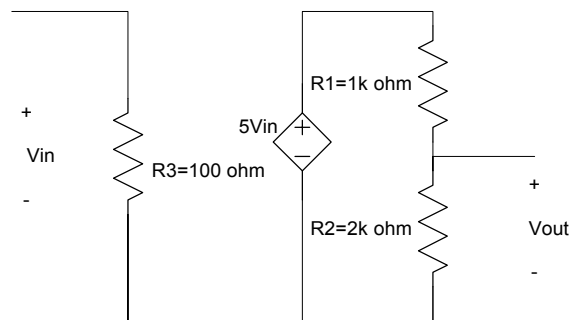
1.2) **Dependent sources.** Consider the following unloaded amplifier circuit:



- Find the open circuit voltage gain,  $V_{out}/V_{in}$ , of this amplifier.


- b) Find  $R_{out}$ , the resistance an ohm-meter would measure between the two output nodes.
- c) Find  $R_{in}$ , the resistance an ohm-meter would measure between the two input nodes.
- d) Draw the standard two-port voltage amplifier that is equivalent to the above circuit.

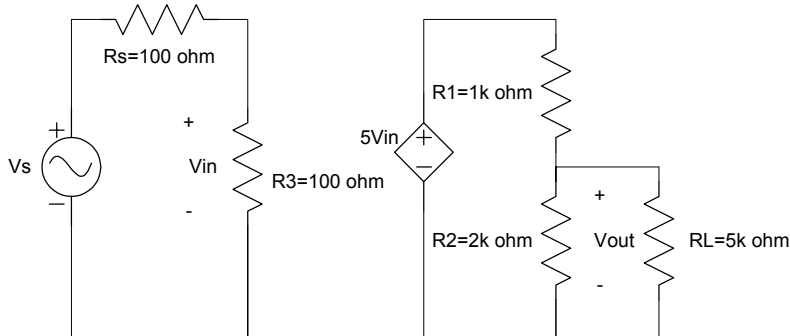1.3) **Sources and loads.** Consider the following loaded amplifier circuit with a non-ideal source.



- a) Find the overall gain of this amplifier,  $V_{out}/V_s$ , and write it in a form so that it is factored into three terms: input voltage divider, open circuit voltage gain, and output voltage divider. Hint: substituting the simplified two-port from part 1.2d into this circuit will make this problem easier.

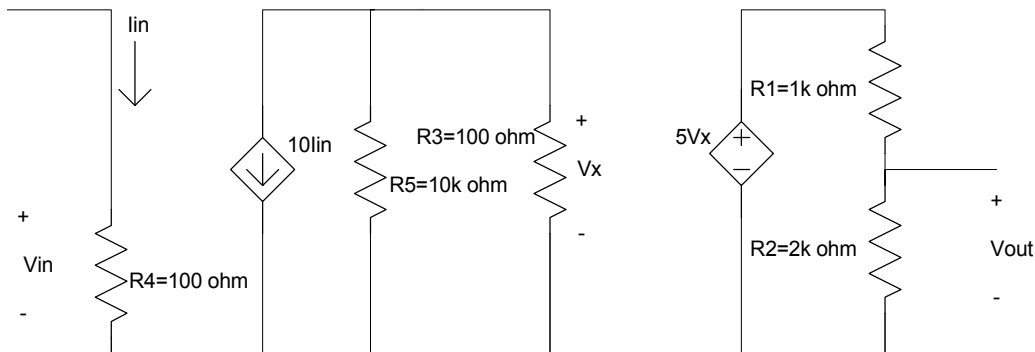1.4) **Cascaded amplifiers.** Consider the following pair of cascaded amplifier circuits:



- a) Draw the single standard two-port voltage amplifier that is equivalent to the above pair of amplifiers.