

Spring 2001 EE105 Homework #11 Solution
by Xuesong Jiang

1.1 (1) when $R_L \rightarrow \infty$, the small signal model of the CE amplifier:



The transistor is in saturation

$$I_D = \frac{1}{2} \mu_n C_0 \times \frac{W}{L} (V_{GS} - V_{TN})^2 (1 + \lambda_n V_{DS})$$

$$g_m = \frac{\partial I_D}{\partial V_{GS}} = \mu_n C_0 \times \frac{W}{L} (V_{GS} - V_{TN}) (1 + \lambda_n V_{DS}) = \frac{2 \cdot I_D}{V_{GS} - V_{TN}}$$


$$1/R_o = \frac{\partial I_D}{\partial V_{DS}} = \lambda_n \frac{1}{2} \mu_n C_0 \times \frac{W}{L} (V_{GS} - V_{TN})^2 = \frac{\lambda_n I_D}{1 + \lambda_n V_{DS}}$$

$$A_V = -g_m R_o = -\frac{2 \cdot I_D}{V_{GS} - V_{TN}} \cdot \frac{1 + \lambda_n V_{DS}}{\lambda_n I_D} = -\frac{2(1 + \lambda_n V_{DS})}{\lambda_n(V_{GS} - V_{TN})} = -100$$

$$\therefore V_{GS} = V_{TN} + \frac{2(1 + \lambda_n V_{DS})}{100 \cdot \lambda_n} = 0.7V + \frac{2 \cdot (1 + 0.05V^2 \cdot 2.5V)}{100 \cdot 0.05V} = 1.15V$$

$$V_{BIAS} = V_{GS} + (-2.5V) = -1.35V$$

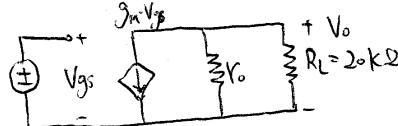When $R_L = 20k\Omega$, follow the similar way when $R_L \rightarrow \infty$



$$A_V = -g_m \cdot (R_o \parallel R_L) = -g_m \cdot \frac{R_o \cdot R_L}{R_o + R_L} = -\underbrace{g_m R_o}_{100} \cdot \frac{R_L}{R_o + R_L} = -20$$

$$\therefore \frac{R_L}{R_o + R_L} = \frac{20}{100} = \frac{1}{5} \Rightarrow R_o = 80k\Omega.$$

$$R_o = \frac{1 + \lambda_n V_{DS}}{\lambda_n I_D} \Rightarrow I_D = \frac{1 + \lambda_n V_{DS}}{\lambda_n R_o} = \frac{1 + 0.05V^2 \cdot 2.5V}{0.05V^2 \cdot 80k\Omega} = 0.28125mA = I_{SUP} \quad (\text{since } V_o = 0V)$$

$$W = \frac{2 \cdot I_{sup} \cdot L}{\mu_n C_{ox} \cdot (V_{SS} - V_{Th})^2 (1 + \lambda V_{DS})} = \frac{2 \cdot 0.28125 \text{ mA} \cdot 2 \mu\text{m}}{50 \text{ mA/V}^2 \cdot (2.45)^2 (1 + 0.5 \cdot 2.5 \text{ V})}$$

$$\approx 98.765 \mu\text{m}$$

(2)

	simulated
V_o	$\sim 100 \text{ mV}$
$A_v (R_L \rightarrow \infty)$	-100.0004
$A_v (R_L = 20 \text{ k}\Omega)$	-19.9999

Based on your assumptions, it is also possible that simulation and hand analysis doesn't match, but the assumptions should be reasonable.

The simulation matches the hand analysis.

If in your answers, the simulation and the hand analysis doesn't match, explain what assumptions you have made.

- (3) when $V_s = 0.1 \text{ V}$, the output waveform distorts and clips
 The peak-to-peak output swing is about 3.9 V when the distortion appears.

For 11.1(2)

ee105hw11

**** Rl->infinity

```
.model nmos nmos level=1 vto=0.7 kp=5e-5 lambda=0.05
m1 d g vss vss nmos w=98.765u l=2u
vdd vdd 0 2.5
vss vss 0 -2.5
isup vdd d 0.28125m
vbias g 0 -1.35

.op
.tf v(d) vbias
.end
```

**** Operating points

+0:d	=	98.0359u	0:g	=	-1.3500	0:vdd	=	2.5000
+0:vss	=	-2.5000						

**** small-signal transfer characteristics

v(d)/vbias				=	-100.0004
input resistance at	vbias			=	1.000e+20
output resistance at v(d)				=	80.0003k

Rl=20kohm

```
.model nmos nmos level=1 vto=0.7 kp=5e-5 lambda=0.05
m1 d g vss vss nmos w=98.765u l=2u
vdd vdd 0 2.5
vss vss 0 -2.5
isup vdd d 0.28125m
vbias g 0 -1.35
r1 d 0 20k
```

```
.op
.tf v(d) vbias
.end
```

**** Operating points

+0:d	=	19.6071u	0:g	=	-1.3500	0:vdd	=	2.5000
+0:vss	=	-2.5000						

**** small-signal transfer characteristics


v(d)/vbias				=	-19.9999
input resistance at	vbias			=	1.000e+20
output resistance at v(d)				=	16.0000k

Wave	Symbol
D0-A0x(d)	*


ee105hw11

For 11.1 (3)

$$V_0 = 0.1V$$

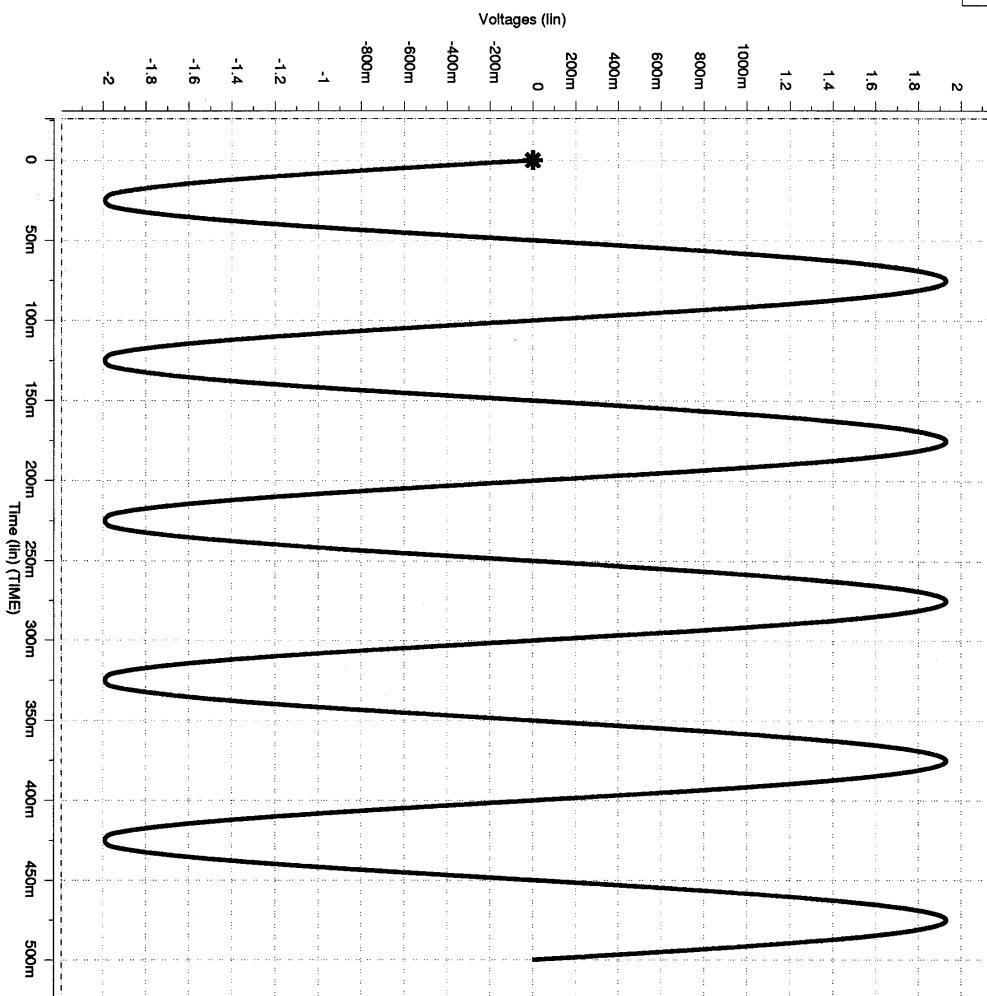

11.2 (1).

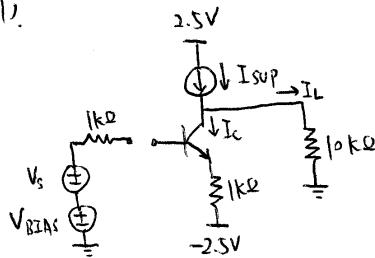

$$I_{SUP} = I_c + I_L$$


$$V_o = 0 \rightarrow I_L = 0$$

$$\therefore I_c = I_{SUP} = 200\mu A, \quad I_B = \frac{I_c}{\beta} = 2\mu A$$

$$V_{BE} = V_T \ln \frac{I_c}{I_S} = 0.026 V \cdot \ln \frac{200\mu A}{10^{-15} A} = 0.676 V$$

$$\therefore V_{BIAS} = I_B \cdot 1k\Omega + V_{BE} + I_B(\beta+1) \cdot 1k\Omega + (-2.5 V) = [-1.62 V]$$

(2) small-signal model

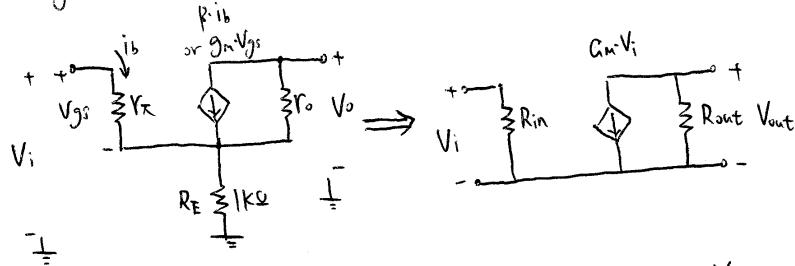

$$R_\pi = \frac{\beta}{g_m} = 13 k\Omega$$

$$g_m = \frac{I_c}{V_T} = \frac{200\mu A}{0.026 V} = 7.69 mS$$

$$R_o = \frac{V_A}{I_c} = 125 k\Omega$$

$$R_{in} = R_\pi (1 + g_m \cdot R_E) = 13 k\Omega \cdot (1 + 7.69 mS \cdot 1k\Omega) = 113 k\Omega$$

$$R_{out} = R_o (1 + g_m \cdot R_E) = 125 k\Omega \cdot (1 + 7.69 mS \cdot 1k\Omega) = 1.086 M\Omega$$


$$(3) G_m = \frac{g_m}{1 + g_m \cdot R_E} = \frac{7.69 mS}{1 + 7.69 mS \cdot 1k\Omega} = 0.885 mS$$

← I will consider this is right if it is just because of different understanding of overall transconductance

Overall transconductance

$$G_m' = \frac{R_{in}}{R_{in} + R_s} G_m \cdot \frac{R_{out}}{R_{out} + R_L} = 0.869 mS$$

(4).

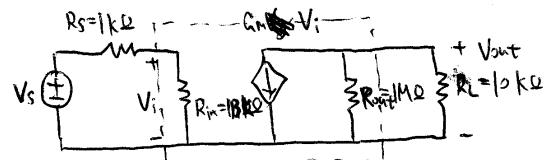


$$A_v = - \frac{R_{in}}{R_s + R_{in}} \cdot G_m \cdot \frac{R_{out} \cdot R_L}{R_{out} + R_L} = - \frac{113k\Omega}{1k\Omega + 113k\Omega} \cdot 0.885mS \cdot \frac{1M\Omega \cdot 10k\Omega}{1M\Omega + 10k\Omega}$$

$$\boxed{= -8.7}$$

II-3 (1) $V_o = 0V$ $I_o = 0A$

$$I_{BIAS} = -I_{SUP} = \boxed{-100\mu A}$$

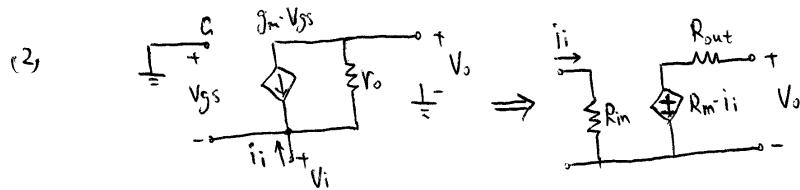Here, I neglect λ_n for g_m calculation


$$g_m = \sqrt{2\mu_n C_{ox} \frac{W}{L} \cdot I_D} = \sqrt{2 \cdot 50mA/V^2 \cdot 4/2 \cdot 100\mu A} = 141.4mS$$

$$R_o = \frac{1}{\lambda_n I_D} = \frac{1}{0.05V^2 \cdot 100\mu A} = 200k\Omega$$

$$R_{in} = \frac{1}{g_m} = \boxed{7.07k\Omega}$$

$$R_{out} = R_o(1 + g_m \cdot R_s) = 200k\Omega \cdot (1 + 141.4mS \cdot 10k\Omega) = \boxed{483k\Omega}$$

(3)

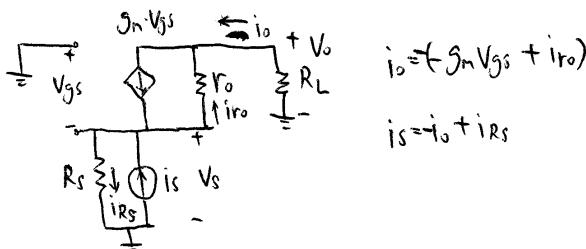

Since $r_o \gg R_s$ ($200\text{ k}\Omega$ vs. $10\text{ k}\Omega$), neglect r_o

$$i_S = i_{DS} - g_m V_{GS} = \frac{V_S}{R_S} + g_m V_S \quad (V_S = -V_{GS})$$

$$i_O = +g_m V_{GS} = -g_m V_S = g_m \cdot \frac{i_S}{g_m + \frac{1}{R_S}} = -\frac{g_m R_S}{1 + g_m R_S} i_S$$

$$\therefore A_V = \frac{i_O}{i_S} = -\frac{g_m R_S}{1 + g_m R_S} = -\frac{141.4 \text{ mS} \cdot 10 \text{ k}\Omega}{1 + 141.4 \text{ mS} \cdot 10 \text{ k}\Omega} = \boxed{-0.586}$$

$$(4). \quad V_o = -i_O \cdot R_L = -A_V \cdot i_S \cdot R_L$$

$$R_H = \frac{V_o}{i_S} = -A_V \cdot R_L = +0.586 \cdot 10 \text{ k}\Omega = \boxed{5.86 \text{ k}\Omega}$$