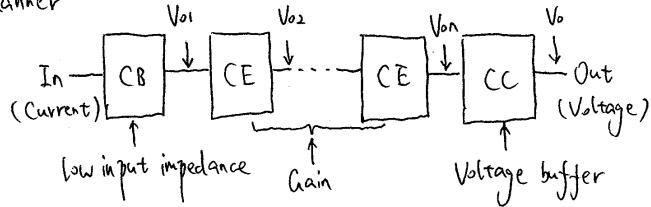


Spring 2001 EE105 Homework #12 Solution

by Xuesong Jiang

12.1. The multistage amplifier will have stages cascaded in the following

manner



The transresistance of the CB stage:

$$|R_m| = \left| \frac{V_{o1}}{I_{in}} \right| = |A_i| \cdot (R_{out_CB} \parallel R_{in_CE}) = 1 \cdot \frac{400k\Omega \cdot 100k\Omega}{400k\Omega + 100k\Omega} = 80k\Omega$$

The voltage gain of the CE stage: (one stage)

$$|Av| = \left| \frac{V_{o2}}{V_{o1}} \right| = |A_v| \cdot (R_{out_CE} \parallel R_{in_CE}) = 4mS \cdot 80k\Omega = 320$$

The voltage gain of CC stage:


$$|Av| = \left| \frac{V_o}{V_{o3}} \right| = |A_v| \cdot \frac{R_L}{R_{out_cc} + R_L} = 1 \cdot \frac{100\Omega}{100\Omega + 100\Omega} = 0.5$$

The overall transresistance is

$$|R_{m_all}| = \left| \frac{V_o}{I_{in}} \right| = |R_m| \cdot |Av| \cdot |Av_cc| = |R_m| \cdot Av \cdot Av_cc = |80k\Omega \cdot 320 \cdot 0.5| > \frac{1V}{1PA} = 10^{12}\Omega$$

$\therefore N \geq 3$

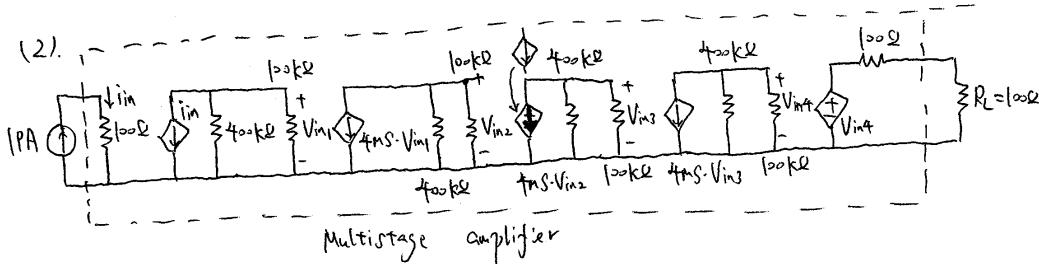(1) At least 3 building blocks are needed for the multistage amplifier



(3). The overall transresistance :

$$|R_{m-all}| = |80 \text{ k}\Omega \cdot 320^3 \cdot 0.5| = \boxed{1.31 \times 10^{12} \Omega}$$

$$(2.2. (1)) I_o = \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (V_{GS1} - V_{Th})^2 = \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (V_{DS1-sat})^2$$

$$V_{b2} = V_{GS2} + V_{DS1} = (V_{Th} + \underbrace{V_{GS2} - V_{Th}}_{V_{DS2-sat} = V_{DS1-sat}}) + 2V_{DS1-sat} = V_{Th} + 3V_{DS1-sat}$$

$$1.9V = 0.7V + 3 \cdot V_{DS1-sat} \Rightarrow V_{DS1-sat} = 0.4V$$

$$V_{b1} = V_{GS1} = V_{Th} + V_{DS1-sat} = \boxed{1.1V}$$

$$\therefore \frac{W}{L} = \frac{2I_o}{\mu_n C_{ox} (V_{DS1-sat})^2} = \frac{2 \cdot 1\text{mA}}{50\mu\text{A}/\text{V}^2 \cdot (0.4\text{V})^2} = \boxed{250}$$


$$(2) \quad \begin{array}{l} M_2(g_{m2}, r_{o2}) \\ M_1(g_{m1}, r_{o1}) \end{array} \quad R_o = r_{o2}(1 + g_{m2} \cdot r_{o1})$$

$$r_{o2} = r_{o1} = \frac{1}{\lambda \cdot I_o} = \frac{1}{0.05\text{V}^{-1} \cdot 1\text{mA}} = 20 \text{ k}\Omega$$

$$g_{m2} = \sqrt{2\mu_n C_{ox} \frac{W}{L} I_D} = \sqrt{2 \times 50\mu\text{A}/\text{V}^2 \cdot \frac{250}{1} \cdot 1\text{mA}}$$

$$= 0.0055$$
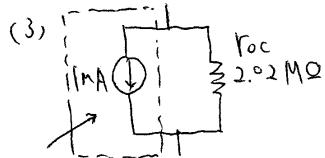
$$\therefore R_o = 20 \text{ k}\Omega \cdot (1 + 0.0055 \cdot 20 \text{ k}\Omega) = \boxed{2.02 \text{ M}\Omega}$$



The current source will be used in large signal analysis

(4). If W/L of M₁ and M₂ are doubled and I_o is kept at 1mA.

$r_{o2} = r_{o1}$ won't change, g_{m2} is proportional to $\sqrt{\frac{W}{L}}$, which will be $\sqrt{2}$ times higher

The source resistance of the current source will increase to 1.414 times the

original result in (2)

$$R_o = 2.86 \text{ M}\Omega \quad \text{or} \quad R_o \text{ is increased to } \boxed{\sqrt{2}} \cdot 2.02 \text{ M}\Omega.$$


(5) If I_o is reduced to 0.5mA, and W/L of M_2 and M_1 remain the same as in part (1).

$$R_{o1} = R_{o2} = \frac{1}{\lambda I_o} = \frac{1}{0.25 \text{ V}^2 \cdot 0.5 \text{ mA}} = 40 \text{ k}\Omega$$

$$g_m = \sqrt{2\mu_n C_{ox} \frac{W}{L}} I_o = 0.0055 \cdot \sqrt{\frac{1}{2}} = 3.54 \text{ mS}$$

$$\therefore R_o = 40 \text{ k}\Omega \cdot (1 + 3.54 \text{ mS} \cdot 40 \text{ k}\Omega) = \boxed{5.704 \text{ M}\Omega}$$

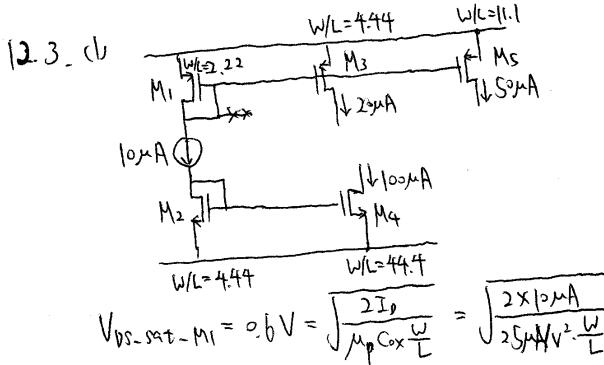The source resistance is increased by a factor of $2 \cdot 2 \cdot \sqrt{\frac{1}{2}} = \boxed{2.828}$



$$V_{ds\text{-sat-}M1} = 0.6 \text{ V} = \sqrt{\frac{2I_o}{\mu_p C_{ox} \frac{W}{L}}} = \sqrt{\frac{2 \times 10 \mu\text{A}}{25 \mu\text{A/V}^2 \cdot 0.3 \text{ V}^2}}$$

$$\therefore \left(\frac{W}{L}\right)_{M1} = 2.22, \quad \left(\frac{W}{L}\right)_{M3} = 2 \cdot \left(\frac{W}{L}\right)_{M1} = 4.44, \quad \left(\frac{W}{L}\right)_{M4} = 5 \cdot \left(\frac{W}{L}\right)_{M1} = 11.1$$

$$\left(\frac{W}{L}\right)_{M2} = \frac{2 \cdot I_o}{\mu_n C_{ox} (V_{ds} - V_{th})^2} = \frac{2 \times 10 \mu\text{A}}{50 \mu\text{A/V}^2 \cdot 0.3 \text{ V}^2} = 4.44$$

$$\left(\frac{W}{L}\right)_{M4} = 10 \cdot \left(\frac{W}{L}\right)_{M2} = 44.4$$

$$(3) \quad r_{oc}(I_o = 20\mu A) = \frac{1}{\lambda_p \cdot I_o} = \frac{1}{20 \cdot 10^{-6} \cdot 20 \cdot 10^{-6}} = \boxed{5 M\Omega}$$

$$r_{oc}(I_o = 50\mu A) = \frac{1}{\lambda_p \cdot I_o} = \frac{1}{20 \cdot 10^{-6} \cdot 50 \cdot 10^{-6}} = \boxed{2 M\Omega}$$

$$r_{oc}(I_o = 100\mu A) = \frac{1}{\lambda_p \cdot I_o} = \frac{1}{20 \cdot 10^{-6} \cdot 100 \cdot 10^{-6}} = \boxed{1 M\Omega}$$