



EECS 105 – Microelectronic Devices and Circuits

Spring 2001,
Dept. EECS,
UC Berkeley

Prof. A. R. Neureuther
510 Cory 642-4590

Office Hours M11, (Tu2), W2, Th2, F11

Course Web Site <http://www-inst.EECS.Berkeley.EDU/~ee105/>


Homework Assignment # 13, Due April 27, 2001

Use the following parameters for all BJT devices.

NPN	PNP
$\beta=100$	$\beta=50$
$V_{CE-SAT}=0.1V$	$V_{EC-SAT}=0.1V$
$V_{BE}=0.7V$	$V_{EB}=0.7V$
$V_A=20V$	$V_A=25V$
$W_B=1\mu m$	$W_B=1\mu m$
$N_{ED}=10^{19}/cm^3$	$N_{EA}=10^{19}/cm^3$
$N_{BA}=5 \times 10^{17}/cm^3$	$N_{BD}=5 \times 10^{17}/cm^3$
$N_{CD}=10^{16}/cm^3$	$N_{CA}=10^{16}/cm^3$

13.1) Common Emitter Design

Consider the following circuit:

 

Find I_{SUP} , V_{BIAS} and A , the area of the base, such that the following constraints are met:

$$V_{OUT}=0V$$

$$r_{oc}=\Gamma_o$$


Overall voltage gain of at least 75 at low frequencies

Lowest frequency pole at 50MHz or higher (the only capacitor you should consider is C_π)

Minimize the large signal power dissipation

13.2) Multistage Frequency Response with Open-Circuit Time Constants

Consider the following circuit:

 


Assuming that $\bar{V}_{OUT}=0$, $r_{oc1}=r_{o1}$, $r_{oc2}=r_{o2}$, and the area of each base is $10\mu\text{m} \times 10\mu\text{m}$, find this circuit's lowest frequency pole and its -3dB frequency, both in Hz. You should consider the effect of C_π and C_μ but not the capacitance to the substrate.

13.3) Miller Approximation

Find the lowest frequency pole for each of the following circuits.

a)

 

b)

