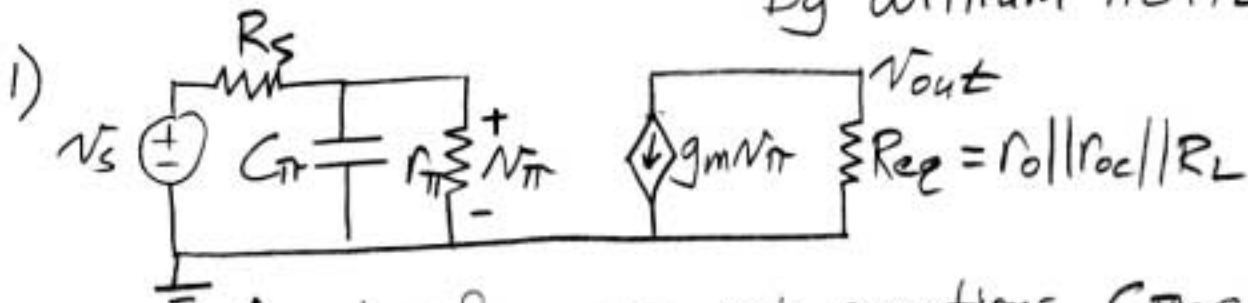


EE130 - Spring 2001 - HW#13 Solution  
 oops, wrong class - EE105  
 by William Holtz



for low frequency gain equations  $C_{\pi}$  can be ignored

$$v_{\pi} = v_s \left( \frac{r_{\pi}}{R_s + r_{\pi}} \right); v_{out} = g_m v_{\pi} R_{eq}$$

$$\frac{v_{out}}{v_s} = g_m \left( \frac{r_{\pi}}{R_s + r_{\pi}} \right) R_{eq} \equiv A_o; r_o = \frac{V_A}{I_c}; g_m = \frac{I_c}{V_{th}}; r_{\pi} = \frac{\beta}{g_m}$$

$$A_o = \frac{I_c}{V_{th}} \left( \frac{\frac{\beta}{g_m}}{R_s + \frac{\beta}{g_m}} \right) \left( \frac{1}{\frac{2I_c}{V_A} + \frac{1}{R_L}} \right) = \frac{I_c}{V_{th}} \left( \frac{\frac{\beta V_{th}}{I_c}}{R_s + \frac{\beta V_{th}}{I_c}} \right) \left( \frac{V_A R_L}{2I_c R_L + V_A} \right)$$

$$A_o = \frac{I_c}{V_{th}} \left( \frac{\beta V_{th}}{I_c R_s + \beta V_{th}} \right) \left( \frac{V_A R_L}{2I_c R_L + V_A} \right) = \frac{I_c \beta V_A R_L}{(I_c R_s + \beta V_{th})(2I_c R_L + V_A)}$$

$$A_o(2I_c^2 R_s R_L + I_c R_s V_A + \beta V_{th} 2I_c R_L + \beta V_{th} V_A) - I_c \beta V_A R_L = 0$$

$$I_c^2(2A_o R_s R_L) + I_c(A_o R_s V_A + 2A_o \beta V_{th} R_L - \beta V_A R_L) + (\beta V_{th} V_A) = 0$$

$$\boxed{I_c = 260.6 \mu A} \text{ or } 16.6 \text{ mA} - \text{use min current for min power}$$

$$Z_{\pi} = \frac{1}{j\omega C_{\pi}} \parallel r_{\pi} = \frac{r_{\pi}}{j\omega C_{\pi} r_{\pi} + 1} = \frac{r_{\pi}}{1 + j\omega r_{\pi} C_{\pi}}$$

for frequency analysis we only need to consider the first half of the circuit as second half of the circuit just causes a frequency independent gain term.

$$\frac{Z_{\pi}}{Z_{\pi} + R_s} = \left( \frac{r_{\pi}}{1 + j\omega r_{\pi} C_{\pi}} \right) \left( \frac{1}{\frac{r_{\pi}}{1 + j\omega r_{\pi} C_{\pi}} + R_s} \right)$$

$$= \left( \frac{r_{\pi}}{1 + j\omega r_{\pi} C_{\pi}} \right) \left( \frac{1 + j\omega r_{\pi} C_{\pi}}{r_{\pi} + R_s + j\omega R_s r_{\pi} C_{\pi}} \right) = \frac{\left( \frac{r_{\pi}}{r_{\pi} + R_s} \right)}{1 + j\omega \left( \frac{R_s r_{\pi} C_{\pi}}{r_{\pi} + R_s} \right)}$$

$$\frac{r_{\pi} + R_s}{R_s r_{\pi} C_{\pi}} = 2\pi f_p \quad f_p \text{ is frequency of first pole}$$

$$\frac{r_{\pi} + R_s}{2\pi f_p R_s r_{\pi}} = C_{\pi} = C_b + C_{jE} = C_F g_m + \sqrt{2} C_{jE0}$$

$$= \frac{W_B^2 I_C}{2 D_{nB} V_{th}} + \sqrt{2} A \sqrt{\frac{q E_s N_a N_{dE}}{2 \phi_B (N_a + N_{dE})}}$$

Solve for area, A

$$\left( \frac{r_{\pi} + R_s}{2\pi f_p R_s r_{\pi}} - \frac{W_B^2 I_C}{2 D_{nB} V_{th}} \right) \left( \frac{q E_s N_a N_{dE}}{2 \phi_B (N_a + N_{dE})} \right)^{-1/2} = A$$


$$D_{nB} = \frac{450 \text{ cm}^2}{\text{Vs}} \cdot 0.026 \text{ V} = 11.7 \text{ cm}^2/\text{s}; \quad \phi_B = 0.06 \left( \log \left( \frac{N_a}{n_i} \right) + \log \left( \frac{N_{dE}}{n_i} \right) \right)$$

$$\phi_B = 1.00 \text{ V}$$


$$\boxed{A = 4.78 \times 10^{-6} \text{ cm}^2}$$

$$V_{BE} = V_{th} \ln \left( \frac{I_C}{I_s} \right); \quad V_{BIAS} - \frac{R_s I_C}{B} - V_{BE} + 2.5 = 0$$
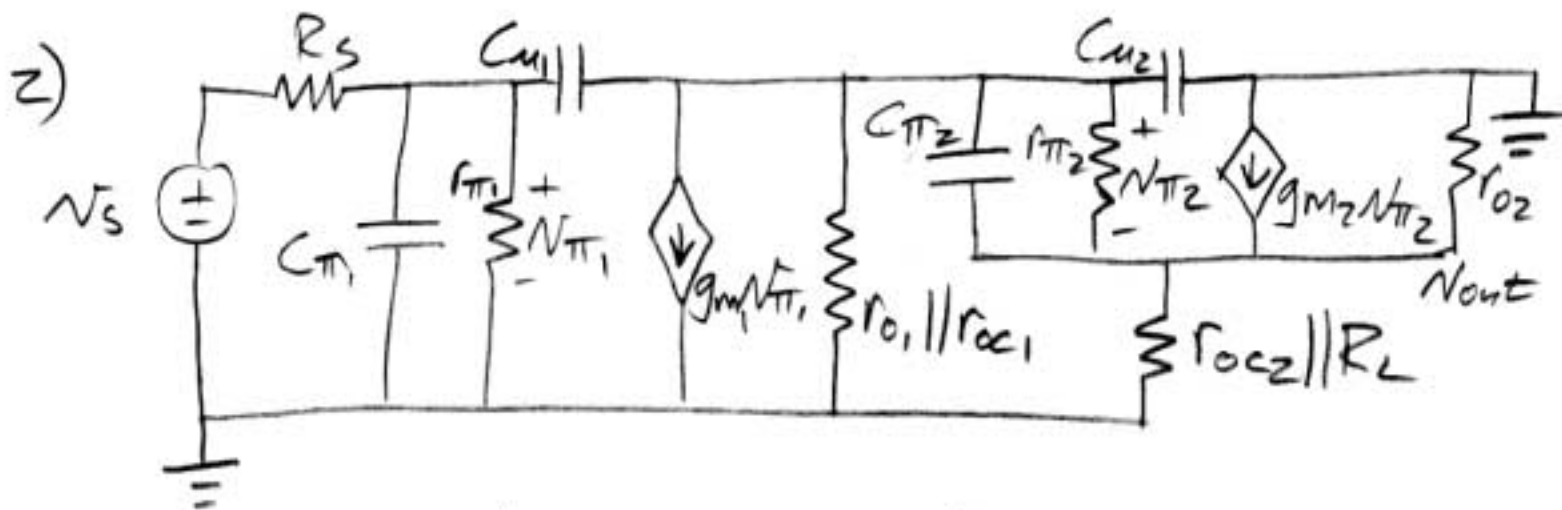
$$V_{BIAS} = \frac{R_s I_C}{B} + V_{th} \ln \left( \frac{I_C}{I_s} \right) - 2.5 = \boxed{-1.755 \text{ V} = V_{BIAS}}$$



Redraw to better group ground

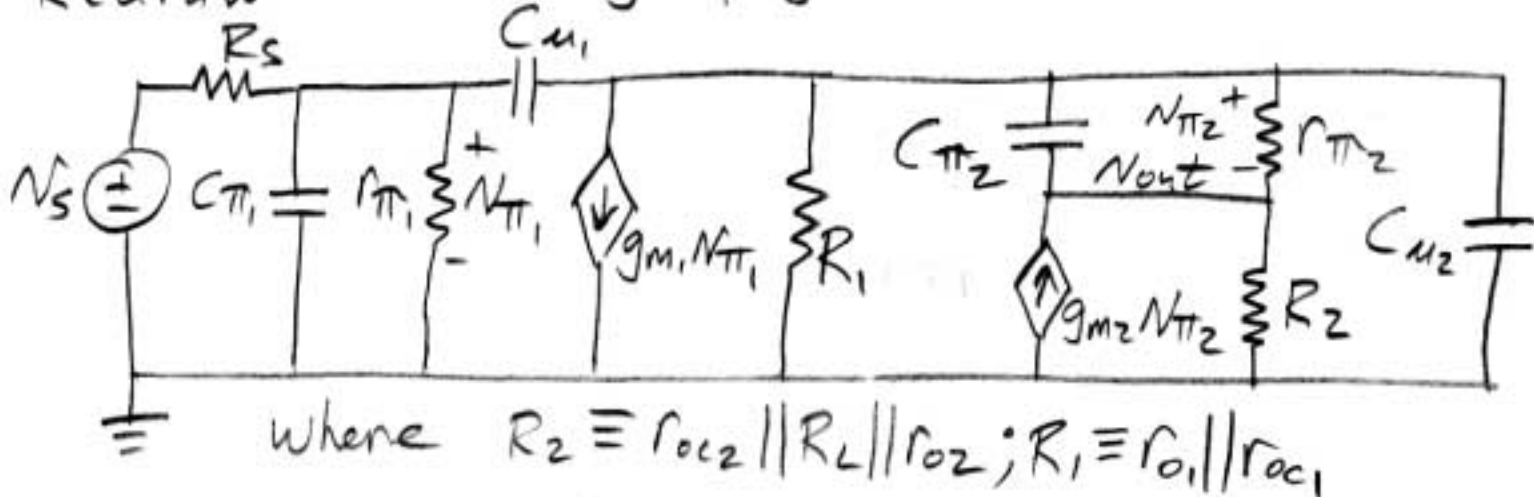

$$I_{E2} = 1 \text{ mA}; \quad I_{C2} = I_{E2} \left( \frac{\beta}{\beta + 1} \right) = 0.99 \text{ mA}; \quad I_{B2} = \frac{I_{C2}}{\beta} = 9.9 \mu\text{A}$$

$$I_{C1} = I_{SUP1} - I_{B2} = 0.99 \text{ mA}; \quad r_o = \frac{V_A}{I_C}; \quad g_m = \frac{I_C}{V_{th}}; \quad r_{\pi} = \frac{\beta}{g_m}$$

$$r_{o1} = r_{o2} = \frac{20}{990 \times 10^{-6}} = 20.2 \text{ k}\Omega$$

$$g_{m1} = g_{m2} = \frac{990 \times 10^{-6}}{0.026} = 38.1 \text{ mS}$$

$$r_{\pi_1} = r_{\pi_2} = \frac{100}{0.0381} = 2626 \Omega$$

$$C_{\pi_1} = C_{\pi_2} = \frac{W_B^2 I_C}{2 D n_B V_{th}} + A \sqrt{\frac{q E_s N_a N_d}{\phi_B (N_a + N_d)}}$$

$$= \frac{(10^{-4})^2 \cdot 990 \times 10^{-6}}{11.7 \times 2 \times 0.026} + (10^{-3})^2 \sqrt{\frac{1.6 \times 10^{-19} \times 1.035 \times 10^{-12} \times 10^{19} \times 5 \times 10^{17}}{1(10^{19} + 5 \times 10^{17})}}$$

$$C_{\pi_1} = C_{\pi_2} = 16.55 \text{ pF}$$

$$C_{M_1} = \frac{C_{M10}}{\sqrt{1 + \frac{V_{CB}}{\phi_{BC}}}} = A \sqrt{\frac{q E_s N_a N_{dc}}{2 \phi_{BC} (N_a + N_{dc})}} \left(1 + \frac{V_{CB}}{\phi_{BC}}\right)^{-1/2}$$

$$\phi_{BC} = 0.06 \left( \log\left(\frac{N_a}{n_i}\right) + \log\left(\frac{N_{dc}}{n_i}\right) \right) = 0.822 \text{ V}$$

$$V_{BE_1} = V_{BE_2} = V_{th} \ln\left(\frac{I_{C1}}{I_s}\right) = 0.778 \text{ V}$$

$$V_{C_1} = V_{out} + V_{BE_2} = 0.778$$

$$V_{CB_1} = V_{C_1} - V_{B_1} = V_{C_1} - (-2.5 + V_{BE_1}) = 2.5 \text{ V}$$

$$C_{M10} = (10^{-3})^2 \sqrt{\frac{1.6 \times 10^{-19} \times 1.035 \times 10^{-12} \times 5 \times 10^{17} \times 10^{16}}{2 \times 0.822 \times (5 \times 10^{17} + 10^{16})}} = 35.3 \text{ fF}$$

$$C_{M_1} = 35.3 \times 10^{-15} \left(1 + \frac{2.5}{0.822}\right)^{-1/2} = 17.6 \text{ fF}$$

$$V_{CB_2} = 2.5 - V_{B_2} = 2.5 - V_{BE_2} = 2.5 - 0.778 = 1.722 \text{ V}$$

$$C_{M_2} = 35.3 \times 10^{-15} \left(1 + \frac{1.722}{0.822}\right)^{-1/2} = 20.1 \text{ fF}$$


Use open circuit time constants

First  $C_{\pi_1}$



$$R_{C_{\pi_1}} = R_s \parallel r_{\pi_1} = \frac{R_s r_{\pi_1}}{R_s + r_{\pi_1}} = 488 \Omega$$
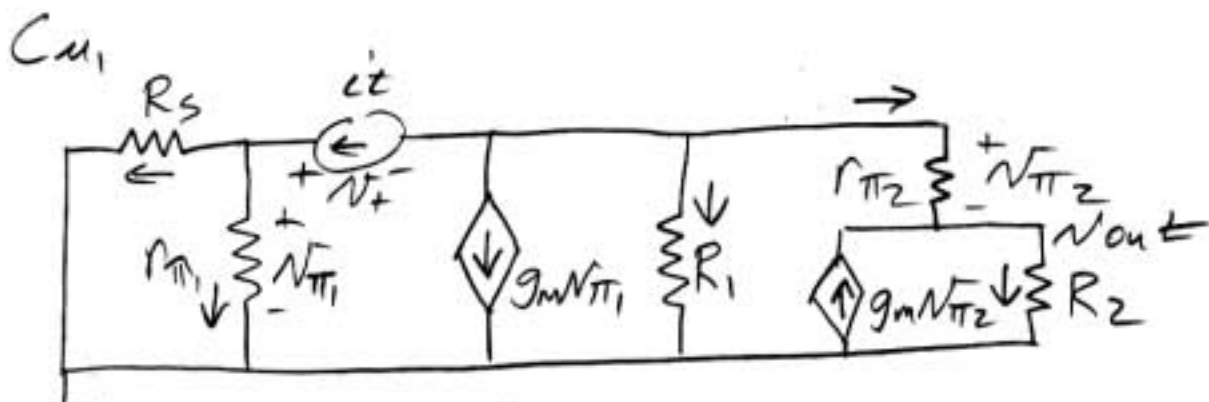
$$\frac{1}{\tau_{C_{\pi_1}}} = \frac{1}{C_{\pi_1} R_{C_{\pi_1}}} = 123.7 \text{ Mrad/s}$$



Let  $R_3 \equiv R_s \parallel r_{\pi 1}$

$$i_t = \frac{V_{\pi 1}}{R_3}; \quad g_m V_{\pi 2} + \frac{V_{\pi 2}}{r_{\pi 2}} = \frac{V_{out}}{R_2}; \quad V_{out} + V_{\pi 2} + V_t = V_{\pi 1}$$

$$i_t + g_m V_{\pi 1} + \frac{V_{\pi 2} + V_{out}}{R_1} + \frac{V_{\pi 2}}{r_{\pi 2}} = 0$$

substitute for  $v_{out}$

$$i_t + g_m V_{\pi 1} + \frac{V_{\pi 2} + V_{\pi 1} - V_{\pi 2} - V_t}{R_1} + \frac{V_{\pi 2}}{r_{\pi 2}} = 0$$

solve for  $V_{\pi 2}$

$$V_{\pi 2} = -r_{\pi 2} \left( i_t + g_m V_{\pi 1} + \frac{V_{\pi 1} - V_t}{R_1} \right)$$

substitute for  $v_{out}$  in remaining equation

$$g_m V_{\pi 2} + \frac{V_{\pi 2}}{r_{\pi 2}} = \frac{V_{\pi 1} - V_{\pi 2} - V_t}{R_2}$$

factor out  $V_{\pi 2}$

$$V_{\pi 2} \left( g_m + \frac{1}{r_{\pi 2}} + \frac{1}{R_2} \right) = \frac{V_{\pi 1} - V_t}{R_2}$$

substitute for  $V_{\pi 2}$

$$-r_{\pi 2} \left( i_t + g_m V_{\pi 1} + \frac{V_{\pi 1} - V_t}{R_1} \right) \left( g_m + \frac{1}{r_{\pi 2}} + \frac{1}{R_2} \right) = \frac{V_{\pi 1} - V_t}{R_2}$$

Substitute for  $N_{\pi_1}$

$$-r_{\pi_2} \left( i_t + g_m i_t R_3 + \frac{i_t R_3 - N_t}{R_1} \right) \left( g_m + \frac{1}{r_{\pi_2}} + \frac{1}{R_2} \right) = \frac{i_t R_3 - N_t}{R_2}$$

$$\text{Let } X \equiv -r_{\pi_2} g_m - 1 - \frac{r_{\pi_2}}{R_2}$$


$$i_t \left( 1 + g_m R_3 + \frac{R_3}{R_1} - \frac{R_3}{R_2 X} \right) = N_t \left( \frac{1}{R_1} - \frac{1}{R_2 X} \right)$$

$$R_{C_{u_1}} = \frac{1 + g_m R_3 + \frac{R_3}{R_1} - \frac{R_3}{R_2 X}}{\frac{1}{R_1} - \frac{1}{R_2 X}} ; \quad R_1 = 10.1K ; R_2 = 5.0K$$

$$R_3 = 488 ; X = -102$$

$$R_{C_{u_1}} = 195K\Omega ; \quad \tau_{C_{u_1}} = R_{C_{u_1}} C_{u_1} = 292 \text{ Mrad/s}$$

$C_{\pi_2}$

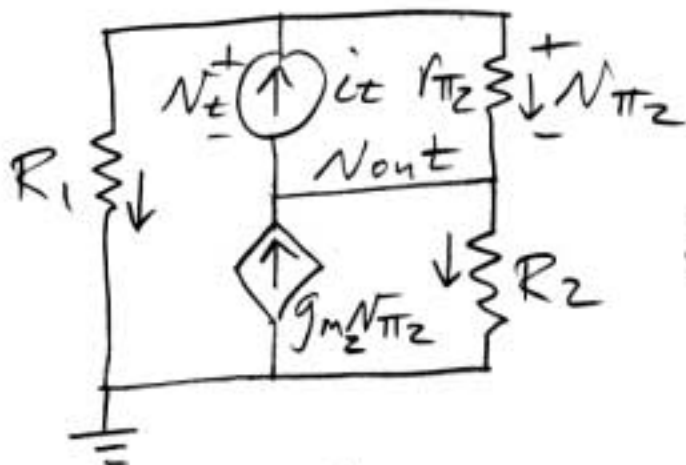

$$i_t = \frac{N_{out} + N_{\pi_2}}{R_1} + \frac{N_{\pi_2}}{r_{\pi_2}}$$

$$g_m \frac{N_{\pi_2}}{2} + \frac{N_{\pi_2}}{r_{\pi_2}} = i_t + \frac{N_{out}}{R_2}$$

$$N_t = N_{\pi_2}$$

Solve for  $N_{out}$

$$R_2 \left( g_m \frac{N_t}{2} + \frac{N_t}{r_{\pi_2}} - i_t \right) = N_{out}$$

substitute to eliminate  $N_{out}$


$$i_t = \frac{R_2 \left( g_m \frac{N_t}{2} + \frac{N_t}{r_{\pi_2}} - i_t \right) + N_t}{R_1} + \frac{N_t}{r_{\pi_2}}$$

$$i_t \left( 1 + \frac{R_2}{R_1} \right) = N_t \left( \frac{R_2 g_m}{R_1} + \frac{R_2}{r_{\pi_2} R_1} + \frac{1}{R_1} + \frac{1}{r_{\pi_2}} \right)$$

$$R_{C\pi_2} = \frac{1 + \frac{R_2}{R_1}}{\left( \frac{R_2 g_{m2}}{R_1} + \frac{R_2}{r_{\pi_2} R_1} + \frac{1}{R_1} + \frac{1}{r_{\pi_2}} \right)} = 76 \Omega$$

$$\frac{1}{\tau_{C\pi_2}} = \frac{1}{R_{C\pi_2} C_{\pi_2}} = 4.6 \times 10^7 \text{ rad/s}$$

$C_{u2}$

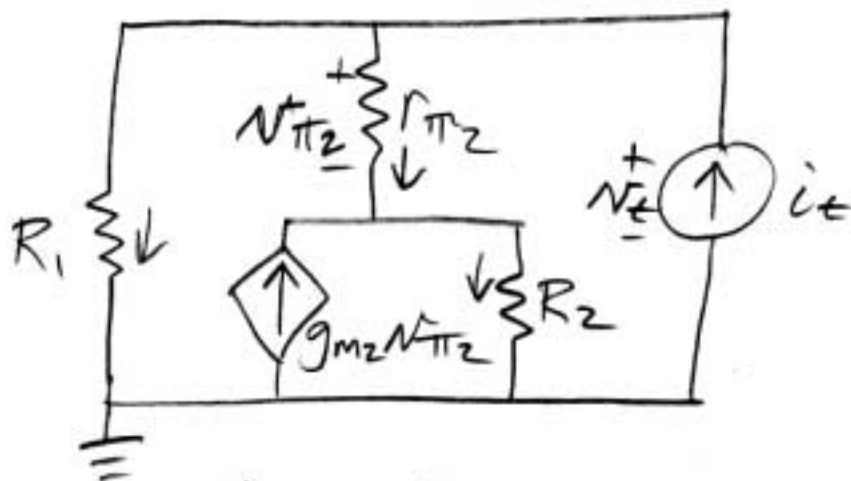

$$i_t = \frac{v_t}{R_1} + \frac{v_{\pi_2}}{r_{\pi_2}} ; \quad g_{m2} v_{\pi_2} + \frac{v_{\pi_2}}{r_{\pi_2}} = \frac{v_t - v_{\pi_2}}{R_2}$$

$$r_{\pi_2} \left( i_t - \frac{v_t}{R_1} \right) = v_{\pi_2} ; \quad v_{\pi_2} \left( g_{m2} + \frac{1}{r_{\pi_2}} + \frac{1}{R_2} \right) = \frac{v_t}{R_2}$$

$$r_{\pi_2} \left( i_t - \frac{v_t}{R_1} \right) \left( g_{m2} + \frac{1}{r_{\pi_2}} + \frac{1}{R_2} \right) = \frac{v_t}{R_2}$$

$$i_t = v_t \left[ \frac{1}{\left( g_{m2} r_{\pi_2} + 1 + \frac{r_{\pi_2}}{R_2} \right) R_2} + \frac{1}{R_1} \right]$$

$$R_{C_{u2}} = \left[ \frac{1}{\left( g_{m2} r_{\pi_2} + 1 + \frac{r_{\pi_2}}{R_2} \right) R_2} + \frac{1}{R_1} \right]^{-1}$$

$$R_{C_{\mu 2}} = 9.9 \text{ k}\Omega; \frac{1}{\tau_{C_{\mu 2}}} = \frac{1}{R_{C_{\mu 2}} C_{\mu 2}} = 5.02 \text{ Grad/sec}$$

Smallest time constant is  $\tau_{C_{\pi 1}}$

$$f_p = \frac{1}{2\pi \tau_{C_{\mu 2}}} = \boxed{19.7 \text{ MHz smallest pole}}$$

should be  $C_{\pi 1}$  not  $C_{\mu 2}$ , but correct value was used...

$$\tau_{-3\text{dB}} = \tau_{C_{\pi 1}} + \tau_{C_{\pi 2}} + \tau_{C_{\mu 1}} + \tau_{C_{\mu 2}} = 1.17 \times 10^{-8} \text{ sec}$$

$$F_{-3\text{dB}} = \frac{1}{2\pi \tau_{-3\text{dB}}} = \boxed{13.6 \text{ MHz } -3\text{dB Freq.}}$$


3) first find low freq gain across 100pF cap.  
Voltage across dependent source is

$$-0.001 V_{in} (20\text{k} + 8\text{k})$$

Voltage on other side of cap is just  $V_{in}$ , so

$$\text{gain is } -0.001 \times 28 \times 10^3 = -28$$
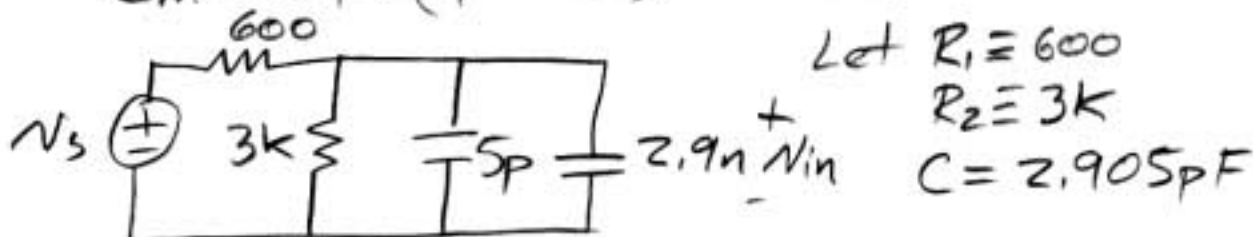
$$C_m = 100 \text{ pF} (1 - -28) = 2.9 \text{ nF}$$



$$R_2 \parallel C = \frac{\frac{R_2}{j\omega C}}{R_2 + \frac{1}{j\omega C}} = \frac{R_2}{1 + j\omega R_2 C}$$

$$V_{in} = V_s \left( \frac{\left( \frac{R_2}{1 + j\omega R_2 C} \right)}{R_1 + \frac{R_2}{1 + j\omega R_2 C}} \right) = \frac{V_s R_2}{R_1 + R_2 + j\omega R_1 R_2 C}$$



$$\frac{V_{in}}{V_s} = \frac{\left(\frac{R_2}{R_1 + R_2}\right)}{1 + j\omega\left(\frac{R_1 R_2 C}{R_1 + R_2}\right)}$$

Pole at  $\frac{1}{2\pi\left(\frac{R_1 R_2 C}{R_1 + R_2}\right)}$

$$F_p = 110 \text{ KHz} \quad \textcircled{a}$$

for part b there is no voltage drop across the 100pF cap ( $V_{in}$  on both sides), so gain across cap is 1

$$C_m = 100 \text{ pF} (1 - 1) = 0$$

can just remove the 100pF cap from circuit

$$\text{let } R_1 = 50 \text{ k}$$

$$R_2 = 400 \text{ k}$$

$$C = 5 \times 10^{-12}$$

using above formula

$$F_p = 716 \text{ KHz} \quad \textcircled{b}$$