

Spring 2001 EE105 Homework #14 Solution

by: Xuesong Jiang


4.1. $I_D = |I_{BQAS}| = I_{SUP} = 200 \mu A$

Neglect λ_n when calculating g_m

$$g_m = \sqrt{2 \cdot \mu_n C_{ox} \frac{W}{L} I_D} = \sqrt{2 \cdot 50 \mu A/V^2 \cdot \frac{100}{2} \cdot 200 \mu A} = 1 mS$$

$$r_o = \frac{1}{\lambda I_D} = \frac{1}{0.05 V^{-1} \cdot 200 \mu A} = 100 k\Omega$$

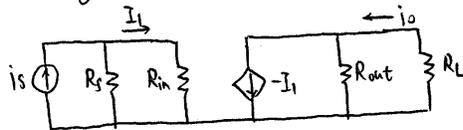Small signal model for low frequency current gain




$$R_{in} = \frac{1}{g_m} = 1 k\Omega$$

$$R_{out} = r_o + g_m \cdot R_s \cdot r_o = 100 k\Omega + 1 mS \cdot 10 k\Omega \cdot 100 k\Omega = 1.1 M\Omega$$

$$A_i = \frac{i_o}{i_s} = -\frac{R_s}{R_s + R_{in}} \cdot \frac{R_{out}}{R_{out} + R_L}$$

Small signal model for ω_{3dB}

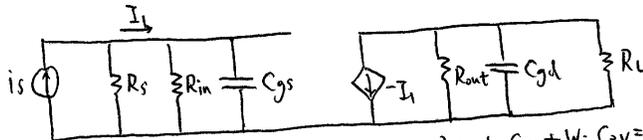

$$T_{Cgs} = (R_s \parallel R_{in}) \cdot C_{gs}$$

$$T_{Cgd} = (R_{out} \parallel R_L) \cdot C_{gd}$$

$$C_{gs} = \frac{2}{3} W \cdot L \cdot C_{ox} + W \cdot C_{ov} = \frac{2}{3} \cdot 100 \mu m \cdot 2 \mu m \cdot 2.3 fF/\mu m^2 + 10 \mu m \cdot 0.5 fF/\mu m$$

$$= 307 fF + 50 fF = 357 fF$$

$$C_{gd} = W \cdot C_{ov} = 50 fF$$

$$\omega_{3dB} = \frac{1}{(R_s \parallel R_{in}) \cdot C_{gs} + (R_{out} \parallel R_L) \cdot C_{gd}}$$

* If you consider source and drain junction capacitance, that will be a more complete solution to this problem and that is more close to the real case, I will encourage you to do it, but junction capacitances are not considered in the textbook, so I neglect junction capacitances in the solution.

(1) $R_S = 100\Omega$ and $R_L = 10k\Omega$.

$$A_i = -\frac{100\Omega}{100\Omega + 1k\Omega} \cdot \frac{1.1M\Omega}{10k\Omega + 1.1M\Omega} = \boxed{-0.09}$$

$$\omega_{3dB} = \frac{1}{(100\Omega \parallel 1k\Omega) \cdot 357fF + (1.1M\Omega \parallel 10k\Omega) \cdot 50fF} = \frac{1}{0.032nS + 0.495nS}$$
$$= \boxed{1.9 \text{ Grad/s}}$$

\uparrow
 10^9

(2) $R_S = 1k\Omega$ and $R_L = 100k\Omega$

$$A_i = -\frac{1k\Omega}{1k\Omega + 1k\Omega} \cdot \frac{1.1M\Omega}{100k\Omega + 1.1M\Omega} = \boxed{-0.458}$$

$$\omega_{3dB} = \frac{1}{(1k\Omega \parallel 1k\Omega) \cdot 357fF + (1.1M\Omega \parallel 100k\Omega) \cdot 50fF} = \frac{1}{0.1785nS + 4.58nS}$$
$$= \boxed{210 \text{ M rad/s}}$$

(3) $R_S = 500\Omega$ and $R_L = 5k\Omega$

$$A_i = -\frac{500\Omega}{500\Omega + 1k\Omega} \cdot \frac{1.1M\Omega}{5k\Omega + 1.1M\Omega} = \boxed{-0.33}$$


$$\omega_{3dB} = \frac{1}{(500\Omega \parallel 1k\Omega) \cdot 357fF + (1.1M\Omega \parallel 5k\Omega) \cdot 50fF} = \frac{1}{0.119nS + 0.249nS}$$
$$= \boxed{2.72 \text{ G rad/s}}$$

H.2 (1) $I_D = I_{sup} = 100 \mu A$

$$g_m = \sqrt{2 \mu_n C_{ox} \frac{W}{L} \cdot I_D} = \sqrt{2 \cdot 50 \mu A / V^2 \cdot \frac{40}{2} \cdot 100 \mu A} = 0.447 \text{ mS}$$


$$r_o = \frac{1}{\lambda \cdot I_D} = \frac{1}{0.05 \text{ V}^{-1} \cdot 100 \mu A} = 200 \text{ k}\Omega$$

Small signal model

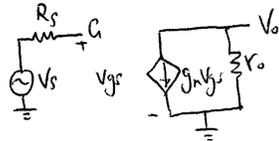


$$A_v = \frac{V_o}{V_s} = \frac{-g_m \cdot r_o \cdot V_{gs}}{V_s} = -\frac{g_m \cdot r_o \cdot V_s}{V_s} = -g_m \cdot r_o = \boxed{-89.4}$$

(2) Small signal model

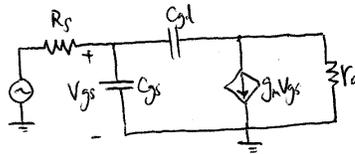

Miller approximation

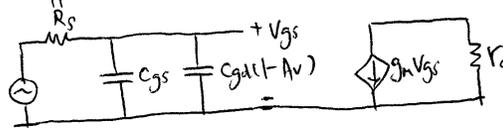

$$C_{gs} = \frac{2}{3} \cdot W \cdot L \cdot C_{ox} + W \cdot C_{ov} = \frac{2}{3} \cdot 40 \mu m \cdot 2 \mu m \cdot 2.3 \text{ fF} / \mu m^2 = 122.7 \text{ fF} + 20 \text{ fF} = 142.7 \text{ fF}$$


$$C_{gd} = W \cdot C_{ov} = 20 \text{ fF}$$

$$\omega_{3dB} = \frac{1}{R_s \cdot [C_{gs} + C_{gd}(1+A_v)]} = \frac{1}{10 \text{ k}\Omega \cdot [142.7 \text{ fF} + 20 \text{ fF} \cdot (1+89.4)]}$$

$$= \boxed{51.3 \text{ M rad/s}}$$

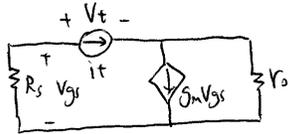(3) Open-circuit time-constant method

$$T_1 = \tau_{Cgs} = R_s \cdot C_{gs} = 10 \text{ k}\Omega \cdot 142.7 \text{ fF} = 1.427 \text{ nS}$$



$$\begin{aligned} V_t &= -i_t \cdot R_s + (g_m V_{gs} - i_t) \cdot R_o \\ &= -i_t \cdot R_s - g_m \cdot R_o \cdot R_s \cdot i_t - i_t \cdot R_o \\ &= -i_t \cdot (R_s + R_o + g_m \cdot R_o \cdot R_s) \end{aligned}$$

$$\therefore R_{cgs} = R_s + R_o + g_m \cdot R_o \cdot R_s$$


$$= 10 \text{ k}\Omega + 200 \text{ k}\Omega + 89.4 \cdot 10 \text{ k}\Omega = 1.104 \text{ M}\Omega$$

$$T_2 = \tau_{Cgd} = R_{cgs} \cdot C_{gd} = 1.104 \text{ M}\Omega \cdot 20 \text{ fF} = 22.08 \text{ nS}$$

$$\sum_{i=1}^2 T_i = 1.427 \text{ nS} + 22.08 \text{ nS} = 23.507 \text{ nS}$$

$$\omega_{3dB} = \frac{1}{\sum_{i=1}^2 T_i} = 42.5 \text{ Mrad/s}$$

14.3. (1) Small signal model

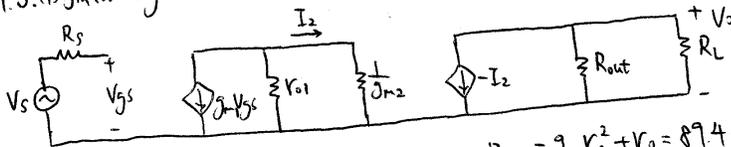


$$R_{out} = g_m R_{o2} \cdot R_{o1} + R_{o2}, \quad V_s = V_{gs}$$

$$R_{out} = g_m R_{o2}^2 + R_{o2} = 89.4 \cdot 200 \text{ k}\Omega + 200 \text{ k}\Omega = 18.08 \text{ M}\Omega$$

$$A_v = \frac{V_o}{V_s} = -g_m \cdot \frac{R_{o1}}{R_{o1} + \frac{1}{g_{m2}}} (R_{out} \parallel R_L)$$

$$= -0.447 \text{ mS} \cdot \frac{200 \text{ k}\Omega}{200 \text{ k}\Omega + \frac{1}{0.447 \text{ mS}}} \cdot 18.08 \text{ M}\Omega = -7992$$

(2) Small signal model

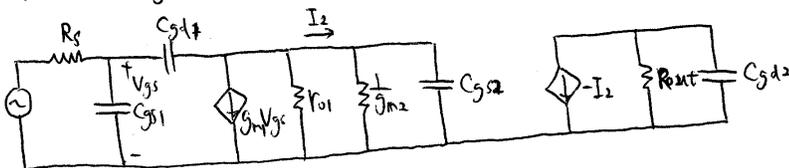

$$T_{Cgs1} = R_s \cdot C_{gs1} = 10 \text{ k}\Omega \cdot 142.7 \text{ fF} = 1.427 \text{ nS}$$

$$R_{eqd1} = R_s + (r_{o1} \parallel g_{m2}) + g_m \cdot R_s \cdot (r_{o1} \parallel g_{m2}) = 10 \text{ k}\Omega + 2.212 \text{ k}\Omega + 9.89 \text{ k}\Omega = 22.1 \text{ k}\Omega$$

$$T_{Cgd1} = R_{eqd1} \cdot C_{gd1} = 22.1 \text{ k}\Omega \cdot 20 \text{ fF} = 0.442 \text{ nS}$$

$$T_{Cgs2} = (r_{o1} \parallel g_{m2}) \cdot C_{gs2} = 2.212 \text{ k}\Omega \cdot 142.7 \text{ fF} = 0.316 \text{ nS}$$

$$T_{Cgd2} = R_{out} \cdot C_{gd2} = 18.08 \text{ M}\Omega \cdot 20 \text{ fF} = 361.6 \text{ nS}$$

$$\therefore \omega_{3dB} = \frac{1}{\sum \tau} = \frac{1}{1.427 \text{ nS} + 0.442 \text{ nS} + 0.316 \text{ nS} + 361.6 \text{ nS}} = \frac{1}{363.8 \text{ nS}}$$
$$= \boxed{2.75 \text{ Mrad/s}}$$
