

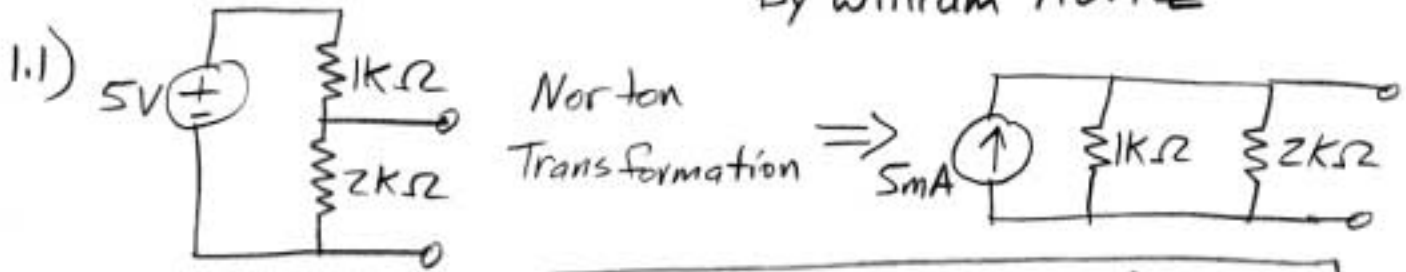


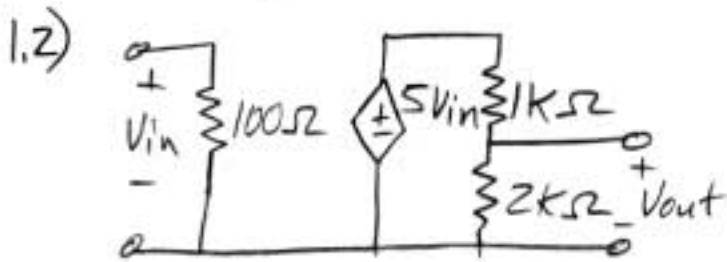EE 105 Spring 2001 - Homework 1 solution  
by William Holtz



combine  
parallel  
resistors

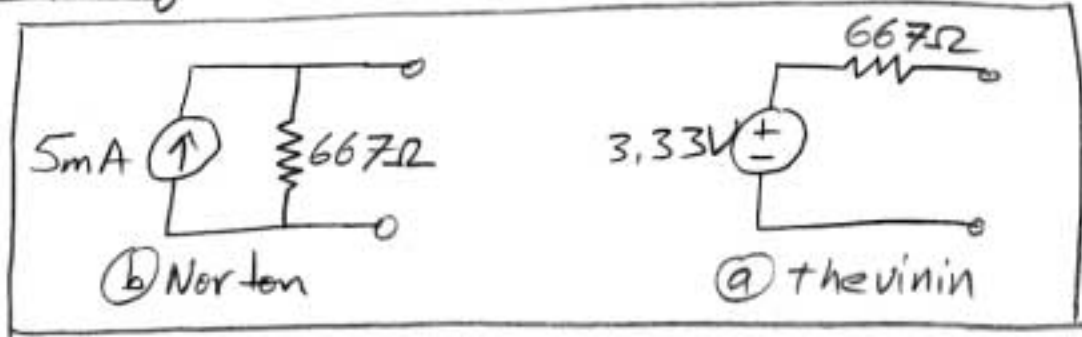


Voltage divider

$$5V_{in} \left( \frac{2k}{1k+2k} \right) = V_{out}$$

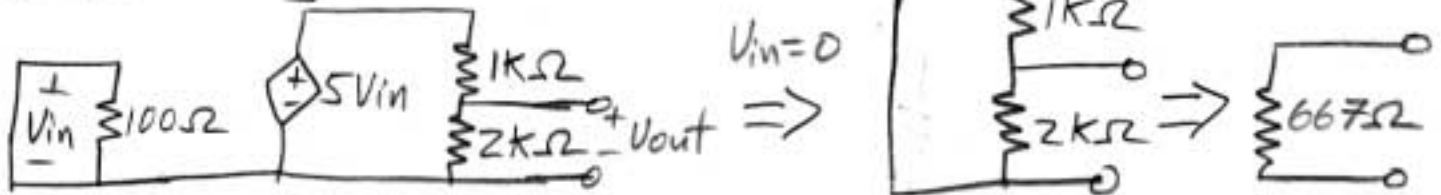(a)  $3.33 = V_{out}/V_{in}$

short independent sources  
before finding  $R_{out}$




(b)  $R_{out} = 667\Omega$


for  $R_{in}$  only right hand side of the circuit matters as the left hand side is only connected by one wire and the right hand side has no dependent sources to receive information from the left hand side  
 $\therefore$  only the  $100\Omega$  resistor is left

(c)  $R_{in} = 100\Omega$


1.2)  
Cont)

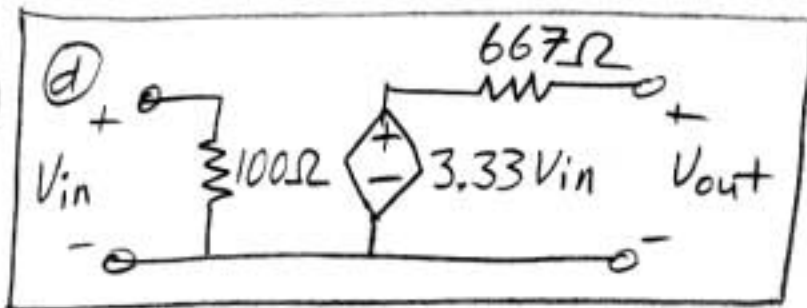

1.3)

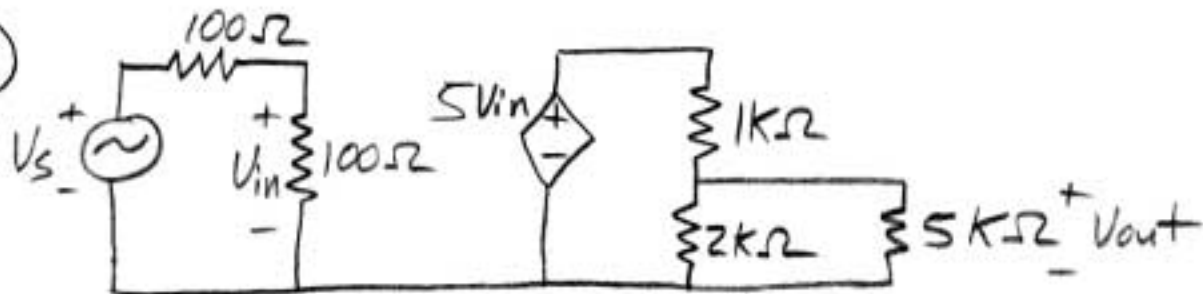

substitute 2-port from 1.2d

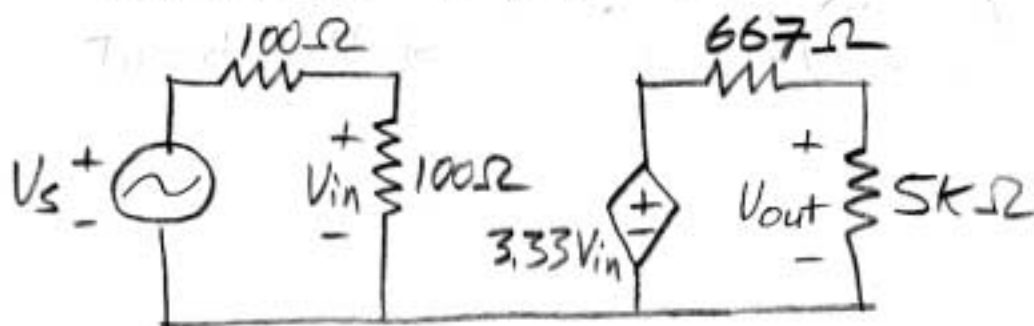


Input voltage divider  $V_s \left( \frac{R_{in}}{R_s + R_{in}} \right) = V_{in}$

Output voltage divider  $3.33 V_{in} \left( \frac{R_L}{R_{out} + R_L} \right) = V_{out}$

$$V_s \left( \frac{R_{in}}{R_s + R_{in}} \right) 3.33 \left( \frac{R_L}{R_{out} + R_L} \right) = V_{out}$$

$$\textcircled{a} \frac{V_{out}}{V_s} = \left( \frac{R_{in}}{R_s + R_{in}} \right) (3.33) \left( \frac{R_L}{R_{out} + R_L} \right) = 1.47$$

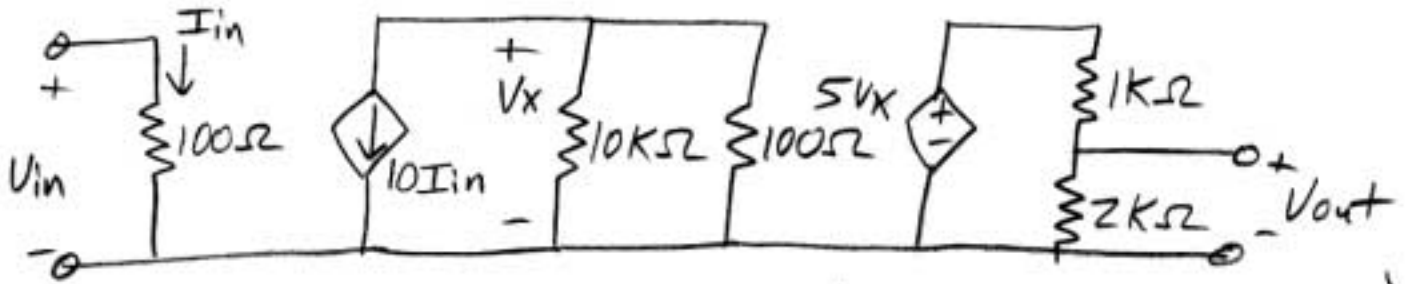1.4) first and last segment are the same so  $R_{in}$  and  $R_{out}$  stay the same. Just need to find  $\frac{V_{out}}{V_{in}}$



$$I_{in} = \frac{V_{in}}{100} ; V_x = 10I_{in} \left( \frac{10000 \cdot 100}{10000 + 100} \right) ; V_{out} = 5V_x \left( \frac{2000}{1000 + 2000} \right)$$

$$5 \cdot 10 \cdot \frac{V_{in}}{100} (99) \left( \frac{2}{3} \right) = V_{out}$$

$$33 = \frac{V_{out}}{V_{in}}$$

A negative sign is missing from this problem.  
 $V_x = -10I_{in}(\dots) \Rightarrow -33 = V_{out}/V_{in}$

