

4.1 EECS 105 SPRING 2001, Solution HW #4

$$\phi_n = (60\text{mV}) \cdot \log\left(\frac{N_d}{10^{10}}\right) = (60\text{mV}) \cdot \log\left(\frac{10^{15}}{10^{10}}\right) = 300\text{ mV}$$

$$\phi_p = -(60\text{mV}) \cdot \log\left(\frac{N_a}{10^{10}}\right) = -(60\text{mV}) \cdot \log\left(\frac{10^{17}}{10^{10}}\right) = -420\text{ mV}$$



$$\phi_B = \phi_n - \phi_p = 300 - (-420) = 720\text{ mV}$$

$$b). X_{d0} = X_{n0} + X_{p0} = \sqrt{\frac{2\varepsilon_s \phi_B}{q}} \left( \frac{1}{N_a} + \frac{1}{N_d} \right)$$

$$= \sqrt{\frac{2(1.7)(8.85 \times 10^{-14} \text{ F/cm}^2)}{1.6 \times 10^{-19} \text{ C}}} \cdot \left( \frac{1}{10^{17} \text{ cm}^{-3}} + \frac{1}{10^{15} \text{ cm}^{-3}} \right)$$

$$= 97\text{ nm}$$

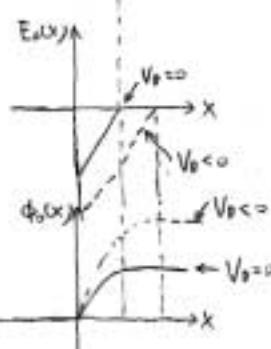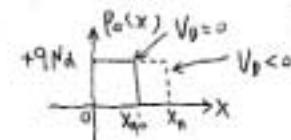c). Assume the PN junction is a one-sided PN junction



$$\frac{dE_d}{dx} = \frac{R(x)}{\varepsilon_s}$$

On the N-side of the depletion region

$$E_d(x) = E_d(x_0) - \int_x^{x_n} \frac{q \cdot N_d}{\varepsilon_s} dx'$$

$$= 0 - \frac{q \cdot N_d}{\varepsilon_s} (x_n - x)$$

$$\phi(x) = \phi_0(0) + \int_0^x -E_d(x') dx'$$

$$= 0 + \int_0^x \frac{q \cdot N_d}{\varepsilon_s} (x_n - x') dx'$$

$$= \frac{q \cdot N_d}{\varepsilon_s} x_n \cdot x - \frac{q \cdot N_d}{2 \varepsilon_s} x^2$$

$$\phi_0(x_n) = \frac{q \cdot N_d}{2 \varepsilon_s} x_n^2$$

Xuesong Jiang  
Feb. 16, 2001

Since  $\phi_B - V_B = \phi_0(x_n) - \phi_0(0) = \phi_0(x_n)$  in the one-sided PN junction

$$\phi_B - V_B = \frac{q \cdot N_d}{2 \varepsilon_s} x_n^2$$

$$\therefore x_n = \sqrt{\frac{2 \varepsilon_s (\phi_B - V_B)}{q \cdot N_d}}$$

4.2.

$$a). V_{DS} > V_{GS} - V_{TN}, \quad \boxed{\text{Saturation}}$$

$$V_{TN} = V_{TOH}$$

$$I_D = (W/2L) \mu_n C_{ox} \cdot (V_{GS} - V_{TN})^2 (1 + \lambda_n V_{DS})$$

$$= \left( \frac{100\text{pm}}{2.2\text{ }\mu\text{m}} \right) \cdot 50 \times 10^{-6} \frac{\text{A}}{\text{V}^2} \cdot (4\text{V})^2 \cdot \left[ 1 + \left( \frac{0.1}{2} \text{V} \right) \cdot 4.5\text{V} \right]$$

$$= 24.5\text{ mA}$$

$$b). V_{TN} = V_{TOH} + V_n \sqrt{-2\phi_p - V_{DS}} - \sqrt{-2\phi_p}$$

$$= 1\text{V} + (0.6\text{V})^{\frac{1}{2}} \cdot \left( \sqrt{-2(-420\text{mV}) + 2\text{V}} - \sqrt{2 \cdot 0.42} \right)$$

$$= 1.46\text{ V}$$

$$V_{DS} > V_{GS} - V_{TN}, \quad \boxed{\text{Saturation}}$$

$$I_D = (W/2L) \mu_n C_{ox} \cdot (V_{GS} - V_{TN})^2 (1 + \lambda V_{DS})$$

$$= \left( \frac{100\text{pm}}{4\text{ }\mu\text{m}} \right) \cdot [50 \times 10^{-6} \frac{\text{A}}{\text{V}^2}] \cdot (3\text{V} - 1.46\text{V})^2 \cdot [1 + (\frac{0.1}{2} \text{V}) \cdot 2.5\text{V}]$$

$$= 3.335\text{ mA}$$

$$V_{SD} < V_{SG} + V_{TP} \quad , \quad \boxed{\text{Triode}} \quad V_{TP} = V_{TAp}$$

$$\begin{aligned} I &= (W/L) \mu_p C_{ox} [V_{SG} + V_{TP} - (V_{SD}/2)] (1 + \lambda_p V_{SD}) V_{SD} \\ &= \left(\frac{100\mu m}{2\mu m}\right) \cdot 2.5 \times 10^{-6} \frac{A}{V^2} \left[4V - 1V - \frac{2.5}{2}V\right] \left[1 + \left(\frac{0.1}{2}V\right) \cdot 2.5V\right] \cdot 2.5V \\ &= \boxed{6.152 \text{ mA}} \end{aligned}$$

$$\begin{aligned} 2). \quad V_{TP} &= V_{TAp} - V_p (\sqrt{2\phi_b - V_{SG}} - \sqrt{2\phi_a}) \\ &= 1V - 0.6V^{\frac{1}{2}} \cdot (\sqrt{2 \cdot 0.42V + 1V} - \sqrt{2 \cdot 0.42V}) \\ &= -1.264V \end{aligned}$$

$$V_{SD} < V_{SG} + V_{TP} \quad \boxed{\text{Triode}}$$

$$\begin{aligned} -I_D &= (W/L) \mu_p C_{ox} [V_{SG} + V_{TP} - (V_{SD}/2)] \cdot (1 + \lambda_p V_{SD}) V_{SD} \\ &= \left(\frac{100\mu m}{2\mu m}\right) \cdot 2.5 \times 10^{-6} \frac{A}{V^2} \cdot \left[3V - 1.264V - \frac{1.5}{2}V\right] \cdot \left[1 + \left(\frac{0.1}{2}V\right) \cdot 1.5V\right] \cdot 1.5V \\ &= \boxed{1.987 \text{ mA}} \end{aligned}$$

3.  $kP = \mu_n C_{ox}$ , from the graph,  $V_{TH} \approx 2V$

a). In triode region

$$I_D = (W/L) \cdot kP \cdot [V_{GS} - V_{TH} - \frac{V_{DS}}{2}] V_{DS} \quad (\text{neglect } \lambda \cdot V_{DS})$$

$$\frac{dI_D}{dV_{DS}} = kP \left(\frac{W}{L}\right) (V_{GS} - V_{TH} - V_{DS})$$

$$\frac{dI_D}{dV_{DS}} (V_{DS} = 0) = kP \left(\frac{W}{L}\right) (V_{GS} - V_{TH}) = kP \cdot \left(\frac{100\mu m}{20\mu m}\right) \cdot (V_{GS} - 0.5V)$$

$$\text{when } V_{GS} = 5V, \quad \frac{dI_D}{dV_{DS}} (V_{DS} = 0) \approx 1 \frac{\text{mA}}{V}$$

$$\therefore kP = \frac{dI_D}{dV_{DS}} (V_{DS} = 0) \cdot \left(\frac{20\mu m}{100\mu m}\right) \cdot \frac{1}{V_{GS} - 0.5V} \cdot 10^{-3} \frac{A}{V} \cdot \frac{1}{5} \cdot \frac{1}{4.5V} = \boxed{49 \text{ mA/V}^2}$$

b). In saturation region

$$I_D = \frac{kP}{2} \frac{W}{L} (V_{GS} - V_{TH})^2$$

$$\text{when } V_{GS} = 5V, \quad V_{DS} = 5V, \quad I_D = 2.25 \text{ mA}$$

$$kP = \frac{2I_D}{\frac{WL}{2} \cdot (V_{GS} - V_{TH})^2} = \frac{2 \cdot 2.25 \text{ mA}}{\frac{100\mu m}{20\mu m} \cdot (5V - 1V)^2} = \boxed{44 \text{ mA/V}^2}$$

44.

a). In triode region,

$$\begin{cases} I_D = (W/L) \mu_n C_{ox} [V_{in} - V_{Th} - \left(\frac{V_{out}}{2}\right)] V_{DS} \\ V_{DS} = V_{out} = SV - I_D \cdot R_L \end{cases}$$

$$\therefore V_{out} = SV - (W/L) \mu_n C_{ox} \cdot \left[V_{in} - V_{Th} - \frac{V_{out}}{2}\right] \cdot V_{out} \cdot R_L$$

$$\therefore (W/L) \mu_n C_{ox} \frac{V_{out}^2}{2} \cdot R_L = [(W/L) \mu_n C_{ox} (V_{in} - V_{Th}) \cdot R_L + 1] \cdot V_{out} + SV = 0$$

$$\therefore V_{out} = \frac{[(W/L) \mu_n C_{ox} (V_{in} - V_{Th}) \cdot R_L + 1] \pm \sqrt{[(W/L) \mu_n C_{ox} (V_{in} - V_{Th}) \cdot R_L + 1]^2 - 4 \cdot SV \cdot R_L}}{2 \cdot (W/L) \mu_n C_{ox} \cdot R_L - \frac{1}{2}}$$

$$\textcircled{A} = \frac{1}{2} (W/L) \mu_n C_{ox} R_L$$

$$(W/L) \mu_n C_{ox} \cdot R_L = 25 \cdot V^{-1}$$

$$\therefore V_{out} = \frac{[(25V^{-1}) \cdot (V_{in} - 1V) + 1] \pm \sqrt{[(25V^{-1}) \cdot (V_{in} - 1V) + 1]^2 - 4 \cdot SV \cdot \frac{1}{2} \cdot 25V^{-1}}}{25V^{-1}}$$

b).  $V_{in} = 3V$ , the MOSFET is in triode region

$$\therefore V_{out} = \frac{[(25V^{-1}) \cdot (3V - 1V) + 1] - \sqrt{[(25V^{-1}) \cdot (3V - 1V) + 1]^2 - 2 \cdot 3V \cdot 25V^{-1}}}{25V^{-1}}$$

$$= \boxed{100 \text{ mV}}$$

$$I_{out} = \frac{3V - V_{out}}{R_L} = \frac{3V - 100 \text{ mV}}{10 \text{ k}\Omega} = \boxed{0.49 \text{ mA}}$$

$$c) V_{in} = V_{in0} + \Delta V_{in}, \quad V_{out} = V_{out0} + \Delta V_{out}$$

From a)

$$V_{out} + \Delta V_{out} = 5V - (W/L) \mu_n C_{ox} [(V_{in0} + \Delta V_{in} - V_{TN}) - \frac{V_{out0} + \Delta V_{out}}{2}] \cdot (V_{out0} + \Delta V_{out}) \cdot R_L$$

$$\therefore \Delta V_{out} = -(W/L) \mu_n C_{ox} \left[ \Delta V_{in} - \frac{\Delta V_{out}}{2} \right] \cdot (V_{out0} + \Delta V_{out}) \cdot R_L$$

$$- (W/L) \mu_n C_{ox} \left[ V_{in0} - V_{TN} - \frac{V_{out0}}{2} \right] \cdot \Delta V_{out} \cdot R_L$$

Neglect higher-order terms and using  $(W/L) \cdot \mu_n C_{ox} \cdot R_L = 25 \text{ V}^{-1}$

$$\therefore \Delta V_{out} = -25 \text{ V}^{-1} \left[ \Delta V_{in} - \frac{\Delta V_{out}}{2} \right] \cdot V_{out0} - 25 \text{ V}^{-1} \left[ V_{in0} - V_{TN} - \frac{V_{out0}}{2} \right] \cdot \Delta V_{out}$$

$$\therefore \frac{\Delta V_{out}}{\Delta V_{in}} = \frac{-V_{out0}}{V_{in0} - V_{TN} - V_{out0} + \frac{1}{25 \text{ V}^{-1}}} = \frac{-100 \text{ mV}}{3V - 1V - 0.1V + 0.04V} = \boxed{-\frac{1}{19.4}}$$

$$\therefore \boxed{-0.0515}$$


$$d) g_m = \frac{\partial I_D}{\partial V_{GS}} = (W/L) \cdot \mu_n C_{ox} \cdot V_{DS} = \left( \frac{100 \text{ nm}}{2 \mu \text{m}} \right) \cdot 50 \mu \text{A/V}^2 \cdot 1.9 \text{ V}$$

$$= 50 \cdot 50 \mu \text{A/V}^2 \cdot 0.1 \text{ V} = \boxed{250 \mu \text{A/V}}$$

$$\frac{1}{r_o} = \frac{\partial I_D}{\partial V_{DS}}$$

$$\therefore r_o = \frac{1}{(W/L) \cdot \mu_n C_{ox} [V_{GS} - V_{TN} - V_{DS}]} = \frac{1}{50 \cdot 50 \mu \text{A/V}^2 \cdot 1.9 \text{ V}} = \boxed{210.5 \Omega}$$

Small signal equivalent circuit

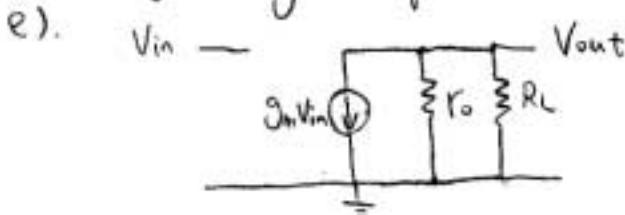

$$\frac{V_{out}}{V_{in}} = -g_m (r_o || R_L) = -(250 \mu \text{A/V}) \cdot (210.5 \Omega || 10 \text{k}\Omega)$$

$$= \boxed{-0.0515}$$