

EE105 - Spring 2001 - Homework 5 Solution
by William Holt

5.1a) for border line between triode and saturation

$V_{DS} = V_{GS} - V_{TN}$. Define I to be drain-to-source current. From Ohm's law $V_{DS} = 5 - 2IR$

$$V_{GS} = 5 - IR; V_{BS} = -IR$$

source and bulk are at different potentials so

$$V_{TN} = V_{TON} + \gamma_n (\sqrt{-2\phi_p} - V_{BS}) - \sqrt{-2\phi_p}$$
 substituting

$$5 - 2IR = 5 - IR - V_{TON} - \gamma_n \sqrt{-2\phi_p + IR} + \gamma_n \sqrt{-2\phi_p}$$

$$\frac{V_{TON} - \gamma_n \sqrt{-2\phi_p} - IR}{-\gamma_n} = \sqrt{-2\phi_p + RI}$$

$$\text{Let } X \equiv V_{TON} - \gamma_n \sqrt{-2\phi_p}$$

$$\frac{(X - IR)^2}{\gamma_n^2} = -2\phi_p + RI$$

$$X^2 - 2XIR + I^2R^2 = (-2\phi_p + RI)\gamma_n^2$$

$$(X^2 + 2\phi_p \gamma_n^2) + (-2X - \gamma_n^2)RI + R^2I^2 = 0$$

$$aI^2 + bI + c = 0$$

$$a = R^2 = 10^8$$

$$b = [-2(V_{TON} - \gamma_n \sqrt{-2\phi_p}) - \gamma_n^2]R = -12,602 \times 10^3$$

$$c = [V_{TON} - \gamma_n \sqrt{-2\phi_p}]^2 + 2\phi_p \gamma_n^2 = -0.0998$$

$$I = -789 \mu A \text{ or } 134 \mu A$$

$$\text{need } I > 0 \text{ so } I = 134 \mu A$$

$$V_{BS} = -IR = -134 \times 10^{-6} \times 10^4 = -1.34 V$$

$$V_{TN} = 1 + 0.6(\sqrt{0.84 + 1.34} - \sqrt{0.84}) = 1.335 V$$

$$I = \frac{w}{2L} \alpha_n \cos(V_{GS} - V_{TN})^2 (1 + \gamma_n V_{DS})$$

solve for γ_n

$$\gamma_n = \left(\frac{2I}{\frac{w}{2} \alpha_n \cos(5 - IR - V_{TN})^2} - 1 \right) \frac{1}{5 - 2IR} = 0.4151$$

$$\gamma_n = \frac{0.1}{L}; L = \frac{0.1}{\gamma_n} = 0.24 \mu m; \frac{w}{L} = \frac{1}{2} \Rightarrow w = 0.12 \mu m$$

5.1b) as shown above $I = 134 \mu A$

5.1c) $\gamma_n = \frac{0.1}{L}$ so increasing $w \Rightarrow$ increasing L
 \Rightarrow decreasing γ_n

$$I \propto (1 + \gamma_n V_{DS})$$

so decreasing $\gamma_n \Rightarrow$ decreasing I and from Ohm's law this implies the voltage drop across the resistors will decrease, resulting in more voltage dropped across the transistor, therefore V_{DS} increases and $V_{GS} - V_T < V_{DS} \Rightarrow$ saturation

$$5.1d) I = \frac{w}{2L} \alpha_n \cos(5 - IR - V_{TN})^2 [1 + \gamma_n (5 - 2IR)]$$

$$- \sqrt{\frac{2I}{\frac{w}{2} \alpha_n \cos[1 + \gamma_n (5 - 2IR)]}} + 5 - IR = V_{TN}$$

set equal to V_{TN} equation


$$5 - IR - \sqrt{\frac{2I}{\frac{w}{2} \alpha_n \cos[1 + \gamma_n (5 - 2IR)]}} = V_{TO_n} + \gamma_n (\sqrt{-2\phi_p + IR} - \sqrt{-2\phi_p})$$

This is nasty, solve for I numerically $I = 120 \mu A$

$$5.1e) g_m = \sqrt{\frac{2w}{2} \mu_F C_{ox} I} = 77.5 \mu A/V$$

$$g_{mb} = \frac{\partial_n g_m}{2\sqrt{2\phi_p - V_{SB}}} = 5.6 \mu A/V$$
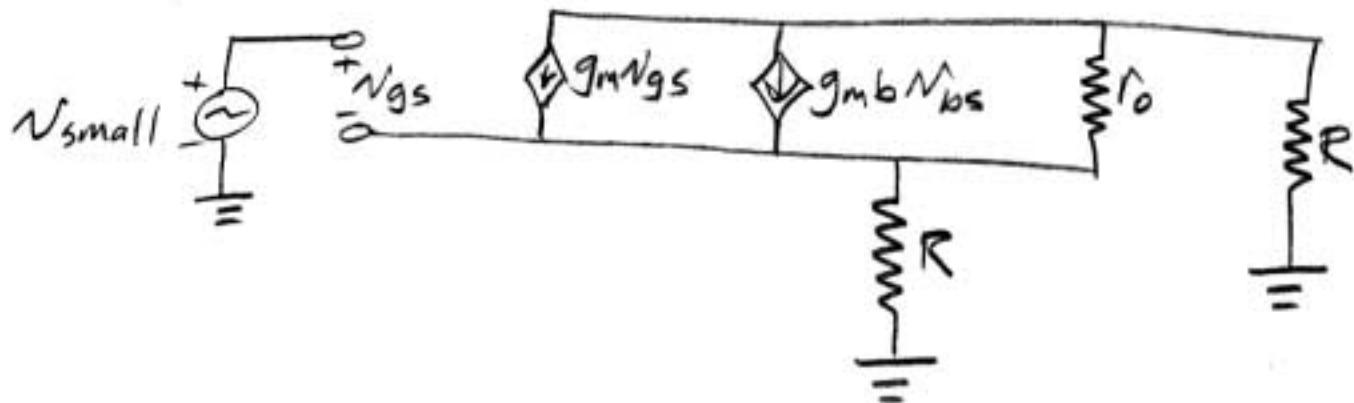
$$r_o = \frac{1}{\partial_n I} = 40.2 k\Omega$$




$$5.2a) I = \frac{w}{2L} \mu_F C_{ox} (V_{SG} + V_{TP})^2 (1 + \lambda_P V_{SD})$$

$$V_{SG} = 5 - 2 ; V_{SD} = 5 - V_{out}$$

$$I = \frac{w}{2L} \mu_F C_{ox} (3 - 1)^2 [1 + \lambda_P (5 - V_{out})]$$


$$I = 230 \times 10^{-6} [1 + 0.01(5 - V_{out})]$$

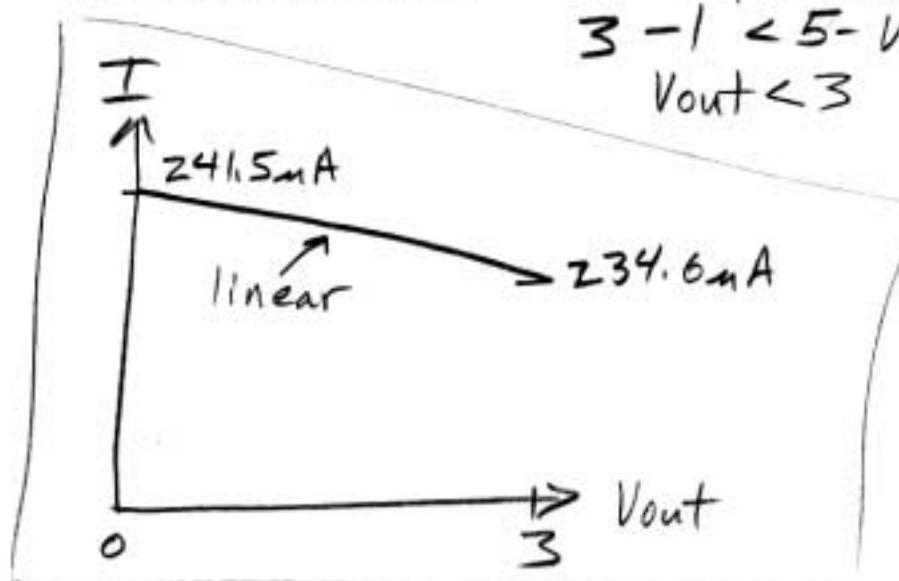for saturation $V_{SG} + V_{TP} < V_{SD}$
 $3 - 1 < 5 - V_{out}$
 $V_{out} < 3$



$$5.2b) I = \frac{w}{2L} m_n C_{ox} (V_{DS} - V_{TN})^2 (1 + 2m_n V_{DS})$$
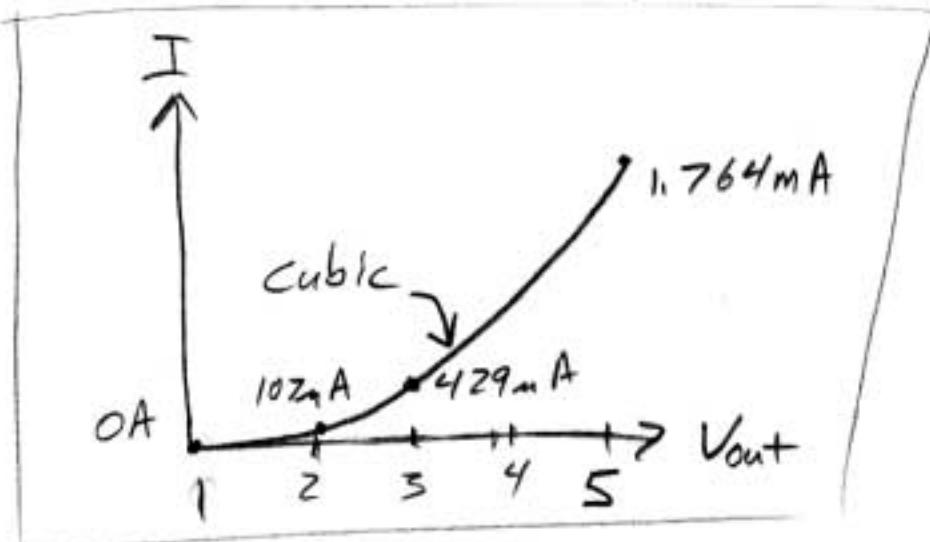
$$I = \frac{42}{2 \times 10} 50 \times 10^{-6} (V_{out} - 1)^2 \left(1 + \frac{0.1}{10} V_{out}\right)$$



5.2c) I could set the current from 5.2a equal to the current from 5.2b and solve for V_{out}, however since the range of I for 5.2a is small compared to 5.2b I'll make some approximations to make this easier.

take average I from 5.2a $\frac{241+234}{2} = 238\text{mA}$
set equal to 5.2b current equation

$$238 \times 10^{-6} = \frac{42}{20} 50 \times 10^{-6} (V_{out} - 1)^2 \left(1 + 0.01 V_{out}\right)$$

only weakly dependent on V_{out}
so guess a V_{out} value and stick into that term
say V_{out} = 2.75

$$238 \times 10^{-6} = 2.1 \times 50 \times 10^{-6} (V_{out} - 1)^2 (1.0275)$$

$$\sqrt{\frac{238 \times 10^{-6}}{2.1 \times 50 \times 10^{-6} \times 1.0275}} + 1 = \boxed{V_{out} = 2.48 \text{ Volts}}$$

$$5.2d) g_{mn} = \sqrt{\frac{2w}{L} n_m \lambda_n I} = 316 \mu A/V$$

$$g_{mp} = \sqrt{\frac{2w}{L} n_p \lambda_p I} = 234 \mu A/V$$

$$r_{on} = \frac{1}{\lambda_n I} = 420 K\Omega$$

$$r_{op} = \frac{1}{\lambda_p I} = \frac{1}{\lambda_n I} = 420 K\Omega$$

