



Homework Assignment # 6, Due March 2, 2001

Unless stated otherwise, use the following parameters in the problems

n-channel MOSFET:

$$\mu_n C_{ox} = 50 \mu A/V^2, V_{TO_n} = 1.0V, \gamma_n = 0.6V^{1/2}, \lambda_n = (0.1/L)V^{-1} (L \text{ in } \mu m), \phi_p = -0.42V$$


p-channel MOSFET:

$$\mu_p C_{ox} = 25 \mu A/V^2, V_{TO_p} = -1.0V, \gamma_p = 0.6V^{1/2}, \lambda_p = (0.1/L)V^{-1} (L \text{ in } \mu m), \phi_n = 0.42V$$

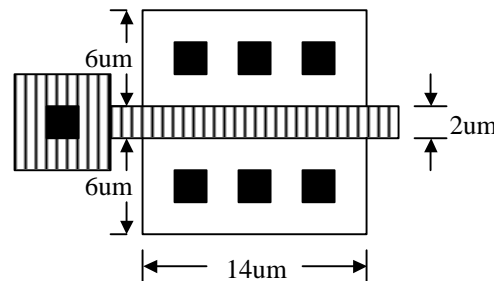6.1 MOSFET Capacitances

The n-channel MOSFET shown in the layout is biased at the operating point: $V_G = 4V$, $V_D = 5V$, $V_S = 1V$, and $V_B = 0V$. For this problem, include $L_D = 0.1 \mu m$ in finding the channel length L from the layout.

- Find the small signal parameters g_m and r_o at this operating point.
- Find the capacitances C_{gs} , C_{gd} , C_{db} , and C_{sb} . In calculating the overlap capacitances, only consider the under diffusion of the drain and source diffusion by L_D . Also you can neglect the sidewall capacitance and use a substrate doping $N_a = 10^{17} \text{ cm}^{-3}$
- Draw the small-signal model for the n-channel MOSFET as is shown in Fig. 4.24. You can neglect C_{gb}




6.2 SPICE Models for the MOSFET

Use the n-channel MOSFET from problem 6.1 in a inverter with a resistive load $R_L = 10k\Omega$


- Write a SPICE .MODEL card for the n-channel MOSFET (See an example in p.244), you can neglect TOX, CJSW, MJ and PB in your .MODEL card
- Write a SPICE device card for M_1 (See an example in p.245)
- Simulate the circuit in SPICE with the cards obtained in (a), (b), find out $V_{OH}(V_i = 0V)$ and $V_{OL}(V_i = 5V)$

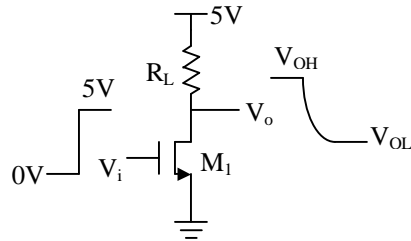d) What's the fall time t_F in your SPICE simulation when V_i switches from 0V to 5V?



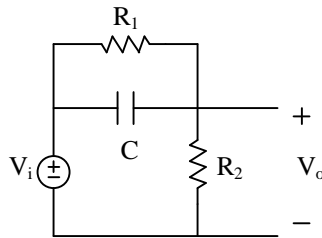6.3 Bode Plot

- Find the voltage transfer function $H(j\omega) = V_o(j\omega)/V_i(j\omega)$
- Draw the Bode plot with $R_1 = 100\text{k}\Omega$, $R_2 = 10\text{k}\Omega$ and $C = 1\text{pF}$ (use radians/sec for the horizontal axis, not Hz)



6.4 Bode Plot

Assume an ideal op-amp is used in this problem

- Find the voltage transfer function $H(j\omega) = V_o(j\omega)/V_i(j\omega)$
- Draw the Bode plot with $R_1 = 10\text{k}\Omega$, $R_2 = 100\text{k}\Omega$ and $C_1 = C_2 = 1\text{pF}$ (use radians/sec for the horizontal axis, not Hz)

