

6. (a) $L_{eff} = L - 2 \cdot L_D = (2 - 2 \times 0.1) \mu m = 1.8 \mu m$

$$g_m = \mu_n C_{ox} \frac{W}{L_{eff}} (V_{GS} - V_{TN})$$

$$V_{TN} = V_{TN0} + V_n (\sqrt{-2\phi_F - V_{BS}} - \sqrt{-2\phi_F}) = 1V + 0.6V^{1/2} (\sqrt{2 \times 0.42V + 1V} - \sqrt{2 \times 0.42V})$$

$$= 1.264V$$

$$\therefore g_m = 5 \times 10^{-6} \frac{A}{V} \times \frac{14 \mu m}{1.8 \mu m} \times (3V - 1.264V) = \boxed{675 \mu S = 6.75 \times 10^{-4} \frac{A}{V}}$$

$$I_D = \frac{1}{2} \mu_n C_{ox} \frac{W}{L_{eff}} (V_{GS} - V_{TN})^2 (1 + \lambda_n V_{DS})$$

$$= \frac{1}{2} \times 5 \times 10^{-6} \frac{A}{V} \times \frac{14}{1.8} \times (3V - 1.264V)^2 (1 + \frac{0.1}{1.8} V^{-1} \times 4V)$$

$$= 716 \mu A$$

$$Y_o = \frac{1}{\frac{1}{2} \mu_n C_{ox} \frac{W}{L_{eff}} (V_{GS} - V_{TN})^2 \lambda_n} = \boxed{30.7 k\Omega}$$

(b) $C_{GS} = \frac{2}{j} W \cdot L_{eff} C_{ox} + W \cdot C_{ov}$

$$C_{ox} = \frac{\epsilon_{ox} \epsilon_0}{T_{ox}} = \frac{3.9 \times 8.85 \times 10^{-14} F/cm}{1.5 \times 10^{-8} cm} = 2.3 fF/\mu m^2$$

$$C_{ov} = \frac{\epsilon_{ox} \epsilon_0}{T_{ox}} \cdot L_D = 2.3 fF/\mu m^2 \cdot 0.1 \mu m = 0.23 fF/\mu m$$

$$\therefore C_{GS} = \frac{2}{j} \times 14 \mu m \times 1.8 \mu m \cdot 2.3 fF/\mu m^2 + 14 \mu m \times 0.23 fF/\mu m$$

$$= \boxed{41.86 fF}$$

$$C_{GD} = W \cdot C_{ov} = \boxed{3.22 fF}$$

$\phi_{n+} = 550 mV$ (heavily doped n-type silicon)

$$\phi_p = -60 mV \cdot \log\left(\frac{N_A}{10^{10}}\right) = -60 mV \cdot \log\left(\frac{10^{17}}{10^{10}}\right) = -420 mV$$

$$\phi_B = \phi_{n+} - \phi_p = 550 mV - (-420 mV) = 970 mV$$

$$C_{jo} = \epsilon_s \sqrt{\frac{q}{2\epsilon_s \phi_B} \left(\frac{1}{N_A} + \frac{1}{N_D}\right)^{-1}} = \sqrt{\frac{q \epsilon_s N_D}{2 \phi_B}}$$


$$\therefore C_{jo} = \sqrt{\frac{1.6 \times 10^{-19} C \times 11.7 \times 8.85 \times 10^{-14} F/cm \times 10^{17} cm^{-3}}{2 \times 0.97V}} = 0.92 fF/\mu m^2$$

$$V_{BS} = -1V$$

$$C_{j0} = \frac{W \cdot L_{eff} \cdot C_{jo}}{\sqrt{1 - V_{BS}/\phi_B}} = \frac{14 \mu m \times 6 \mu m \times 0.92 fF/\mu m^2}{\sqrt{1 - (-1V)/0.97V}} = \boxed{54.2 fF}$$


$$V_{BD} = -5V$$
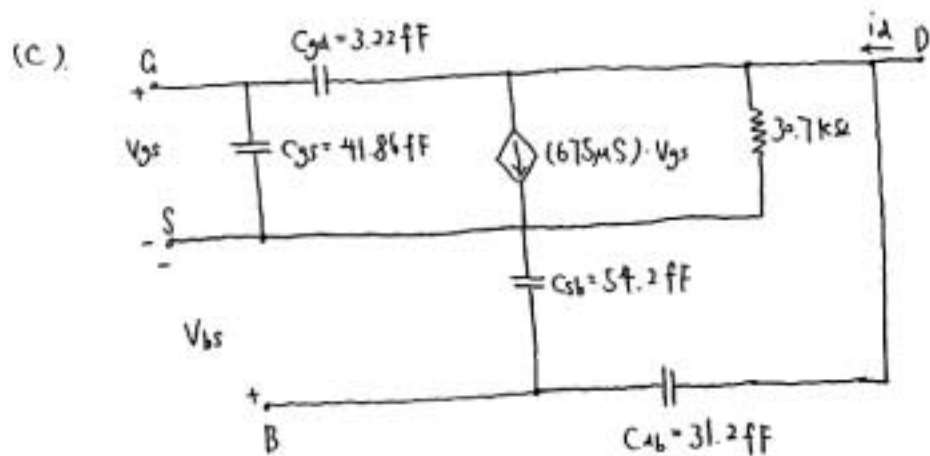
$$C_{d0} = \frac{W \cdot L_{eff} \cdot C_{jo}}{\sqrt{1 - V_{BD}/\phi_B}} = \frac{14 \mu m \times 6 \mu m \times 0.92 fF/\mu m^2}{\sqrt{1 - (-5V)/0.97V}} = \boxed{31.2 fF}$$



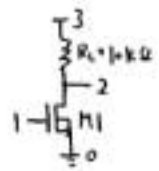6.2 (a)

```
.MODEL NMOS NMOS LEVEL=1 VTO=1
+ KP=50U LAMBDA=0.056 GAMMA=0.6
+ PHI=0.42 CGDO=2.3E-10 CGSO=2.3E-10
+ CJ=9.2E-4
```




where $V_{TO} = V_{T0n}$, $KP = \mu_n C_{ox}$, $LAMBDA = \lambda_n (L_{eff}) = \frac{0.1}{1.8} = 0.056$
 $GAMMA = \eta$, $PHI = -\phi_p$, $CGDO = C_{ov}$, $CGSO = C_{ov}$, $CJ = C_{jo}$


```
(b) M1 3 0 0 0 NMOS W=14U L=2U AD=8.4E-11 AS=8.4E-11
+ PD=2.6E-5 PS=2.6E-5
```

(c) From SPICE, $V_{OH} = 5V$, $V_{OL} = 0.34V$

(d) From SPICE, $t_f = 0.09ns$

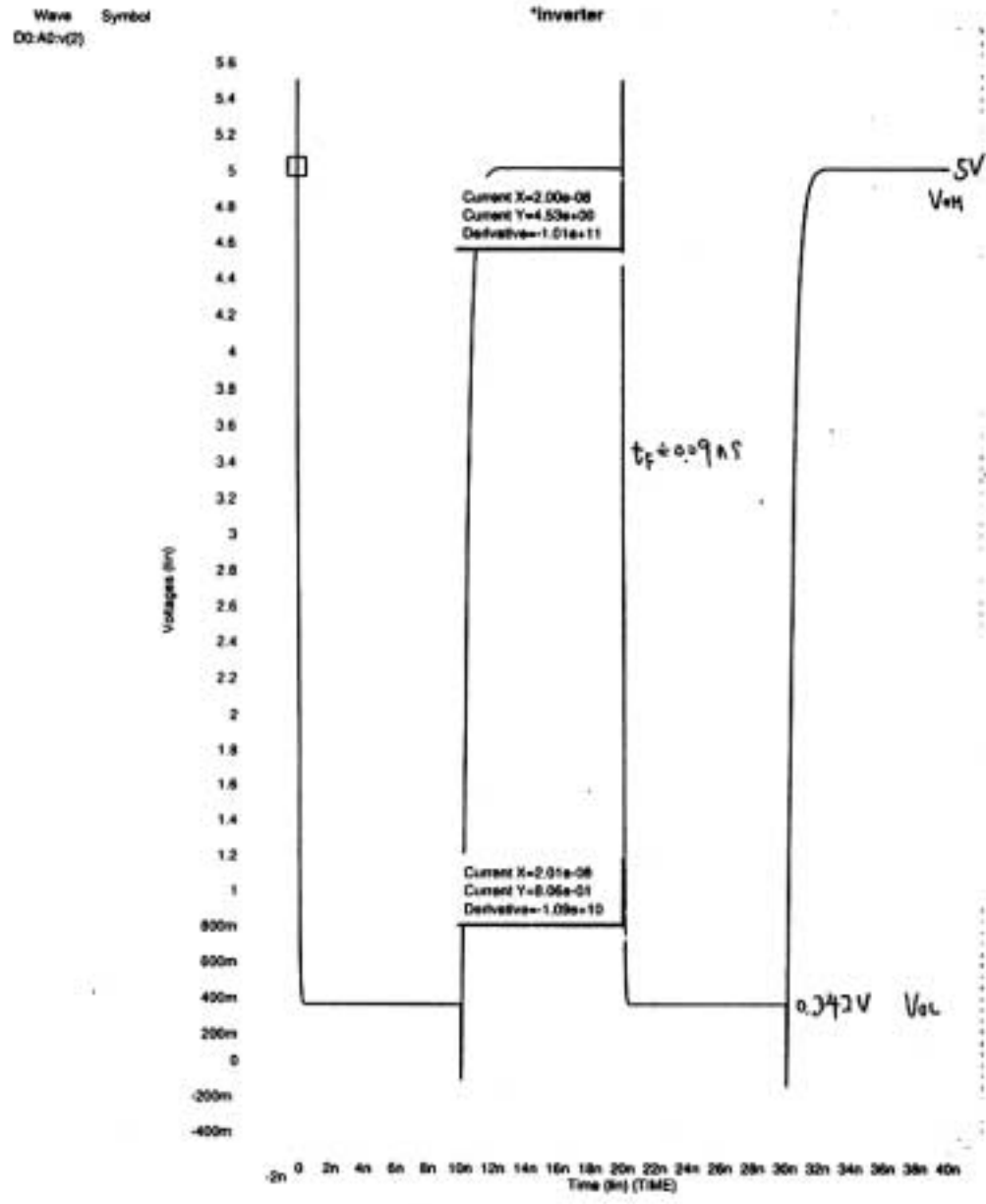

6.3. (a)

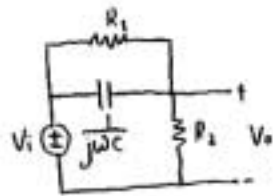

$$\frac{V_o(j\omega)}{V_i(j\omega)} = \frac{R_2}{R_2 + (R_1 \parallel \frac{1}{j\omega C})} = \frac{R_2}{R_2 + \frac{R_1}{1 + j\omega R_1 C}} = \frac{R_2(1 + j\omega R_1 C)}{R_1 + R_2 + j\omega R_1 R_2 C}$$

$$= \frac{R_2}{R_1 + R_2} \cdot \frac{1 + j\omega R_1 C}{1 + j\omega \frac{R_1 R_2}{R_1 + R_2} C}$$


↑
DC gain

pole $\frac{1}{\frac{R_1 R_2}{R_1 + R_2} C}$
zero: $\frac{1}{R_1 C}$


(b) DC gain = $\frac{R_2}{R_1 + R_2} = 0.09$

pole $\frac{1}{\frac{R_1 R_2}{R_1 + R_2} C} = \frac{1}{\frac{10 \times 10^3 \times 10^3}{10 + 10^4} \times 10^{-6}} = 1.1 \times 10^8 \text{ rad/sec}$

zero: $1/(R_1 C) = 10^7 \text{ rad/sec}$

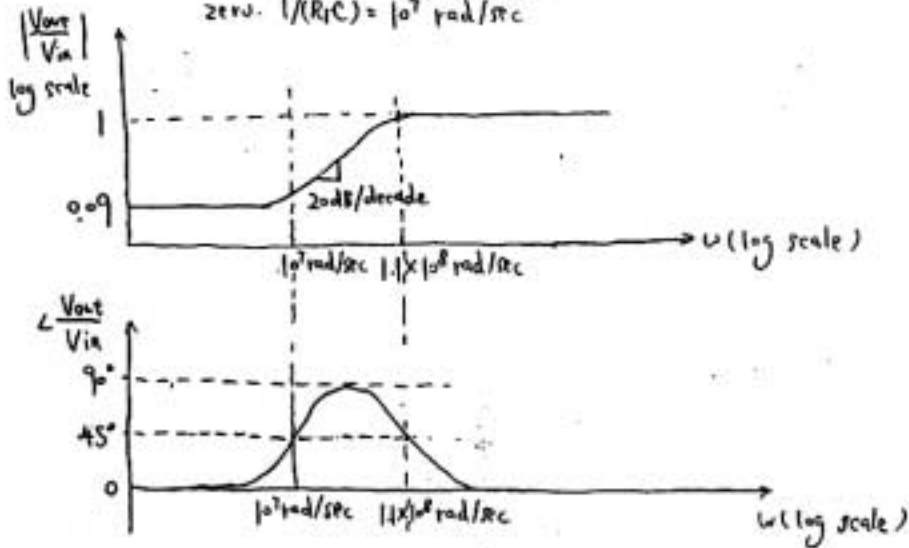

6.4 (a)

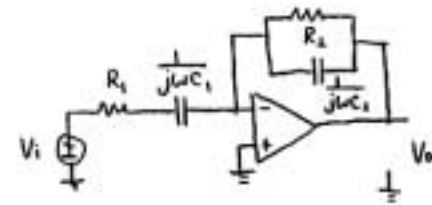

$$\frac{V_i}{R_1 + \frac{1}{j\omega C_1}} = -\frac{V_o}{R_2 \parallel \frac{1}{j\omega C_2}}$$

$$\therefore \frac{V_o(j\omega)}{V_i(j\omega)} = \frac{R_2 \parallel \frac{1}{j\omega C_2}}{R_1 + \frac{1}{j\omega C_1}} = -\frac{j\omega R_2 C_1}{(1 + j\omega R_1 C_1)(1 + j\omega R_2 C_2)}$$

$\omega = 0, \frac{V_o(j\omega)}{V_i(j\omega)} = 0, \quad \omega \rightarrow \infty, \frac{V_o(j\omega)}{V_i(j\omega)} = 0$

pole 1: $\frac{1}{R_1 C_1} = 10^7 \text{ rad/sec}$, pole 2: $\frac{1}{R_2 C_2} = 10^8 \text{ rad/sec}$

