



# EECS 105 – Microelectronic Devices and Circuits

Spring 2001,  
Dept. EECS,  
UC Berkeley

Prof. A. R. Neureuther  
510 Cory 642-4590

Office Hours M11, (Tu2), W2, Th2, F11

Course Web Site <http://www-inst.EECS.Berkeley.EDU/~ee105/>

## Homework Assignment # 9, Due *Wednesday* March 21, 2001


The second mid-term exam will be on **Friday March 23** from 10:10-11am.  
Please try to show up early so we can start on time and give you the full 50 minutes.

Use the following parameters for all BJT devices.

NPN	PNP
$\beta=100$	$\beta=50$
$V_{CE-SAT}=0.1V$	$V_{EC-SAT}=0.1V$
$V_{BE}=0.7V$	$V_{EB}=0.7V$
$V_A=20V$	$V_A=25V$
$W_B=1\mu m$	$W_B=1\mu m$
$N_{ED}=10^{19}/cm^3$	$N_{EA}=10^{19}/cm^3$
$N_{BA}=5 \times 10^{17}/cm^3$	$N_{BD}=5 \times 10^{17}/cm^3$
$N_{CD}=10^{16}/cm^3$	$N_{CA}=10^{16}/cm^3$
Area= $10\mu m \times 10\mu m$	Area= $10\mu m \times 10\mu m$

### 8.1) Common Collector Amplifier (Using the bipolar models in circuits).

Consider the following circuit:

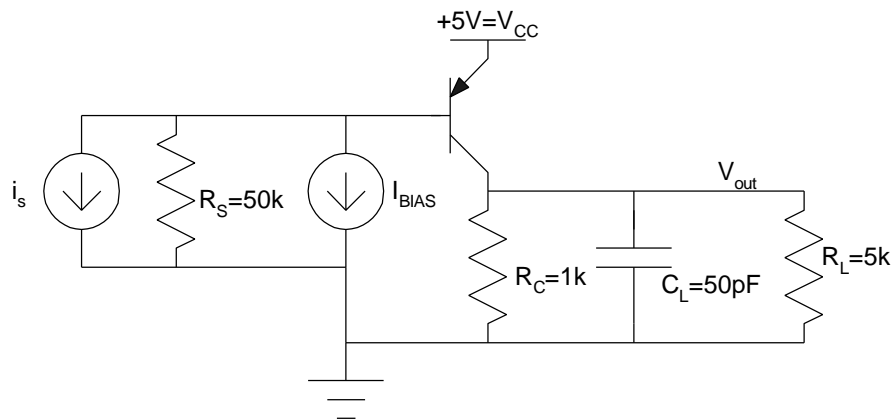

- If  $V_{OUT}=2.5V$ , what region is the BJT operating in?
- Solve for the large signal current exiting the collector,  $I_C$ .
- Determine  $I_{BIAS}$  such that  $V_{OUT}=2.5V$ .
- Draw the small signal version of the circuit and find values for all components. For the transistor small signal model only include  $C_p$ ,  $r_p$ ,  $r_o$  and the dependent source. Let  $n_i^2=10^{20}/cm^3$ .
- Symbolically solve for the overall small signal voltage gain of the circuit,  $v_{out}/v_{in}$  as a function of ?. You can leave your answer in terms of the small signal components. You will want to do a Norton to Thevenin transformation on  $i_s$  and  $R_s$  to get  $v_{in}$ .

- f) Draw the approximate (straight lines only) magnitude Bode plot of voltage gain for this circuit. Use radian/sec for the horizontal axis, not Hertz. Label all important values.
- g) Draw the approximate (straight lines only) phase Bode plot of voltage gain for this circuit. Use radian/sec for the horizontal axis, not Hertz. Label all important values.


**8.2) Base Doping (Review of basic physics through examining assumptions)**

In this class we are making the assumption that  $V_{BE}=0.7V$  for an NPN BJT that has a positive current going from collector to emitter. This is good enough to get a first order feel for what the circuits are doing, however you should understand this is far from exact. For an NPN BJT with  $N_{ED}=10^{19}/cm^3$ ,  $W_B=1\mu m$  and a cross sectional area of  $10\mu m$  by  $10\mu m$ :

- a) Determine the doping in the base such that  $V_{BE}=0.7V$  and current exiting the emitter is  $1mA$ . Since the doping of the emitter is high, you only need to consider the current from electrons. Let  $n_i^2=10^{20}/cm^3$ .
- b) Repeat for  $100\mu A$ .
- c) Repeat for  $10\mu A$ .

**8.3) Regions of Operation (Review of basic circuits)**

Consider the following circuit:

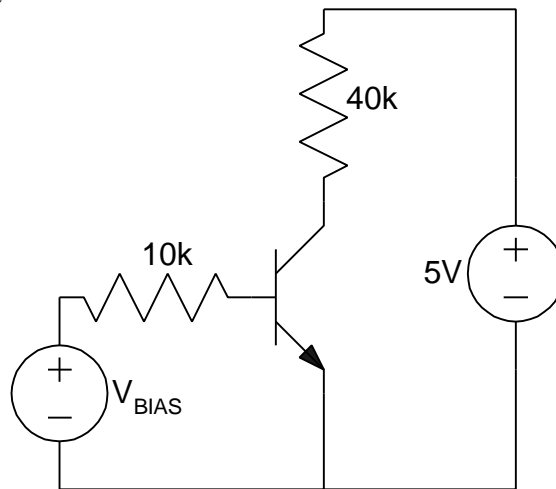

Find  $V_{BIAS}$  such that the transistor is at the transition point between saturation and forward active.