

EE 105 - Spring 2001 - Homework #9 solutions
by William Holtz

1a) $V_{CE} = 2.5 > V_{CE_{SAT}} = 0.1 \Rightarrow$ not saturation
by Ohm's law there is a current through R_C
and by KCL this current must come from the
collector \therefore not cutoff. Current is exiting
collector so not reverse active \Rightarrow Forward Active

1b) Let $Z_{eq} = R_C \parallel C_L \parallel R_L = \frac{1}{\frac{1}{R_C} + j\omega C_L + \frac{1}{R_L}}$

$Z_{eq}(\omega=0) = 833 \Omega$

$I_C = \frac{V_{out}}{Z_{eq}(\omega=0)} = \frac{2.5}{833} = 3 \text{ mA} = I_C$



1c) $I_B = \frac{I_C}{\beta} = \frac{5 - V_{BE}}{R_S} + I_{BIAS}$; $I_{BIAS} = \frac{I_C}{\beta} - \frac{5 - V_{BE}}{R_S} = \frac{3 \times 10^{-3}}{50} - \frac{4.3}{50 \text{ k}}$

$I_{BIAS} = -26 \mu\text{A}$

1d)



$g_m = \frac{I_C}{V_{th}} = \frac{3 \times 10^{-3}}{26 \times 10^{-3}} = 0.115 \text{ A/V}$

$r_{\pi} = \frac{\beta}{g_m} = \frac{50}{0.115} = 433 \Omega$

$r_o = \frac{V_A}{I_C} = \frac{25}{0.115} = 217 \Omega$

In the r_o expression, the value plugged in for I_C is incorrect. Therefore $r_o = 8333 \text{ ohms}$.

$$C_{\pi} = C_b + C_{j0E} = g_m \frac{W_B^2}{2D_{nB}} + A \sqrt{\frac{q \epsilon_s N_A E N_{DB}}{2 \phi_B (N_A E + N_{DB})}}$$

$$\mu_{nB} = 450 \text{ cm}^2/\text{Vs}$$


$$D_{nB} = \mu_{nB} V_{th} = 11.7 \text{ cm}^2/\text{s}$$

$$\phi_B = 60 \log\left(\frac{10^{19}}{10^{10}}\right) + 60 \log\left(\frac{5 \times 10^{17}}{10^{10}}\right) = 1.00 \text{ V}$$

$$C_{\pi} = 0.115 \frac{(10^{-4})^2}{2 \times 11.7} + (10^{-3})^2 \sqrt{\frac{1.6 \times 10^{-19} \times 1.035 \times 10^{-12} \times 10^{19} \times 5 \times 10^{17}}{2 \times 1 \times (10^{19} + 5 \times 10^{17})}}$$

$$C_{\pi} = 49 \text{ pF}$$
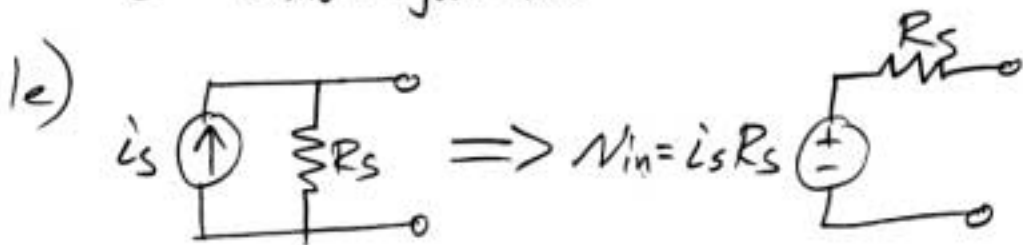
$$Z_{eq} = \frac{1}{1.2 \times 10^{-3} + j\omega 50 \times 10^{-12}} \Omega$$



$$\text{Let } Z_{\pi} = C_{\pi} \parallel r_{\pi}$$

$$V_{\pi} = i_s \left(\frac{R_s Z_{\pi}}{R_s + Z_{\pi}} \right); \quad V_{out} = g_m V_{\pi} \left(\frac{r_o Z_{eq}}{r_o + Z_{eq}} \right)$$

$$V_{\pi} = V_{in} \left(\frac{Z_{\pi}}{R_s + Z_{\pi}} \right); \quad V_{out} = g_m V_{in} \left(\frac{Z_{\pi}}{R_s + Z_{\pi}} \right) \left(\frac{r_o Z_{eq}}{r_o + Z_{eq}} \right)$$

$$\frac{V_{out}}{V_{in}} = g_m \left(\frac{Z_{\pi}}{R_s + Z_{\pi}} \right) \left(\frac{r_o Z_{eq}}{r_o + Z_{eq}} \right)$$

$$\text{Where } Z_{\pi} = C_{\pi} \parallel r_{\pi} \text{ - and } Z_{eq} = R_c \parallel C_L \parallel R_L$$

If) expand out equation from part e so that the poles and zeros are easy to see

$$\frac{z_{\pi}}{R_s + z_{\pi}} = \frac{\left(\frac{r_{\pi}}{1 + j\omega r_{\pi} C_{\pi}}\right)}{\left(R_s + \frac{r_{\pi}}{1 + j\omega r_{\pi} C_{\pi}}\right)} = \frac{r_{\pi}}{R_s + r_{\pi} + j\omega R_s r_{\pi} C_{\pi}}$$

$$\frac{r_o z_{ee}}{r_o + z_{ee}} = R_c \parallel R_L \parallel r_o \parallel C_L = \frac{1}{\frac{1}{R_c} + \frac{1}{R_L} + \frac{1}{r_o} + j\omega C_L}$$

$$= \frac{R_c R_L r_o}{R_c r_o + R_c R_L + j\omega R_c R_L r_o C_L}$$

$$\frac{v_{out}}{v_{in}} = \frac{\left[\frac{g_m r_{\pi} R_c R_L r_o}{(R_s + r_{\pi})(R_c r_o + R_c R_L + R_c R_L)} \right]}{\left[1 + \frac{j\omega R_s r_{\pi} C_{\pi}}{R_s + r_{\pi}} \right] \left[1 + \frac{j\omega R_c R_L r_o C_L}{R_c r_o + R_c R_L + R_c R_L} \right]}$$

due to updated r_o value...
the numerator is 0.748

$$\frac{v_{out}}{v_{in}} = \frac{0.17}{(1 + j\omega 21 \times 10^{-9})(1 + j\omega 8.6 \times 10^{-9})}$$


and the 8.6×10^{-9} gets replaced with 3.79×10^{-8}

$$\text{Poles at } \frac{1}{21 \times 10^{-9}} = 47.6 \text{ Mrad/s}$$


$$\text{and } \frac{1}{8.6 \times 10^{-9}} = 116 \text{ Mrad/s} \quad 1/3.79 \times 10^{-8} = 26.4 \text{ Mrad/s}$$

$$20 \log(0.17) = -15.4 \text{ dB} \quad 20 \log(0.748) = -2.52 \text{ dB}$$

1f) cont) $\left| \frac{V_{out}}{V_{in}} \right|_{dB}$

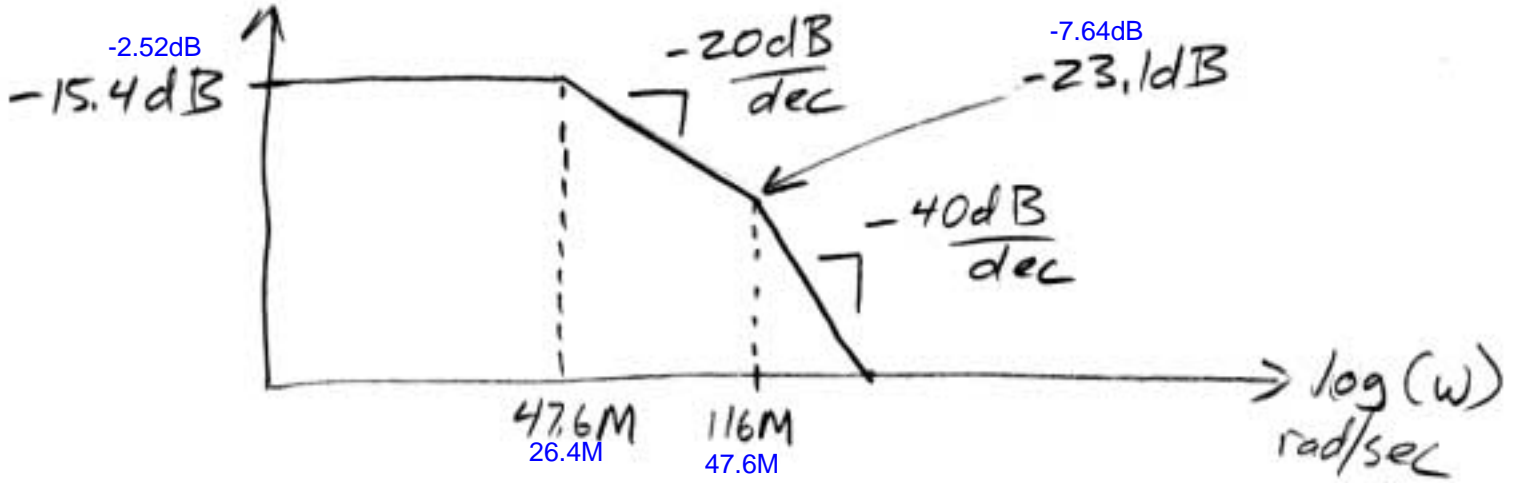
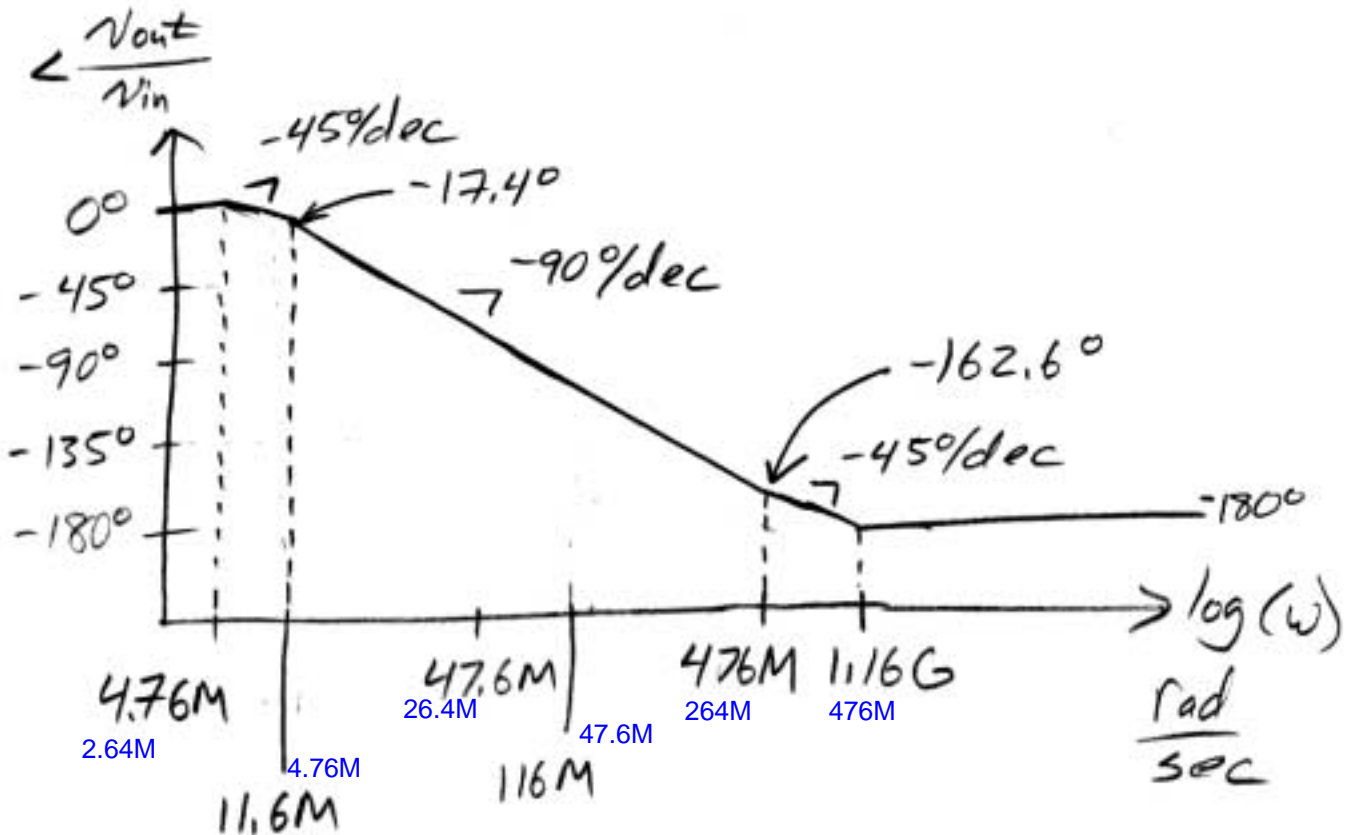
$$-15.4 - 20 \log\left(\frac{116}{47.6}\right) = -23.1 \text{ dB} \quad -2.52 - 20 \log(47.6/26.4) = -7.64 \text{ dB}$$



$$0 - 45 \log\left(\frac{11.6}{4.76}\right) = -17.4^\circ \quad -45 \log(4.76/2.64) = -11.52$$

$$-17.4 - 90 \log\left(\frac{476}{11.6}\right) = -162.6^\circ \quad -11.52 - 90 \log(264/4.76) = -168.5$$

$$-162^\circ - 45 \log\left(\frac{1.16}{0.476}\right) = -180^\circ \quad -168.5 - 45 \log(476/264) = -180$$

4/5

$$2a) I_D = q n_i^2 A \left(\frac{D_{nB}}{N_{AB} W_B} \right) \left(e^{V_{BE}/V_{th}} - 1 \right)$$

D_{nB} is a function of N_{AB} , so solve for

$\frac{D_{nB}}{N_{AB}}$ then use trial + error to find a value

$$\frac{I_D W_B}{q n_i^2 A \left(e^{V_{BE}/V_{th}} - 1 \right)} = \frac{D_{nB}}{N_{AB}}$$

$$\frac{10^{-3} \times 10^{-4}}{1.6 \times 10^{-19} 10^{20} (10^{-3})^2 \left(e^{0.7/0.026} - 1 \right)} = 12.69 \times 10^{-15} = \frac{D_{nB}}{N_{AB}}$$

Guess $D_{nB} = 10 \Rightarrow N_{AB} \sim 10^{15} \Rightarrow \mu_n = 1375 \text{ cm}^2/\text{Vs}$

need larger try $N_{AB} = 10^{16} \Rightarrow \mu_n = 1200 \text{ cm}^2/\text{Vs}$

$$\boxed{N_{AB} \approx 3 \times 10^{15} / \text{cm}^3}$$

$$2b) 1.269 \times 10^{-15} = \frac{D_{nB}}{N_{AB}} \quad \boxed{N_{AB} \approx 2.3 \times 10^{16} / \text{cm}^3}$$

$$2c) 1.269 \times 10^{-16} = \frac{D_{nB}}{N_{AB}} \quad \boxed{N_{AB} \approx 1.7 \times 10^{17} / \text{cm}^3}$$

3) saturated $\Rightarrow V_{CE} = V_{CESAT} = 0.1 \text{ V}$

$$I_C = \frac{5 - 0.1}{40 \times 10^3} = 123 \mu\text{A}$$

forward active $\Rightarrow I_B = \frac{I_C}{\beta}$

$$I_B = \frac{123 \mu\text{A}}{100} = 1.23 \mu\text{A}$$

$$V_{BIAS} - I_B 10\text{K} - V_{BE} = 0$$

$$V_{BIAS} = V_{BE} + I_B 10\text{K} = 0.7 + (1.23 \times 10^{-6})(10^4) = \boxed{0.712 \text{ V} = V_{BIAS}}$$