

Lecture 10

OUTLINE

- BJT Amplifiers (3)
 - Emitter follower (Common-collector amplifier)
 - Analysis of emitter follower core
 - Impact of source resistance
 - Impact of Early effect
 - Emitter follower with biasing


Reading: Chapter 5.3.3-5.4

EE105 Spring 2008

Lecture 10, Slide 1

Prof. Wu, UC Berkeley

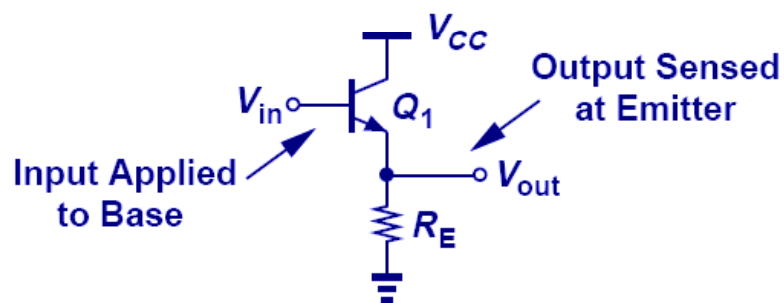Emitter Follower (Common Collector Amplifier)




EE105 Spring 2008

Lecture 10, Slide 2

Prof. Wu, UC Berkeley

Emitter Follower Core

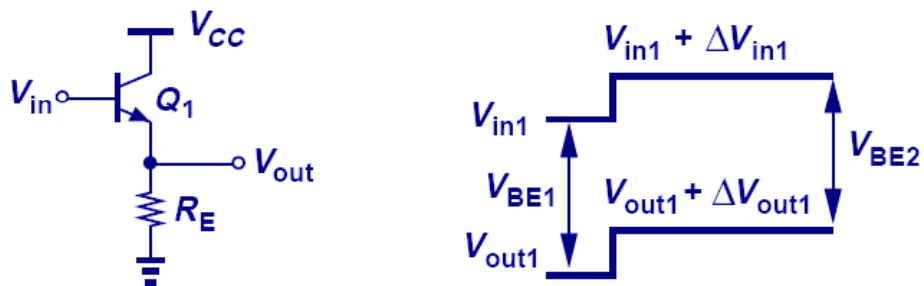


- When the input is increased by ΔV , output is also increased by an amount that is less than ΔV due to the increase in collector current and hence the increase in potential drop across R_E .
- However the absolute values of input and output differ by a V_{BE} .

EE105 Spring 2008

Lecture 10, Slide 3

Prof. Wu, UC Berkeley

Small-Signal Model of Emitter Follower

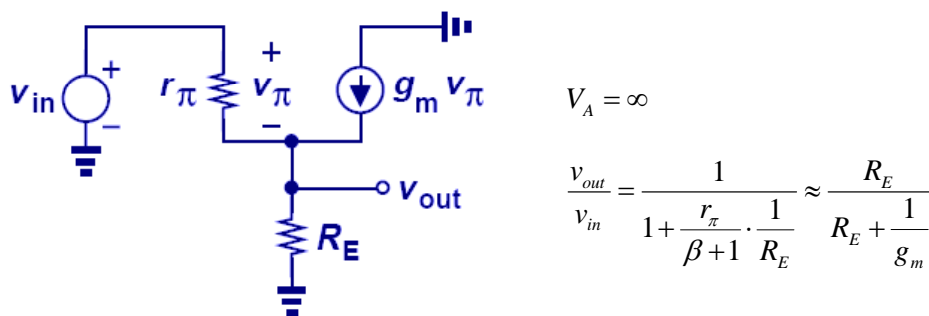


- As shown above, the voltage gain is less than unity and positive.

EE105 Spring 2008

Lecture 10, Slide 4

Prof. Wu, UC Berkeley

Unity-Gain Emitter Follower

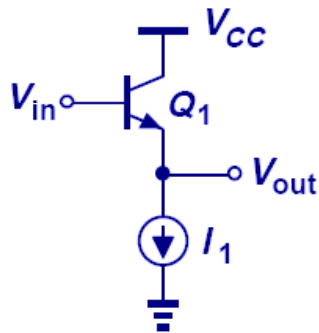

$$V_A = \infty$$

$$A_v = 1$$





- The voltage gain is unity because a constant collector current ($= I_1$) results in a constant V_{BE} , and hence V_{out} follows V_{in} exactly.

EE105 Spring 2008

Lecture 10, Slide 5

Prof. Wu, UC Berkeley

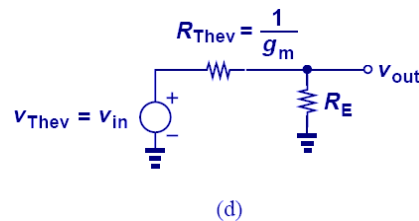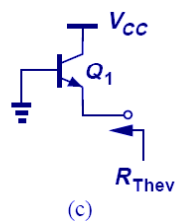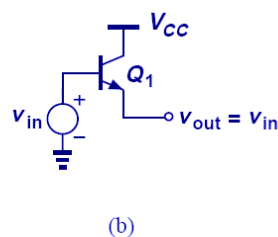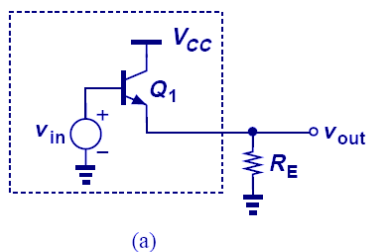Analysis of Emitter Follower as a Voltage Divider




$$V_A = \infty$$

EE105 Spring 2008

Lecture 10, Slide 6

Prof. Wu, UC Berkeley

Emitter Follower with Source Resistance

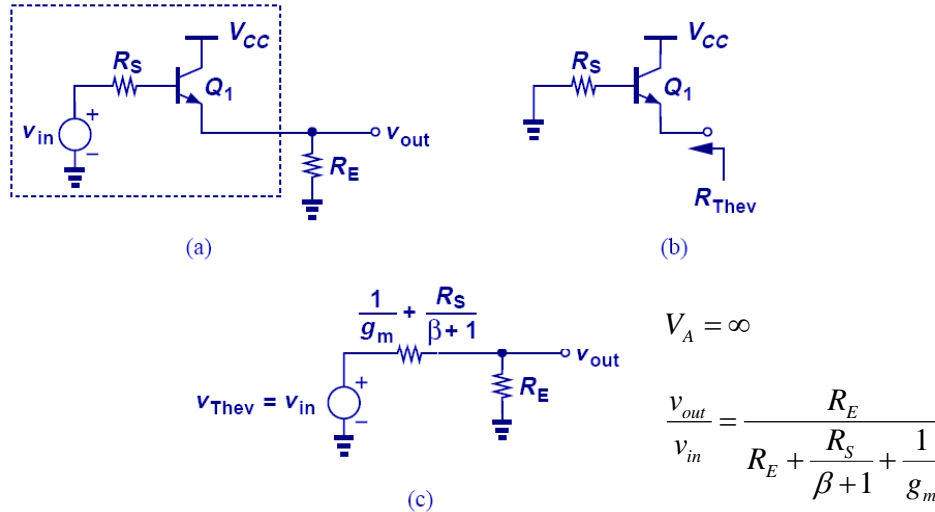


EE105 Spring 2008

Lecture 10, Slide 7

Prof. Wu, UC Berkeley

Input Impedance of Emitter Follower

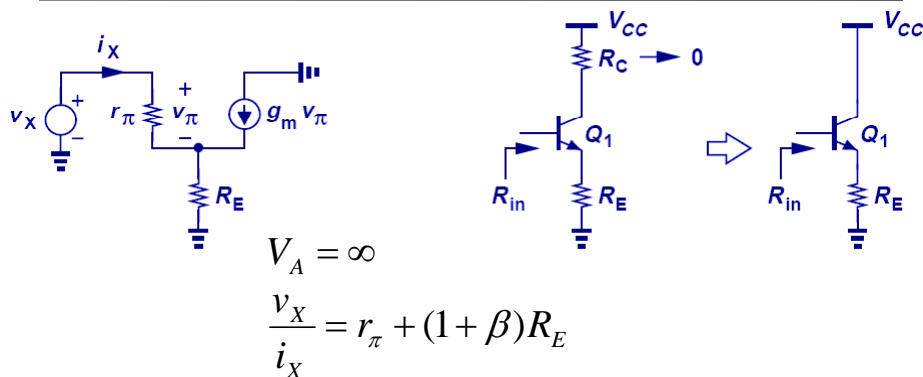


- The input impedance of emitter follower is exactly the same as that of CE stage with emitter degeneration. This is not surprising because the input impedance of CE with emitter degeneration does not depend on the collector resistance.

EE105 Spring 2008

Lecture 10, Slide 8

Prof. Wu, UC Berkeley

Emitter Follower as Buffer

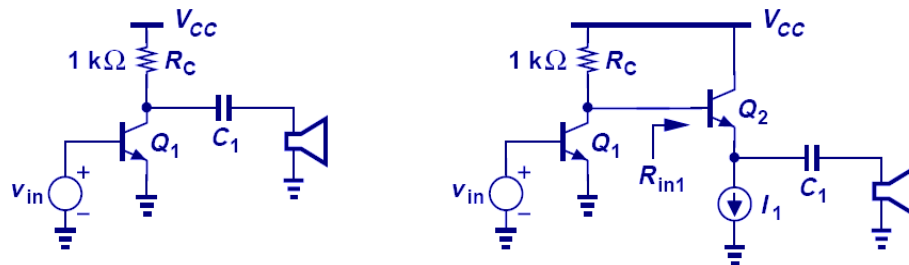


- Since the emitter follower increases the load resistance to a much higher value, it is suited as a buffer between a CE stage and a heavy load resistance to alleviate the problem of gain degradation.

EE105 Spring 2008

Lecture 10, Slide 9

Prof. Wu, UC Berkeley

Output Impedance of Emitter Follower

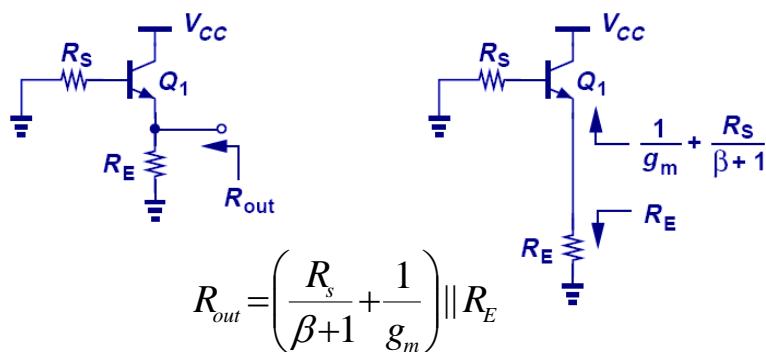


- Emitter follower lowers the source impedance by a factor of $\beta + 1 \rightarrow$ improved driving capability.

EE105 Spring 2008

Lecture 10, Slide 10

Prof. Wu, UC Berkeley

Emitter Follower with Early Effect

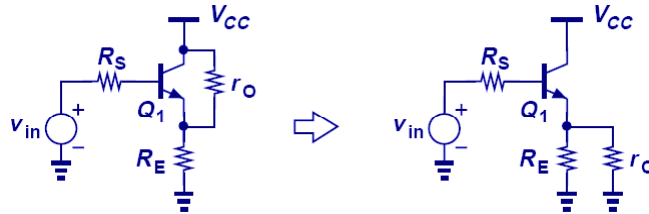

$$A_v = \frac{R_E \parallel r_o}{R_E \parallel r_o + \frac{R_S}{\beta+1} + \frac{1}{g_m}}$$

$$R_{in} = R_S + r_{\pi} + (\beta+1)(R_E \parallel r_o)$$

$$R_{out} = \left(\frac{R_S}{\beta+1} + \frac{1}{g_m} \right) \parallel R_E \parallel r_o$$


- Since r_o is in parallel with R_E , its effect can be easily incorporated into voltage gain and input and output impedance equations.

EE105 Spring 2008

Lecture 10, Slide 11

Prof. Wu, UC Berkeley

Current Gain

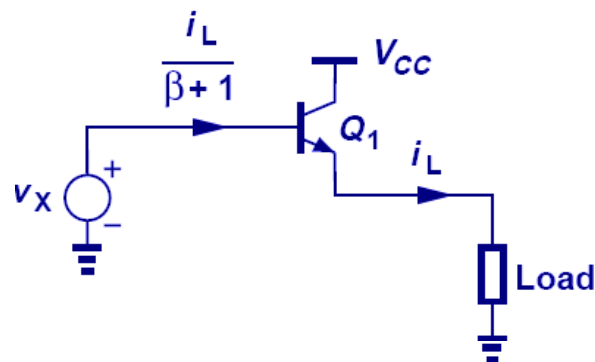


- There is a current gain of $(\beta+1)$ from base to emitter.
- Effectively speaking, the load resistance is multiplied by $(\beta+1)$ as seen from the base.

EE105 Spring 2008

Lecture 10, Slide 12

Prof. Wu, UC Berkeley

Emitter Follower with Biasing

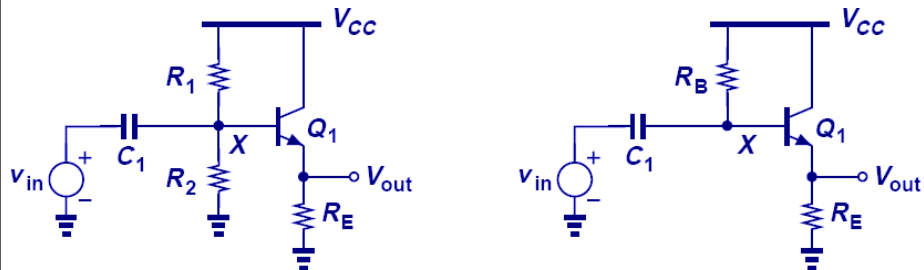


- A biasing technique similar to that of CE stage can be used for the emitter follower.
- Also, V_b can be close to V_{cc} because the collector is also at V_{cc} .

EE105 Spring 2008

Lecture 10, Slide 13

Prof. Wu, UC Berkeley

Supply-Independent Biasing

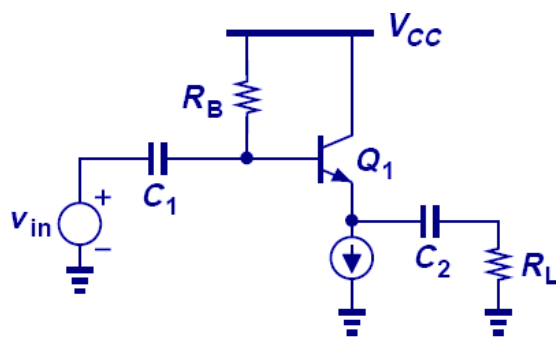


- By putting a constant current source at the emitter, the bias current, V_{BE} , and $I_B R_B$ are fixed regardless of the supply value.

EE105 Spring 2008

Lecture 10, Slide 14

Prof. Wu, UC Berkeley

Summary of Amplifier Topologies

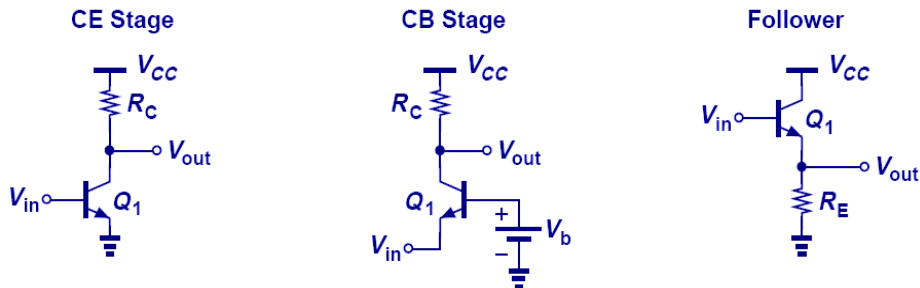


- The three amplifier topologies studied so far have different properties and are used on different occasions.
- CE and CB have voltage gain with magnitude greater than one, while follower's voltage gain is at most one.

EE105 Spring 2008

Lecture 10, Slide 15

Prof. Wu, UC Berkeley

Amplifier Example I

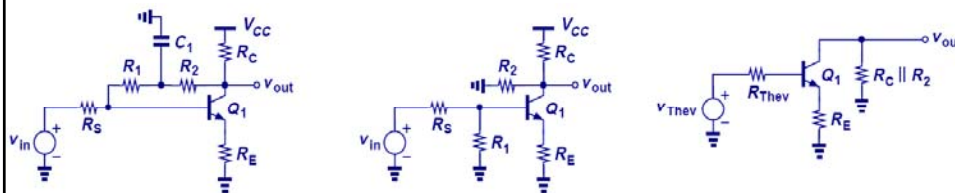

$$\frac{v_{out}}{v_{in}} = - \frac{R_2 \parallel R_C}{\frac{R_1 \parallel R_S}{\beta + 1} + \frac{1}{g_m} + R_E} \cdot \frac{R_1}{R_1 + R_S}$$


- The keys in solving this problem are recognizing the AC ground between R_1 and R_2 , and Thevenin transformation of the input network.

EE105 Spring 2008

Lecture 10, Slide 16

Prof. Wu, UC Berkeley

Amplifier Example II

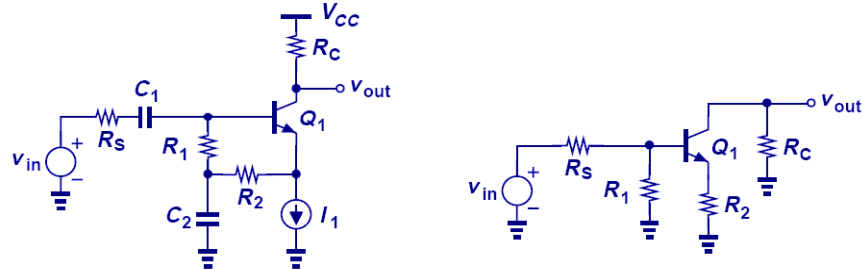

$$\frac{v_{out}}{v_{in}} = - \frac{R_C}{\frac{R_S \parallel R_1 + \frac{1}{g_m} + R_2}} \cdot \frac{R_1}{R_1 + R_S}$$


- Again, AC ground/short and Thevenin transformation are needed to transform the complex circuit into a simple stage with emitter degeneration.

EE105 Spring 2008

Lecture 10, Slide 17

Prof. Wu, UC Berkeley

Amplifier Example III

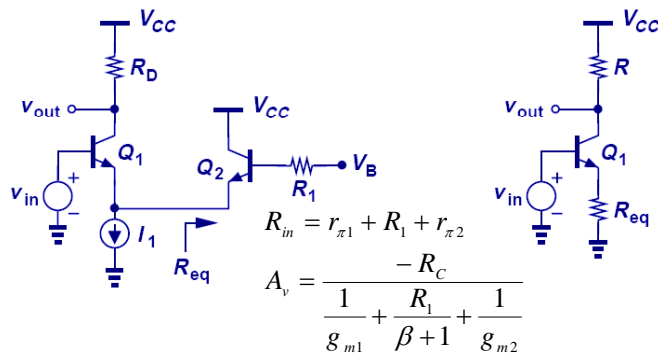

$$R_{in} = r_{\pi 1} + R_1 + r_{\pi 2}$$

$$A_v = \frac{-R_C}{\frac{1}{g_{m1}} + \frac{R_1}{\beta + 1} + \frac{1}{g_{m2}}}$$


- The key for solving this problem is first identifying R_{eq} , which is the impedance seen at the emitter of Q_2 in parallel with the infinite output impedance of an ideal current source. Second, use the equations for degenerated CE stage with R_E replaced by R_{eq} .

EE105 Spring 2008

Lecture 10, Slide 18

Prof. Wu, UC Berkeley

Amplifier Example IV

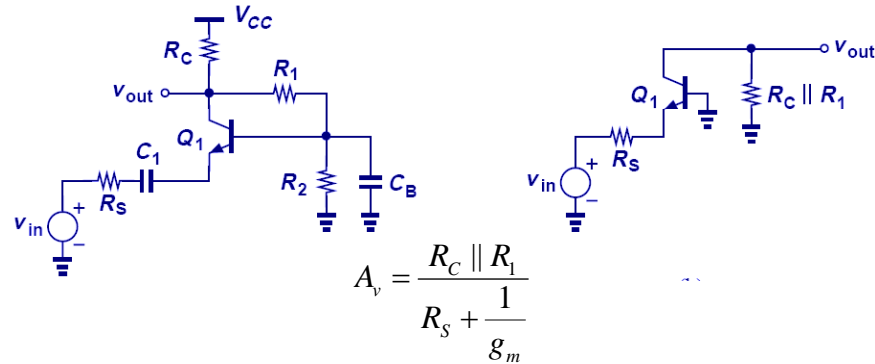


- The key for solving this problem is recognizing that C_B at frequency of interest shorts out R_2 and provide a ground for R_1 .
- R_1 appears in parallel with R_C and the circuit simplifies to a simple CB stage.

EE105 Spring 2008

Lecture 10, Slide 19

Prof. Wu, UC Berkeley

Amplifier Example V

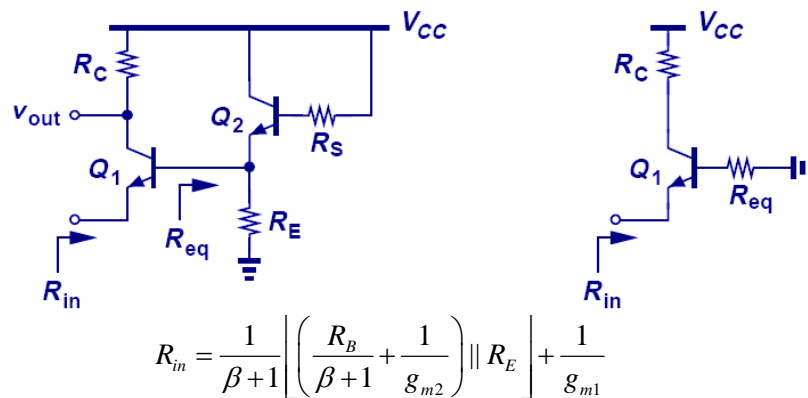


- The key for solving this problem is recognizing the equivalent base resistance of Q_1 is the parallel connection of R_E and the impedance seen at the emitter of Q_2 .

EE105 Spring 2008

Lecture 10, Slide 20

Prof. Wu, UC Berkeley

Amplifier Example VI

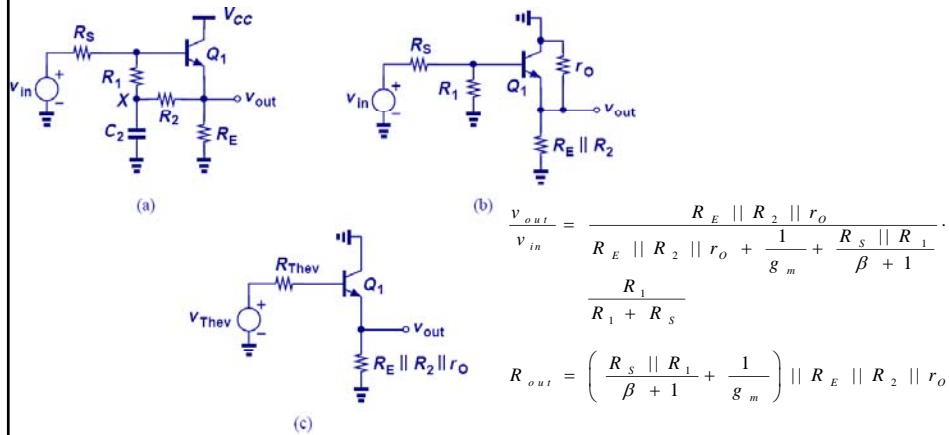


- The key in solving this problem is recognizing a DC supply is actually an AC ground and using Thevenin transformation to simplify the circuit into an emitter follower.

EE105 Spring 2008

Lecture 10, Slide 21

Prof. Wu, UC Berkeley

Amplifier Example VII

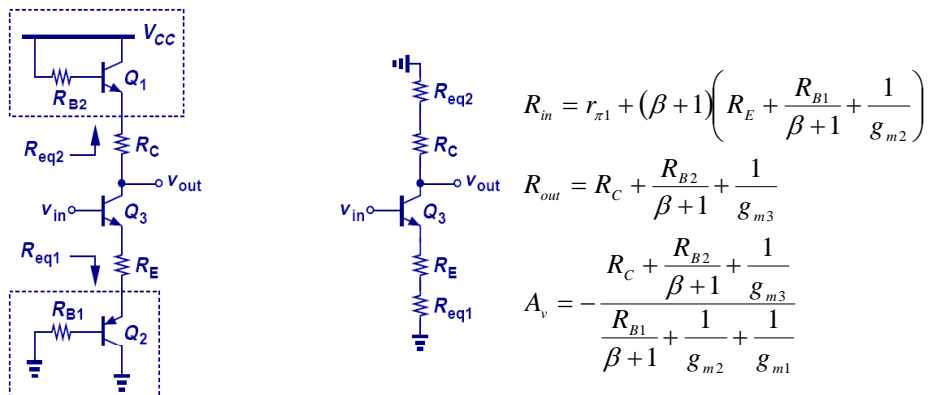

- Impedances seen at the emitter of Q₁ and Q₂ can be lumped with R_C and R_E, respectively, to form the equivalent emitter and collector impedances.

EE105 Spring 2008

Lecture 10, Slide 22

Prof. Wu, UC Berkeley