

## Lecture 10

### OUTLINE

- BJT Amplifiers (3)
  - Emitter follower (Common-collector amplifier)
  - Analysis of emitter follower core
  - Impact of source resistance
  - Impact of Early effect
  - Emitter follower with biasing


Reading: Chapter 5.3.3-5.4

EE105 Spring 2008

Lecture 10, Slide 1

Prof. Wu, UC Berkeley
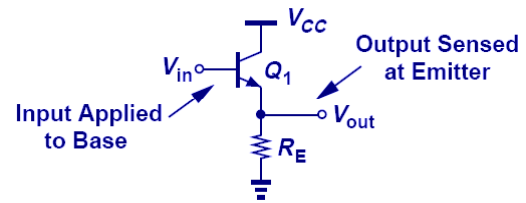
## Emitter Follower (Common Collector Amplifier)




EE105 Spring 2008

Lecture 10, Slide 2

Prof. Wu, UC Berkeley

## Emitter Follower Core

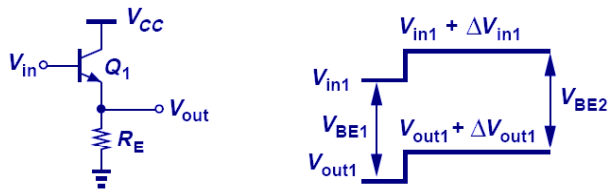


- When the input is increased by  $\Delta V$ , output is also increased by an amount that is less than  $\Delta V$  due to the increase in collector current and hence the increase in potential drop across  $R_E$ .
- However the absolute values of input and output differ by a  $V_{BE}$ .

EE105 Spring 2008

Lecture 10, Slide 3

Prof. Wu, UC Berkeley
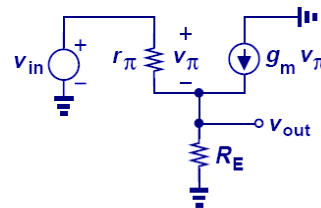
## Small-Signal Model of Emitter Follower



$V_A = \infty$

$$\frac{v_{out}}{v_{in}} = \frac{1}{1 + \frac{r_{\pi}}{\beta + 1} \cdot \frac{1}{R_E}} \approx \frac{R_E}{R_E + \frac{1}{g_m}}$$


- As shown above, the voltage gain is less than unity and positive.

EE105 Spring 2008

Lecture 10, Slide 4

Prof. Wu, UC Berkeley

### Unity-Gain Emitter Follower

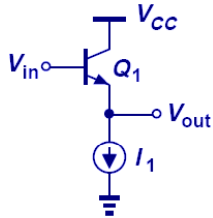

$$V_A = \infty$$

$$A_v = 1$$





- The voltage gain is unity because a constant collector current ( $= I_1$ ) results in a constant  $V_{BE}$ , and hence  $V_{out}$  follows  $V_{in}$  exactly.

EE105 Spring 2008

Lecture 10, Slide 5

Prof. Wu, UC Berkeley
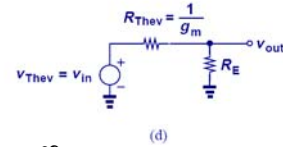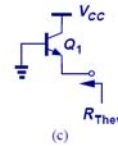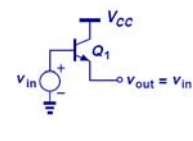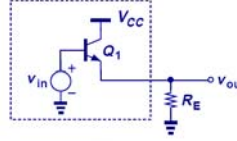
### Analysis of Emitter Follower as a Voltage Divider






$$V_A = \infty$$

EE105 Spring 2008

Lecture 10, Slide 6

Prof. Wu, UC Berkeley
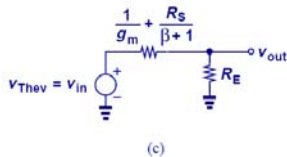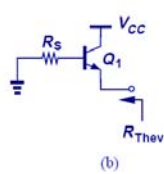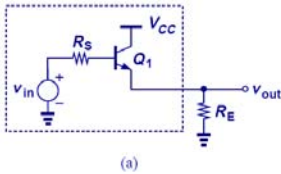
### Emitter Follower with Source Resistance



$$V_A = \infty$$



$$\frac{v_{out}}{v_{in}} = \frac{R_E}{R_E + \frac{R_S}{\beta + 1} + \frac{1}{g_m}}$$

EE105 Spring 2008

Lecture 10, Slide 7

Prof. Wu, UC Berkeley

### Input Impedance of Emitter Follower

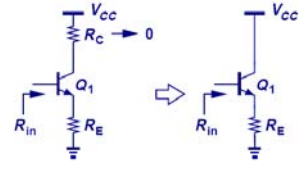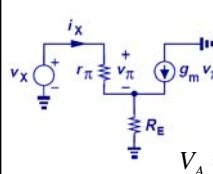

$$V_A = \infty$$

$$\frac{v_X}{i_X} = r_\pi + (1 + \beta)R_E$$


- The input impedance of emitter follower is exactly the same as that of CE stage with emitter degeneration. This is not surprising because the input impedance of CE with emitter degeneration does not depend on the collector resistance.

EE105 Spring 2008

Lecture 10, Slide 8

Prof. Wu, UC Berkeley


### Emitter Follower as Buffer

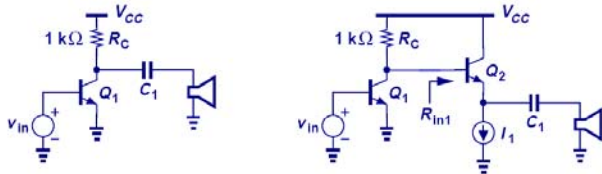

- Since the emitter follower increases the load resistance to a much higher value, it is suited as a buffer between a CE stage and a heavy load resistance to alleviate the problem of gain degradation.

EE105 Spring 2008      Lecture 10, Slide 9      Prof. Wu, UC Berkeley

### Output Impedance of Emitter Follower

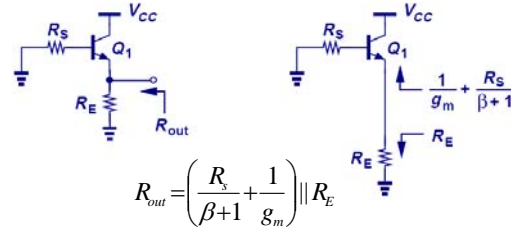


$$R_{out} = \left( \frac{R_s}{\beta+1} + \frac{1}{g_m} \right) \parallel R_E$$

- Emitter follower lowers the source impedance by a factor of  $\beta+1 \rightarrow$  improved driving capability.

EE105 Spring 2008      Lecture 10, Slide 10      Prof. Wu, UC Berkeley

### Emitter Follower with Early Effect

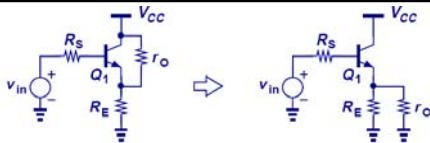

$$A_v = \frac{R_E \parallel r_o}{R_E \parallel r_o + \frac{R_s}{\beta+1} + \frac{1}{g_m}}$$


$$R_{in} = R_s + r_e + (\beta+1)(R_E \parallel r_o)$$

$$R_{out} = \left( \frac{R_s}{\beta+1} + \frac{1}{g_m} \right) \parallel R_E \parallel r_o$$

- Since  $r_o$  is in parallel with  $R_E$ , its effect can be easily incorporated into voltage gain and input and output impedance equations.

EE105 Spring 2008      Lecture 10, Slide 11      Prof. Wu, UC Berkeley


### Current Gain

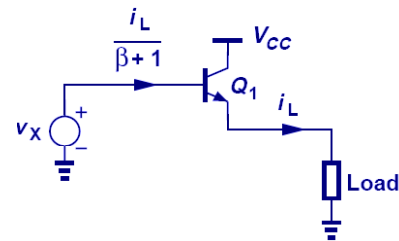

- There is a current gain of  $(\beta+1)$  from base to emitter.
- Effectively speaking, the load resistance is multiplied by  $(\beta+1)$  as seen from the base.

EE105 Spring 2008      Lecture 10, Slide 12      Prof. Wu, UC Berkeley

### Emitter Follower with Biasing

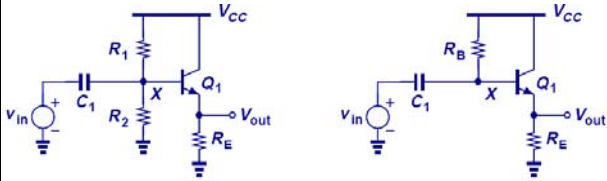


- A biasing technique similar to that of CE stage can be used for the emitter follower.
- Also,  $V_b$  can be close to  $V_{cc}$  because the collector is also at  $V_{cc}$ .

EE105 Spring 2008

Lecture 10, Slide 13

Prof. Wu, UC Berkeley

### Supply-Independent Biasing

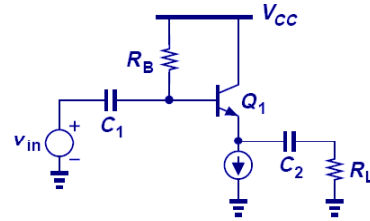


- By putting a constant current source at the emitter, the bias current,  $V_{BE}$ , and  $I_B R_B$  are fixed regardless of the supply value.

EE105 Spring 2008

Lecture 10, Slide 14

Prof. Wu, UC Berkeley

### Summary of Amplifier Topologies

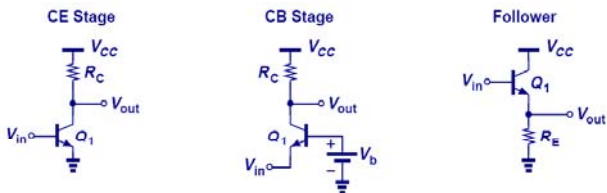


- The three amplifier topologies studied so far have different properties and are used on different occasions.
- CE and CB have voltage gain with magnitude greater than one, while follower's voltage gain is at most one.

EE105 Spring 2008

Lecture 10, Slide 15

Prof. Wu, UC Berkeley

### Amplifier Example I

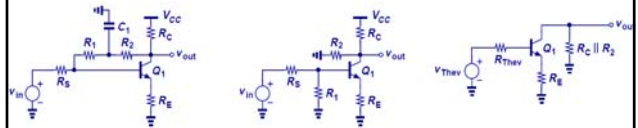

$$\frac{v_{out}}{v_{in}} = - \frac{R_2 \parallel R_C}{\frac{R_1 \parallel R_S}{\beta + 1} + R_E} \cdot \frac{R_1}{R_1 + R_S}$$


- The keys in solving this problem are recognizing the AC ground between  $R_1$  and  $R_2$ , and Thevenin transformation of the input network.

EE105 Spring 2008

Lecture 10, Slide 16

Prof. Wu, UC Berkeley

### Amplifier Example II

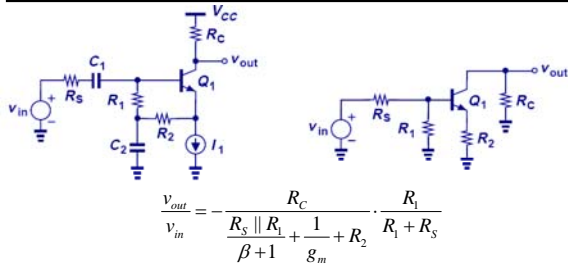


- Again, AC ground/short and Thevenin transformation are needed to transform the complex circuit into a simple stage with emitter degeneration.

EE105 Spring 2008

Lecture 10, Slide 17

Prof. Wu, UC Berkeley

### Amplifier Example III

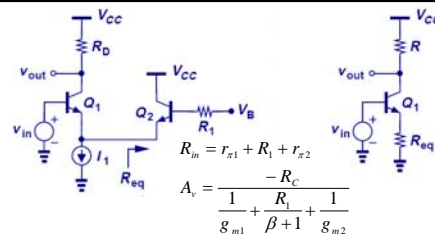


- The key for solving this problem is first identifying  $R_{eq}$ , which is the impedance seen at the emitter of  $Q_2$  in parallel with the infinite output impedance of an ideal current source. Second, use the equations for degenerated CE stage with RE replaced by  $R_{eq}$ .

EE105 Spring 2008

Lecture 10, Slide 18

Prof. Wu, UC Berkeley

### Amplifier Example IV

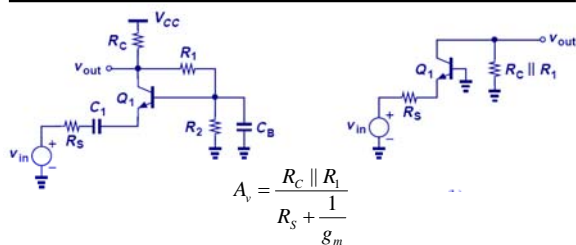


- The key for solving this problem is recognizing that CB at frequency of interest shorts out  $R_2$  and provide a ground for  $R_1$ .
- $R_1$  appears in parallel with RC and the circuit simplifies to a simple CB stage.

EE105 Spring 2008

Lecture 10, Slide 19

Prof. Wu, UC Berkeley

### Amplifier Example V

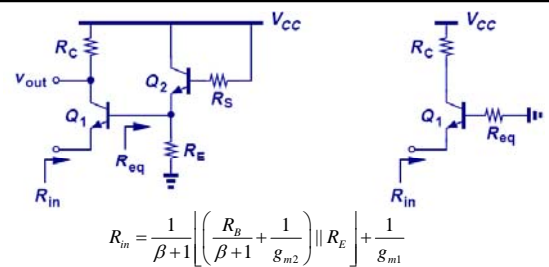


- The key for solving this problem is recognizing the equivalent base resistance of  $Q_1$  is the parallel connection of RE and the impedance seen at the emitter of  $Q_2$ .

EE105 Spring 2008

Lecture 10, Slide 20

Prof. Wu, UC Berkeley

### Amplifier Example VI

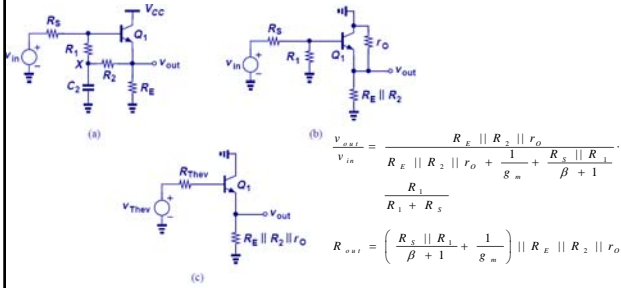


$$v_{o,ac} = \frac{R_E \parallel R_C \parallel r_o}{R_E \parallel R_C \parallel r_o + \frac{1}{g_m} + \frac{R_s \parallel R_1}{\beta + 1}}$$

$$R_o = \left( \frac{R_s \parallel R_1}{\beta + 1} + \frac{1}{g_m} \right) \parallel R_E \parallel R_C \parallel r_o$$

- The key in solving this problem is recognizing a DC supply is actually an AC ground and using Thevenin transformation to simplify the circuit into an emitter follower.

EE105 Spring 2008      Lecture 10, Slide 21      Prof. Wu, UC Berkeley

### Amplifier Example VII

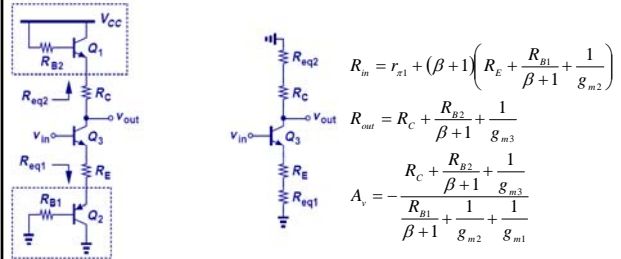

$$R_m = r_{\pi 1} + (\beta + 1) \left( R_E + \frac{R_{B1}}{\beta + 1} + \frac{1}{g_{m2}} \right)$$

$$R_{out} = R_C + \frac{R_{B2}}{\beta + 1} + \frac{1}{g_{m3}}$$

$$A_v = - \frac{R_C + \frac{R_{B2}}{\beta + 1} + \frac{1}{g_{m3}}}{\frac{R_{B1}}{\beta + 1} + \frac{1}{g_{m2}} + \frac{1}{g_{m1}}}$$

- Impedances seen at the emitter of  $Q_3$  and  $Q_2$  can be lumped with  $R_C$  and  $R_E$ , respectively, to form the equivalent emitter and collector impedances.

EE105 Spring 2008      Lecture 10, Slide 22      Prof. Wu, UC Berkeley