

## Lecture 11

---

### OUTLINE




- Cascode Stage

Reading: Chapter 9.1

EE105 Spring 2008      Lecture 11, Slide 1      Prof. Wu, UC Berkeley

## Ideal Current Source

---

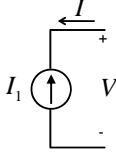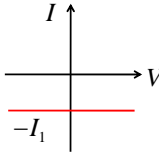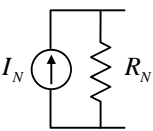Circuit Symbol	I-V Characteristic	Equivalent Circuit
		

- An ideal current source has infinite output impedance.


*How can we increase the output impedance of a BJT that is used as a current source?*

EE105 Spring 2008      Lecture 11, Slide 2      Prof. Wu, UC Berkeley
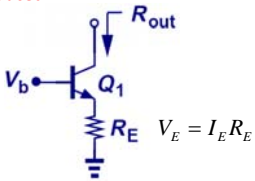
## Boosting the Output Impedance

---

- Recall that emitter degeneration boosts the impedance seen looking into the collector.
  - This improves the gain of the CE or CB amplifier. **However, headroom is reduced.**



$V_E = I_E R_E$


$$R_{out} = [1 + g_m (R_E \parallel r_\pi)] r_o + R_E \parallel r_\pi$$

EE105 Spring 2008      Lecture 11, Slide 3      Prof. Wu, UC Berkeley
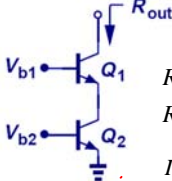
## Cascode Stage

---

- In order to relax the trade-off between output impedance and voltage headroom, we can use a transistor instead of a degeneration resistor:



$$R_{out} = [1 + g_m (r_{o2} \parallel r_{\pi1})] r_{o1} + r_{o2} \parallel r_{\pi1}$$

$$R_{out} \approx g_{m1} r_{o1} (r_{o2} \parallel r_{\pi1})$$


$$I_{C2} = I_{E1} \cong I_{C1} \text{ if } \beta_1 \gg 1$$

- $V_{CE}$  for  $Q_2$  can be as low as  $\sim 0.4V$  ("soft saturation")

EE105 Spring 2008      Lecture 11, Slide 4      Prof. Wu, UC Berkeley

## Maximum Bipolar Cascode Output Impedance

---

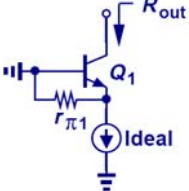

$$R_{out,max} \approx g_{m1} r_{o1} r_{\pi1}$$


$$R_{out,max} \approx \beta_1 r_{o1}$$

- The maximum output impedance of a bipolar cascode is bounded by the ever-present  $r_\pi$  between emitter and ground of  $Q_1$ .

EE105 Spring 2008      Lecture 11, Slide 5      Prof. Wu, UC Berkeley

## PNP Cascode Stage

---

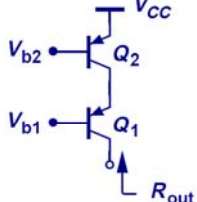

$$R_{out} = [1 + g_m (r_{o2} \parallel r_{\pi1})] r_{o1} + r_{o2} \parallel r_{\pi1}$$

$$R_{out} \approx g_{m1} r_{o1} (r_{o2} \parallel r_{\pi1})$$

EE105 Spring 2008      Lecture 11, Slide 6      Prof. Wu, UC Berkeley

### False Cascodes

(a)

$$R_{out} = \left[ 1 + g_{m1} \left( \frac{1}{g_{m2}} \parallel r_{O2} \parallel r_{\pi1} \right) \right] r_{O1} + \frac{1}{g_{m2}} \parallel r_{O2} \parallel r_{\pi1}$$

$$R_{out} \approx \left( 1 + \frac{g_{m1}}{g_{m2}} \right) r_{O1} + \frac{1}{g_{m2}} \approx 2r_{O1}$$

(b)

- When the emitter of  $Q_1$  is connected to the emitter of  $Q_2$ , it's no longer a cascode since  $Q_2$  becomes a diode-connected device instead of a current source.

EE105 Spring 2008      Lecture 11, Slide 7      Prof. Wu, UC Berkeley

### Short-Circuit Transconductance

- The **short-circuit transconductance** of a circuit is a measure of its strength in converting an input voltage signal into an output current signal.

$$G_m \equiv \left. \frac{i_{out}}{v_{in}} \right|_{v_{out}=0}$$

EE105 Spring 2008      Lecture 11, Slide 8      Prof. Wu, UC Berkeley

### Voltage Gain of a Linear Circuit

- By representing a linear circuit with its Norton equivalent, the relationship between  $V_{out}$  and  $V_{in}$  can be expressed by the product of  $G_m$  and  $R_{out}$ .

(a)

**Norton Equivalent Circuit**

(b)

**Computation of short-circuit output current:**

$$v_{out} = -i_{out} R_{out} = -G_m v_{in} R_{out}$$

$$v_{out} / v_{in} = -G_m R_{out}$$

EE10      Prof. Wu, UC Berkeley

### Example: Voltage Gain

(a)

(b)

$$G_m \equiv \left. \frac{i_{out}}{v_{in}} \right|_{v_{out}=0} = g_{m1}$$

(c)

$$R_{out} \equiv \frac{v_x}{i_x} = r_{O1}$$

$$A_v = -g_{m1} r_{O1}$$

EE105 Spring 2008      Lecture 11, Slide 10      Prof. Wu, UC Berkeley

### Comparison of CE and Cascode Stages

- Since the output impedance of the cascode is higher than that of a CE stage, its voltage gain is also higher.

$$A_v = -g_{m1} r_{O1} = -\frac{V_A}{V_T}$$

$$A_v \approx -g_{m1} r_{O2} g_{m2} (r_{O1} \parallel r_{\pi2})$$

EE105 Spring 2008      Lecture 11, Slide 11      Prof. Wu, UC Berkeley

### Voltage Gain of Cascode Amplifier

- Since  $r_o$  is much larger than  $1/g_m$ , most of  $I_{C,Q1}$  flows into diode-connected  $Q_2$ . Using  $R_{out}$  as before,  $A_v$  is easily calculated.

(a)

(b)

$$i_{out} = g_{m1} v_{in}$$

$$\Rightarrow G_m = g_{m1}$$


$$A_v = -G_m R_{out}$$

$$= -g_{m1} [(1 + g_{m2} (r_{O1} \parallel r_{\pi2})) r_{O2} + r_{O1} \parallel r_{\pi2}]$$

$$\approx -g_{m1} [g_{m2} (r_{O1} \parallel r_{\pi2}) r_{O2}]$$

EE105 Spring 2008      Lecture 11, Slide 12      Prof. Wu, UC Berkeley

### Alternate View of Cascode Amplifier

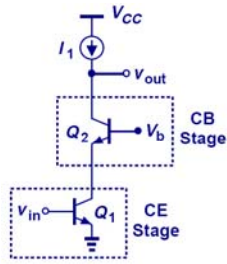


- A bipolar cascode amplifier is also a CE stage in series with a CB stage.

EE105 Spring 2008

Lecture 11, Slide 13

Prof. Wu, UC Berkeley

### Practical Cascode Stage

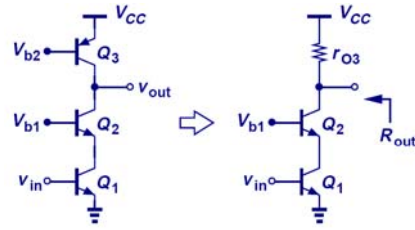

$$R_{out} \approx r_{O3} \parallel g_{m2}r_{O2}(r_{O1} \parallel r_{\pi2})$$


- Since no current source can be ideal, the output impedance drops.

EE105 Spring 2008

Lecture 11, Slide 14

Prof. Wu, UC Berkeley

### Improved Cascode Stage

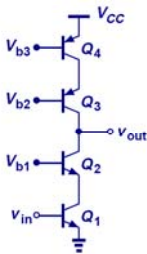

$$R_{out} \approx [g_{m3}r_{O3}(r_{O4} \parallel r_{\pi3})] \parallel [g_{m2}r_{O2}(r_{O1} \parallel r_{\pi2})]$$

$$A_v = -g_{m1}R_{out}$$

- In order to preserve the high output impedance, a cascode PNP current source is used.

EE105 Spring 2008

Lecture 11, Slide 15

Prof. Wu, UC Berkeley