

Lecture 12

OUTLINE

- Current Mirrors
- Reading: Chapter 9.2


EE105 Spring 2008

Lecture 12, Slide 1

Prof. Wu, UC Berkeley

Temperature and Supply-Voltage Dependence of Bias Current

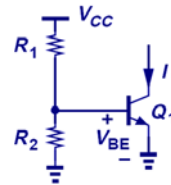- Circuits should be designed to operate properly over a range of supply voltages and temperatures.
- For the biasing scheme shown below, I_1 depends on the temperature as well as the supply voltage, since V_T and I_S depend on temperature.



$$I_1 = I_S e^{V_{BE}/V_T}$$

$$V_{BE} \cong \frac{R_2}{R_1 + R_2} V_{CC}$$


EE105 Spring 2008

Lecture 12, Slide 2

Prof. Wu, UC Berkeley

Concept of a Current Mirror

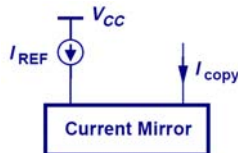- Circuit designs to provide a supply- and temperature-independent current exist, but require many transistors to implement.
→ "golden current source"
- A **current mirror** is used to replicate the current from a "golden current source" to other locations.



EE105 Spring 2008


Lecture 12, Slide 3

Prof. Wu, UC Berkeley


Current Mirror Circuitry

- Diode-connected Q_{REF} produces an output voltage V_X that forces I_{copy1} to be equal to I_{REF} if Q_1 is identical to Q_{REF} .


Current mirror concept

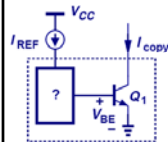

Generation of required V_{BE}

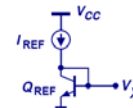

Current Mirror Circuitry

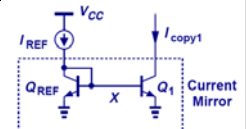

$$V_X = V_T \ln \left(\frac{I_{copy1}}{I_{S,1}} \right) = V_T \ln \left(\frac{I_{REF}}{I_{S,REF}} \right)$$


$$I_{copy1} = \frac{I_{S,1}}{I_{S,REF}} I_{REF}$$

EE105 Spring 2008

Lecture 12, Slide 4

Prof. Wu, UC Berkeley

Bad Current Mirror Example I

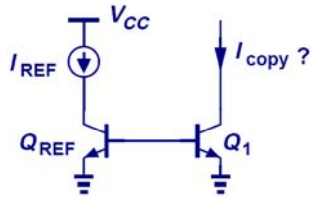


- Without shorting the collector and base of Q_{REF} together, there will not be a path for the base currents to flow, therefore, I_{copy} is zero.

EE105 Spring 2008

Lecture 12, Slide 5

Prof. Wu, UC Berkeley

Bad Current Mirror Example II

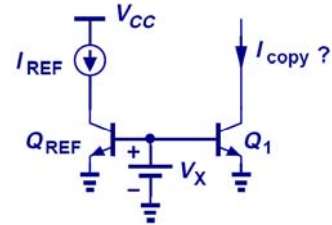


- Although a path for base currents exists, this technique of biasing is no better than resistive divider.

EE105 Spring 2008

Lecture 12, Slide 6

Prof. Wu, UC Berkeley

Multiple Copies of I_{REF}

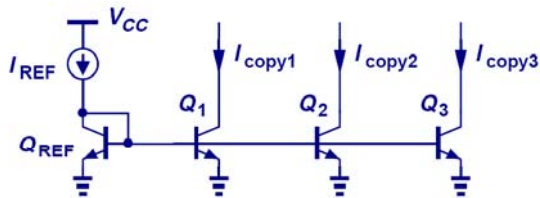

$$I_{copy,j} = \frac{I_{S,j}}{I_{S,REF}} I_{REF}$$


- Multiple copies of I_{REF} can be generated at different locations by simply applying the idea of current mirror to more transistors.

EE105 Spring 2008

Lecture 12, Slide 7

Prof. Wu, UC Berkeley

Current Scaling

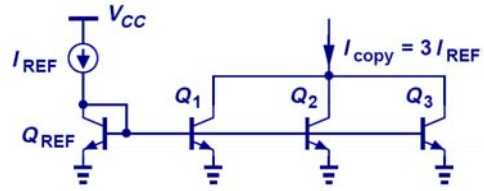

$$I_{copy,j} = n I_{REF}$$


- By scaling the emitter area of Q_j n times with respect to Q_{REF} , $I_{copy,j}$ is also n times larger than I_{REF} . This is equivalent to placing n unit-size transistors in parallel.

EE105 Spring 2008

Lecture 12, Slide 8

Prof. Wu, UC Berkeley

Example: Scaled Current

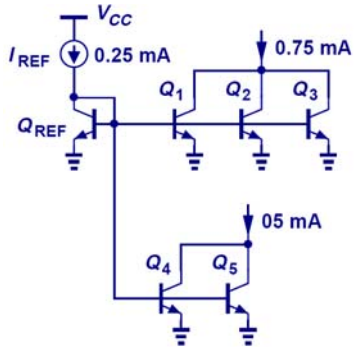


EE105 Spring 2008

Lecture 12, Slide 9

Prof. Wu, UC Berkeley

Fractional Scaling

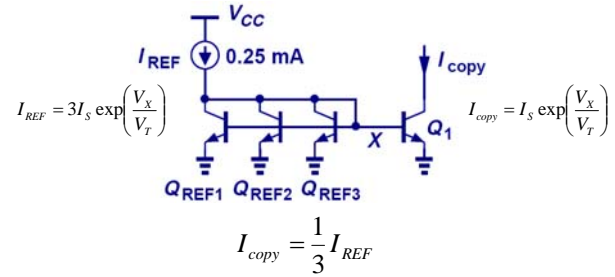- A fraction of I_{REF} can be created in Q_1 by scaling up the emitter area of Q_{REF} .




EE105 Spring 2008

Lecture 12, Slide 10

Prof. Wu, UC Berkeley

Example: Different Mirroring Ratio

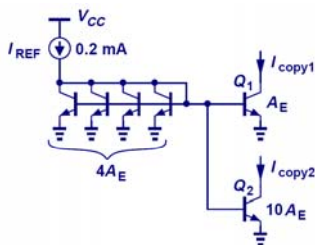


- Using the idea of current scaling and fractional scaling, I_{copy2} is 0.5mA and I_{copy1} is 0.05mA respectively. All coming from a source of 0.2mA.

EE105 Spring 2008

Lecture 12, Slide 11

Prof. Wu, UC Berkeley

Effect of Base Currents

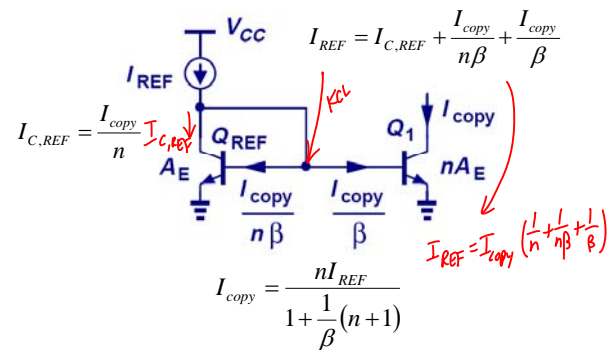

EE105 Spring 2008


Lecture 12, Slide 12

Prof. Wu, UC Berkeley

Improved Mirroring Accuracy

- Use Q_F (rather than I_{REF}) to supply the base currents of Q_{REF} and Q_1 , reduce the mirroring error by a factor of β .

$$I_{REF} = I_{B,F} + I_{C,REF}$$

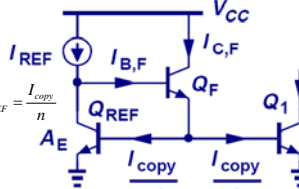

$$I_{C,F} \cong I_{E,F} = \frac{I_{copy}}{n\beta} + \frac{I_{copy}}{\beta}$$

$$I_{B,F} \cong \frac{I_{copy}}{\beta^2} \left(\frac{1}{n} + 1 \right)$$


$$I_{copy} = \frac{nI_{REF}}{1 + \frac{1}{\beta^2}(n+1)}$$

EE105 Spring 2008

Lecture 12, Slide 13

Prof. Wu, UC Berkeley

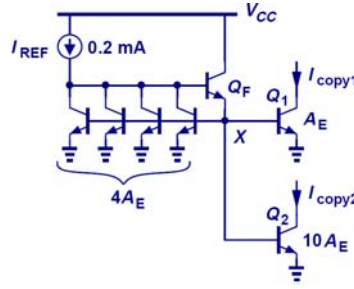Example: Different Mirroring Ratio Accuracy



$$I_{C,F} = \frac{I_{C,REF}}{\beta} + \frac{I_{copy1}}{\beta} + \frac{I_{copy2}}{\beta}$$

$$= \frac{4I_{copy1}}{\beta} + \frac{I_{copy1}}{\beta} + \frac{10I_{copy1}}{\beta}$$

$$= \frac{15I_{copy1}}{\beta}$$

$$I_{REF} = \frac{15I_{copy1}}{\beta^2} + I_{C,REF}$$

$$= \frac{15I_{copy1}}{\beta^2} + 4I_{copy1}$$

$$I_{copy1} = \frac{I_{REF}}{4 + \frac{15}{\beta^2}}$$


$$I_{copy2} = \frac{10I_{REF}}{4 + \frac{15}{\beta^2}}$$

EE105 Spring 2008

Lecture 12, Slide 14

Prof. Wu, UC Berkeley

PNP Current Mirror

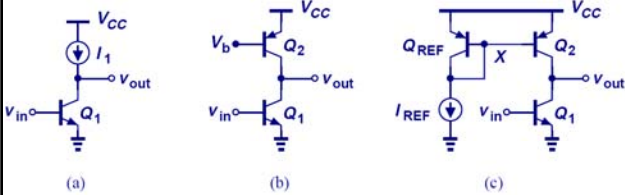


- PNP current mirror is used as a current source load to an NPN amplifier stage.

EE105 Spring 2008

Lecture 12, Slide 15

Prof. Wu, UC Berkeley

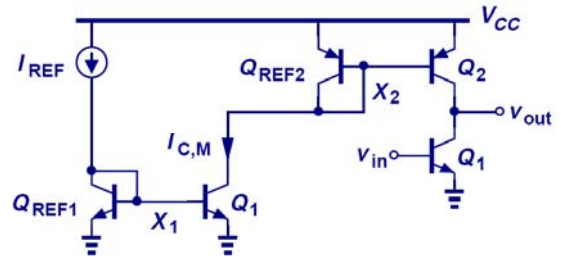Generation of I_{REF} for PNP Current Mirror




EE105 Spring 2008

Lecture 12, Slide 16

Prof. Wu, UC Berkeley

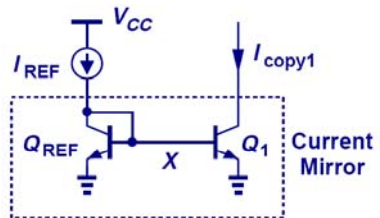Example: Current Mirror with Discrete Devices



- Let Q_{REF} and Q_1 be discrete NPN devices. I_{REF} and I_{copy1} can vary in large magnitude due to I_S mismatch.