

# Lecture 13

---

## OUTLINE

- Frequency Response
  - General considerations
  - High-frequency BJT model
  - Miller's Theorem
  - Frequency response of CE stage

Reading: Chapter 11.1-11.3

# Review: Sinusoidal Analysis


---

- Any voltage or current in a linear circuit with a sinusoidal source is a sinusoid of the same frequency ( $\omega$ ).
    - We only need to keep track of the amplitude and phase, when determining the response of a linear circuit to a sinusoidal source.
  - Any time-varying signal can be expressed as a sum of sinusoids of various frequencies (and phases).
- Applying the principle of superposition:
- The current or voltage response in a linear circuit due to a time-varying input signal can be calculated as the sum of the sinusoidal responses for each sinusoidal component of the input signal.
 
# High Frequency “Roll-Off” in $A_v$


---

- Typically, an amplifier is designed to work over a limited range of frequencies.
  - At “high” frequencies, the gain of an amplifier decreases.


 
# $A_v$ Roll-Off due to $C_L$


- A capacitive load ( $C_L$ ) causes the gain to decrease at high frequencies.
  - The impedance of  $C_L$  decreases at high frequencies, so that it shunts some of the output current to ground.



$$A_v = -g_m \left( R_C \parallel \frac{1}{j\omega C_L} \right)$$
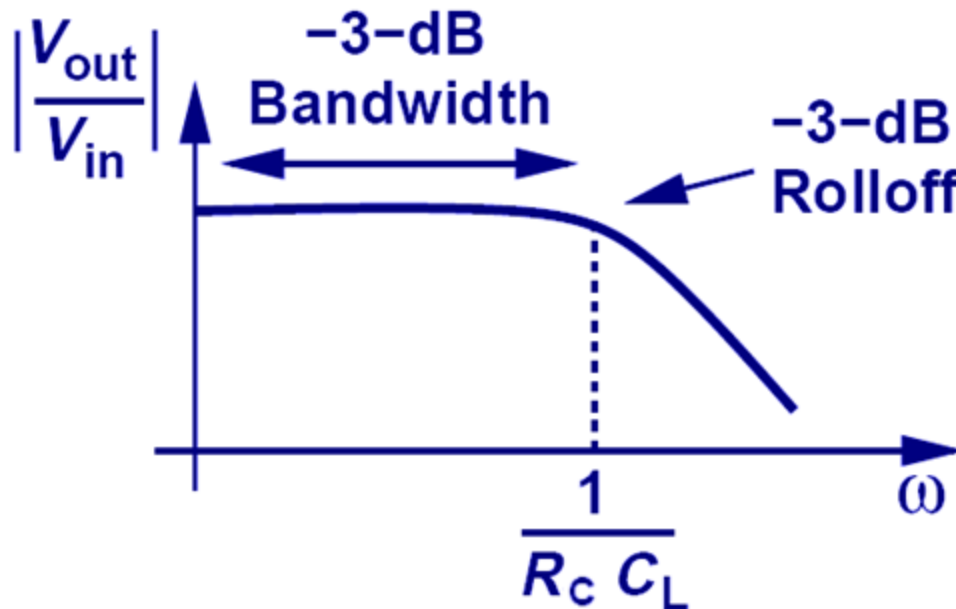
# Frequency Response of the CE Stage

- At low frequency, the capacitor is effectively an open circuit, and  $A_v$  vs.  $\omega$  is flat. At high frequencies, the impedance of the capacitor decreases and hence the gain decreases. The “breakpoint” frequency is  $1/(R_C C_L)$ .




$$A_v = -g_m \frac{R_C \frac{1}{j\omega C_L}}{R_C + \frac{1}{j\omega C_L}}$$

$$= \frac{-g_m R_C}{1 + j\omega R_C C_L}$$

$$|A_v| = \frac{g_m R_C}{\sqrt{R_C^2 C_L^2 \omega^2 + 1}}$$
 
# Amplifier Figure of Merit (FOM)

- The gain-bandwidth product is commonly used to benchmark amplifiers.
  - We wish to maximize both the gain and the bandwidth.
- Power consumption is also an important attribute.
  - We wish to minimize the power consumption.



$$\frac{\text{Gain} \times \text{Bandwidth}}{\text{Power Consumption}} = \frac{(g_m R_C) \left( \frac{1}{R_C C_L} \right)}{I_C V_{CC}}$$
$$= \frac{1}{V_T V_{CC} C_L}$$

**Operation at low  $T$ , low  $V_{CC}$ , and with small  $C_L \rightarrow$  superior FOM**

# Bode Plot

---

- The transfer function of a circuit can be written in the general form


$$H(j\omega) = A_0 \frac{\left(1 + \frac{j\omega}{\omega_{z1}}\right)\left(1 + \frac{j\omega}{\omega_{z2}}\right)\dots}{\left(1 + \frac{j\omega}{\omega_{p1}}\right)\left(1 + \frac{j\omega}{\omega_{p2}}\right)\dots}$$

$A_0$  is the low-frequency gain  
 $\omega_{zj}$  are “zero” frequencies  
 $\omega_{pj}$  are “pole” frequencies

- Rules for generating a Bode magnitude vs. frequency plot:
  - As  $\omega$  passes each **zero** frequency, the **slope of  $|H(j\omega)|$  increases** by 20dB/dec.
  - As  $\omega$  passes each **pole** frequency, the **slope of  $|H(j\omega)|$  decreases** by 20dB/dec.

# Bode Plot Example

- This circuit has only one pole at  $\omega_{p1} = 1/(R_C C_L)$ ; the slope of  $|A_v|$  decreases from 0 to -20dB/dec at  $\omega_{p1}$ .

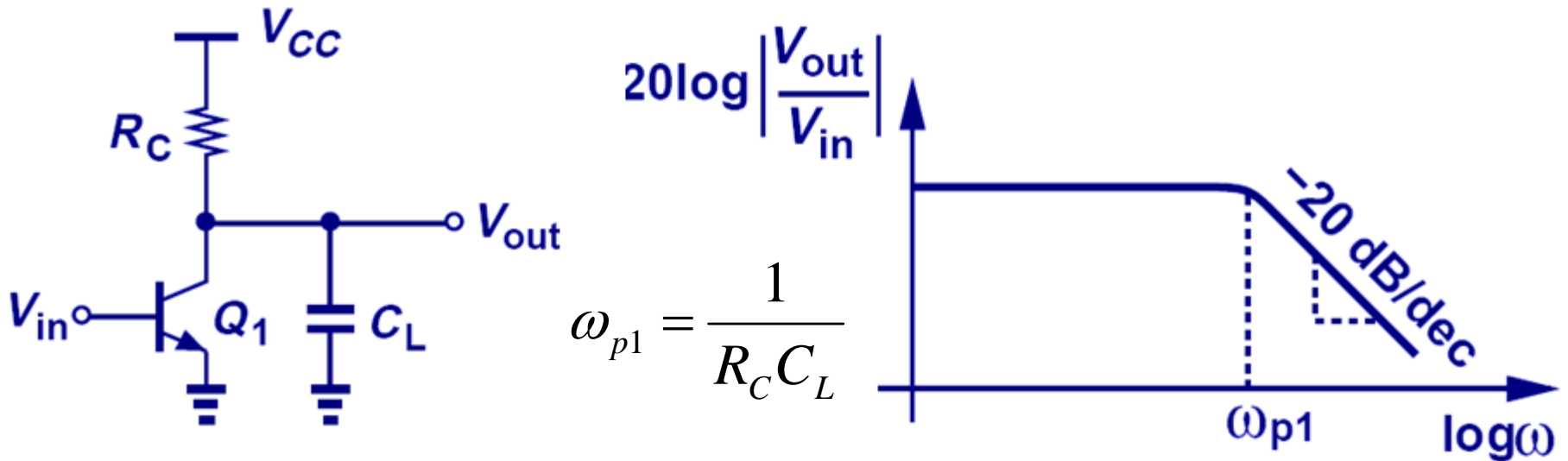


- In general, if **node  $j$  in the signal path** has a small-signal resistance of  $R_j$  to ground and a capacitance  $C_j$  to ground, then it contributes a **pole at frequency  $(R_j C_j)^{-1}$**



# Pole Identification Example

---

 

$$\omega_{p1} = \frac{1}{R_S C_{in}}$$



$$\omega_{p2} = \frac{1}{R_C C_L}$$

# High-Frequency BJT Model

- The BJT inherently has junction capacitances which affect its performance at high frequencies.

Collector junction: **depletion** capacitance,  $C_\mu$

  Emitter junction: **depletion** capacitance,  $C_{je}$ , and also **diffusion** capacitance,  $C_b$ .




$$C_\pi \equiv C_b + C_{je}$$


# BJT High-Frequency Model (cont'd)

- In an integrated circuit, the BJTs are fabricated in the surface region of a Si wafer substrate; another junction exists between the collector and substrate, resulting in substrate junction capacitance,  $C_{CS}$ .

BJT cross-section

 


BJT small-signal model

 
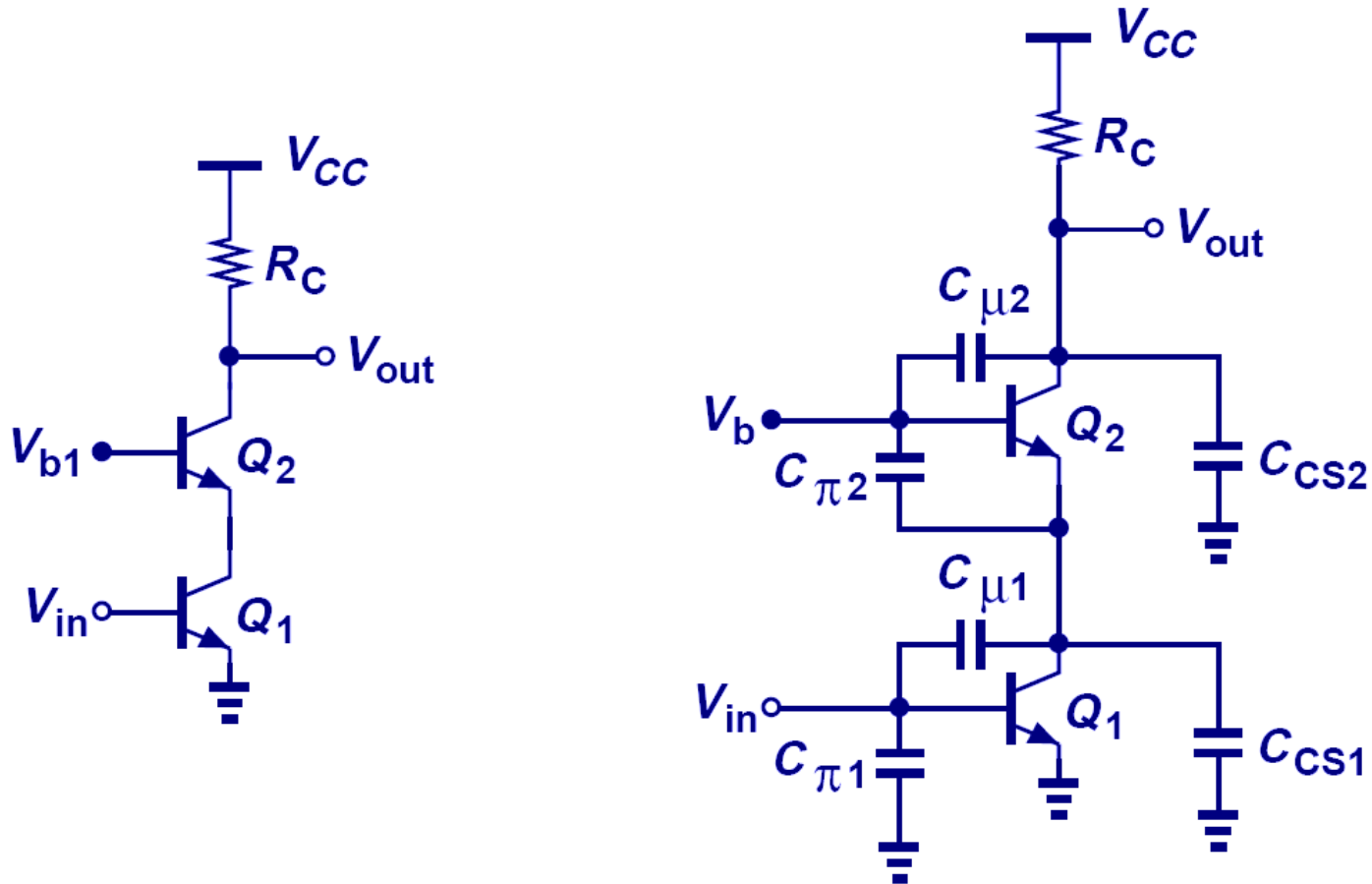
# Example: BJT Capacitances


- The various junction capacitances within each BJT are explicitly shown in the circuit diagram on the right.



# Transit Frequency, $f_T$

- The “transit” or “cut-off” frequency,  $f_T$ , is a measure of the intrinsic speed of a transistor, and is defined as the frequency where the current gain falls to 1.

## Conceptual set-up to measure $f_T$

 


$$\left| \frac{I_{out}}{I_{in}} \right| = |g_m Z_{in}| = \left| g_m \left( \frac{1}{j\omega_T C_{in}} \right) \right| = 1$$

$$\Rightarrow \omega_T = \frac{g_m}{C_{in}}$$

$$2\pi f_T = \frac{g_m}{C_{\pi}}$$
 
# Dealing with a Floating Capacitance


- Recall that a pole is computed by finding the resistance and capacitance between a node and GROUND.
- It is not straightforward to compute the pole due to  $C_{\mu 1}$  in the circuit below, because neither of its terminals is grounded.


 
# Miller's Theorem

- If  $A_v$  is the voltage gain from node 1 to 2, then a floating impedance  $Z_F$  can be converted to two grounded impedances  $Z_1$  and  $Z_2$ :


$$\frac{V_1 - V_2}{Z_F} = \frac{V_1}{Z_1} \Rightarrow Z_1 = Z_F \frac{V_1}{V_1 - V_2} = Z_F \frac{1}{1 - A_v} = Z_1$$



$$\frac{V_1 - V_2}{Z_F} = -\frac{V_2}{Z_2} \Rightarrow Z_2 = -Z_F \frac{V_2}{V_1 - V_2} = Z_F \frac{1}{1 - 1/A_v} = Z_2$$

 
# Miller Multiplication

- Applying Miller's theorem, we can convert a floating capacitance between the input and output nodes of an amplifier into two grounded capacitances.
- The capacitance at the input node is larger than the original floating capacitance.**






# Application of Miller's Theorem

 


$$\omega_{p,in} = \frac{1}{R_S (1 + g_m R_C) C_F} \Rightarrow \text{Dominant Pole since } \omega_{p,in} > \omega_{p,out}$$

$$\omega_{p,out} = \frac{1}{R_C \left( 1 + \frac{1}{g_m R_C} \right) C_F}$$

# Small-Signal Model for CE Stage

 

# ... Applying Miller's Theorem

 

$$V_{Thev} = V_{in} \frac{r_{\pi}}{r_{\pi} + R_S}$$

$$R_{Thev} = R_S \parallel r_{\pi}$$

$$C_X = C_{\mu} (1 + g_m R_C)$$

$$C_Y = C_{\mu} \left( 1 + \frac{1}{g_m R_C} \right)$$

$$\omega_{p,in} = \frac{1}{R_{Thev} \left( C_{in} + (1 + g_m R_C) C_{\mu} \right)}$$

$\Rightarrow$  Dominant pole

$$\omega_{p,out} = \frac{1}{R_C \left( C_{out} + \left( 1 + \frac{1}{g_m R_C} \right) C_{\mu} \right)}$$

# Direct Analysis of CE Stage


---

- Direct analysis yields slightly different pole locations and an extra zero:


$$\omega_z = \frac{g_m}{C_\mu}$$

$$\omega_{p1} = \frac{1}{(1 + g_m R_C) C_\mu R_{Thev} + R_{Thev} C_{in} + R_C (C_\mu + C_{out})}$$
$$\omega_{p2} = \frac{(1 + g_m R_C) C_\mu R_{Thev} + R_{Thev} C_{in} + R_C (C_\mu + C_{out})}{R_{Thev} R_C (C_{in} C_\mu + C_{out} C_\mu + C_{in} C_{out})}$$

# I/O Impedances of CE Stage

 
 
$$Z_{in} \approx \frac{1}{j\omega[C_\pi + (1 + g_m(R_C \parallel r_o))C_\mu]} \parallel r_\pi$$



$$Z_{out} = \frac{1}{j\omega[C_\mu + C_{CS}]} \parallel R_C \parallel r_o$$