

Lecture 13

OUTLINE

- Frequency Response
 - General considerations
 - High-frequency BJT model
 - Miller's Theorem
 - Frequency response of CE stage
- Reading: Chapter 11.1-11.3

EE105 Spring 2008

Lecture 13, Slide 1

Prof. Wu, UC Berkeley

Review: Sinusoidal Analysis

- Any voltage or current in a linear circuit with a sinusoidal source is a sinusoid of the same frequency (ω).
 - We only need to keep track of the amplitude and phase, when determining the response of a linear circuit to a sinusoidal source.
 - Any time-varying signal can be expressed as a sum of sinusoids of various frequencies (and phases).
- Applying the principle of superposition:
- The current or voltage response in a linear circuit due to a time-varying input signal can be calculated as the sum of the sinusoidal responses for each sinusoidal component of the input signal.


EE105 Spring 2008

Lecture 13, Slide 2

Prof. Wu, UC Berkeley

High Frequency "Roll-Off" in A_v

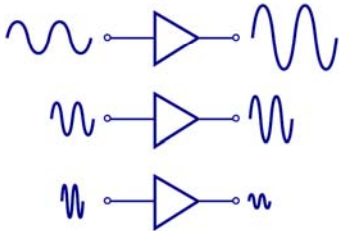- Typically, an amplifier is designed to work over a limited range of frequencies.
 - At "high" frequencies, the gain of an amplifier decreases.




EE105 Spring 2008

Lecture 13, Slide 3

Prof. Wu, UC Berkeley

A_v Roll-Off due to C_L

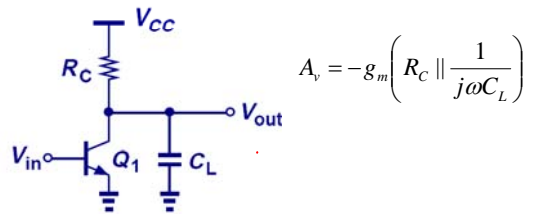- A capacitive load (C_L) causes the gain to decrease at high frequencies.
 - The impedance of C_L decreases at high frequencies, so that it shunts some of the output current to ground.




EE105 Spring 2008

Lecture 13, Slide 4

Prof. Wu, UC Berkeley

Frequency Response of the CE Stage

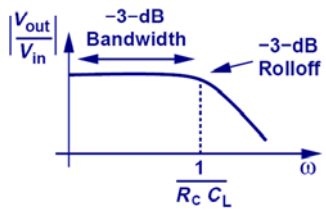- At low frequency, the capacitor is effectively an open circuit, and A_v vs. ω is flat. At high frequencies, the impedance of the capacitor decreases and hence the gain decreases. The "breakpoint" frequency is $1/(R_C C_L)$.



$$A_v = -g_m \frac{R_C \frac{1}{j\omega C_L}}{R_C + \frac{1}{j\omega C_L}}$$

$$= \frac{-g_m R_C}{1 + j\omega R_C C_L}$$

$$|A_v| = \frac{g_m R_C}{\sqrt{R_C^2 C_L^2 \omega^2 + 1}}$$


EE105 Spring 2008

Lecture 13, Slide 5

Prof. Wu, UC Berkeley

Amplifier Figure of Merit (FOM)

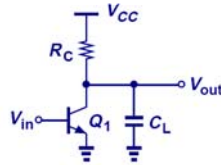- The gain-bandwidth product is commonly used to benchmark amplifiers.
 - We wish to maximize both the gain and the bandwidth.
- Power consumption is also an important attribute.
 - We wish to minimize the power consumption.



$$\frac{\text{Gain} \times \text{Bandwidth}}{\text{Power Consumption}} = \frac{(g_m R_C) \left(\frac{1}{R_C C_L} \right)}{I_C V_{CC}}$$

$$= \frac{1}{V_T V_{CC} C_L}$$

Operation at low T , low V_{CC} , and with small $C_L \rightarrow$ superior FOM

EE105 Spring 2008

Lecture 13, Slide 6

Prof. Wu, UC Berkeley

Bode Plot

- The transfer function of a circuit can be written in the general form

$$H(j\omega) = A_0 \frac{\left(1 + \frac{j\omega}{\omega_{z1}}\right) \left(1 + \frac{j\omega}{\omega_{z2}}\right) \dots}{\left(1 + \frac{j\omega}{\omega_{p1}}\right) \left(1 + \frac{j\omega}{\omega_{p2}}\right) \dots}$$

A_0 is the low-frequency gain
 ω_{zj} are "zero" frequencies
 ω_{pj} are "pole" frequencies

- Rules for generating a Bode magnitude vs. frequency plot:
 - As ω passes each **zero** frequency, the **slope of $|H(j\omega)|$** increases by 20dB/dec.
 - As ω passes each **pole** frequency, the **slope of $|H(j\omega)|$** decreases by 20dB/dec.


EE105 Spring 2008

Lecture 13, Slide 7

Prof. Wu, UC Berkeley

Bode Plot Example

- This circuit has only one pole at $\omega_{p1} = 1/(R_C C_L)$; the slope of $|A_v|$ decreases from 0 to -20dB/dec at ω_{p1} .

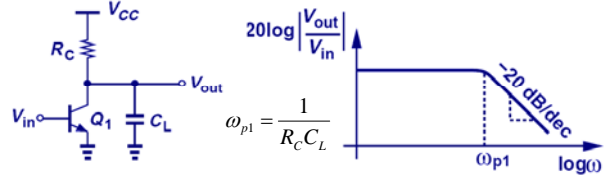


- In general, if **node j** in the signal path has a small-signal resistance of R_j to ground and a capacitance C_j to ground, then it contributes a **pole at frequency $(R_j C_j)^{-1}$** .

EE105 Spring 2008

Lecture 13, Slide 8

Prof. Wu, UC Berkeley

Pole Identification Example

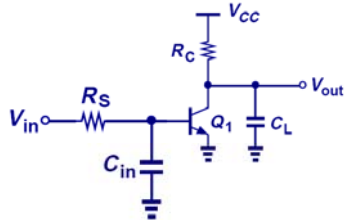

$$\omega_{p1} = \frac{1}{R_S C_{in}}$$

$$\omega_{p2} = \frac{1}{R_C C_L}$$

EE105 Spring 2008

Lecture 13, Slide 9


Prof. Wu, UC Berkeley

High-Frequency BJT Model

- The BJT inherently has junction capacitances which affect its performance at high frequencies.

Collector junction: depletion capacitance, C_{μ}

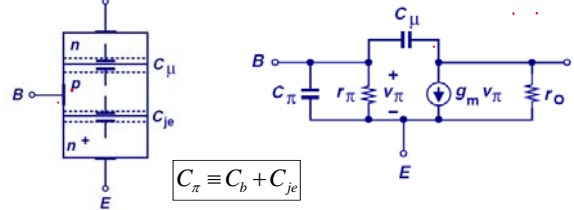Emitter junction: depletion capacitance, C_{je} , and also diffusion capacitance, C_b .



EE105 Spring 2008

Lecture 13, Slide 10


Prof. Wu, UC Berkeley

BJT High-Frequency Model (cont'd)

- In an integrated circuit, the BJTs are fabricated in the surface region of a Si wafer substrate; another junction exists between the collector and substrate, resulting in substrate junction capacitance, C_{CS} .

BJT cross-section

BJT small-signal model

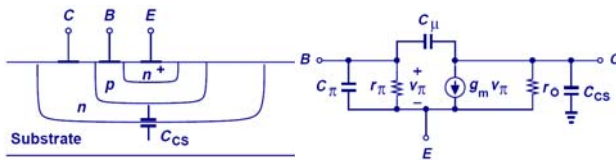


EE105 Spring 2008

Lecture 13, Slide 11

Prof. Wu, UC Berkeley

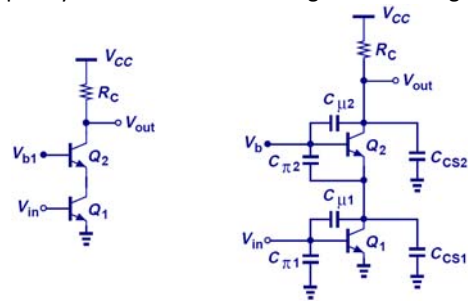Example: BJT Capacitances

- The various junction capacitances within each BJT are explicitly shown in the circuit diagram on the right.



EE105 Spring 2008


Lecture 13, Slide 12

Prof. Wu, UC Berkeley

Transit Frequency, f_T

- The "transit" or "cut-off" frequency, f_T , is a measure of the intrinsic speed of a transistor, and is defined as the frequency where the current gain falls to 1.

Conceptual set-up to measure f_T

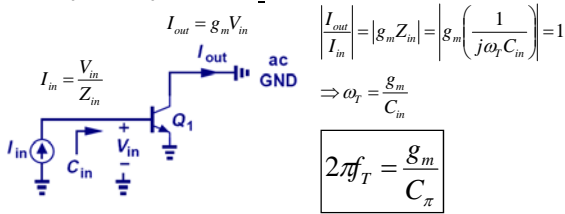


EE105 Spring 2008

Lecture 13, Slide 13

Prof. Wu, UC Berkeley

Dealing with a Floating Capacitance

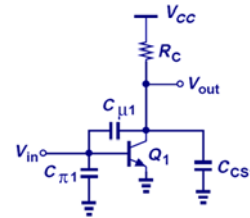- Recall that a pole is computed by finding the resistance and capacitance between a node and GROUND.
- It is not straightforward to compute the pole due to $C_{\mu 1}$ in the circuit below, because neither of its terminals is grounded.




EE105 Spring 2008

Lecture 13, Slide 14

Prof. Wu, UC Berkeley

Miller's Theorem

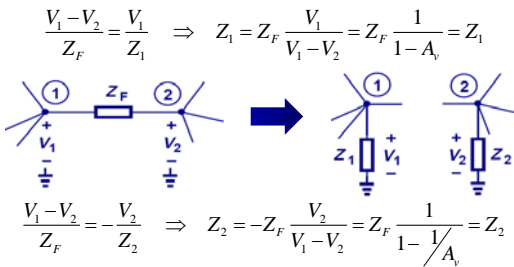- If A_v is the voltage gain from node 1 to 2, then a floating impedance Z_F can be converted to two grounded impedances Z_1 and Z_2 :




EE105 Spring 2008

Lecture 13, Slide 15

Prof. Wu, UC Berkeley

Miller Multiplication

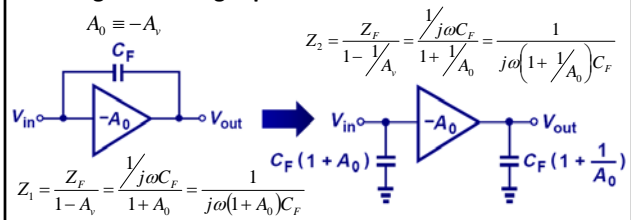- Applying Miller's theorem, we can convert a floating capacitance between the input and output nodes of an amplifier into two grounded capacitances.
- The capacitance at the input node is larger than the original floating capacitance.




EE105 Spring 2008

Lecture 13, Slide 16

Prof. Wu, UC Berkeley

Application of Miller's Theorem

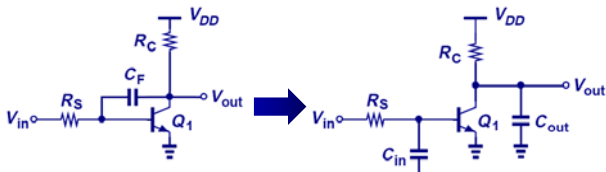

$$\omega_{p,in} = \frac{1}{R_S (1 + g_m R_C) C_F} \Rightarrow \text{Dominant Pole since } \omega_{p,in} > \omega_{p,out}$$


$$\omega_{p,out} = \frac{1}{R_C \left(1 + \frac{1}{g_m R_C}\right) C_F}$$

EE105 Spring 2008

Lecture 13, Slide 17

Prof. Wu, UC Berkeley

Small-Signal Model for CE Stage

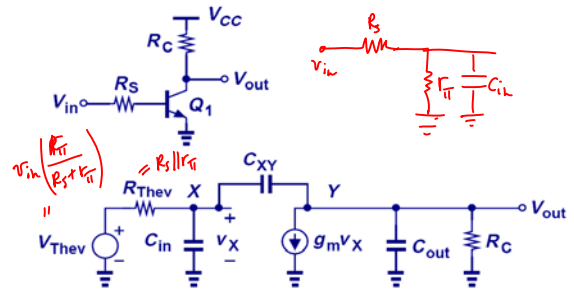


EE105 Spring 2008

Lecture 13, Slide 18

Prof. Wu, UC Berkeley

... Applying Miller's Theorem

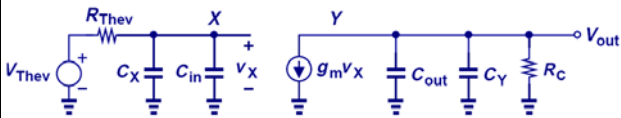

$$V_{Thev} = V_{in} \frac{r_{\pi}}{r_{\pi} + R_S}$$

$$R_{Thev} = R_S \parallel r_{\pi}$$

$$C_X = C_{\mu} (1 + g_m R_C)$$

$$C_Y = C_{\mu} \left(1 + \frac{1}{g_m R_C}\right)$$

$$\omega_{p,in} = \frac{1}{R_{Thev} (C_{in} + (1 + g_m R_C) C_{\mu})}$$

\Rightarrow Dominant pole

$$\omega_{p,out} = \frac{1}{R_C \left(C_{out} + \left(1 + \frac{1}{g_m R_C}\right) C_{\mu}\right)}$$

EE105 Spring 2008

Lecture 13, Slide 19

Prof. Wu, UC Berkeley

Direct Analysis of CE Stage

- Direct analysis yields slightly different pole locations and an extra zero:

$$\omega_z = \frac{g_m}{C_{\mu}}$$

$$\omega_{p1} = \frac{1}{(1 + g_m R_C) C_{\mu} R_{Thev} + R_{Thev} C_{in} + R_C (C_{\mu} + C_{out})}$$


$$\omega_{p2} = \frac{(1 + g_m R_C) C_{\mu} R_{Thev} + R_{Thev} C_{in} + R_C (C_{\mu} + C_{out})}{R_{Thev} R_C (C_{in} C_{\mu} + C_{out} C_{\mu} + C_{in} C_{out})}$$

EE105 Spring 2008

Lecture 13, Slide 20

Prof. Wu, UC Berkeley

I/O Impedances of CE Stage

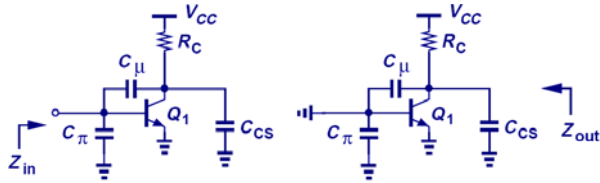

$$Z_{in} \approx \frac{1}{j\omega[C_{\pi} + (1 + g_m(R_C \parallel r_o))C_{\mu}]} \parallel r_{\pi}$$

$$Z_{out} = \frac{1}{j\omega[C_{\mu} + C_{CS}]} \parallel R_C \parallel r_o$$