

Lecture 14

OUTLINE

- Frequency Response (cont'd)
 - CB stage
 - Emitter follower
 - Cascode stage

Reading: Chapter 11.4-11.6

EE105 Spring 2008


Lecture 14, Slide 1

Prof. Wu, UC Berkeley

CB Stage: Pole Frequencies

- Note that there is no capacitance between input & output nodes
→ No Miller multiplication effect!

CB stage with BJT capacitances shown

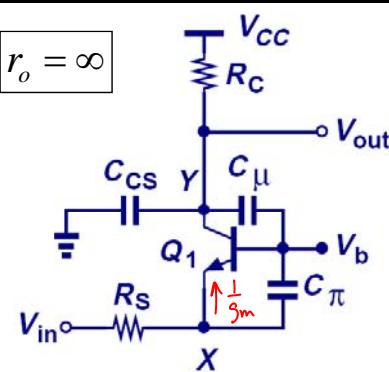

$$\omega_{p,Y} = \frac{1}{R_c C_Y}$$

$$C_Y = C_\mu + C_{CS}$$

$$\omega_{p,X} = \frac{1}{\left(R_s \parallel \frac{1}{g_m} \right) C_X} > \omega_T$$

$$C_X = C_\pi$$

EE105 Spring 2008

Lecture 14, Slide 2


Prof. Wu, UC Berkeley

Emitter Follower


- Recall that the emitter follower provides high input impedance and low output impedance, and is used as a voltage buffer.

Follower stage with BJT capacitances shown

• C_L is the load capacitance

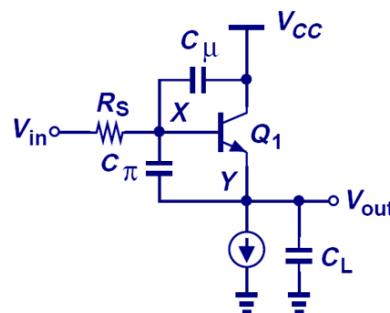

Circuit for small-signal analysis (A_v)

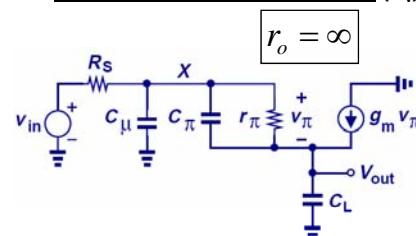

EE105 Spring 2008

Lecture 14, Slide 3


Prof. Wu, UC Berkeley

AC Analysis of Emitter Follower

$$v_X = v_{out} + v_\pi$$

- KCL at node X:
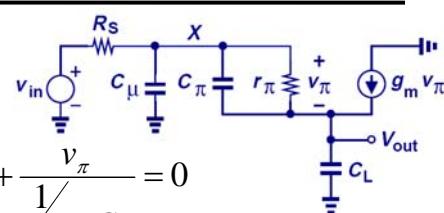
$$\frac{v_{out} + v_\pi - v_{in}}{R_S} + \frac{v_{out} + v_\pi}{1/j\omega C_\mu} + \frac{v_\pi}{r_\pi} + \frac{v_\pi}{1/j\omega C_\pi} = 0$$



- KCL at output node: $\frac{v_\pi}{r_\pi} + \frac{v_\pi}{1/j\omega C_\pi} + g_m v_\pi = \frac{v_{out}}{1/j\omega C_L}$

$$\Rightarrow \frac{v_{out}}{v_{in}} \cong \frac{1 + \frac{C_\pi(j\omega)}{g_m}}{a(j\omega)^2 + b(j\omega) + 1} \quad a = \frac{R_S}{g_m} (C_\mu C_\pi + C_\mu C_L + C_\pi C_L) \\ b = R_S C_\mu + \frac{C_\pi}{g_m} + \left(1 + \frac{R_S}{r_\pi}\right) \frac{C_L}{g_m}$$

EE105 Spring 2008

Lecture 14, Slide 4

Prof. Wu, UC Berkeley

Follower: Zero and Pole Frequencies

$$\frac{v_{out}}{v_{in}} \cong \frac{1 + \frac{C_\pi}{g_m}(j\omega)}{a(j\omega)^2 + b(j\omega) + 1}$$

$$a = \frac{R_S}{g_m} (C_\mu C_\pi + C_\mu C_L + C_\pi C_L)$$

$$b = R_S C_\mu + \frac{C_\pi}{g_m} + \left(1 + \frac{R_S}{r_\pi}\right) \frac{C_L}{g_m}$$

- The follower has one zero:

$$\omega_z = \frac{g_m}{C_\pi} = 2\pi f_T$$

- The follower has two poles at lower frequencies:

$$a(j\omega)^2 + b(j\omega) + 1 = \left(1 + \frac{j\omega}{\omega_{p1}}\right) \left(1 + \frac{j\omega}{\omega_{p2}}\right) = 1 + \left(\frac{1}{\omega_{p1}} + \frac{1}{\omega_{p2}}\right)(j\omega) + \left(\frac{1}{\omega_{p1}\omega_{p2}}\right)(j\omega)^2$$

$$a = \frac{1}{\omega_{p1}\omega_{p2}} ; \quad b = \frac{1}{\omega_{p1}} + \frac{1}{\omega_{p2}}$$


EE105 Spring 2008

Lecture 14, Slide 5

Prof. Wu, UC Berkeley

Emitter Follower: Input Capacitance

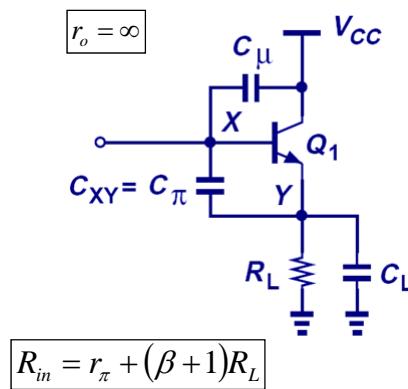- Recall that the voltage gain of an emitter follower is $A_v = \frac{R_L}{R_L + \frac{1}{g_m}}$
- Follower stage with BJT capacitances shown



- C_{XY} can be decomposed into C_X and C_Y at the input and output nodes, respectively:

$$C_X = (1 - A_v)C_\pi = \frac{C_\pi}{1 + g_m R_L}$$

$$C_Y = \left(1 - \frac{1}{A_v}\right)C_\pi = \frac{-C_\pi}{g_m R_L}$$

$$C_{in} = C_\mu + \frac{C_\pi}{1 + g_m R_L}$$


EE105 Spring 2008

Lecture 14, Slide 6


Prof. Wu, UC Berkeley

Emitter Follower: Output Impedance

$$r_o = \infty$$

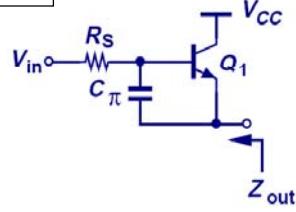

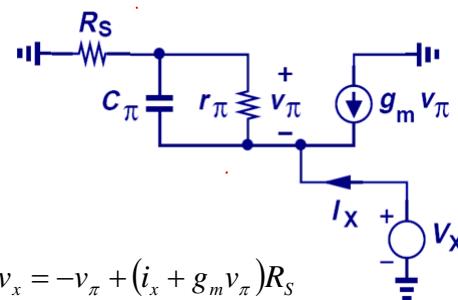Circuit for small-signal analysis (R_{out})



$$v_\pi = -(i_x + g_m v_\pi) \left(r_\pi \parallel \frac{1}{j\omega C_\pi} \right)$$

$$v_x = -v_\pi + (i_x + g_m v_\pi) R_s$$

$$Z_{out} \equiv \frac{v_x}{i_x} = \frac{R_s r_\pi C_\pi (j\omega) + r_\pi + R_s}{r_\pi C_\pi (j\omega) + \beta + 1} = \frac{r_\pi + R_s}{\beta + 1} \cdot \frac{1 + \frac{j\omega}{(r_\pi + R_s)/R_s r_\pi C_\pi}}{1 + \frac{j\omega}{(\beta + 1)/r_\pi C_\pi}} = \begin{cases} \frac{r_\pi + R_s}{1 + \beta} & \text{for low } \omega \\ R_s & \text{for high } \omega \end{cases}$$

EE105 Spring 2008

Lecture 14, Slide 7

Prof. Wu, UC Berkeley


Emitter Follower as Active Inductor

$$Z_{out} \equiv \frac{v_x}{i_x} = \frac{R_s r_\pi C_\pi (j\omega) + r_\pi + R_s}{r_\pi C_\pi (j\omega) + \beta + 1} = \left(\frac{r_\pi + R_s}{\beta + 1} \right) \cdot \frac{\frac{1 + \frac{j\omega}{(r_\pi + R_s)/R_s r_\pi C_\pi}}{1 + \frac{j\omega}{(\beta + 1)/r_\pi C_\pi}}}{\frac{1 + \frac{j\omega}{(r_\pi + R_s)/R_s r_\pi C_\pi}}{1 + \frac{j\omega}{(\beta + 1)/r_\pi C_\pi}}}$$


CASE 1: $R_s < 1/g_m$

$$\left(\frac{1}{g_m} + \frac{R_s}{\beta + 1} \right)$$

CASE 2: $R_s > 1/g_m$

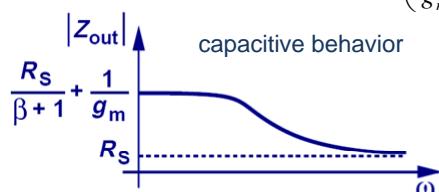

capacitive behavior

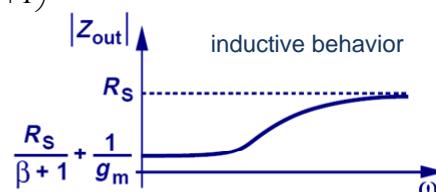

inductive behavior

- A follower is typically used to lower the driving impedance
→ $R_s > 1/g_m$ so that the “active inductor” characteristic on the right is usually observed.


EE105 Spring 2008

Lecture 14, Slide 8

Prof. Wu, UC Berkeley

Cascode Stage

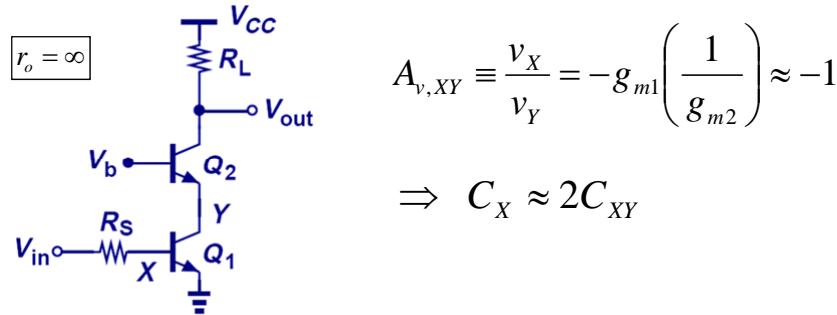- Review:
 - A CE stage has large R_{in} but suffers from the Miller effect.
 - A CB stage is free from the Miller effect, but has small R_{in} .
- **A cascode stage provides high R_{in} with minimal Miller effect.**



EE105 Spring 2008


Lecture 14, Slide 9

Prof. Wu, UC Berkeley

Cascode Stage: Pole Frequencies

Cascode stage with BJT capacitances shown

(Miller approximation applied)

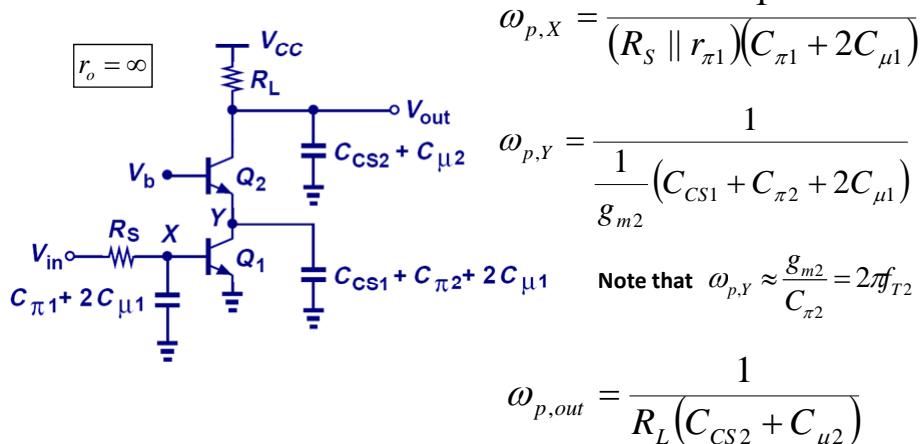


EE105 Spring 2008

Lecture 14, Slide 10

Prof. Wu, UC Berkeley

Cascode Stage: I/O Impedances

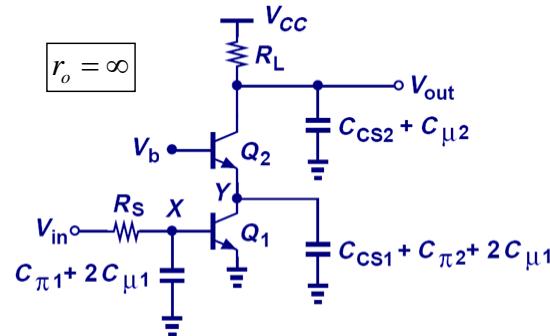

$$Z_{in} = r_{\pi 1} \parallel \frac{1}{j\omega(C_{\pi 1} + 2C_{\mu 1})}$$

$$Z_{out} = R_L \parallel \frac{1}{j\omega(C_{\mu 2} + C_{CS2})}$$

EE105 Spring 2008

Lecture 14, Slide 11

Prof. Wu, UC Berkeley

Summary of Cascode Stage Benefits

- A cascode stage has high output impedance, which is advantageous for
 - achieving high voltage gain
 - use as a current source
- In a cascode stage, the Miller effect is reduced, for improved performance at high frequencies.

EE105 Spring 2008

Lecture 14, Slide 12

Prof. Wu, UC Berkeley