

# Lecture 22



---

## OUTLINE

- Differential Amplifiers
  - General considerations
  - BJT differential pair
    - Qualitative analysis
    - Large-signal analysis
    - Small-signal analysis
    - Frequency response
- Reading: Chapter 10.1-10.2

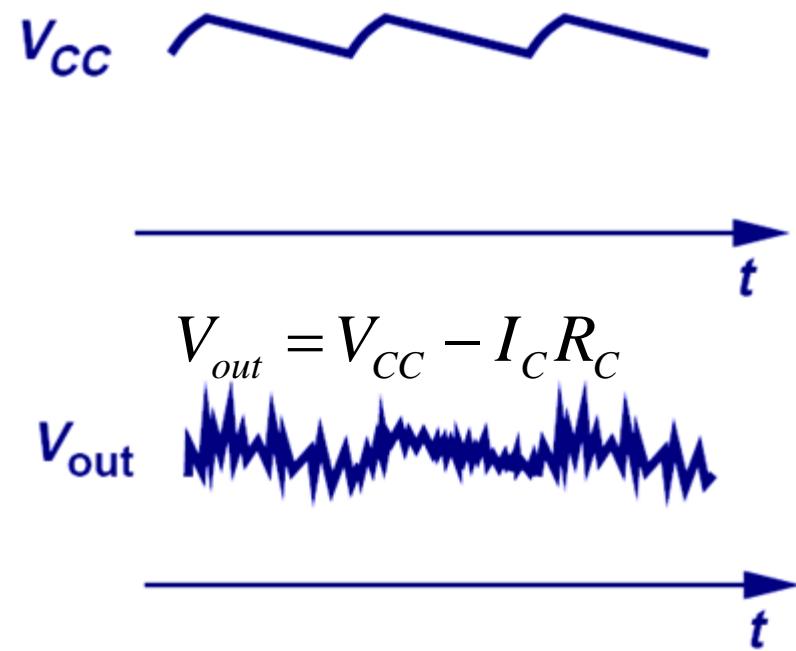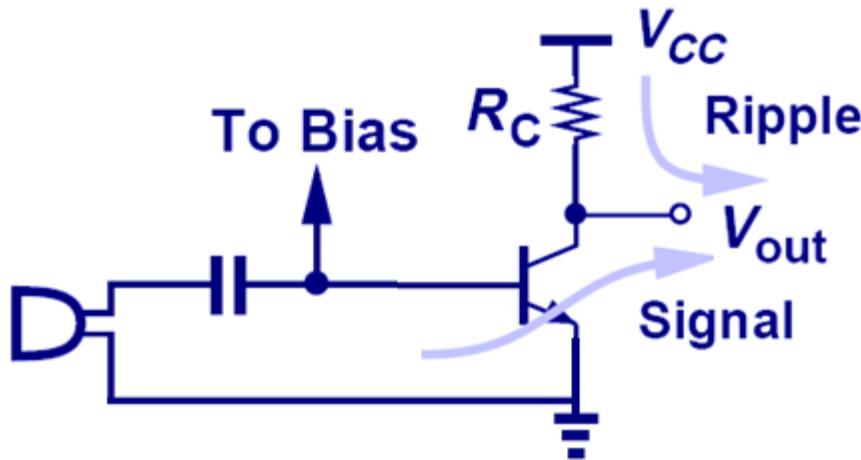
# “Humming” Noise in Audio Amplifier

- Consider the amplifier below which amplifies an audio signal from a microphone.
- If the power supply ( $V_{CC}$ ) is time-varying, it will result in an additional (undesirable) voltage signal at the output, perceived as a “humming” noise by the user.


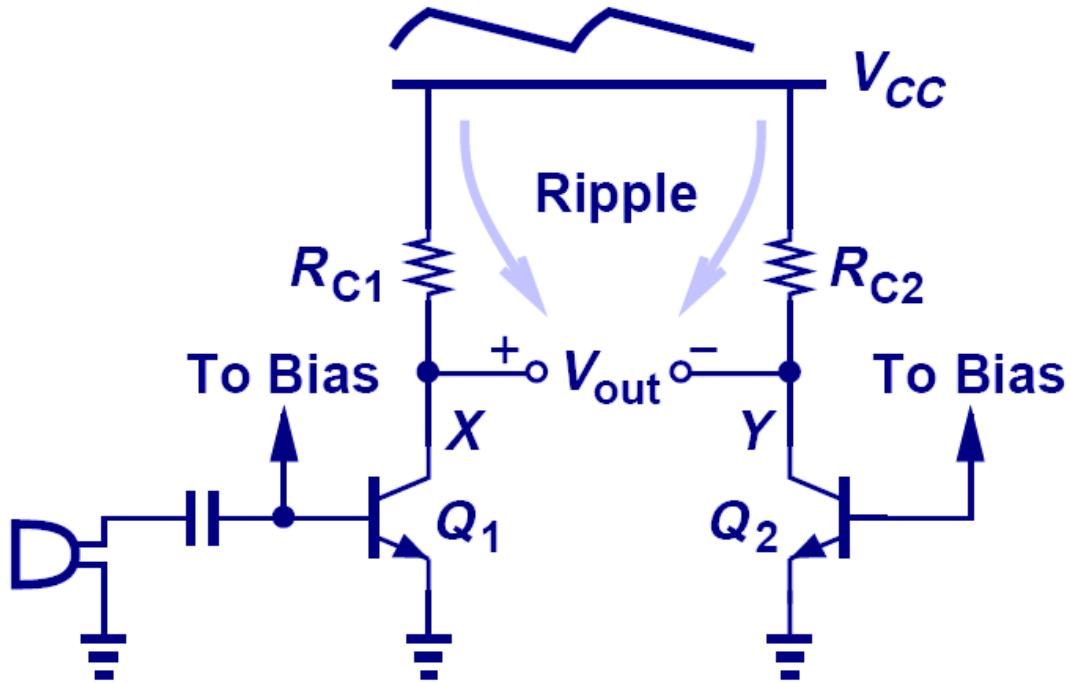
# Supply Ripple Rejection

- Since node X and Y each see the voltage ripple, their voltage difference will be free of ripple.




$$v_X = A_v v_{in} + v_r$$

$$v_Y = v_r$$

$$v_X - v_Y = A_v v_{in}$$

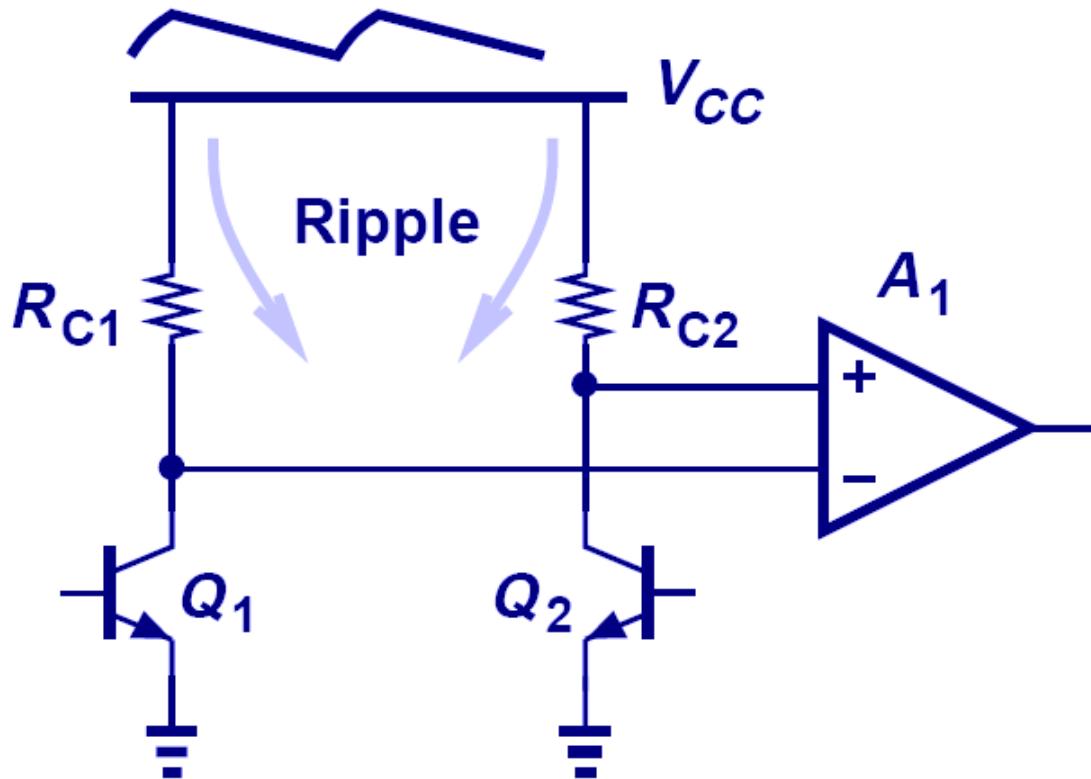
# Ripple-Free Differential Output

- If the input signal is to be a voltage difference between two nodes, an amplifier that senses a *differential signal* is needed.


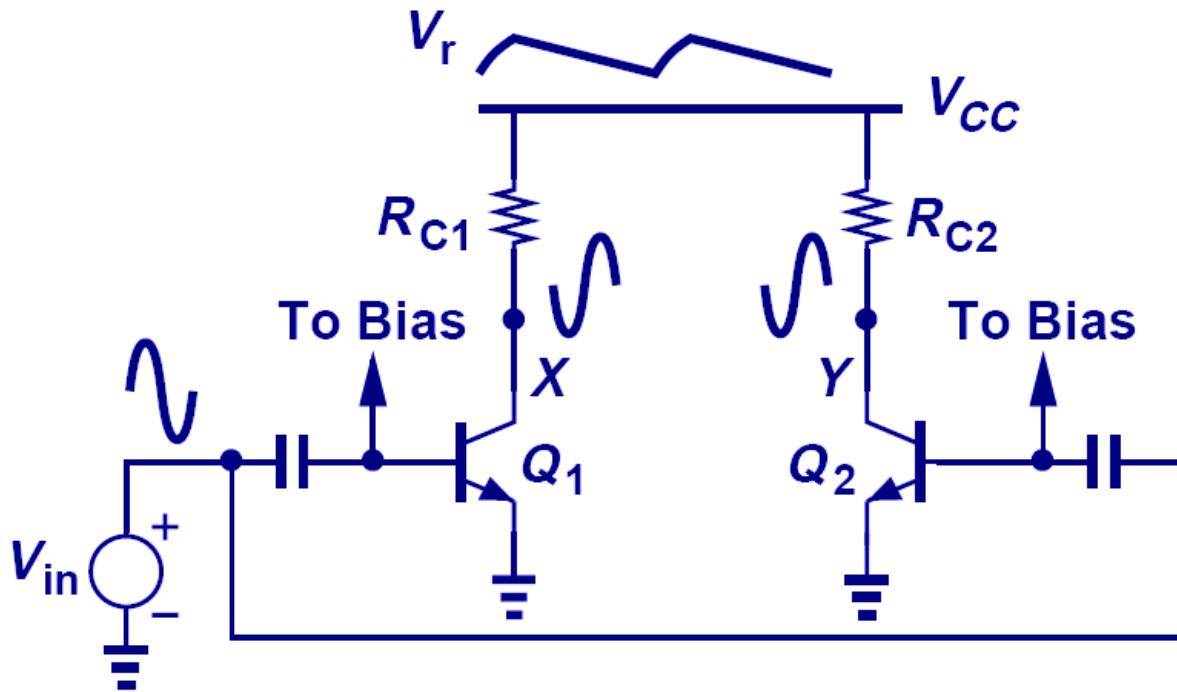
# Common Inputs to Differential Amp.

- The voltage signals applied to the input nodes of a differential amplifier cannot be in phase; otherwise, the differential output signal will be zero.




$$v_X = A_v v_{in} + v_r$$

$$v_Y = A_v v_{in} + v_r$$

$$v_X - v_Y = 0$$
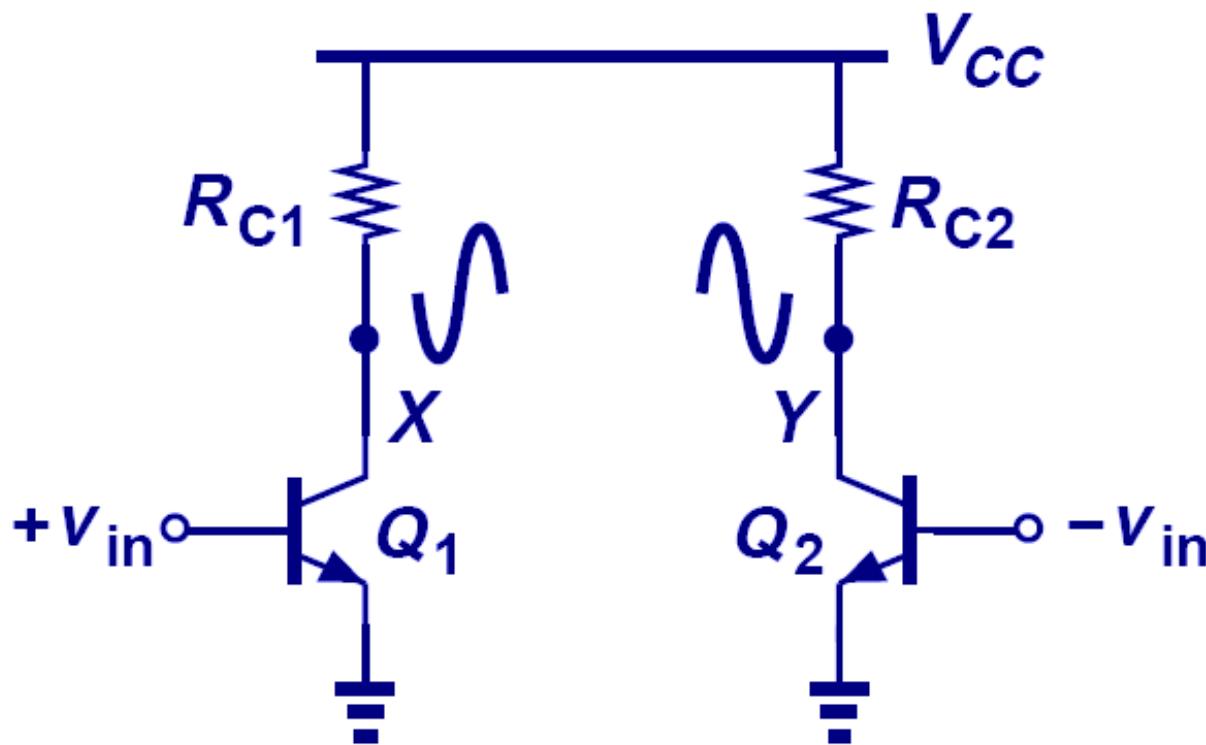
# Differential Inputs to Differential Amp.

- When the input voltage signals are  $180^\circ$  out of phase, the resultant output node voltages are  $180^\circ$  out of phase, so that their difference is enhanced.





$$v_X = A_v v_{in} + v_r$$

$$v_Y = -A_v v_{in} + v_r$$


$$v_X - v_Y = 2A_v v_{in}$$
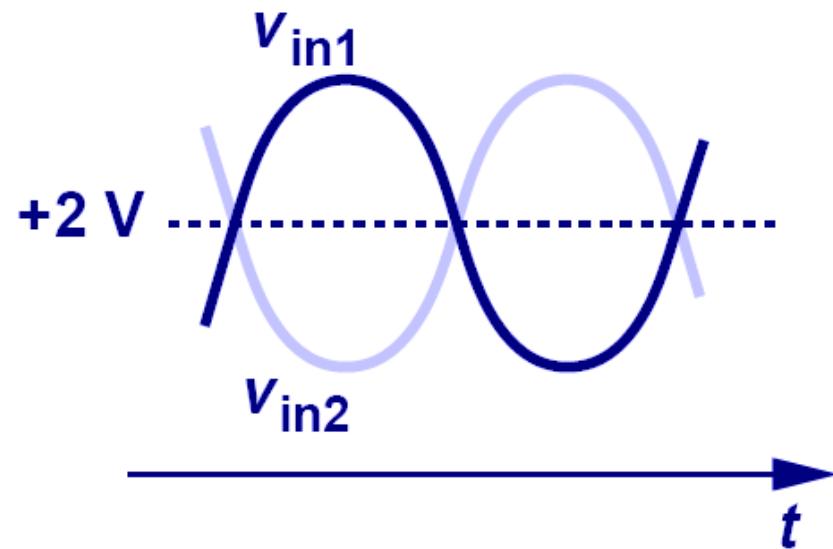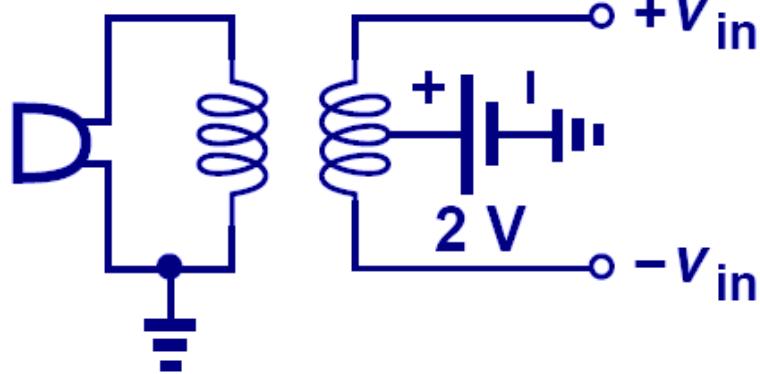
# Differential Signals


- Differential signals share the same average DC value and are equal in magnitude but opposite in phase.
- A pair of differential signals can be generated, among other ways, by a transformer.



# Single-Ended vs. Differential Signals

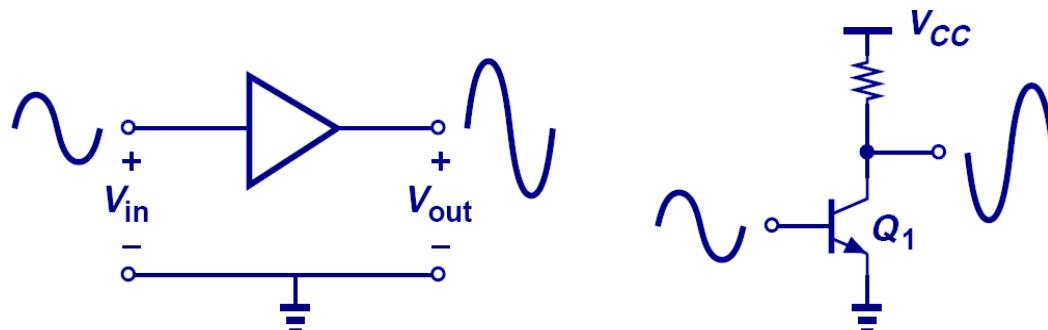


(a)

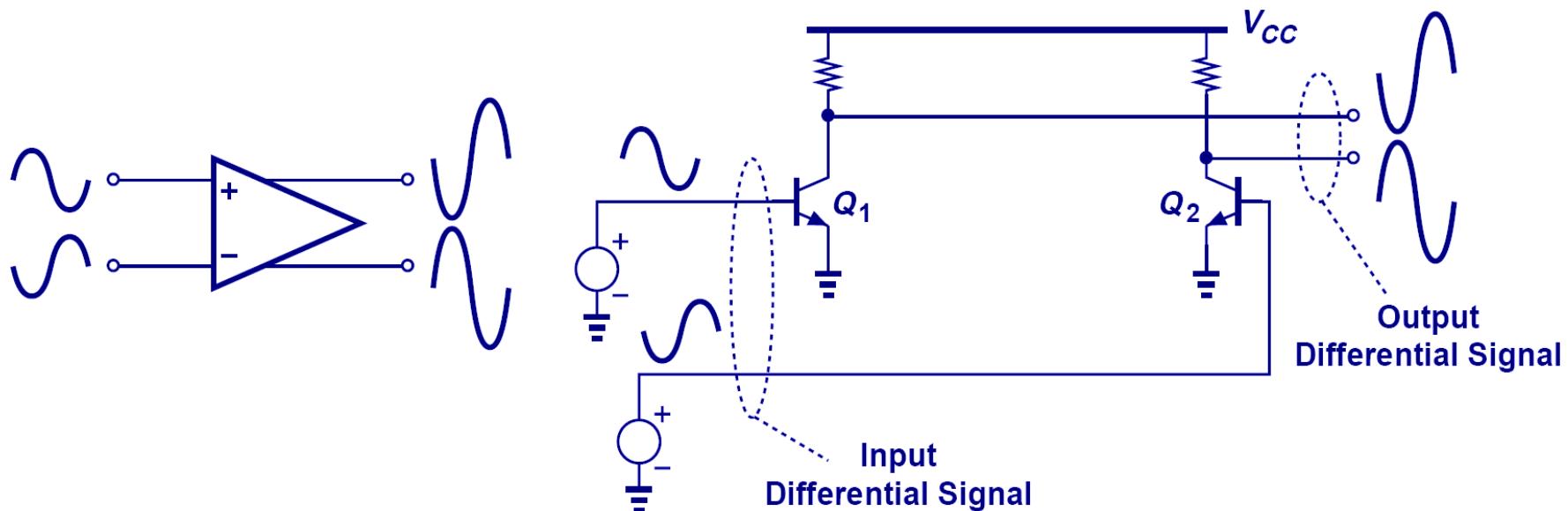


(b)

# Differential Pair

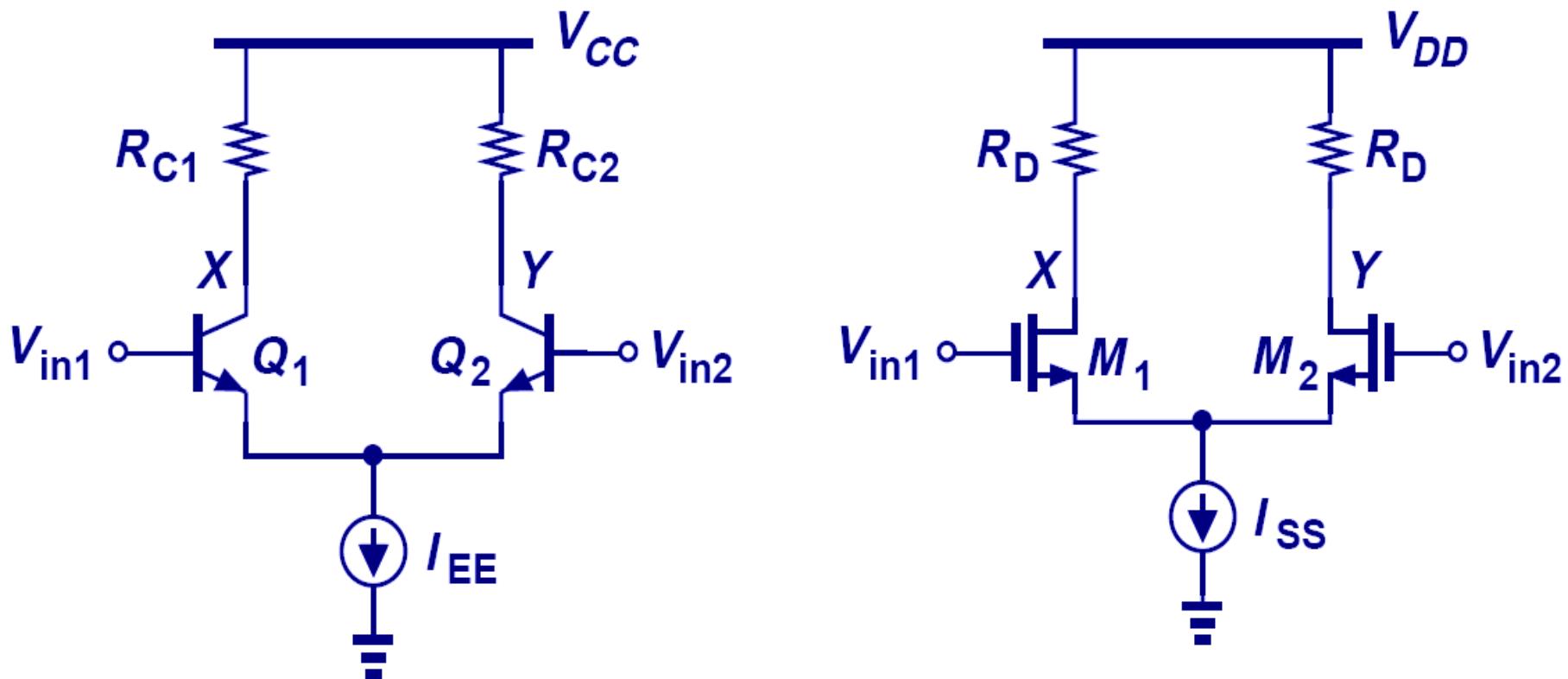

- With the addition of a tail current, the circuits above operate as an elegant, yet robust differential pair.

# Common-Mode Response

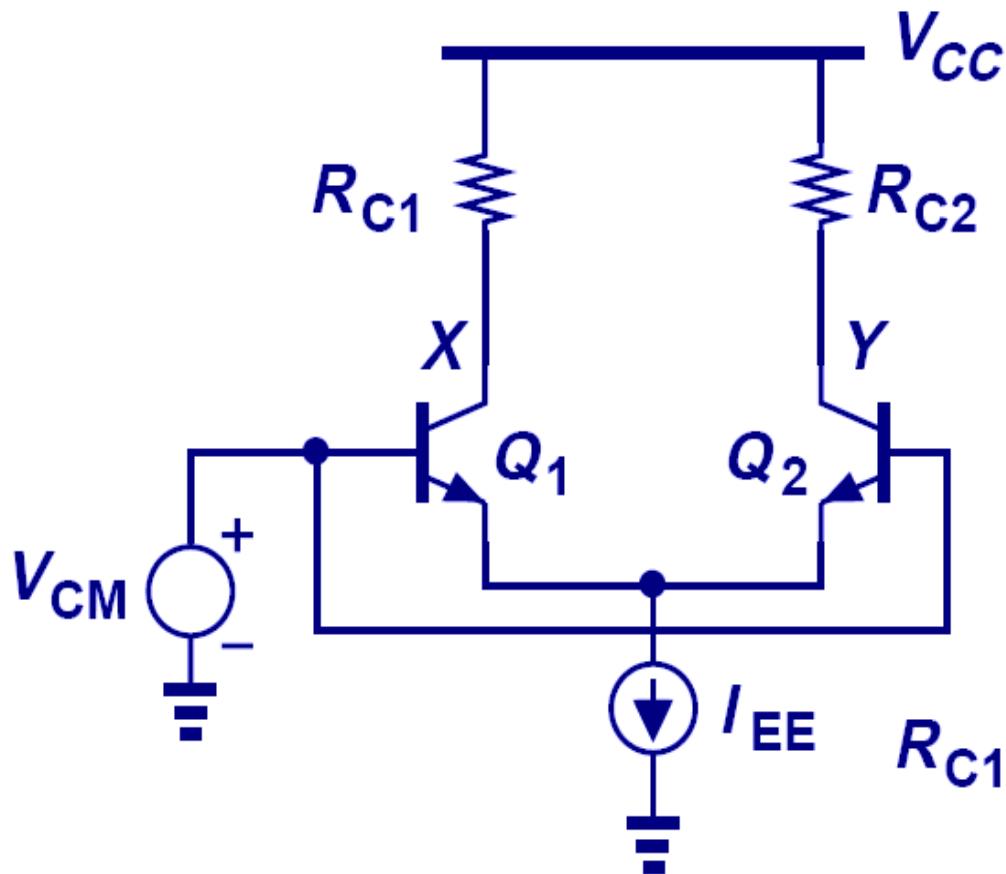


$$V_{BE1} = V_{BE2}$$

$$I_{C1} = I_{C2} = \frac{I_{EE}}{2}$$

$$V_X = V_Y = V_{CC} - R_C \frac{I_{EE}}{2}$$

$$R_{C1} = R_{C2} = R_C$$

# Differential Response

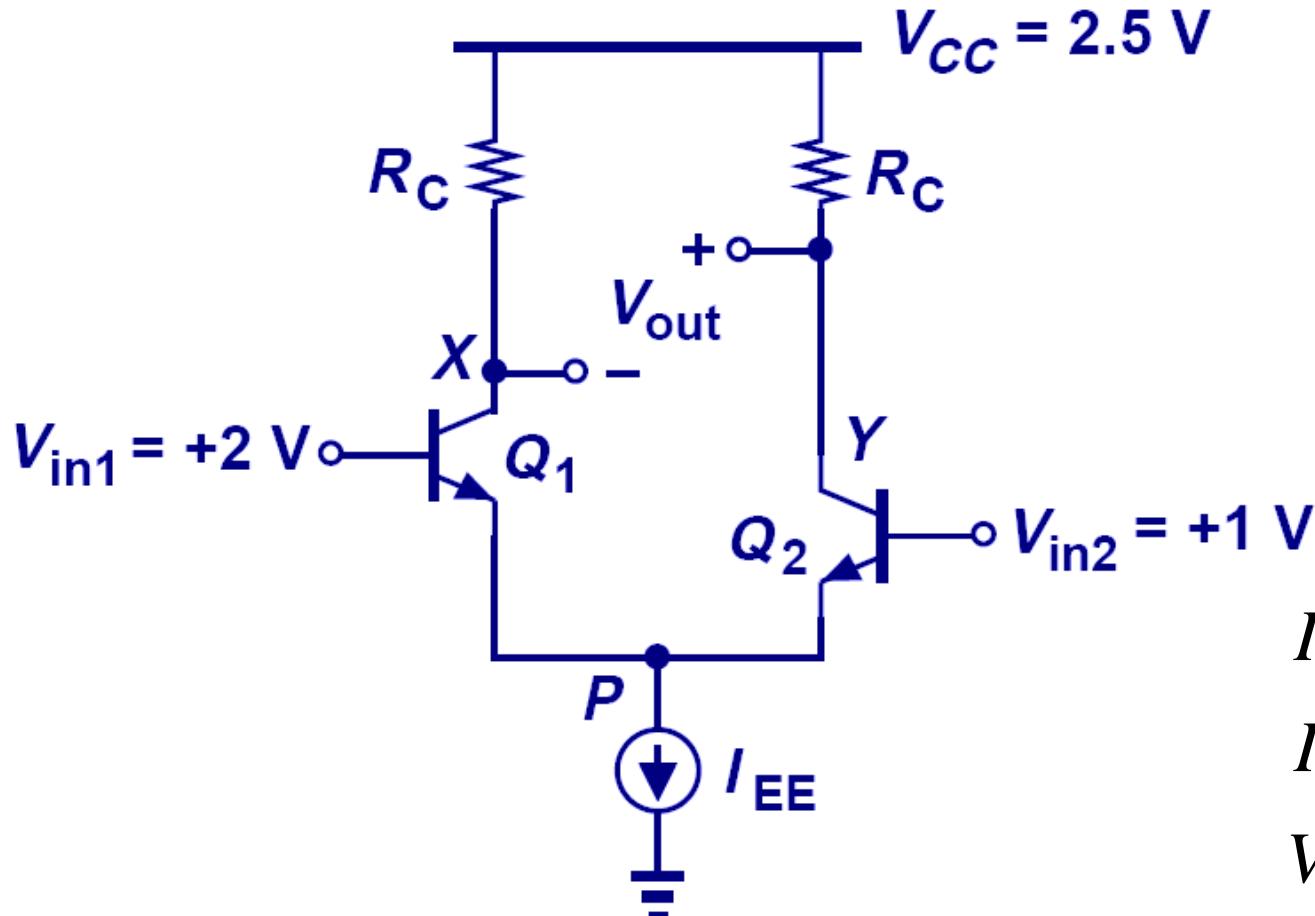


$$I_{C1} = I_{EE}$$

$$I_{C2} = 0$$

$$V_X = V_{CC} - R_C I_{EE}$$

$$V_Y = V_{CC}$$

# Differential Response (cont'd)

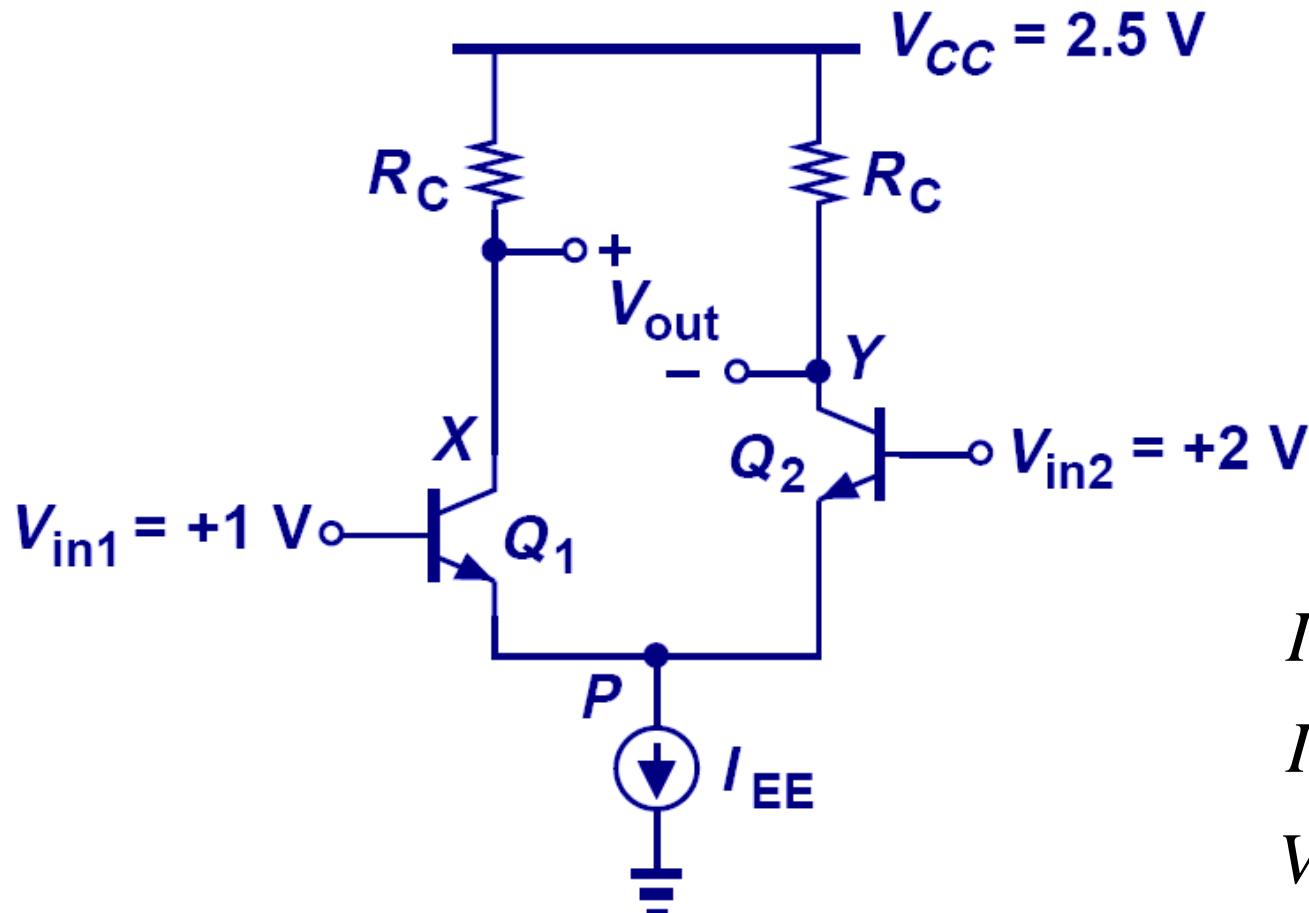

$$I_{C2} = I_{EE}$$


$$I_{C1} = 0$$

$$V_Y = V_{CC} - R_C I_{EE}$$

$$V_X = V_{CC}$$

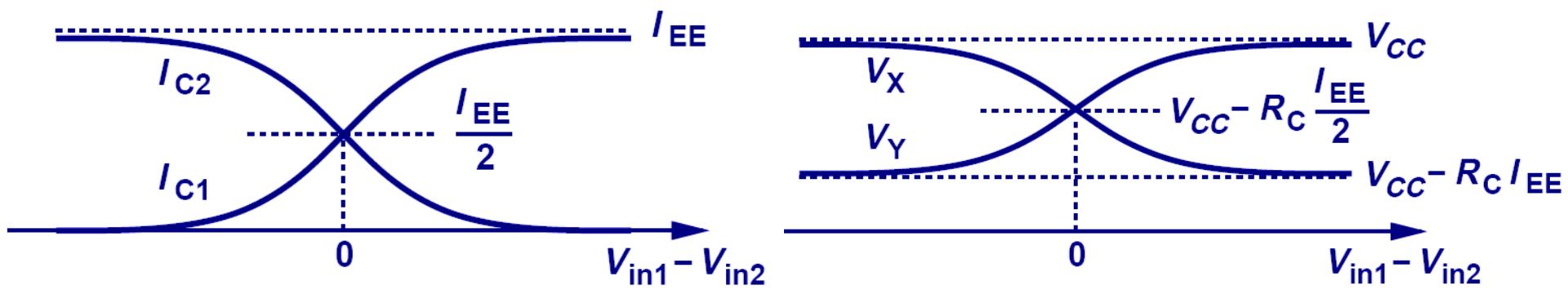
# Differential Pair Characteristics

- A differential input signal results in variations in the output currents and voltages, whereas a common-mode input signal does not result in any output current/voltage variations.


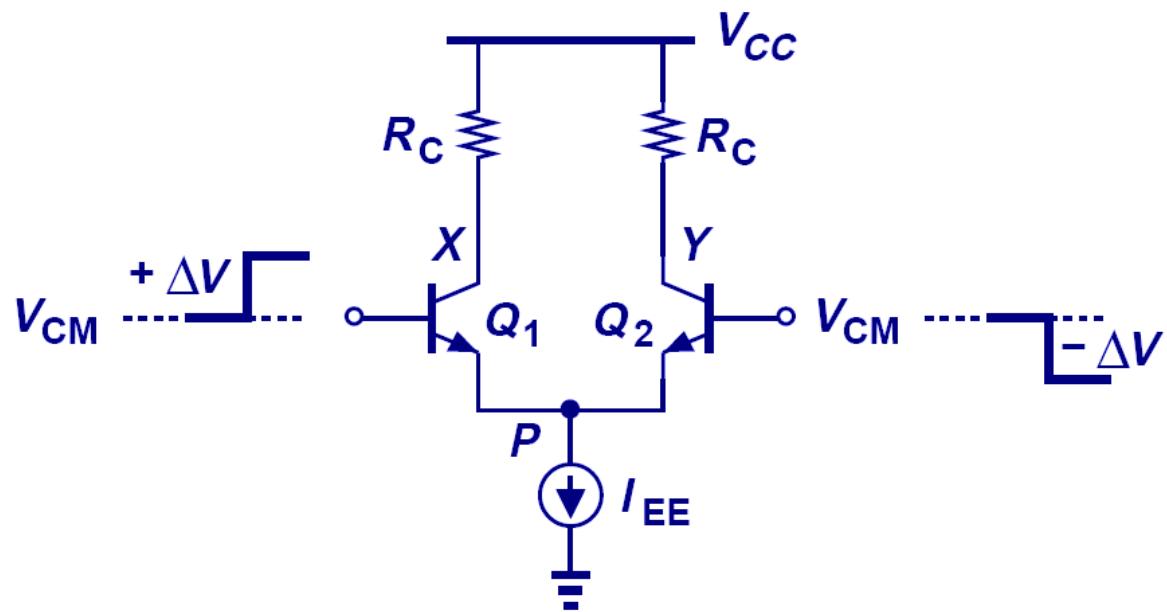
# Virtual Ground

- For small input voltages ( $+\Delta V$  and  $-\Delta V$ ), the  $g_m$  values are  $\sim$ equal, so the increase in  $I_{C1}$  and decrease in  $I_{C2}$  are  $\sim$ equal in magnitude. Thus, the voltage at node P is constant and can be considered as AC ground.



$$I_{C1} = \frac{I_{EE}}{2} + \Delta I$$

$$I_{C2} = \frac{I_{EE}}{2} - \Delta I$$

$$\Delta I_{C1} = g_m (\Delta V - \Delta V_P)$$


$$\Delta I_{C2} = g_m (-\Delta V - \Delta V_P)$$

$$\Delta I_{C1} = -\Delta I_{C2}$$

$$\Rightarrow \Delta V_P = 0$$

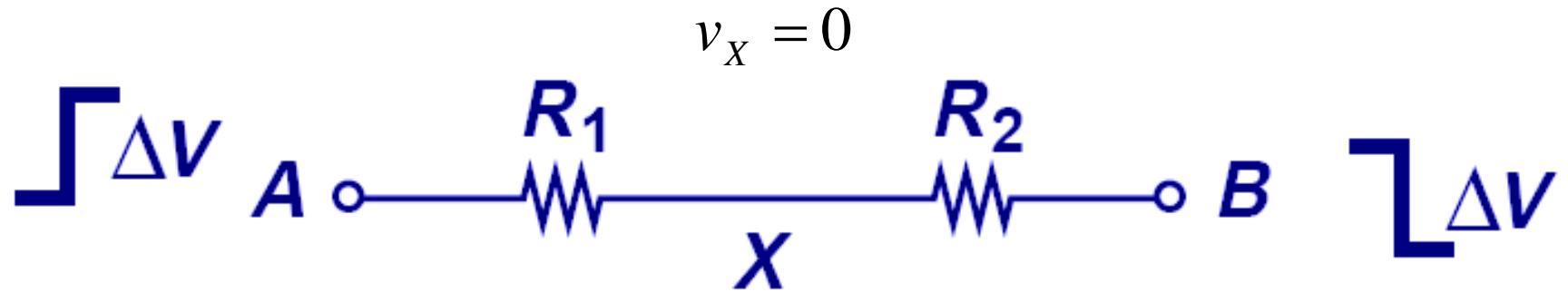
# Extension of Virtual Ground

- It can be shown that if  $R_1 = R_2$ , and the voltage at node A goes up by the same amount that the voltage at node B goes down, then the voltage at node X does not change.



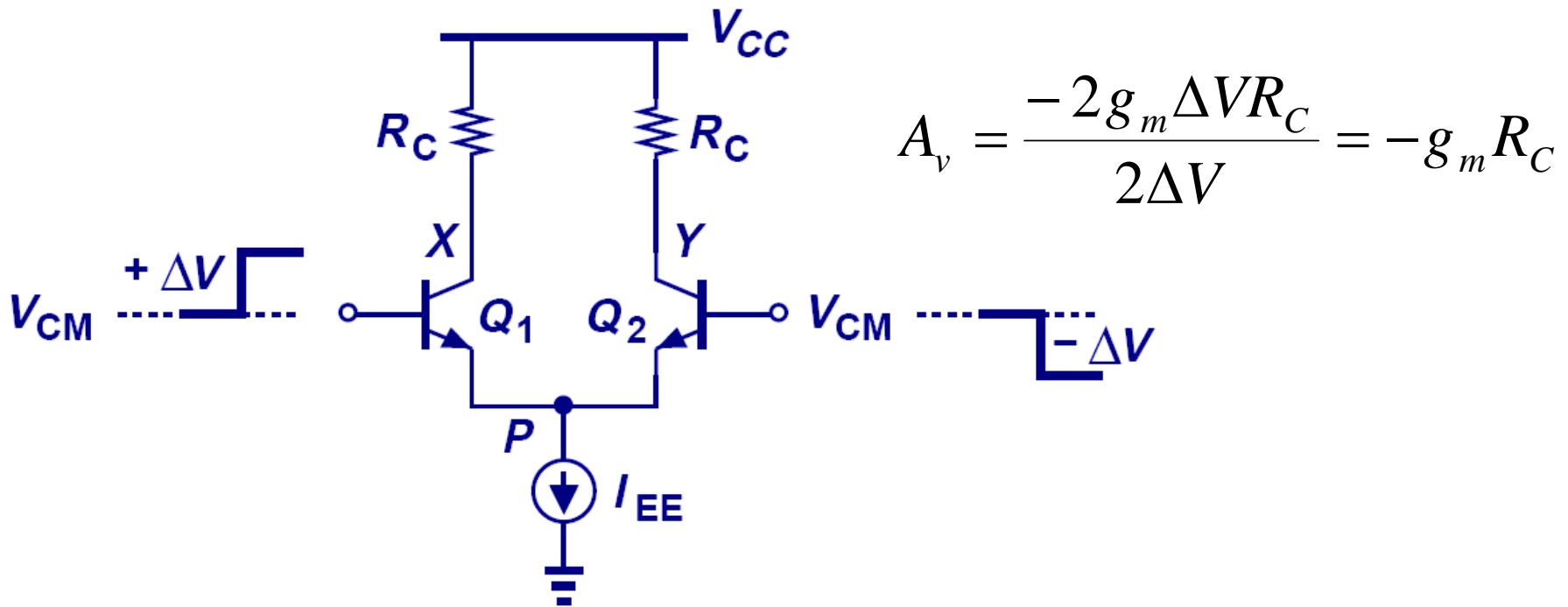
# Small-Signal Differential Gain

- Since the output signal changes by  $-2g_m\Delta VR_C$  when the input signal changes by  $2\Delta V$ , the small-signal voltage gain is  $-g_m R_C$ .
- Note that the voltage gain is the same as for a CE stage, but that the power dissipation is doubled.




# Large-Signal Analysis

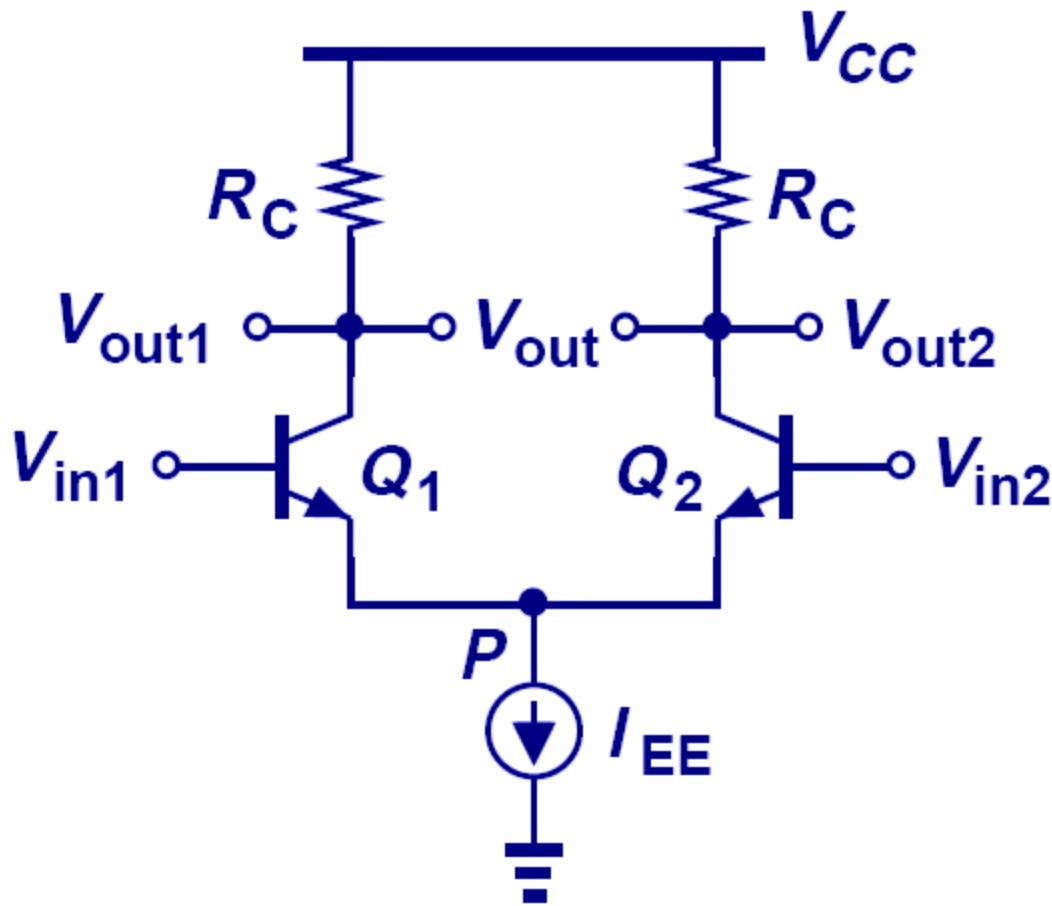

$$\begin{aligned}V_{in1} - V_{in2} &= V_{BE1} - V_{BE2} \\&= V_T \ln\left(\frac{I_{C1}}{I_S}\right) - V_T \ln\left(\frac{I_{C2}}{I_S}\right) \\&= V_T \ln\left(\frac{I_{C1}}{I_{C2}}\right) \\I_{C1} + I_{C2} &= I_{EE} \\I_{C1} &= \frac{I_{EE} e^{\frac{V_{in1}-V_{in2}}{V_T}}}{1 + e^{\frac{V_{in1}-V_{in2}}{V_T}}} \\I_{C2} &= \frac{I_{EE}}{1 + e^{\frac{V_{in1}-V_{in2}}{V_T}}}\end{aligned}$$


# Input/Output Characteristics

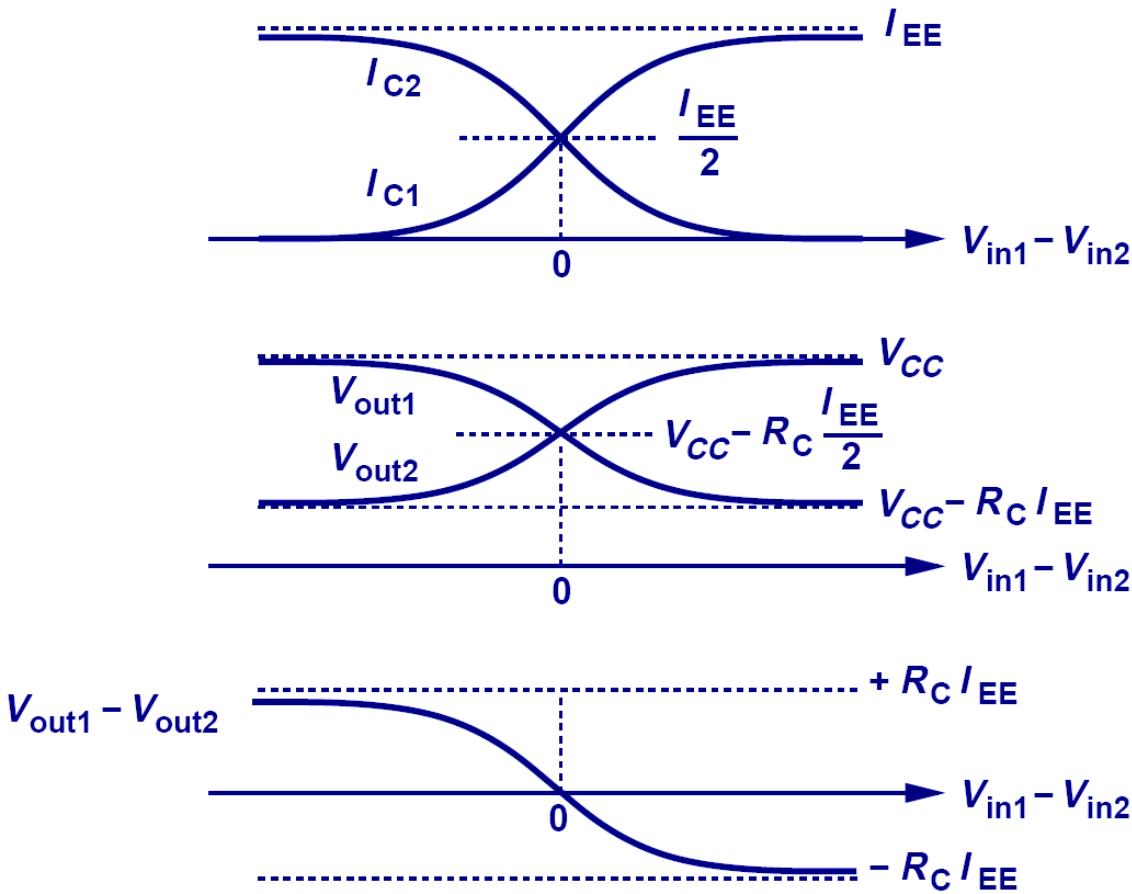


$$\begin{aligned}
 & V_{out1} - V_{out2} \\
 &= (V_{CC} - I_{C1}R_C) \\
 &\quad - (V_{CC} - I_{C2}R_C) \\
 &= (I_{C2} - I_{C1})R_C \\
 &= -R_C I_{EE} \tanh\left(\frac{V_{in1} - V_{in2}}{2V_T}\right)
 \end{aligned}$$

# Linear/Nonlinear Regions of Operation


Amplifier operating in linear region

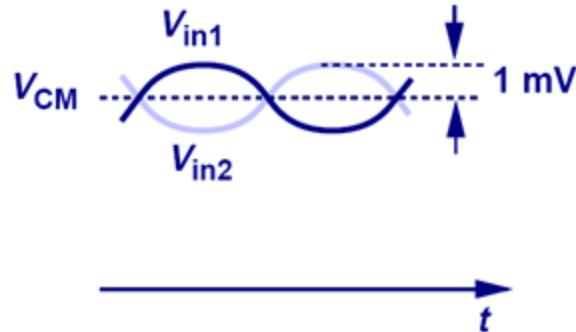


(b)

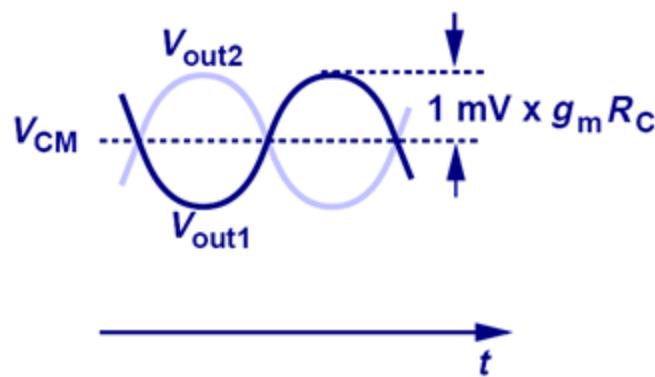


Amplifier operating in non-linear region

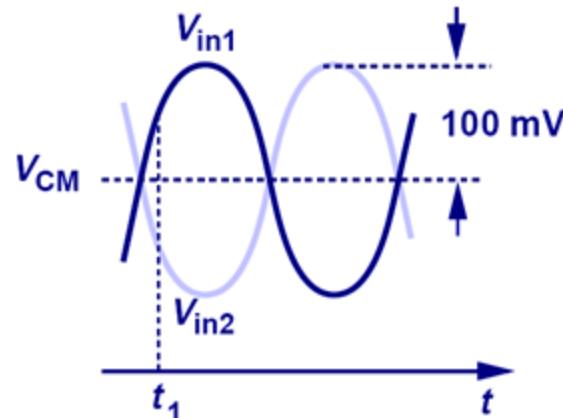

(c)

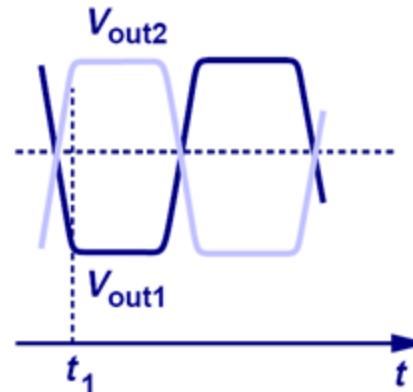


# Small-Signal Analysis

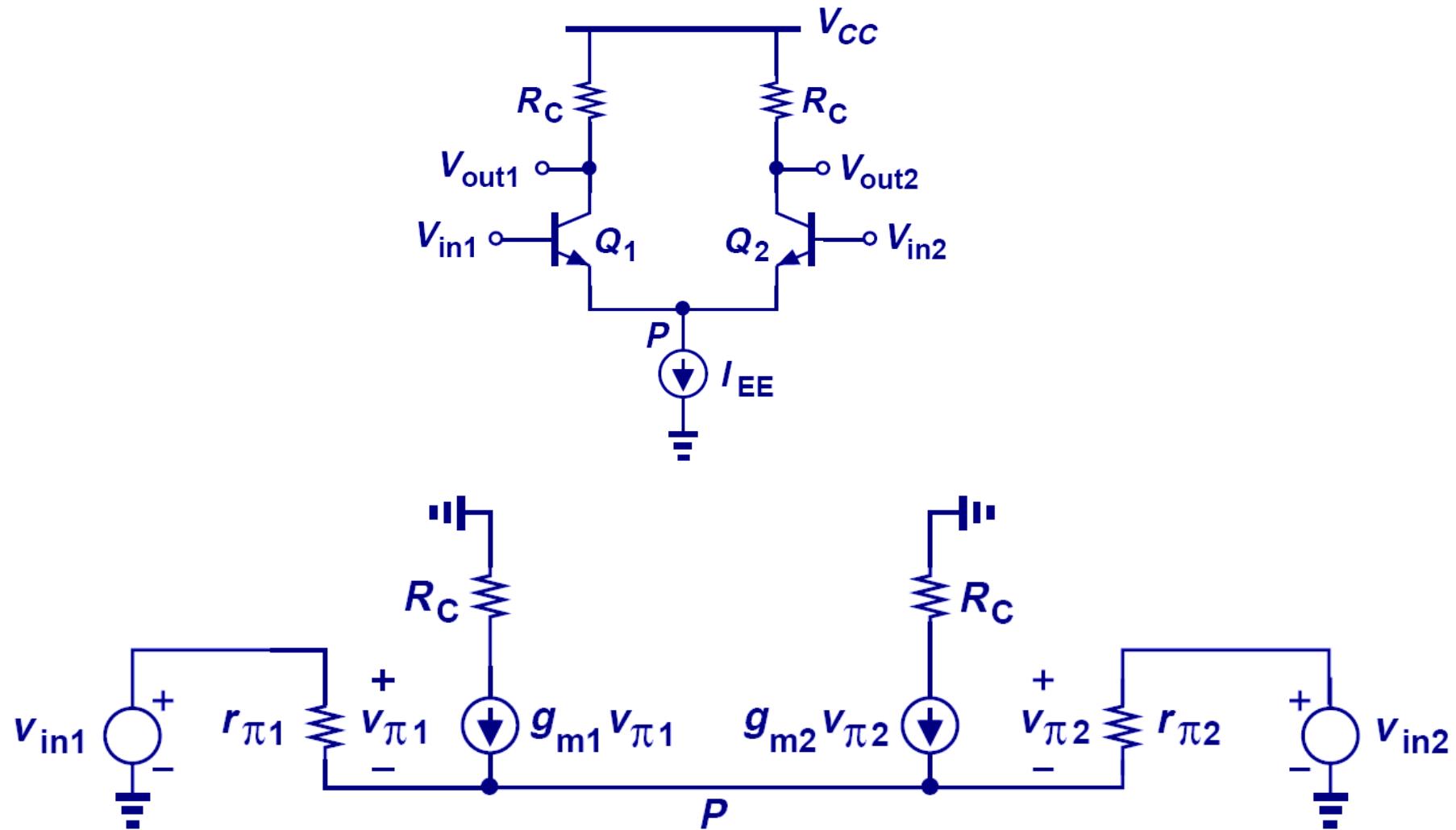

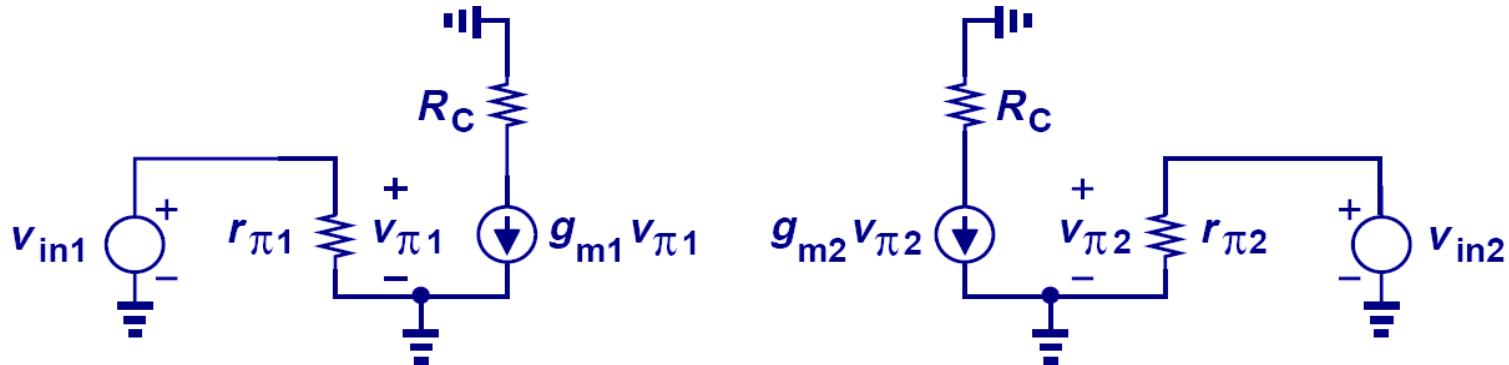
# Half Circuits

- Since node  $P$  is AC ground, we can treat the differential pair as two CE “half circuits.”




(b)

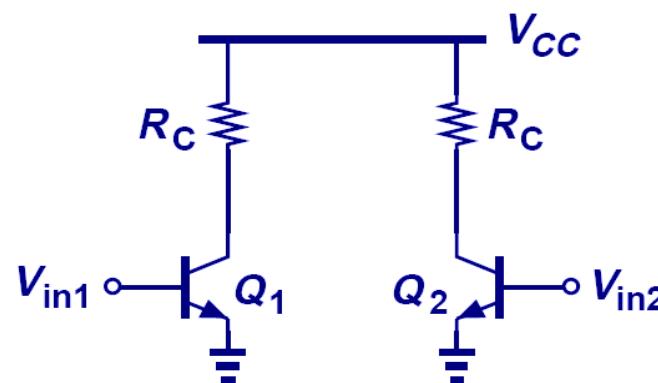

(c)


$$\frac{v_{out1} - v_{out2}}{v_{in1} - v_{in2}} = -g_m R_C$$

# Half Circuit Example 1


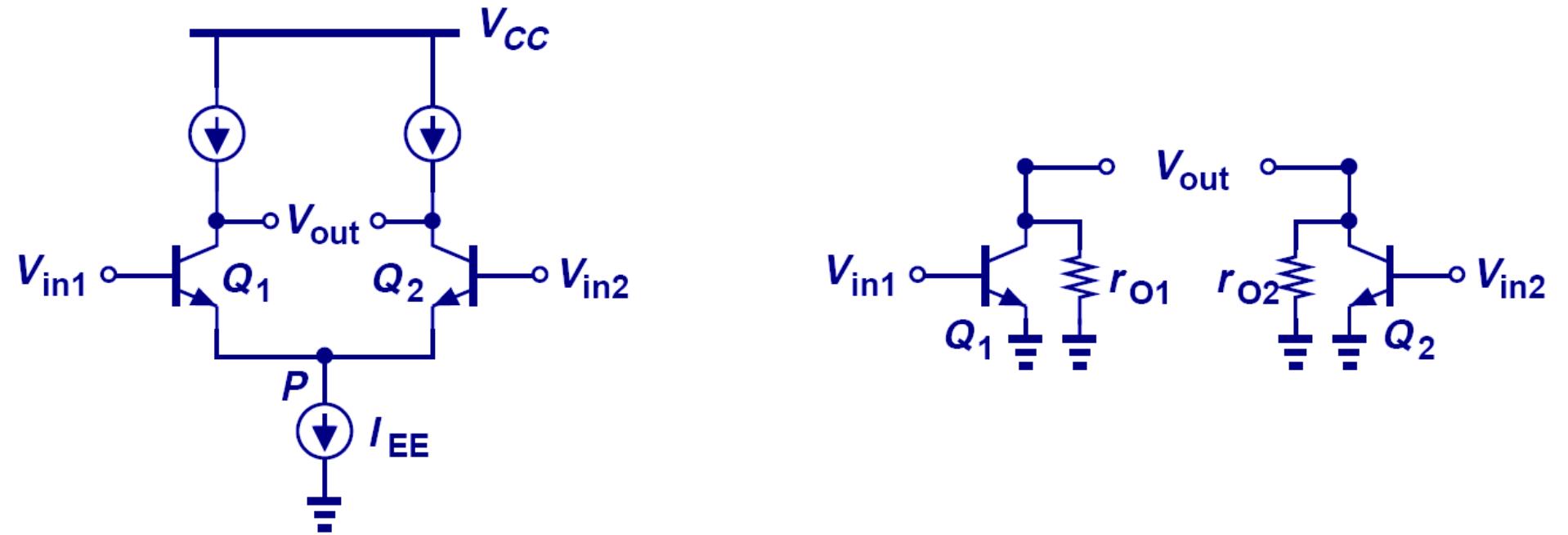


$$\frac{V_{out1} - V_{out2}}{V_{in1} - V_{in2}} = -g_m r_o$$

# Half Circuit Example 2

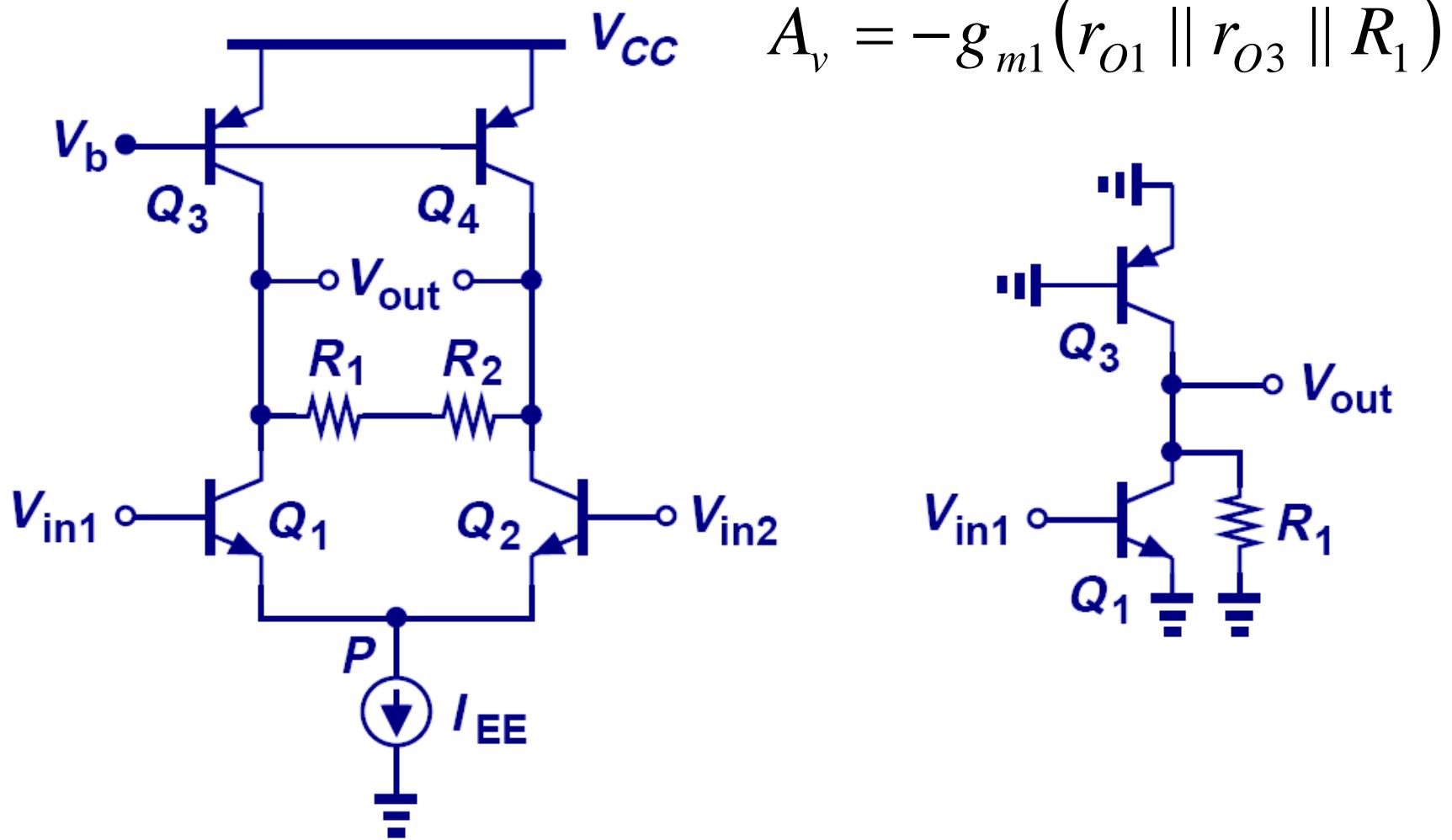


# Half Circuit Example 3

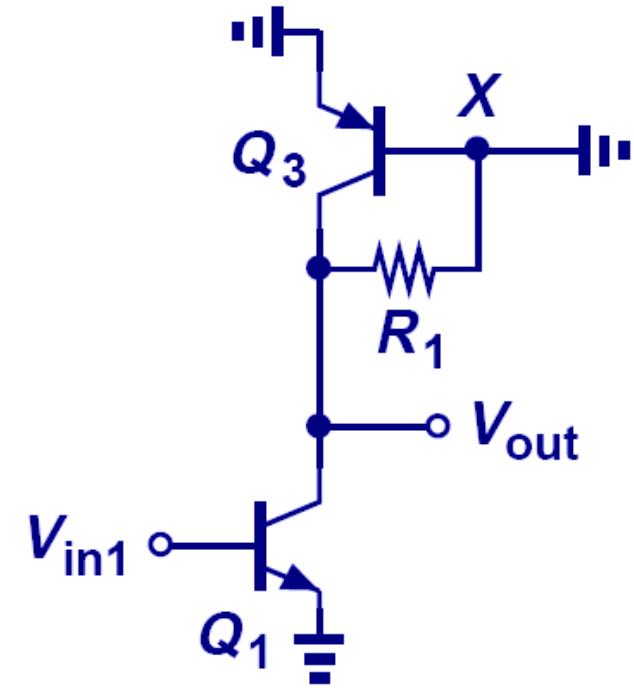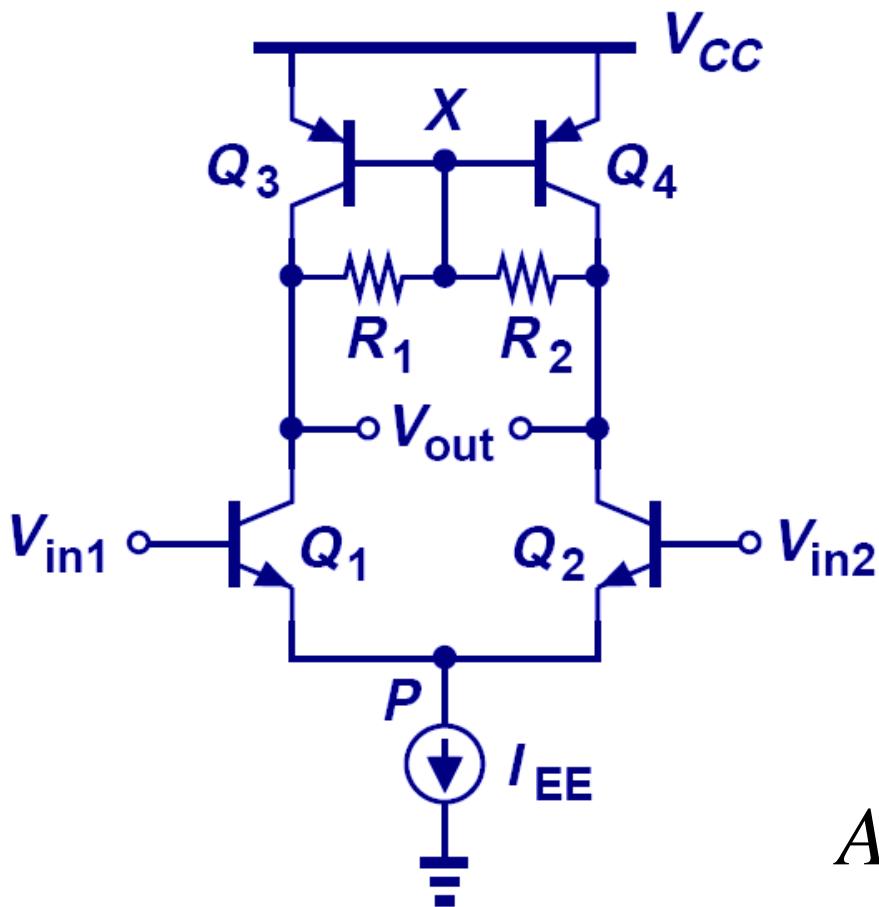

$$A_v = -g_m (r_{o1} \parallel r_{o3} \parallel R_1)$$

# Half Circuit Example 4

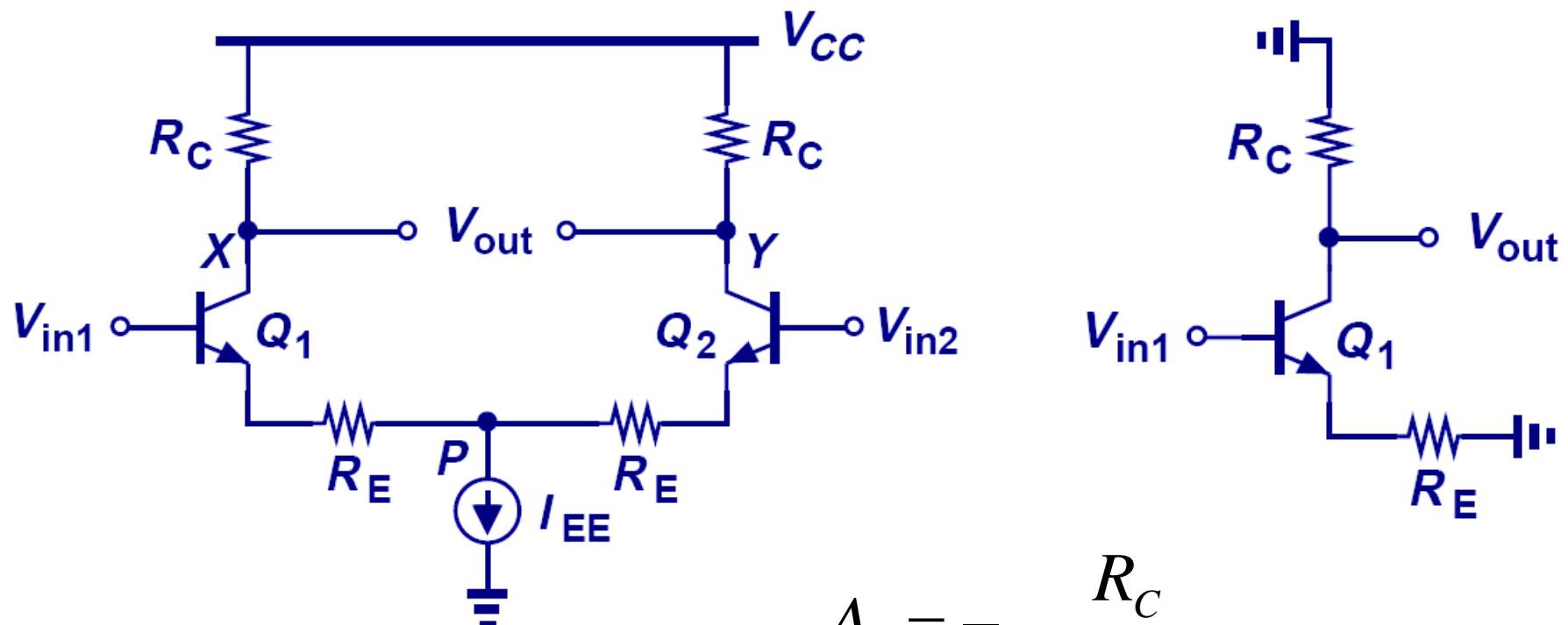

$$A_v = -\frac{R_C}{\frac{1}{g_m} + R_E}$$

# Differential Pair Frequency Response

- Since the differential pair can be analyzed using its half circuit, its transfer function, I/O impedances, locations of poles/zeros are the same as that of its half circuit.

