

Lecture 22

OUTLINE

- Differential Amplifiers
 - General considerations
 - BJT differential pair
 - Qualitative analysis
 - Large-signal analysis
 - Small-signal analysis
 - Frequency response
- Reading: Chapter 10.1-10.2


EE105 Spring 2008

Lecture 22, Slide 1

Prof. Wu, UC Berkeley

“Humming” Noise in Audio Amplifier

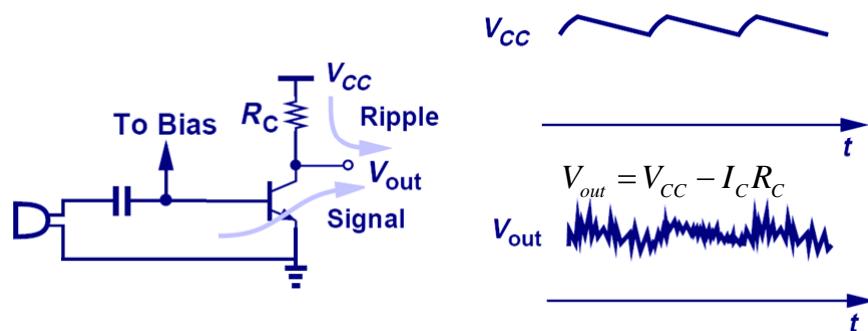- Consider the amplifier below which amplifies an audio signal from a microphone.
- If the power supply (V_{CC}) is time-varying, it will result in an additional (undesirable) voltage signal at the output, perceived as a “humming” noise by the user.




EE105 Spring 2008

Lecture 22, Slide 2

Prof. Wu, UC Berkeley

Supply Ripple Rejection

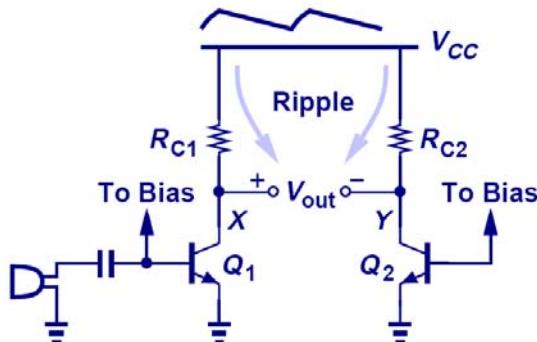- Since node X and Y each see the voltage ripple, their voltage difference will be free of ripple.



$$v_X = A_v v_{in} + v_r$$

$$v_Y = v_r$$

$$v_X - v_Y = A_v v_{in}$$


EE105 Spring 2008

Lecture 22, Slide 3

Prof. Wu, UC Berkeley

Ripple-Free Differential Output

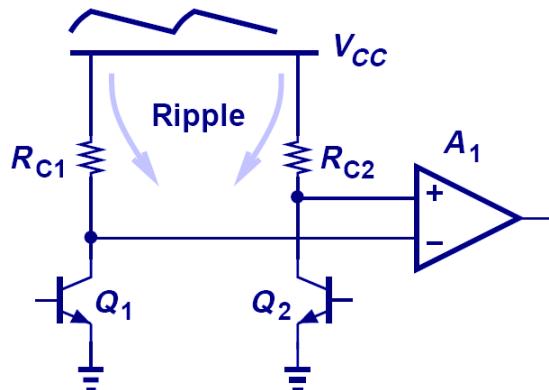- If the input signal is to be a voltage difference between two nodes, an amplifier that senses a **differential signal** is needed.




EE105 Spring 2008

Lecture 22, Slide 4

Prof. Wu, UC Berkeley

Common Inputs to Differential Amp.

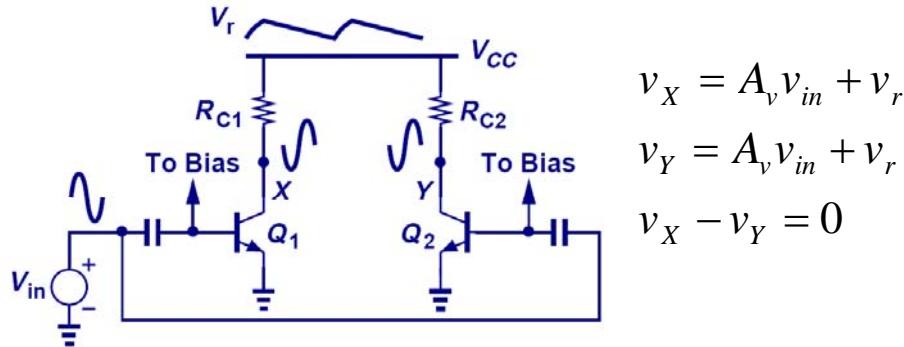- The voltage signals applied to the input nodes of a differential amplifier cannot be in phase; otherwise, the differential output signal will be zero.




EE105 Spring 2008

Lecture 22, Slide 5

Prof. Wu, UC Berkeley

Differential Inputs to Differential Amp.

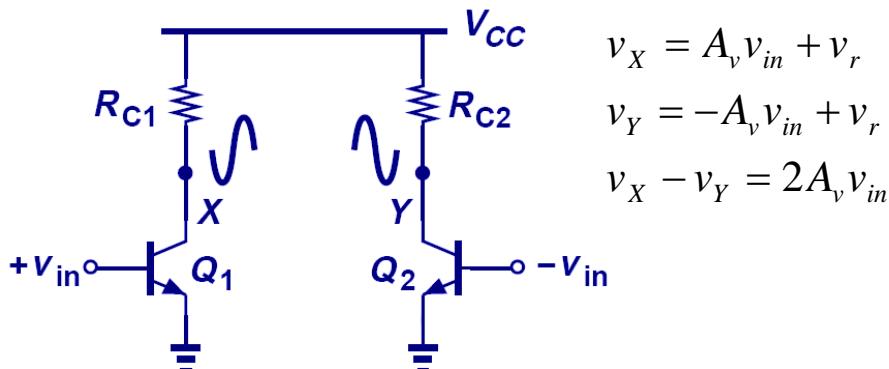- When the input voltage signals are 180° out of phase, the resultant output node voltages are 180° out of phase, so that their difference is enhanced.




EE105 Spring 2008

Lecture 22, Slide 6

Prof. Wu, UC Berkeley

Differential Signals

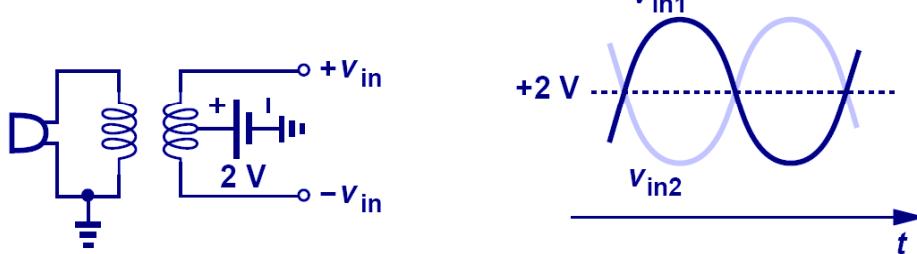- Differential signals share the same average DC value and are equal in magnitude but opposite in phase.
- A pair of differential signals can be generated, among other ways, by a transformer.




EE105 Spring 2008

Lecture 22, Slide 7

Prof. Wu, UC Berkeley

Single-Ended vs. Differential Signals

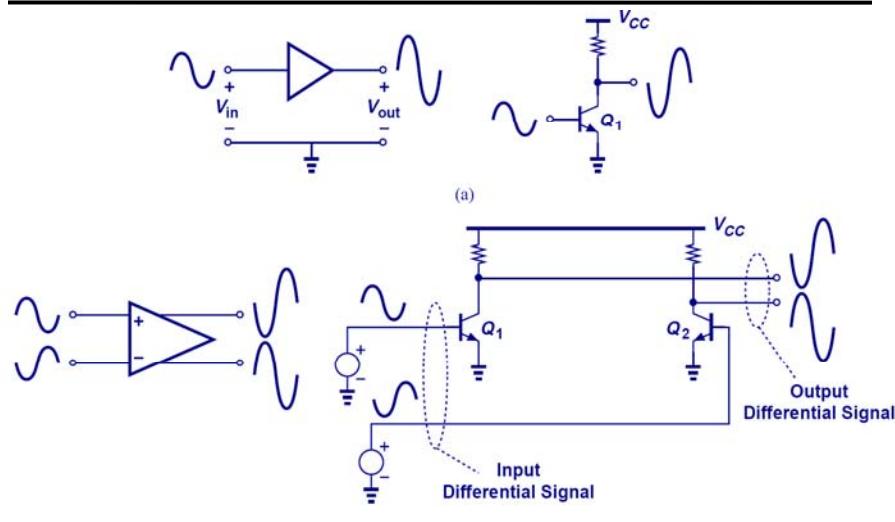


EE105 Spring 2008

Lecture 22, Slide 8

Prof. Wu, UC Berkeley

Differential Pair

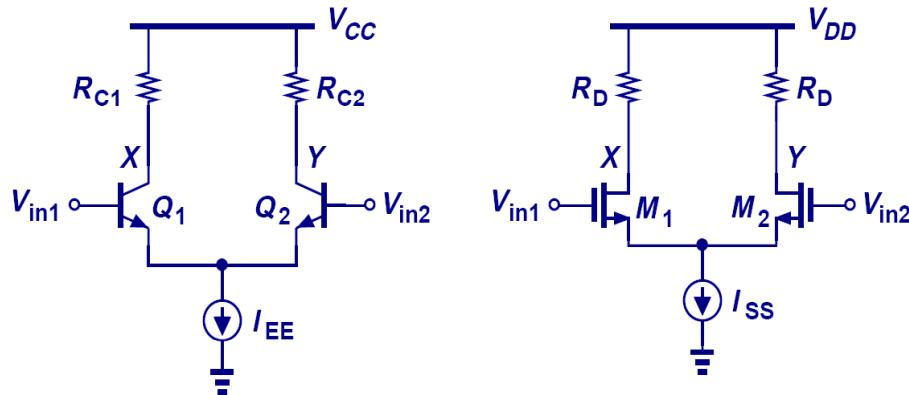


- With the addition of a tail current, the circuits above operate as an elegant, yet robust differential pair.

EE105 Spring 2008

Lecture 22, Slide 9

Prof. Wu, UC Berkeley

Common-Mode Response

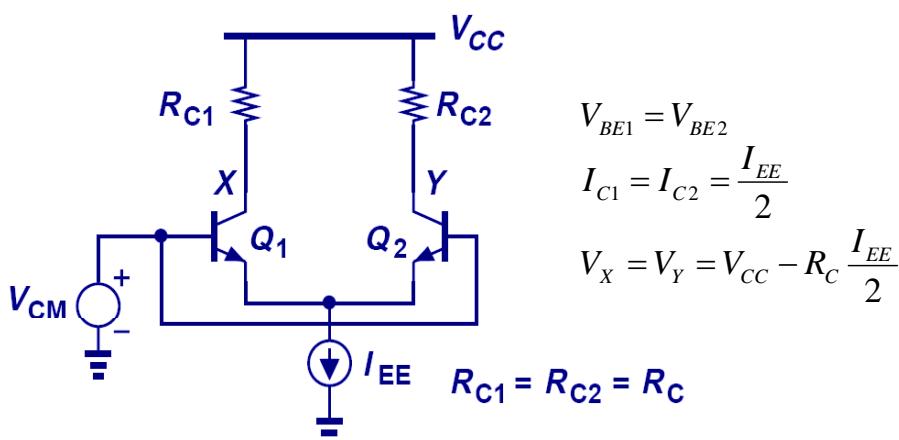


EE105 Spring 2008

Lecture 22, Slide 10

Prof. Wu, UC Berkeley

Differential Response

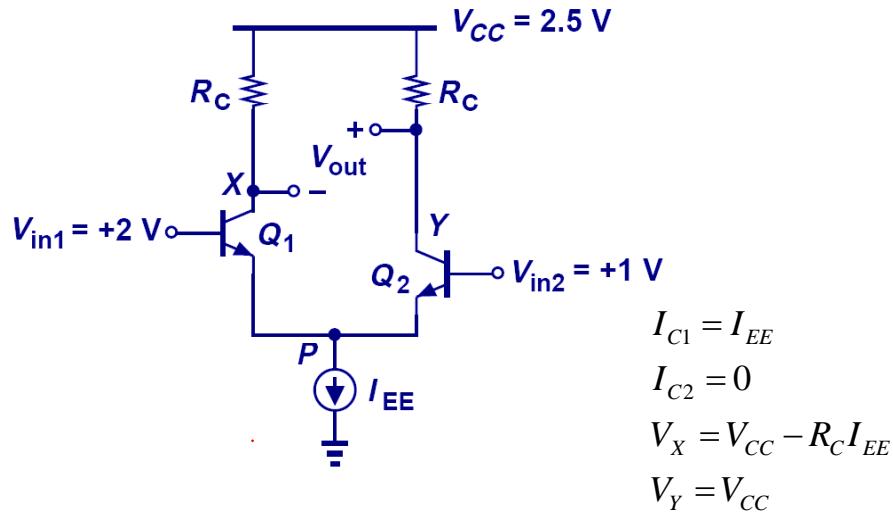


EE105 Spring 2008

Lecture 22, Slide 11

Prof. Wu, UC Berkeley

Differential Response (cont'd)

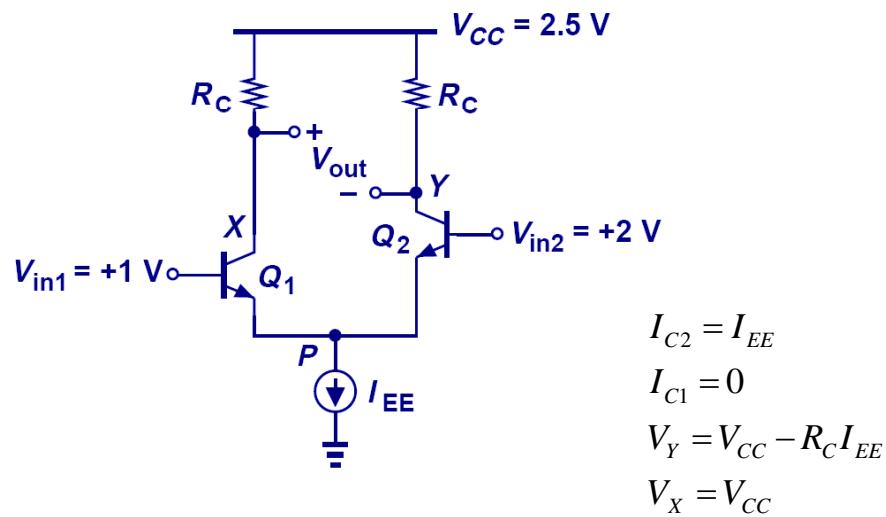


EE105 Spring 2008

Lecture 22, Slide 12

Prof. Wu, UC Berkeley

Differential Pair Characteristics

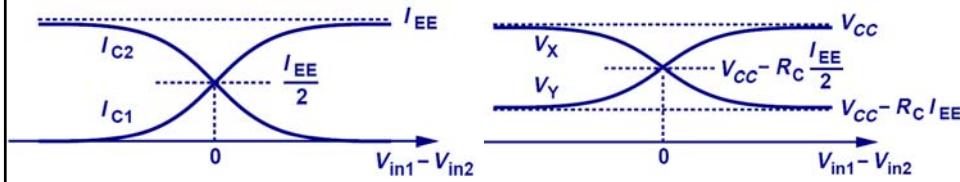- A differential input signal results in variations in the output currents and voltages, whereas a common-mode input signal does not result in any output current/voltage variations.




EE105 Spring 2008

Lecture 22, Slide 13

Prof. Wu, UC Berkeley

Virtual Ground

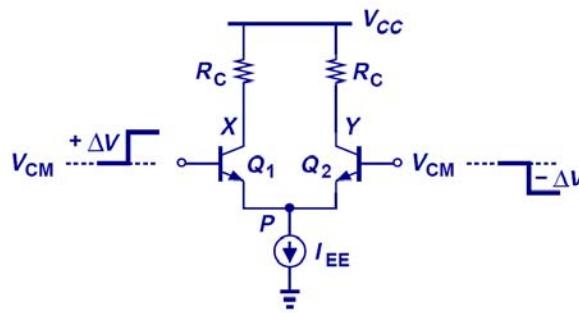- For small input voltages ($+\Delta V$ and $-\Delta V$), the g_m values are ~equal, so the increase in I_{C1} and decrease in I_{C2} are ~equal in magnitude. Thus, the voltage at node P is constant and can be considered as AC ground.



$$\begin{aligned} I_{C1} &= \frac{I_{EE}}{2} + \Delta I \\ I_{C2} &= \frac{I_{EE}}{2} - \Delta I \\ \Delta I_{C1} &= g_m (\Delta V - \Delta V_P) \\ \Delta I_{C2} &= g_m (-\Delta V - \Delta V_P) \\ \Delta I_{C1} &= -\Delta I_{C2} \\ \Rightarrow \Delta V_P &= 0 \end{aligned}$$


EE105 Spring 2008

Lecture 22, Slide 14

Prof. Wu, UC Berkeley

Extension of Virtual Ground

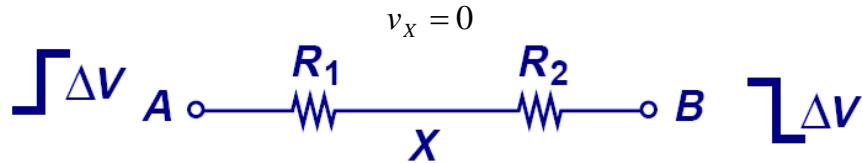- It can be shown that if $R_1 = R_2$, and the voltage at node A goes up by the same amount that the voltage at node B goes down, then the voltage at node X does not change.




EE105 Spring 2008

Lecture 22, Slide 15

Prof. Wu, UC Berkeley

Small-Signal Differential Gain

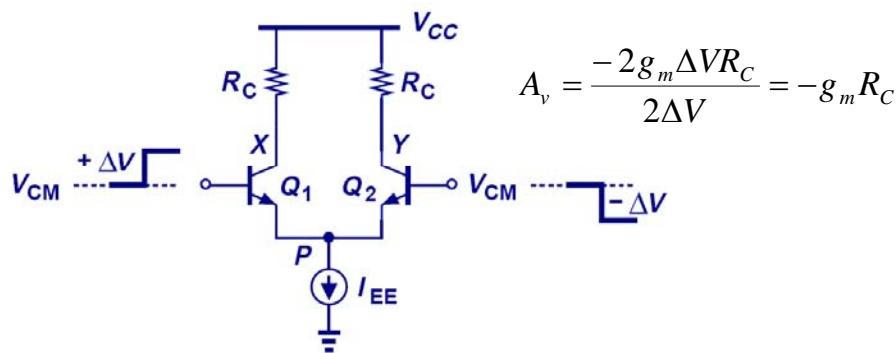- Since the output signal changes by $-2g_m\Delta VR_C$ when the input signal changes by $2\Delta V$, the small-signal voltage gain is $-g_mR_C$.
- Note that the voltage gain is the same as for a CE stage, but that the power dissipation is doubled.




EE105 Spring 2008

Lecture 22, Slide 16

Prof. Wu, UC Berkeley

Large-Signal Analysis

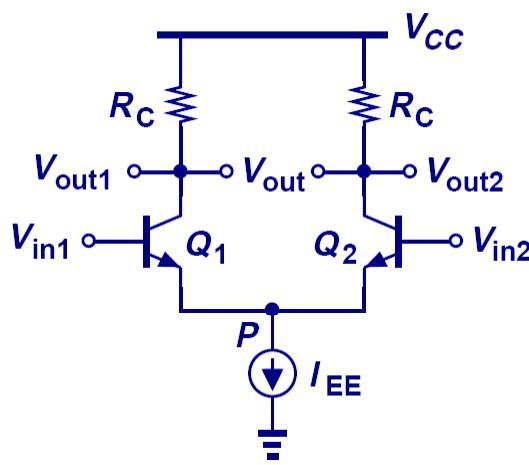


$$\begin{aligned}
 V_{in1} - V_{in2} &= V_{BE1} - V_{BE2} \\
 &= V_T \ln\left(\frac{I_{C1}}{I_S}\right) - V_T \ln\left(\frac{I_{C2}}{I_S}\right) \\
 &= V_T \ln\left(\frac{I_{C1}}{I_{C2}}\right) \\
 I_{C1} + I_{C2} &= I_{EE} \\
 I_{C1} &= \frac{I_{EE} e^{\frac{V_{in1}-V_{in2}}{V_T}}}{1 + e^{\frac{V_{in1}-V_{in2}}{V_T}}} \\
 I_{C2} &= \frac{I_{EE} e^{-\frac{V_{in1}-V_{in2}}{V_T}}}{1 + e^{-\frac{V_{in1}-V_{in2}}{V_T}}}
 \end{aligned}$$

EE105 Spring 2008

Lecture 22, Slide 17

Prof. Wu, UC Berkeley

Input/Output Characteristics

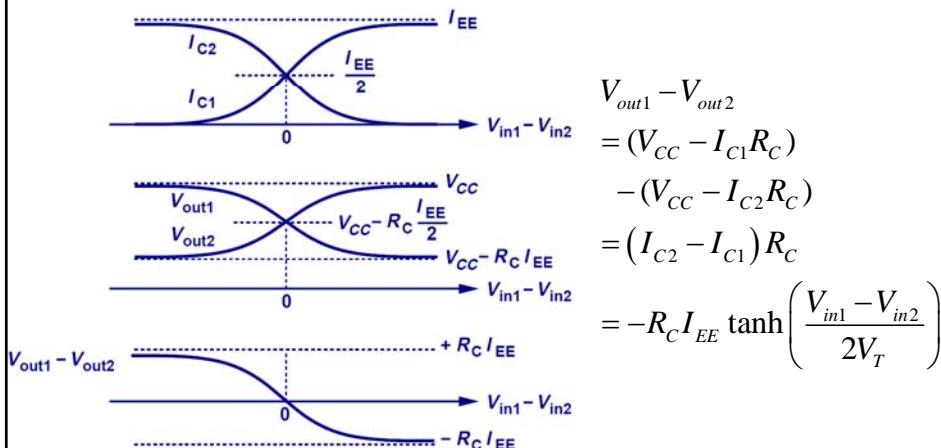

$$\begin{aligned}
 V_{out1} - V_{out2} &= (V_{CC} - I_{C1}R_C) \\
 &\quad - (V_{CC} - I_{C2}R_C) \\
 &= (I_{C2} - I_{C1})R_C \\
 &= -R_C I_{EE} \tanh\left(\frac{V_{in1} - V_{in2}}{2V_T}\right)
 \end{aligned}$$


EE105 Spring 2008

Lecture 22, Slide 18


Prof. Wu, UC Berkeley

Linear/Nonlinear Regions of Operation

Amplifier operating in linear region

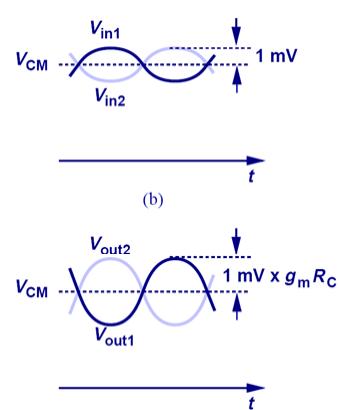

Amplifier operating in non-linear region

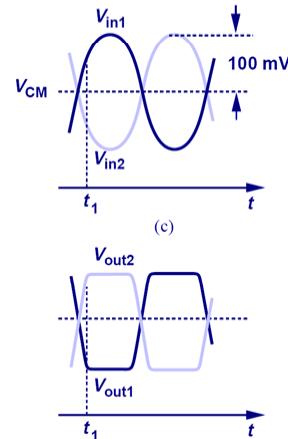


EE105 Spring 2008

Lecture 22, Slide 19

Prof. Wu, UC Berkeley

Small-Signal Analysis

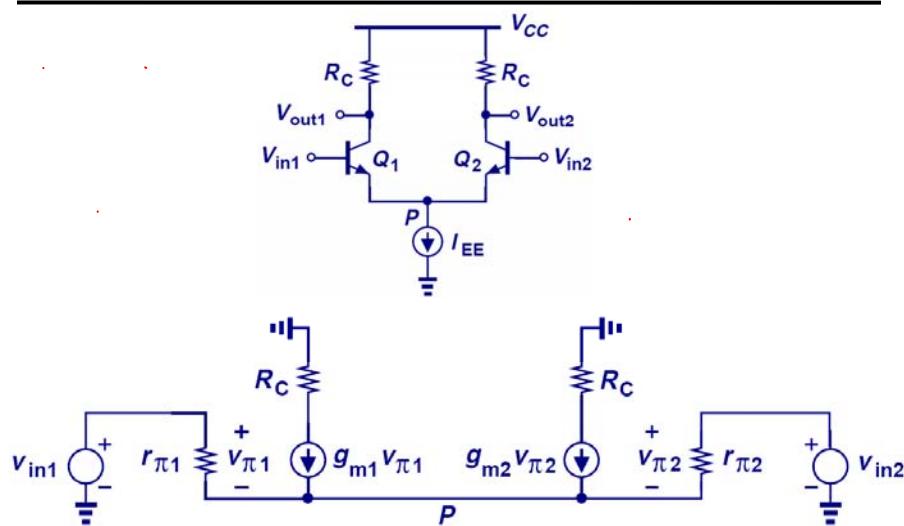


EE105 Spring 2008

Lecture 22, Slide 20

Prof. Wu, UC Berkeley

Half Circuits

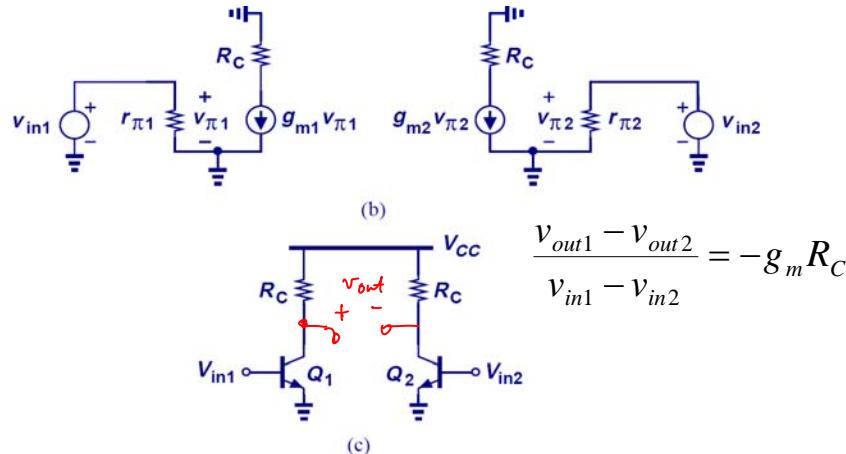- Since node P is AC ground, we can treat the differential pair as two CE "half circuits."




EE105 Spring 2008

Lecture 22, Slide 21

Prof. Wu, UC Berkeley

Half Circuit Example 1

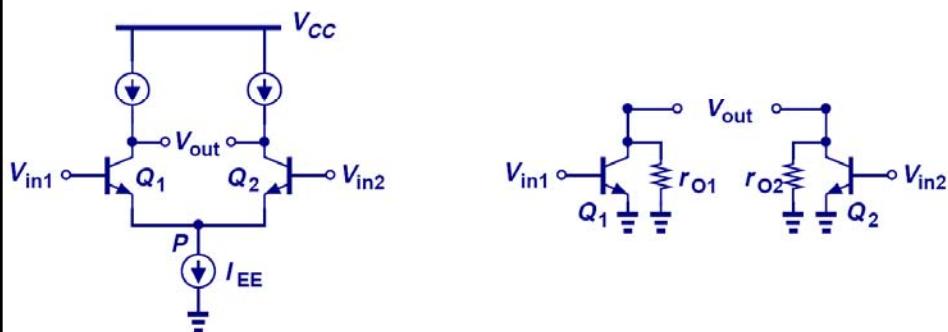


$$\frac{V_{out1} - V_{out2}}{V_{in1} - V_{in2}} = -g_m r_o$$

EE105 Spring 2008

Lecture 22, Slide 22

Prof. Wu, UC Berkeley

Half Circuit Example 2

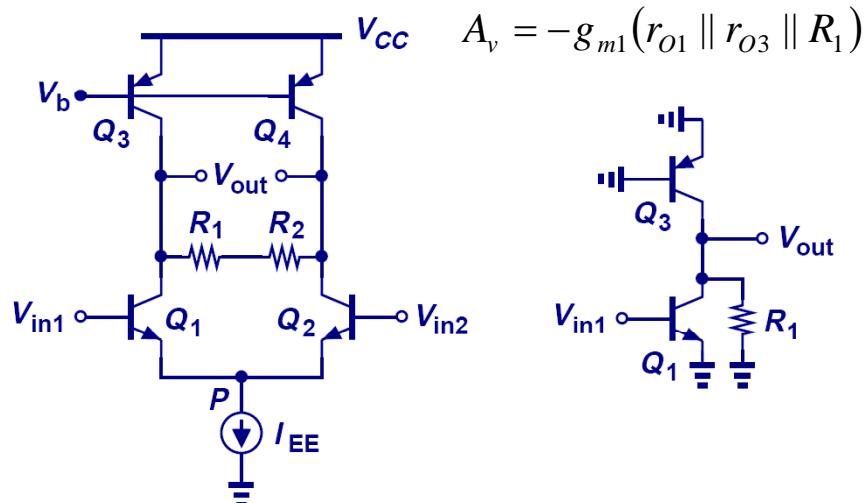


EE105 Spring 2008

Lecture 22, Slide 23

Prof. Wu, UC Berkeley

Half Circuit Example 3

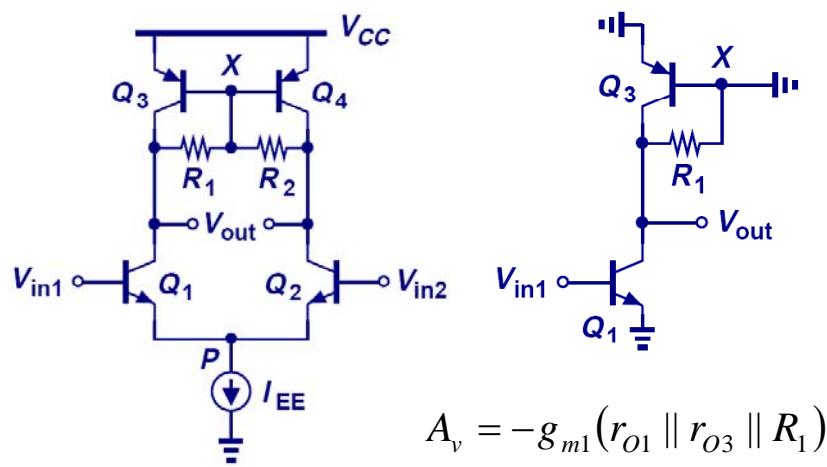


EE105 Spring 2008

Lecture 22, Slide 24

Prof. Wu, UC Berkeley

Half Circuit Example 4

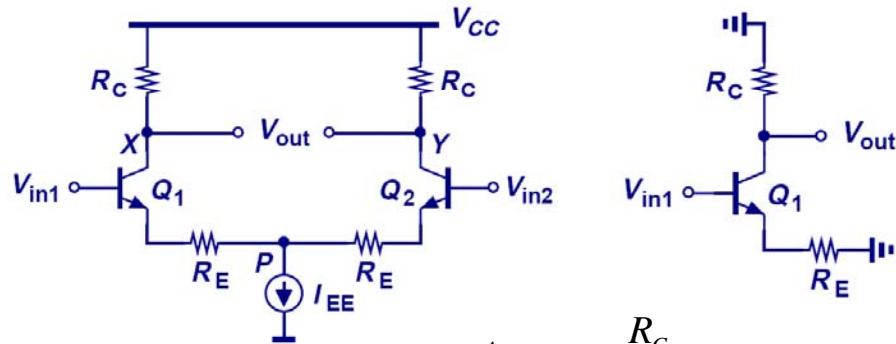

$$A_v = -\frac{R_C}{\frac{1}{g_m} + R_E}$$


EE105 Spring 2008

Lecture 22, Slide 25

Prof. Wu, UC Berkeley

Differential Pair Frequency Response

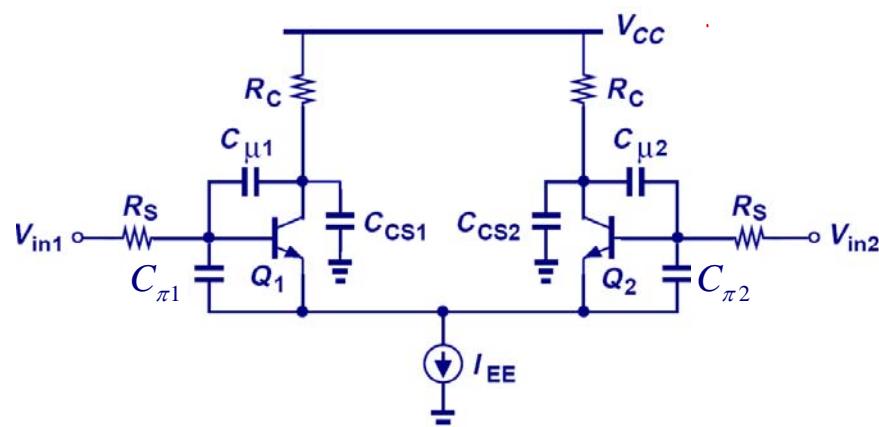- Since the differential pair can be analyzed using its half circuit, its transfer function, I/O impedances, locations of poles/zeros are the same as that of its half circuit.



EE105 Spring 2008

Lecture 22, Slide 26

Prof. Wu, UC Berkeley